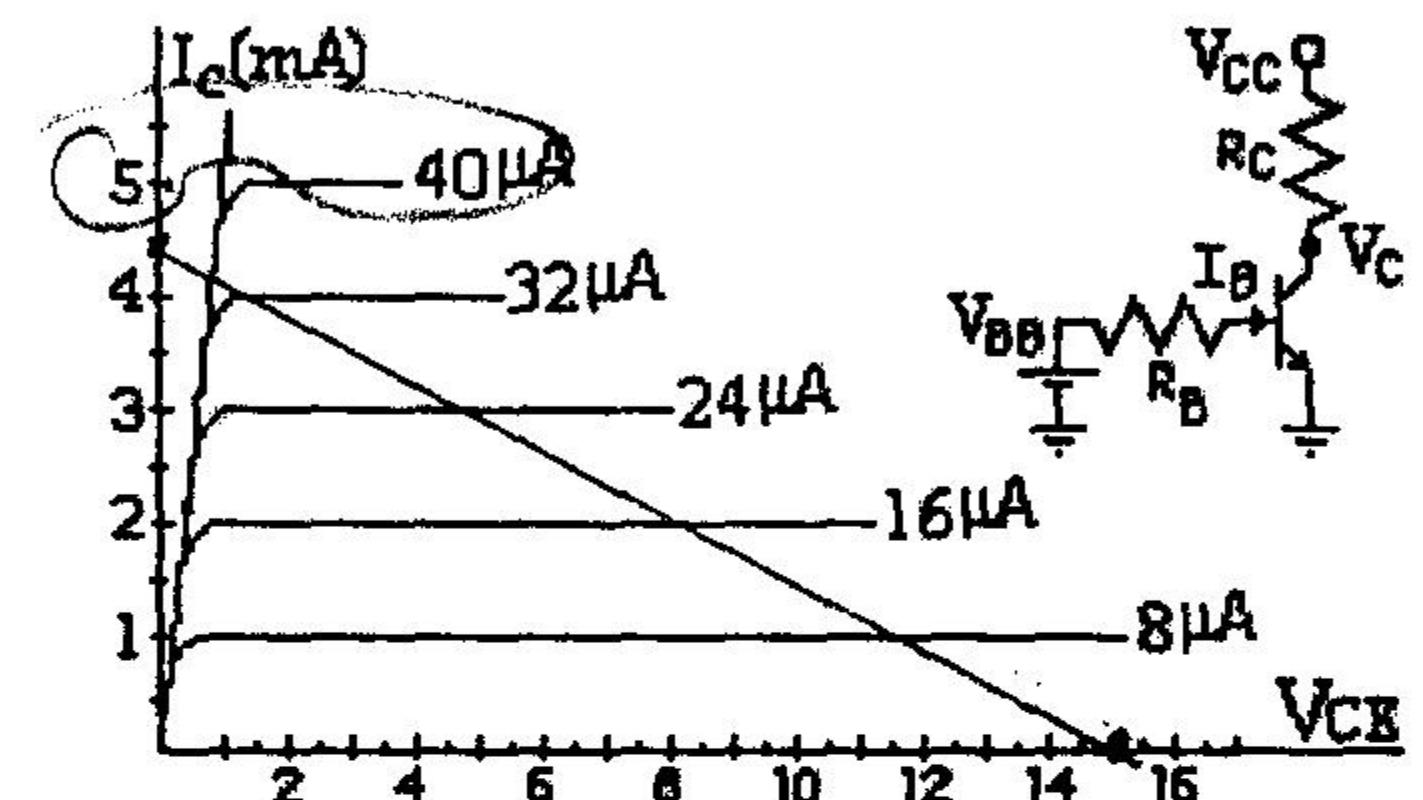





1. Take  $V_{CC} = V_{BB} = 15v$ ,  $R_C = 3.3K\Omega$
- Estimate  $\beta$  using the I-V curve  $\beta = 125$  (3 pts.)
  - Draw the Load Line  $\frac{V_C}{V_{CC}} = \frac{15 - V_C}{3.3K\Omega}$  (4 pts.)
  - What is the value of  $I_B$  for the  $V_C = \frac{1}{2} V_{CC}$ ? (5 pts.)  $I_B = 12\mu A$
  - ~~Calculate  $R_B$~~   $412.5$  (4 pts.)
  - Replace the transistor with its model and draw the ac equivalent circuit ?? (5 pts.)



Note: Answering part b on this sheet.

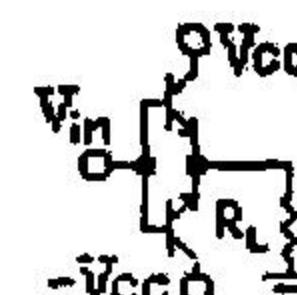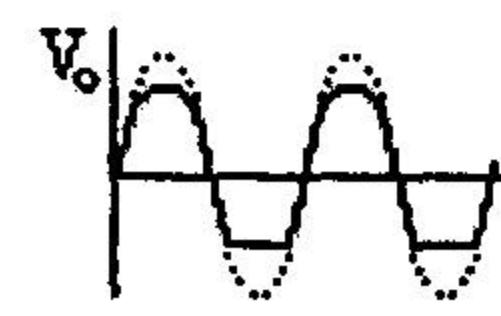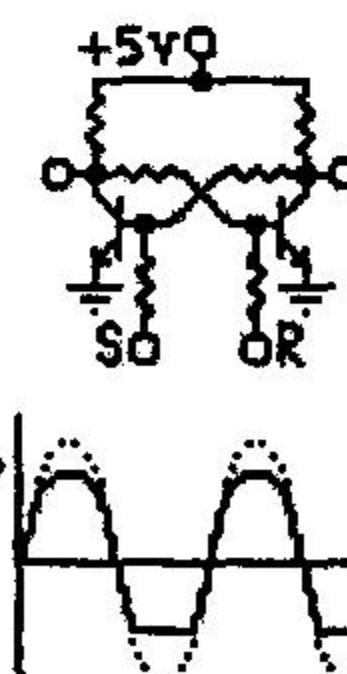2. Answer 7 of the following 11 questions briefly. ( $7 \times 7 = 49$  pts.)  
The 8th answer will be ignored.



- Why is the reverse current in a diode independent of voltage? (see figure)
- Why are some voltage regulator chips screwed to metal plates?
- What is the difference between energy bands of metals, insulators and semiconductors?
- Identify the two transistor circuit opposite. What do S & R stand for?
- How does a varactor diode function?
- ~~Explain the distortions in the amplifier output ( $V_o$ ) shown to the right~~
- Why aren't Intrinsic semiconductors used in electronic gadgets like radios?
- Why does  $C_E$  increase the gain?
- Why is the two transistor amplifier shown energy efficient?
- Is the current in a photocell proportional to the intensity of light in the open circuit ( $I \sim 0$ ) or the short circuit ( $V \sim 0$ ) mode?
- What is the role of the capacitors at the I/O of transistor amplifiers?



3. Answer 3 of the following 4 questions. (3x10 = 30 points)


- 3A. Take  $V_{ZO} = 6.25v$ ,  $R_S = 25\Omega$ ,  $R_L = 100\Omega$ , and  $r = 5\Omega$   
Calculate  $V$  for  $V_i = 25v$

$$12.5V$$

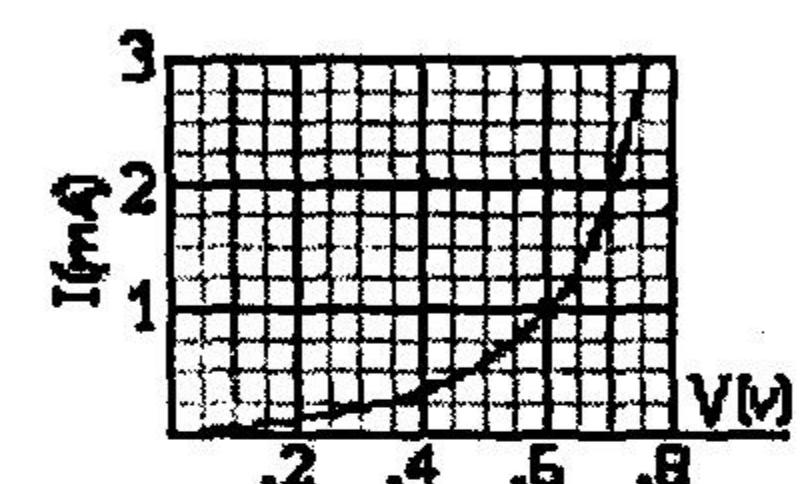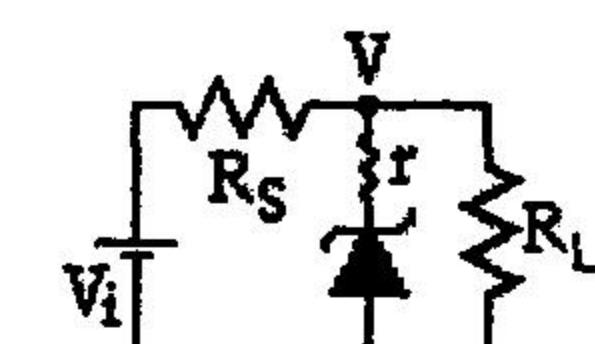


- 3B. Calculate the a.c and D.C. resistances at the highlighted point of the I-V characteristic curve of a diode shown to the right.

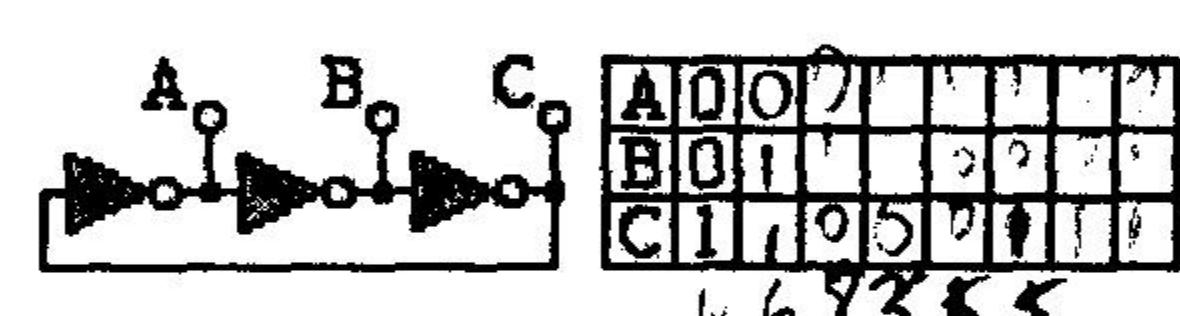- 3C. Continue the sequence of ABC for the cascade shown.  
What is its "illegal cycle?"



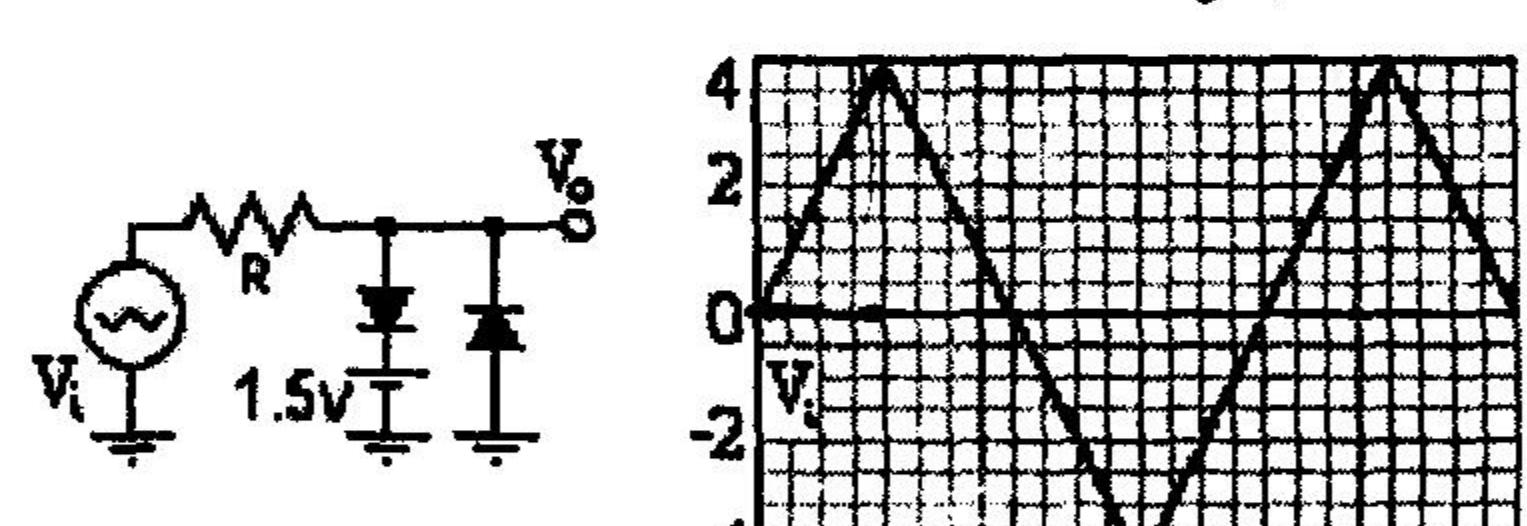- 3D. The figure shows a clipper circuit and the waveform for  $V_i$ . Take  $V_D = 0.5v$  and draw  $V_o$  on the same graph.



Good Luck!

21 + 49 + 30 = 100