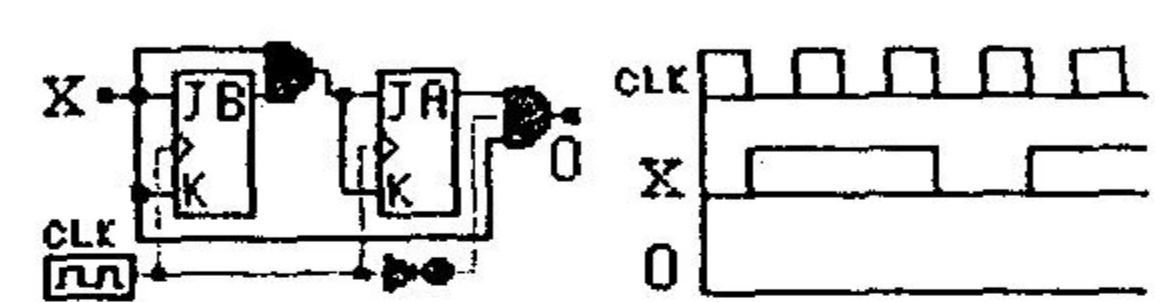


1. Answer ONE of the following two questions: (20 pts.)


1A. For the circuit shown to the right

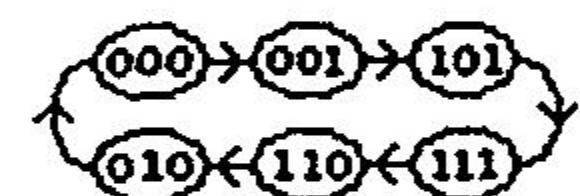- a. Prepare the present state next state table. (7 pts.)
- b. Draw the State Transition Diagram. (9 pts.)
- c. Draw the output (O) on the timing diagram. (4 pts.)




1B. The figure shows the state transition diagram of a counter (0,1,5,7,6,2,0...)

- Show self comp*
- a. Prepare the Present state / next state table. (6 pts.)
 - b. Prepare the Karnaugh maps for D Flip Flops. (8 pts.)
 - c. Convert the maps to that for JK Flip Flops. (6 pts.)
 - d. Draw the counter circuit. (5 pts.)




2. For the state transition diagram shown

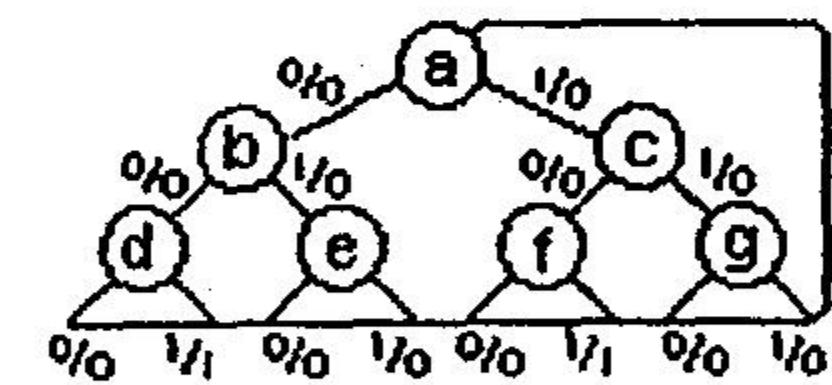- a. Reduce the number of states by the method of grouping (Note: No points for other methods). (12 pts.)
- b. Draw the reduced state transition diagram. (3 pts.)



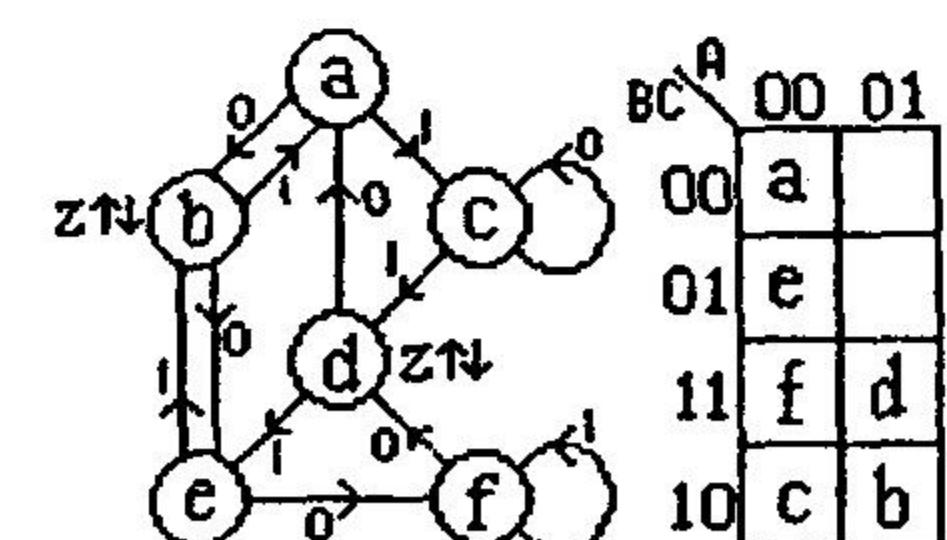3. To what degree does the state assignment shown satisfy the 4 rules for the state transition diagram shown? (15 pts.)

Note: You must justify your answers explicitly.



4. Realize the 4 state machine shown by the One-Hot method, using D-Flip Flops. You are free to use gates or multiplexers.

Note: No points for other methods. (15 pts.)



$$\begin{aligned} 4 \rightarrow \text{tds} \\ \Rightarrow 2^4 = 4 \quad n = 2 \text{ bits} \end{aligned}$$

5. Answer 5 of the following 7 questions. (7x5 = 35 pts.)

Note: The 6th answer will be ignored.



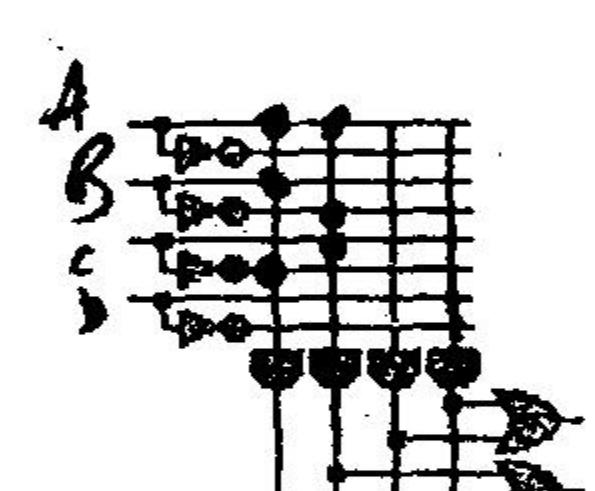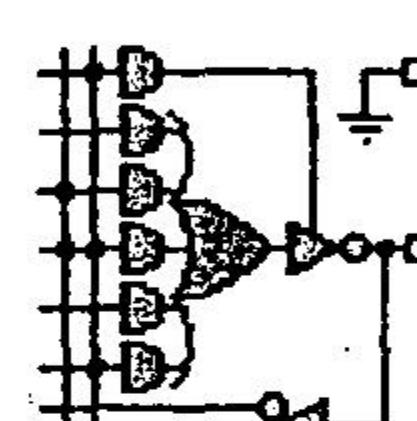- a. Identify the Read Only Memory circuit shown in the figure opposite. Justify your answer briefly.
- b. How many 16x4bit memory chips would you need to construct a 1Kx8bit memory?
- c. To what extent is the Alternate State Transition Method applied in Question 1?
- d. In which type of chips would you find the AND/OR fragment shown to the right? Justify your answer briefly.
- e. How many unique ways are there to assign the labels A, B to an state machine of just two states (a, b)? Justify your answer any which way you can (graphic, algebraic,...)
- f. Perform the division 1000.11/10.1 explicitly. (no points for saying $8.75 \div 2.5 = 3.5$)
- g. Realize the function F = A(BXC) using the array shown.



Good Luck!

20 + 3X15 + 35 = 100