

ELE 201: Electrical Circuits I Exam 2 – Spring 2015

Duration: 1 hour 20 minutes
Start Time: 9:30 am

Date: 7/4/2015
Dr. Dani TANNIR

Name: SOLUTION ID#: _____

INSTRUCTIONS:



- Answer each of the following questions in the space provided.
- This is a closed-book exam.
- If something is not clear, state your assumptions.
- Programmable calculators are not allowed.
- The number of marks for each question is specified next to it.
- The total number of marks is 50.

1	2	3	4	Total
/13	/12	/13	/12	50 /50

Question 1 (13 marks)

- Use superposition to determine the value of I_L in the $2k\Omega$ load resistance R_L :
- If R_L is to be replaced with another resistor such that the power transferred to it is maximized, determine the required value of R_L .


6mA source

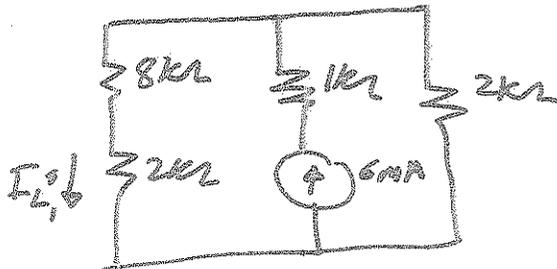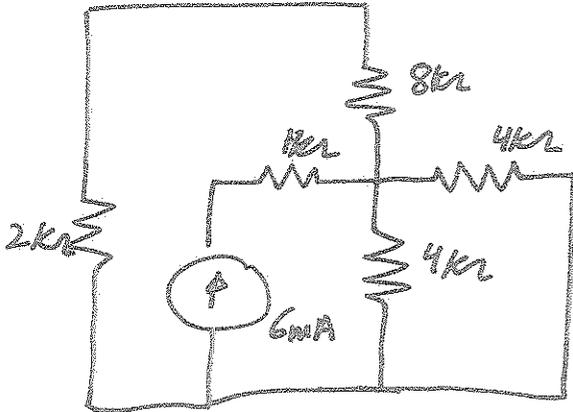


current divider

$$I_{L1} = \frac{2k}{2k + (8k + 2k)} (6m)$$

$$= \frac{2}{12} (6) = 1mA$$

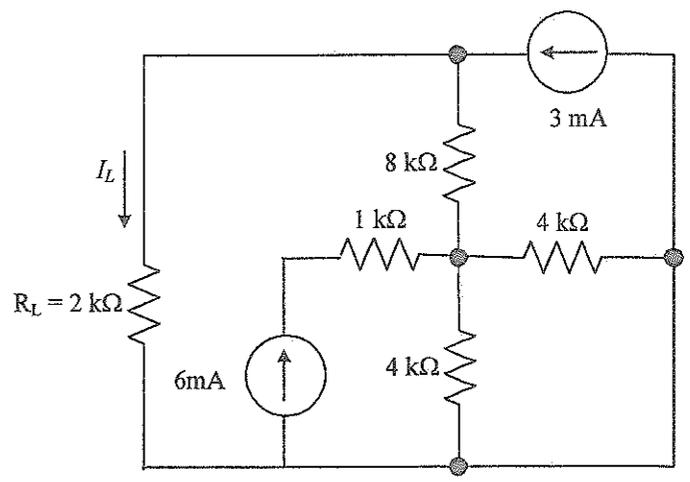

3mA source

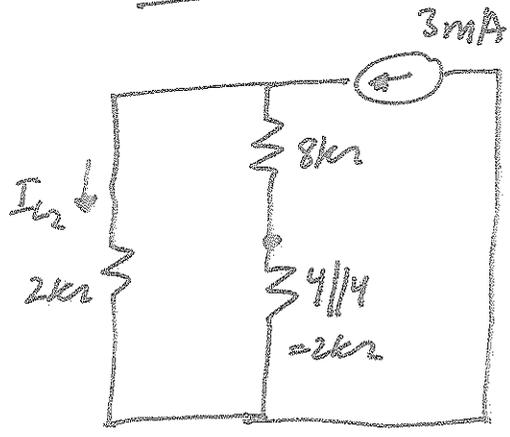


current divider

$$I_{L2} = \frac{10k}{2k + 10k} (3m) = \frac{10}{12} (3)$$

$$= 2.5mA$$

$$I_L = I_{L1} + I_{L2} = \boxed{3.5mA}$$

b) $R_L = R_{eq}$

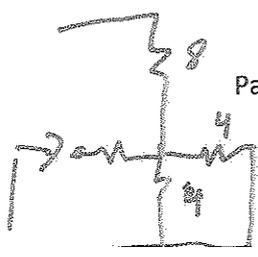

$$= (4||4) + 8 = \boxed{10k\Omega}$$

Question 2 (12 marks)



Determine the Norton Equivalent Circuit at Terminals a-b

No independent sources

$$I_N = I_{SC} = 0$$

$$R_{Th} = \frac{V_T}{I_T}$$

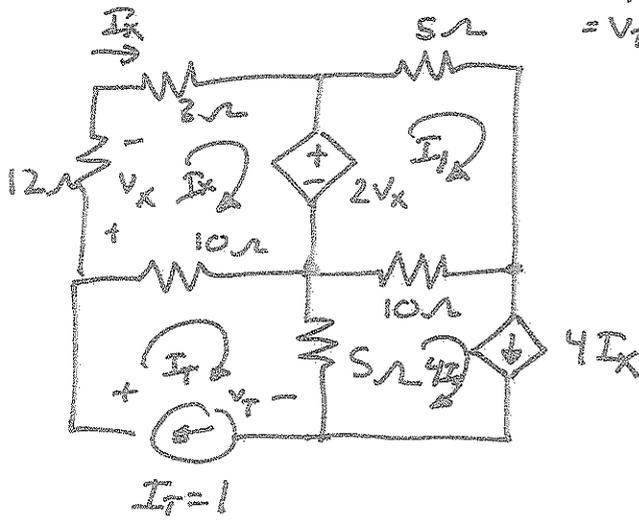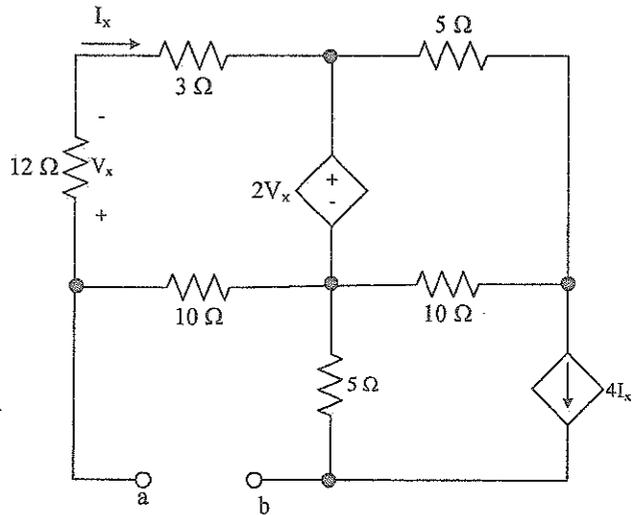Take $I_T = 1 \Rightarrow R_{Th} = \frac{V_T}{1} = V_T$



$$I_T = 1 \quad V_x = 12I_x$$

$$15I_x + 2V_x + 10(I_x - I_T) = 0$$

$$15I_x + 24I_x + 10I_x - 10 = 0$$

$$49I_x = 10$$

$$I_x = \frac{10}{49}$$

$$V_T = 10(I_T - I_x) + 5(I_T - 4I_x)$$


$$= 15I_T - 30I_x$$

$$= 15 - \frac{300}{49} = 8.88 \text{ V}$$


$$\Rightarrow R_{Th} = 8.88 \Omega$$

Question 3 (13 marks)

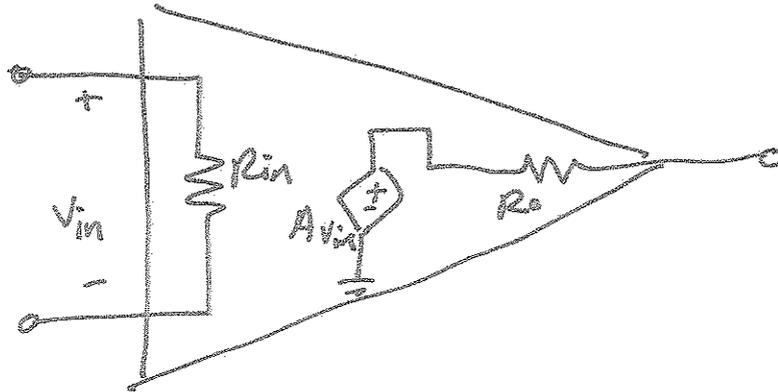- a. Draw and label the linear equivalent circuit of an operational amplifier



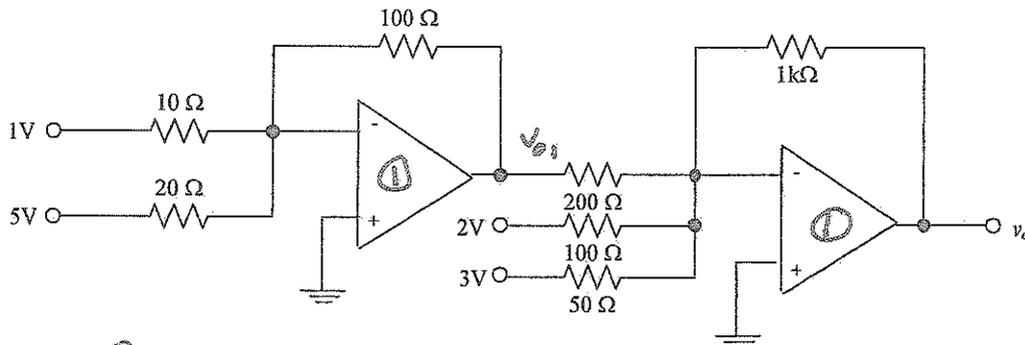- b. Assuming an ideal op-amp, determine the value of v_o in the following circuit



①

$$V_+ = V_- = 0V$$

$$-\frac{1}{10} - \frac{5}{20} - \frac{v_{o1}}{100} = 0$$

$$\Rightarrow v_{o1} = -\frac{100}{10} - \frac{500}{20}$$

$$= -10 - 25$$

$$= -35V$$

②

$$V_+ = V_- = 0V$$

$$-\frac{v_{o1}}{200} - \frac{2}{100} - \frac{3}{50} - \frac{v_o}{1k} = 0$$

$$v_o = -\frac{1000}{200}(-35) - \frac{(2)(1000)}{100}$$







Page 6 of 9

$$\frac{(3)(1000)}{50} = +175 - 20$$

$$= 155V$$

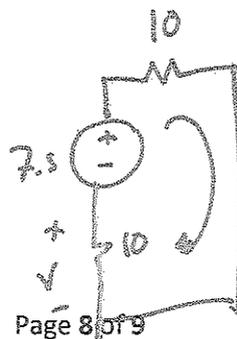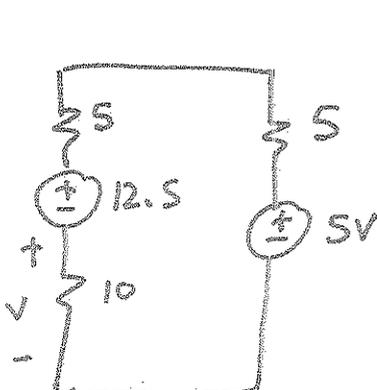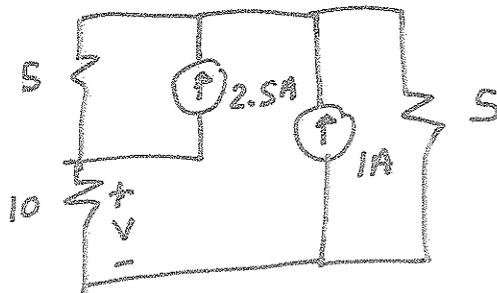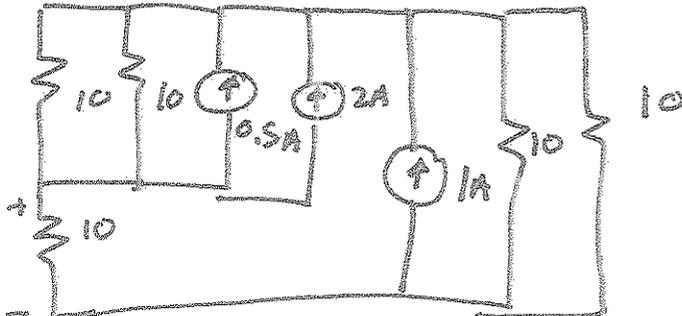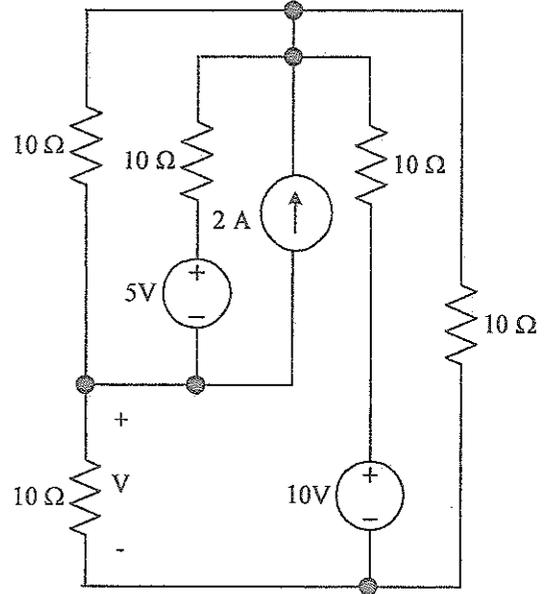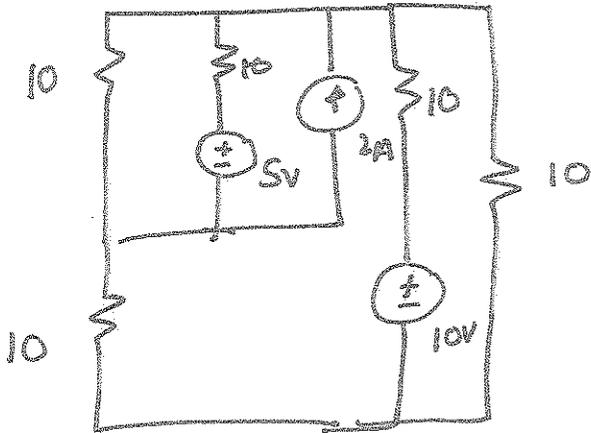Question 4 (12 marks)

Use source transformation to first simplify the following circuit to one that contains a single source, and then determine the value of the voltage V from the simplified circuit.



$$I = \frac{7.5}{20} = 0.375$$

$$V = (-10)(0.375)$$

$$= \boxed{-3.75V}$$

