

ELE 201: Electrical Circuits I Exam 1 – Spring 2015

Duration: 1 hour 20 minutes
Start Time: 9:30 am

Date: 5/3/2015
Dr. Dani TANNIR

Name: <u>SOLUTION</u>	ID#: _____
-----------------------	------------


INSTRUCTIONS:

- Answer each of the following questions in the space provided.
- This is a closed-book exam.
- If something is not clear, state your assumptions.
- Programmable calculators are not allowed.
- The number of marks for each question is specified next to it.
- The total number of marks is 50.


1	2	3	4	Total
/16	/11	/11	/12	/50

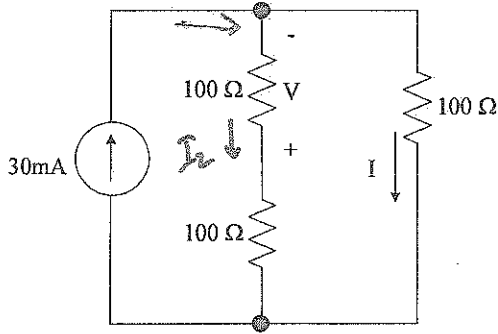Question 1 (16 marks)


Use current division and/or voltage division combined with Ohm's Law to determine the values of V and I as labeled for the following circuits:




(a)

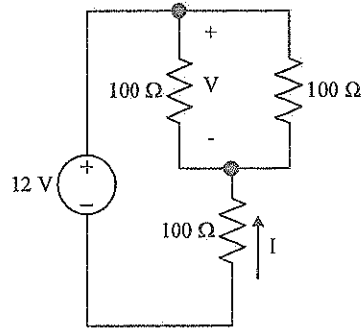

(b)

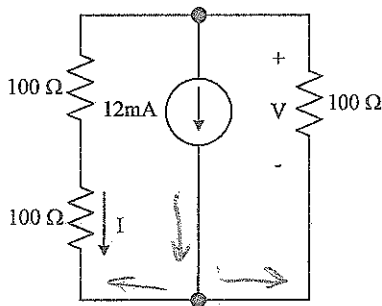

(c)

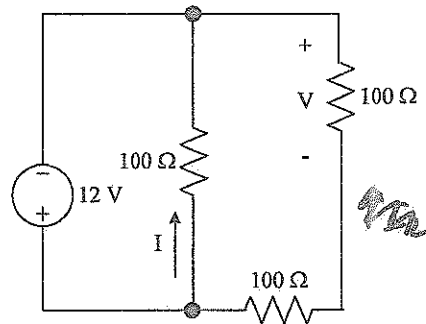

(d)

$$a) \quad I = \frac{200}{300} (30) = \boxed{20\text{mA}}$$

$$V = -I_2 (100) \quad I_2 = 30 - 20 = 10\text{mA}$$

$$\Rightarrow V = -(10\text{m})(100) = \boxed{-1\text{V}}$$

$$b) \quad 100 // 100 = 50\Omega \quad V = \frac{50}{150} (12) = \boxed{4\text{V}}$$

$$I = -\frac{12}{150} = \boxed{-80\text{mA}}$$

$$c) \quad I = -\frac{100}{300} (12\text{m}) = \boxed{-4\text{mA}}$$

$$V = I (200) = \boxed{-0.8\text{V}}$$


~~$$d) \quad I = \frac{12}{300} = 0.04\text{A}$$~~

~~$$V = -\frac{100}{300} (12) = -4\text{V}$$~~

~~$$V = -\frac{100}{300} (12) = \boxed{-6\text{V}}$$~~

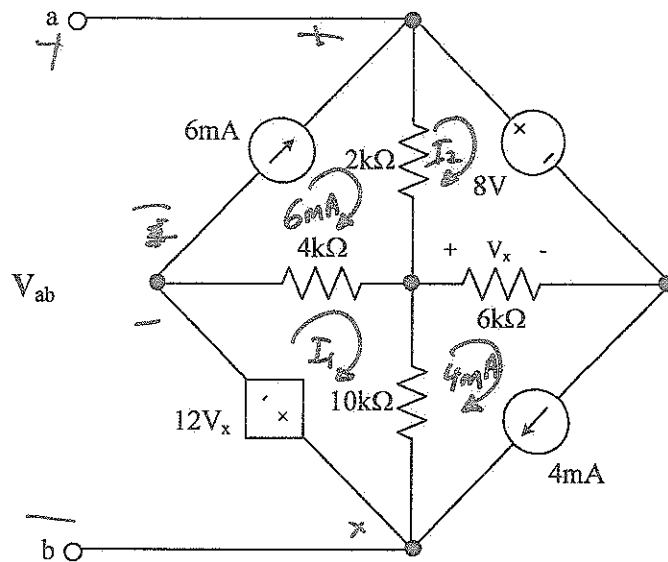Question 2 (11 marks)

Determine the value of V_{ab} using Mesh Analysis



$$12V_x + 4k(I_1 - 6m) + 10k(I_1 - 4m) = 0 \quad (1)$$

~~12V_x + 4k(I_1 - 6m) + 10k(I_1 - 4m) = 0~~

$$8 + 6k(I_2 - 4m) + 2k(I_2 - 6m) = 0 \quad (2)$$

$$\Rightarrow 8kI_2 = 28$$

$$I_2 = 3.5mA$$

$$V_x = (4m - I_2)(6k) = \underline{3V}$$

$$(1) \Rightarrow (12)(3) + 4k(I_1 - 6m) + 10k(I_1 - 4m) = 0$$


$$I_1 = 2mA$$

$$V_{ab} = 2k(6m - 3.5m) + 10k(2m - 4m) = \boxed{-15V}$$

2

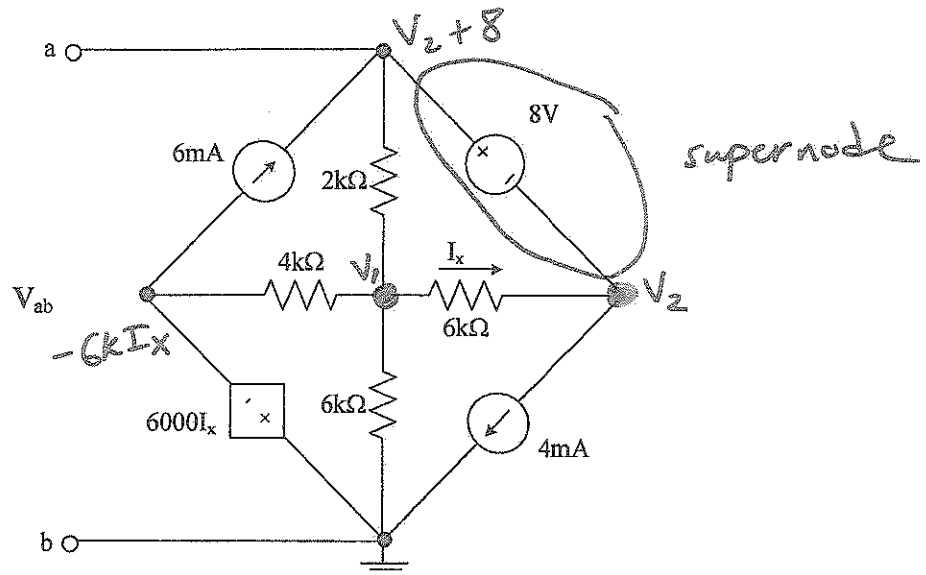Question 3 (11 marks)

Determine the value of V_{ab} using Node Analysis



$$I_x = \frac{V_1 - V_2}{6k}$$

Node equation at V_1

$$\frac{V_1 + 6kI_x}{4k} + \frac{V_1}{6k} + \frac{V_1 - V_2}{6k} + \frac{V_1 - (V_2 + 8)}{2k} = 0$$

$$\Rightarrow 16V_1 - 11V_2 = 48 \quad (1)$$

Node equation at supernode


$$\frac{(V_2 + 8) - V_1}{2k} - 6m + \frac{V_2 - V_1}{6k} + 4m = 0$$

$$\Rightarrow -4V_1 + 4V_2 = -12 \quad (2)$$

$$(1) \& (2) \Rightarrow \begin{aligned} V_1 &= 3 \\ V_2 &= 0 \end{aligned}$$

$$\boxed{V_{ab} = V_2 + 8 = 8V}$$

Question 4 (12 marks)

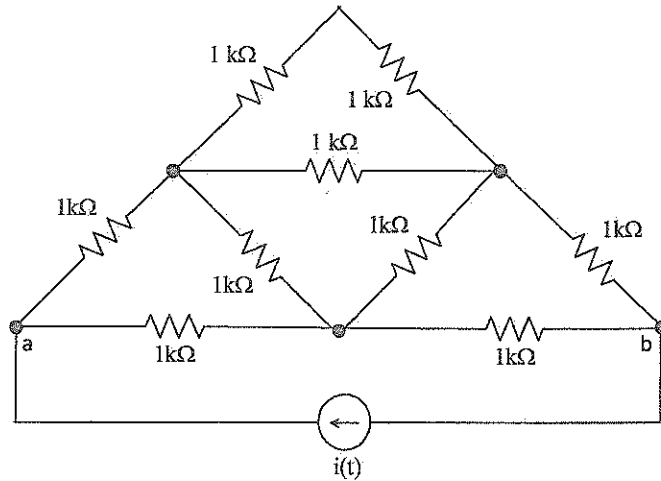

For the given circuit, determine:

- a. The equivalent resistance seen by the source between terminals 'a' and 'b'

The charge supplied by the current source is given by the expression $q(t) = -12e^{-2t}$ mC. The power delivered to the equivalent resistance is $p(t) = 2.4e^{-3t}$ W. Compute:

- b. The current $i(t)$ supplied by the source.
- c. The voltage across the current source (across terminals 'a' and 'b').
- d. The energy supplied by the source in the time interval $0 < t < 100$ ms.

a)

For balanced Y- Δ

$$Z_Y = \frac{Z_\Delta}{3}$$

$$Z_\Delta = 1k$$

$$\Rightarrow Z_Y = \frac{1}{3}k$$

$$R_{eq} = \frac{10}{9}k\Omega$$

Page 8 of 10

$$b) i(t) = \frac{dq}{dt} = 24e^{-2t} \text{ mA}$$

$$c) p = 2.4e^{-3t} \quad i = 24e^{-2t}$$

$$v = \frac{p}{i} = \frac{2.4e^{-3t}}{24e^{-2t} \text{ m}} = 100e^{-t} \text{ V}$$


$$d) E = \int_0^{100\text{m}} 2.4e^{-3t} dt$$

$$= \left[\frac{2.4}{-3} e^{-3t} \right]_0^{100\text{m}} = \left[-0.8 e^{-3t} \right]_0^{100\text{m}}$$

$$= \left[-5.33 + 0.8 \right] = -1.866 \text{ J}$$

$$0.207$$

Useful Equations:

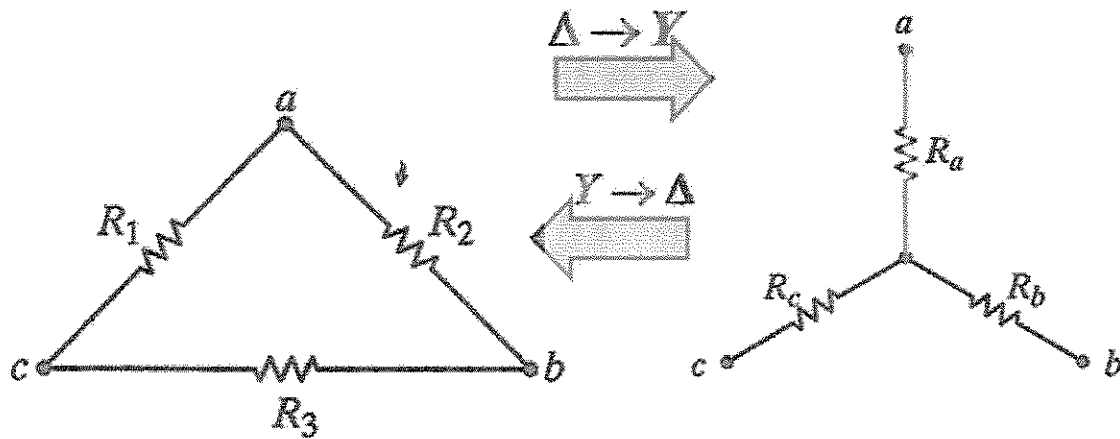

$$R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$$

$$R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$$

$$R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$$

$$R_1 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_b}$$

$$R_2 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_c}$$

$$R_3 = \frac{R_a R_b + R_b R_c + R_a R_c}{R_a}$$