

EECE 310 - Lecture 15

Outline


► **Small-Signal Operation and Models**

Small-Signal Operation and Models

- ▶ linear amplification can be obtained by biasing the MOSFET to operate in the saturation region and by keeping the input signal small
- ▶ we explore the small-signal operation
- ▶ MOS transistor is biased by applying a dc voltage V_{GS}
- ▶ input signal to be amplified, v_{gs} , is superimposed on the dc bias voltage V_{GS}
- ▶ output voltage is taken at the drain

The DC Bias Point

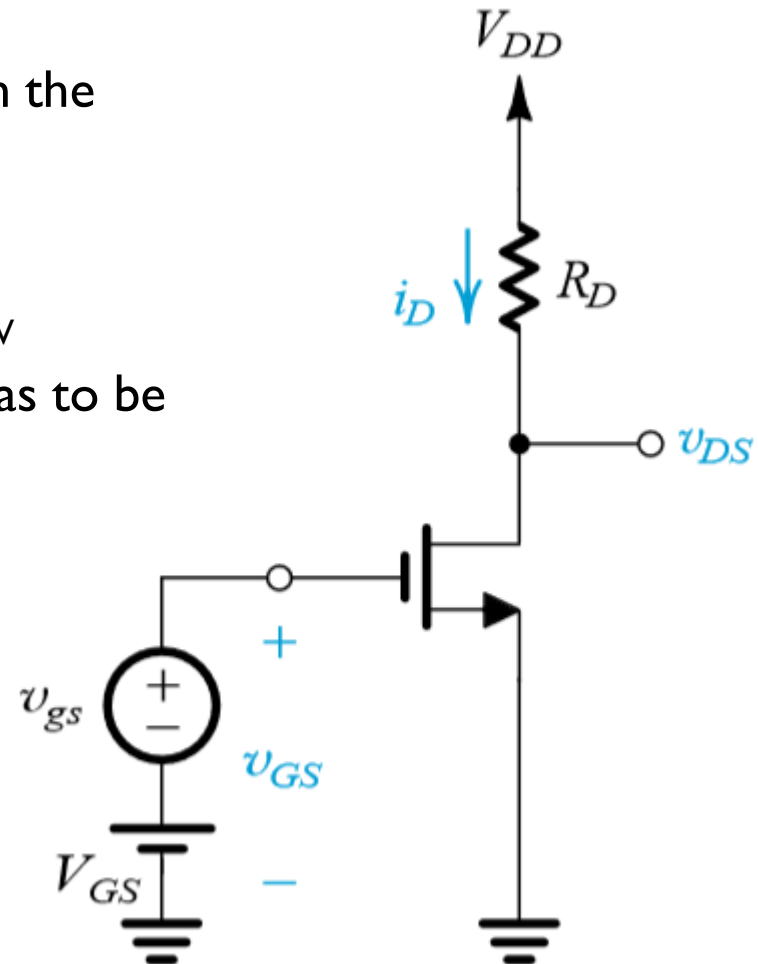- ▶ $I_D = \frac{1}{2} * k_n (V_{GS} - V_t)^2 = \frac{1}{2} * k_n V_{OV}^2$
- ▶ The overdrive voltage $V_{OV} = V_{GS} - V_t$ at which the MOSFET is biased to operate
- ▶ DC Voltage at drain $V_{DS} = V_{DD} - R_D I_D$
- ▶ For saturation-region operation $\rightarrow V_{DS} > V_{OV}$
- ▶ To allow for the required signal swing V_{DS} has to be sufficiently greater than V_{OV}



The Signal Current in the Drain Terminal

- ▶ Total instantaneous gate-to-source voltage will be: $v_{GS} = V_{GS} + v_{gs}$
- ▶ Total instantaneous drain current i_D ,

$$\begin{aligned} i_D &= \frac{1}{2} k_n (V_{GS} + v_{gs} - V_t)^2 \\ &= \underbrace{\frac{1}{2} k_n (V_{GS} - V_t)^2}_{I_D} + \underbrace{k_n (V_{GS} - V_t) v_{gs}}_{i_d} + \frac{1}{2} k_n v_{gs}^2 \end{aligned}$$

- ▶ where
 - ▶ I_D is the DC bias current
 - ▶ i_d represents a current component that is directly proportional to the input signal v_{gs}
 - ▶ The third term is a current component that is proportional to the square of the input signal. This component is undesirable because it represents nonlinear distortion
 - to reduce this distortion, the input signal should be kept small i.e. small signal

The Signal Current in the Drain Terminal

- ▶ So we need:

$$\frac{1}{2} k_n v_{gs}^2 \ll k_n (V_{GS} - V_t) v_{gs}$$

$$\rightarrow v_{gs} \ll 2 (V_{GS} - V_t) \rightarrow v_{gs} \ll 2V_{OV}$$

- ▶ If this small-signal condition is satisfied, we may neglect the last term

$$\rightarrow i_D \approx I_D + i_d \quad \text{where } i_d = k_n (V_{GS} - V_t) v_{gs}$$

- ▶ MOSFET transconductance:

$$g_m \equiv i_d / v_{gs} = k_n (V_{GS} - V_t) \rightarrow g_m = k_n V_{OV}$$

- ▶ It can be shown that $g_m = 2I_D/V_{OV}$ (even with channel length modulation)
- ▶ g_m is equal to the slope of the i_D - v_{GS} characteristic at the bias point,

$$g_m \equiv \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{v_{GS} = V_{GS}}$$

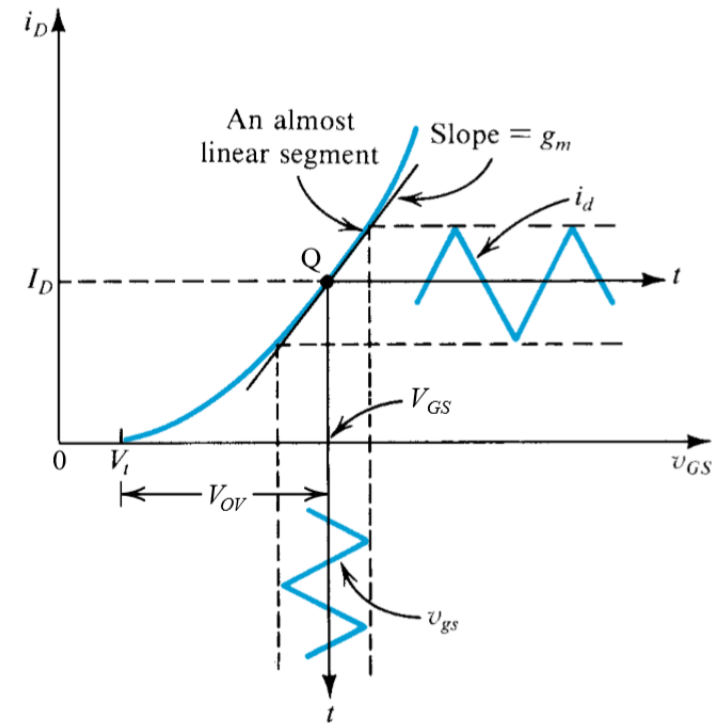


Figure 5.35 Small-signal operation of the MOSFET amplifier.

The Voltage Gain

- ▶ $v_{DS} = V_{DD} - R_D i_D$

- ▶ Under small signal condition:

$$v_{DS} = V_{DD} - R_D (I_D + i_d) \quad \rightarrow \quad v_{DS} = V_{DS} - R_D i_d$$

$$\rightarrow v_{ds} = -i_D R_D = -g_m v_{gs} R_D$$

$$\rightarrow A_v \equiv v_{ds} / v_{gs} = -g_m R_D$$

The minus sign indicates that the output signal v_{ds} is 180° out of phase with respect to the input signal v_{gs}

The Voltage Gain

- ▶ The input signal is assumed to have a triangular waveform
- ▶ amplitude $\ll 2(V_{GS} - V_t)$, the small-signal condition (**for linear operation**)
- ▶ For saturation region at all times →
 - a. minimum value of v_{DS} should not fall below the corresponding value of v_{GS} by more than V_t
 - b. maximum value of v_{DS} should be smaller than V_{DD} ; (otherwise cutoff region and the peaks of the output signal waveform will be clipped off)

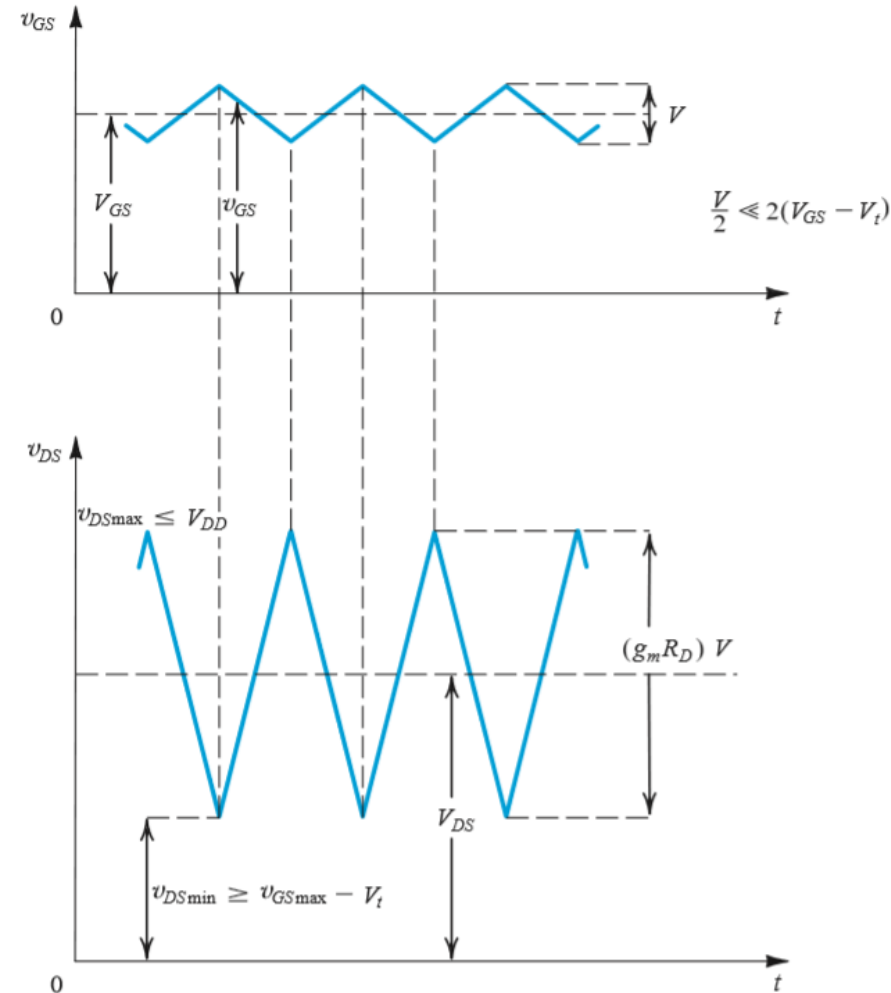


Figure 5.36 Total instantaneous voltages v_{GS} and v_{DS} for the circuit in Fig. 5.34.

Separating the DC Analysis and the Signal Analysis

- ▶ Under the small-signal approximation
 - signal quantities are superimposed on dc quantities
- ▶ total drain current i_D = equals the dc current I_D plus the signal current i_d
- ▶ total drain voltage $v_{DS} = V_{DS} + v_{ds} \dots$
- ▶ → the analysis and design can be greatly simplified by:
separating dc (bias calculations) from small-signal calculations
→
 1. Establish a stable dc operating point and calculate all dc quantities
 2. Perform signal analysis ignoring dc quantities

Steps for Analysis

1. DC Analysis: Assume signal quantities are zeros – Find I_D, V_{GS}, V_{DS}
(Capacitors open circuits)
2. Find g_m
3. Signal Analysis: Assume DC quantities are zeros –
DC Voltage supplies are short circuits –
DC current sources are open circuits –
Capacitors are short circuits
- 3.5 Replace MOSFETs by small signal Model
4. Find i_d and other quantities
5. $i_D = I_D + i_d$

Small-Signal Equivalent-Circuit Models

- ▶ From a signal point of view, the FET behaves as a voltage-controlled current source

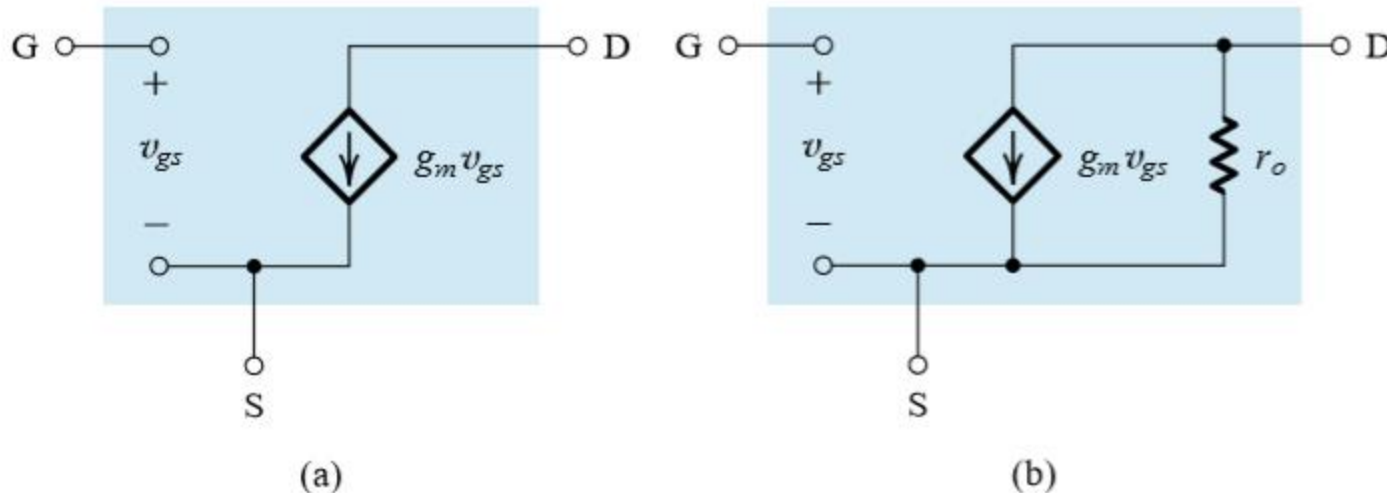


Figure 5.37 Small-signal models for the MOSFET: (a) neglecting the dependence of i_D on v_{DS} in saturation (the channel-length modulation effect); and (b) including the effect of channel-length modulation, modeled by output resistance $r_o = |V_A|/I_D$.

- ▶ where $V_A = 1/\lambda$ is a MOSFET parameter proportional to the channel length
- ▶ Voltage gain: $A_v \equiv v_{ds}/v_{gs} = -g_m (R_D || r_o)$
- ▶ $g_m = 2I_D/V_{OV}$

Example

Analyze this amplifier circuit to determine:


- ▶ small-signal voltage gain
- ▶ input resistance
- ▶ largest allowable input signal

Given:

$$V_t = 1.5 \text{ V}; k'_n(\text{W/L}) = 0.25 \text{ mA/V}_2;$$

$$V_A = 50 \text{ V}$$

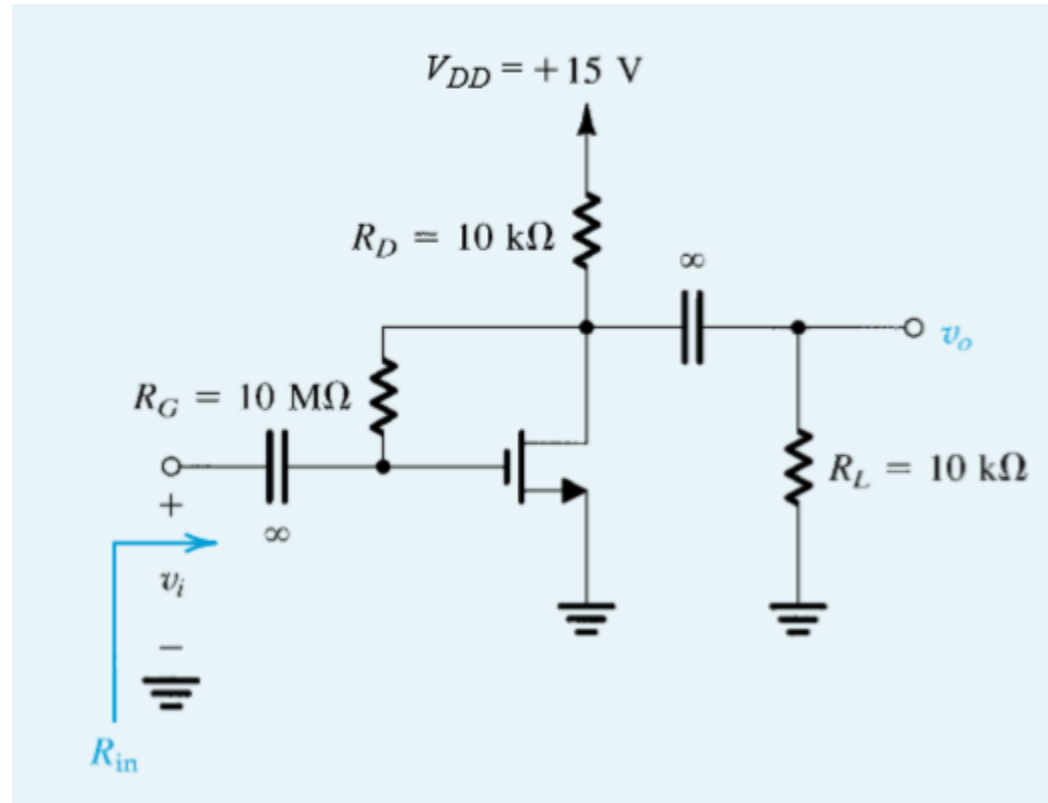
Assume the coupling capacitors to be sufficiently large so as to act as short circuits at the signal frequencies of interest.



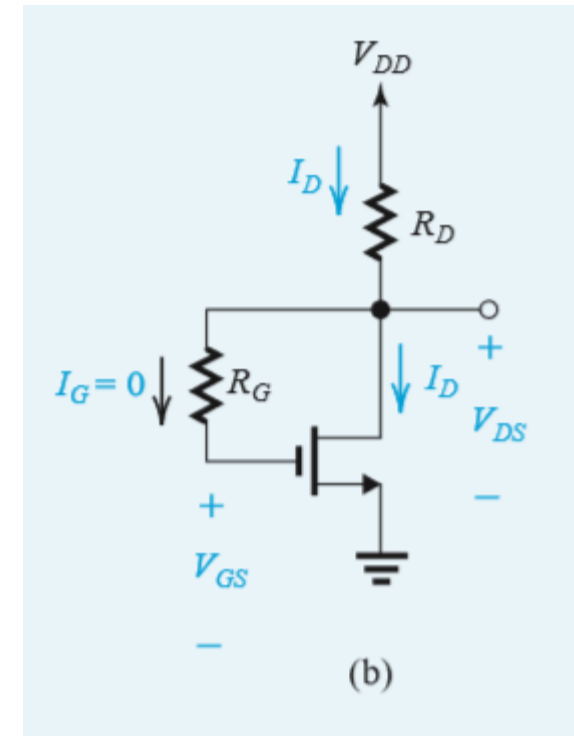Example

Step 1: DC Analysis

- ▶ Determine the dc operating point
- ▶ eliminate the input signal v_i ,
- ▶ Open circuit the two coupling capacitors
- ▶ $I_G=0 \rightarrow V_{GS}=V_{DS}=V_{DD}-R_D I_D \rightarrow I_D = (V_{DD}-V_{DS})/R_D$
- ▶ SAT: $I_D = \frac{1}{2} * k_n (V_{GS}-V_t)^2 (1+\lambda V_{DS})$
- ▶ Solving the two equations:
- ▶ $I_D=1.06\text{mA}$ and $V_{DS} = V_{GS} = 4.4 \text{ V}$
- ▶ And $V_{OV} = 4.4 - 1.5 = 2.9 \text{ V}$



Example


Step 2: small-signal analysis

- ▶ replace coupling capacitors with short circuits

- ▶ Replace DC voltage supply with a short circuit to ground.

- ▶ $g_m = k_n V_{OV} = 0.25 \times 2.9 = 0.725 \text{ mA/V}$

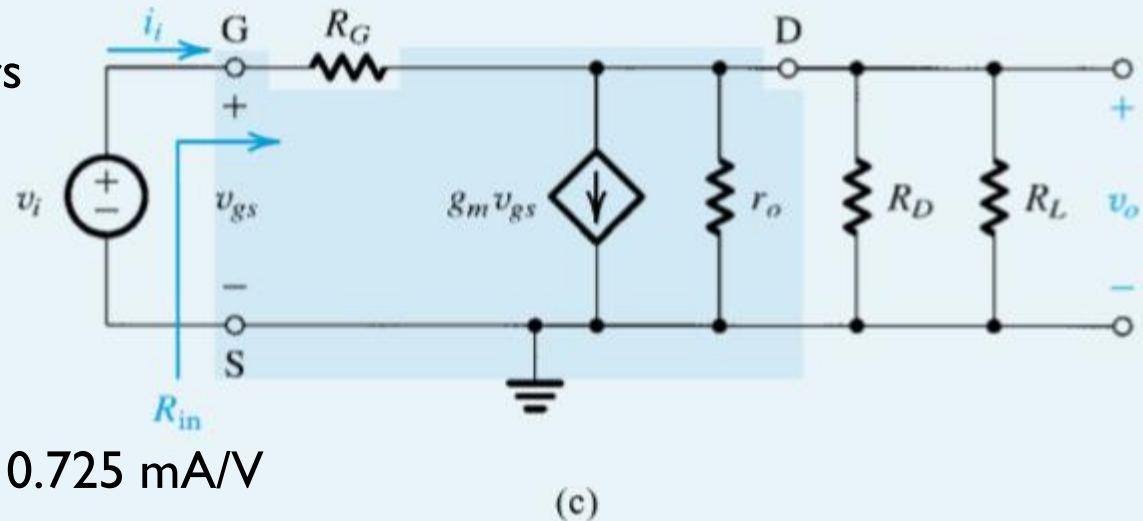- ▶ $r_o = V_A / I_D = 50 / 1.06 = 47 \text{ K}\Omega$



Example

▶ $R'_L = R_L || R_D || r_o = 10 || 10 || 47 = 4.52 \text{ k}\Omega$

▶ $v_o = (i_i - g_m v_{gs}) R'_L$

▶ $i_i = (v_{gs} - v_o) / R_G$

▶ $\rightarrow A_v = v_o / v_i =$

$A_v = -g_m R'_L [1 - (1 / g_m R_G) / (1 + (R'_L / R_G))]$

▶ Since R_G is very large


$A_v \approx -g_m R'_L = -3.3 \text{ V/V}$

▶ $R_{in} = v_i / i_i = v_{gs} / i_i = R_G / (1 + g_m R'_L) = 2.33 \text{ M}\Omega$

▶ Largest allowable input signal is constrained by the need to keep the transistor in saturation at all times $\rightarrow v_{DS} \geq v_{GS} - V_t \rightarrow v_{DSmin} = v_{GSmax} - V_t$


▶ $\rightarrow V_{DS} - |A_v| v_i = V_{GS} + v_i - V_t$ But $V_{DS} = V_{GS} \rightarrow v_i = V_t / (|A_v| + 1) \rightarrow v_i = 1.5 / (3.3 + 1) = 0.35 \text{ V}$

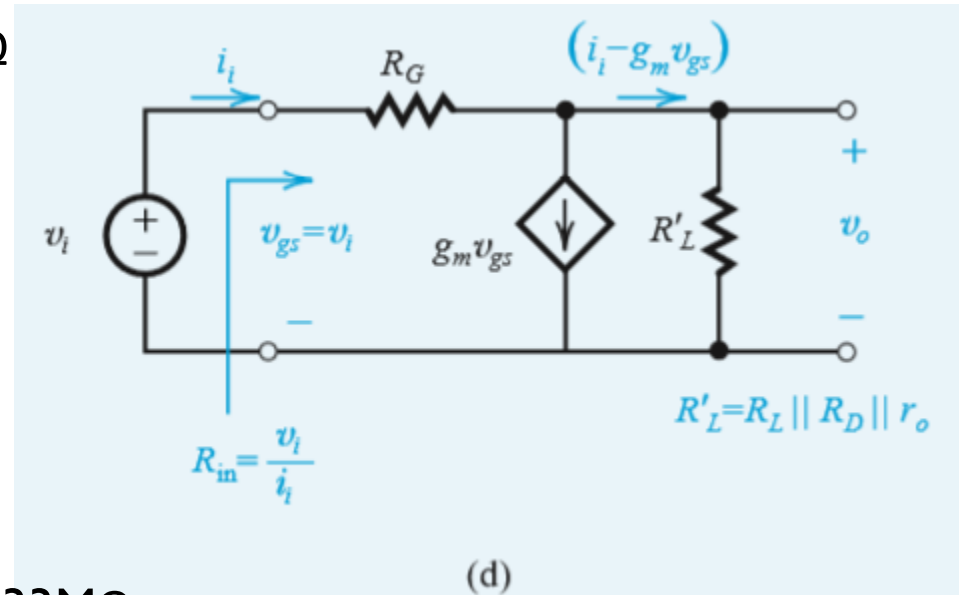▶ Check $V_{GS} > V_t \rightarrow 4.4 \pm 0.35 > 1.5 \rightarrow$ we will never reach cutoff region.



Exact Calculations

- ▶ Including the Channel Length Modulation and the Body Effect
- ▶ $i_D = f(v_{GS}, v_{DS}, v_{BS}) = g_m v_{gs} + g_{ds} v_{ds} + g_{mb} v_{bs}$
- ▶ $g_{mb} = X g_m$ where $X = \frac{\delta}{2\sqrt{|-2\phi_F + V_{SB}|}}$

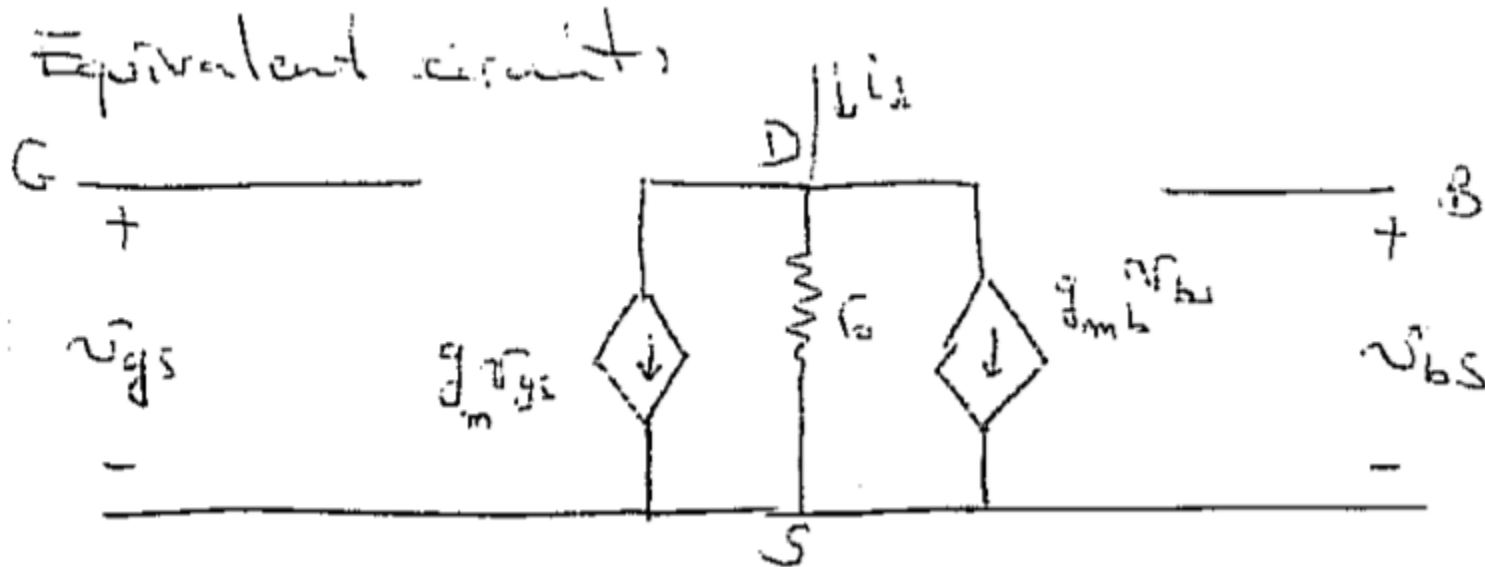

The T Equivalent-Circuit Model

All the previously discussed models are referred to as *π - Model*

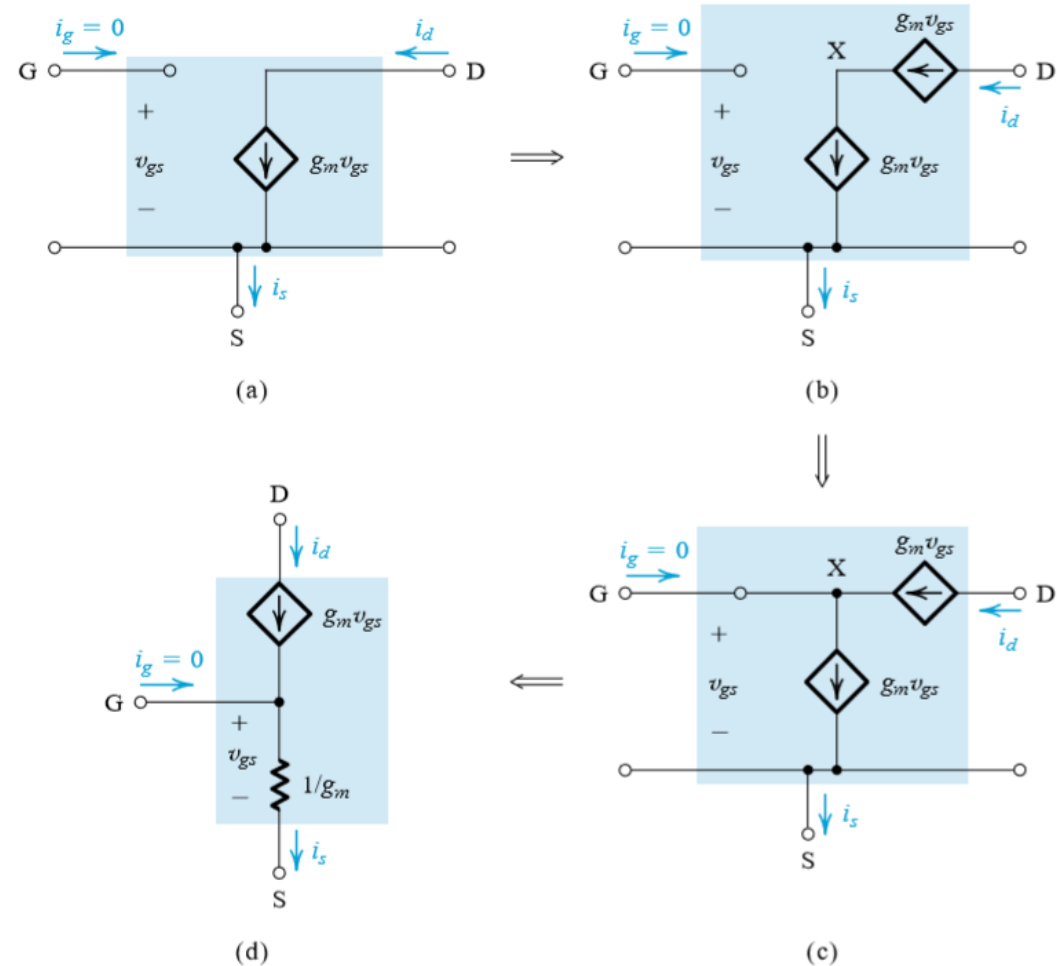


Figure 5.40 Development of the T equivalent-circuit model for the MOSFET. For simplicity, r_o has been omitted; however, it may be added between D and S in the T model of (d).

The T Equivalent-Circuit Model

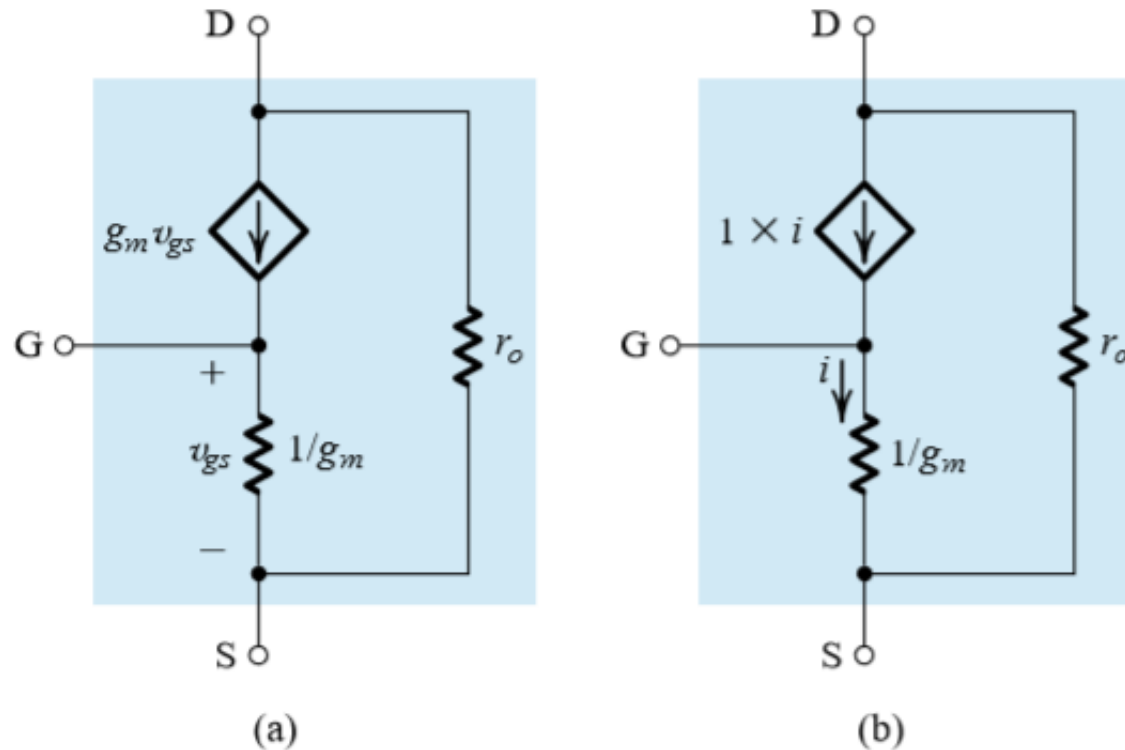


Figure 5.41 (a) The T model of the MOSFET augmented with the drain-to-source resistance r_o . (b) An alternative representation of the T model.

Small Signal Circuits

Table 5.3 Small-Signal Equivalent-Circuit Models for the MOSFET

Small-Signal Parameters

NMOS transistors

■ Transconductance:

$$g_m = \mu_n C_{ox} \frac{W}{L} V_{OV} = \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = \frac{2I_D}{V_{OV}}$$


■ Output resistance:

$$r_o = V_A / I_D = 1 / \lambda I_D$$

PMOS transistors

Same formulas as for NMOS *except* using $|V_{OV}|$, $|V_A|$, and replacing μ_n with μ_p .

Small-Signal Equivalent Circuit Models

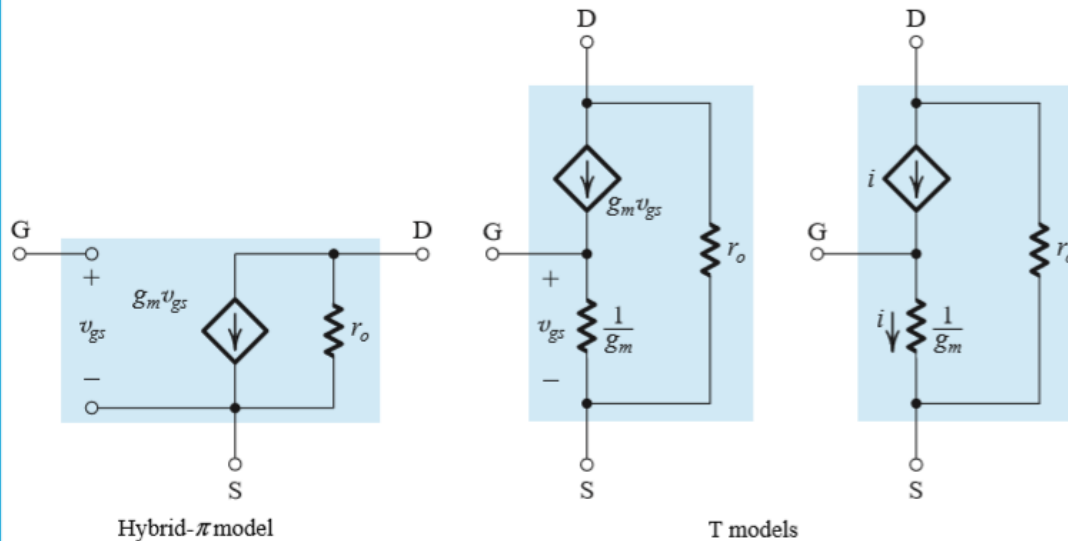

Thank you !