

EECE 310 - Lecture 14

Outline



▶ **MOSFET Biasing**

MOSFET BIASING


- ▶ An essential step in the design of a MOSFET amplifier circuit is the establishment of an appropriate dc operating point for the transistor.
- ▶ This is known as biasing or bias design.
- ▶ An appropriate **dc operating point** or **bias point** is characterized by:
 - ▶ stable and predictable I_D
 - ▶ V_{DS} that ensures operation in the **saturation region** for all expected input

Fixing V_{GS}

- ▶ Most straightforward approach
- ▶ Fix V_{GS} to provide the desired I_D
- ▶ can be derived from V_{DD} through the use of an appropriate voltage divider
- ▶ NOT a good approach for biasing

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

 - ▶ values of V_t , C_{ox} , and (to a lesser extent) the aspect ratio vary widely among devices of supposedly the same size and type
- ▶ both V_t and μ_n depend on temperature \rightarrow (if V_{GS} is fixed) I_D becomes temperature dependent
- ▶ For the fixed value of V_{GS} , the resultant spread in the values of the drain current can be substantial




Fixing V_G and Connecting a Resistance in the Source

- ▶ Excellent biasing technique

$$V_G = V_{GS} + R_S I_D$$

 - ▶ The action of R_S works to keep I_D as constant as possible
- ▶ if $V_G \gg V_{GS} \rightarrow I_D$ will be determined by V_G and R_S
- ▶ if V_G not much larger than $V_{GS} \rightarrow R_S$ provides negative feedback and stabilizes the bias current I_D .
- ▶ I_D increases but V_G constant $\rightarrow V_{GS}$ must decrease. $\rightarrow I_D$ decreases back to bias



Fixing V_G and Connecting a Resistance in the Source

 



Figure 5.52 Biasing using a fixed voltage at the gate, V_G , and a resistance in the source lead, R_S : (a) basic arrangement; (b) reduced variability in I_D ; (c) practical implementation using a single supply; (d) coupling of a signal source to the gate using a capacitor C_{C1} ; (e) practical implementation using two supplies.

C_{C1} blocks dc and prevents disturbing dc bias point.

C_{C1} should be large enough to approximate a short circuit at all signal frequencies of interest

 
Example

- ▶ Design for $I_D = 0.5 \text{ mA}$.
- ▶ $V_t = 1 \text{ V}$
- ▶ $V_{DD} = 15 \text{ V}$.
- ▶ Calculate the percentage change in the value of I_D obtained when MOSFET is replaced with another unit having the same $k'_n W/L$ but $V_t = 1.5 \text{ V}$.



 
Example

- ▶ Rule of thumb for designing this classical biasing circuit we choose R_D and R_S to provide one-third of V_{DD} as a drop across each of R_D , the transistor (i.e., V_{DS}) and R_S .
- ▶ $V_{DD} = 15V \rightarrow V_S = 5V$ and $V_D = 10V$
- ▶ $\rightarrow R_D = (V_{DD} - V_D) / I_D = (15 - 10) / 0.5 = 10\text{ k}\Omega$ and $R_S = 5\text{ k}\Omega$
- ▶ $I_D = \frac{1}{2} * k'_n (W/L)(V_{GS} - V_t)^2 \rightarrow V_{GS} = 2V$
- ▶ $V_G = 7V$
- ▶ Choose $R_{G1} = 8\text{ M}\Omega$ and $R_{G2} = 7\text{ M}\Omega$
- ▶ Observe that the dc voltage at the drain (+10V) allow: for a positive signal swing of +5V (i.e., up to V_{DD}) and negative signal swing of -4V [i.e., down to $(V_G - V_t)$].



 
Example

- ▶ Observe that V_D (+10 V) allows for a positive signal swing of +5 V (up to V_{DD}) and a negative signal swing of -4 V [down to $(V_G - V_t)$].
- ▶ If NMOS is replaced with another having $V_t = 1.5$ V
- ▶ new $I_D = \frac{1}{2} \times I \times (V_{GS} - 1.5)^2$
- ▶ But $V_G = V_{GS} + I_D R_S \rightarrow 7 = V_{GS} + 10 I_D$
- ▶ $\rightarrow I_D = 0.455$ mA
- ▶ $\rightarrow \Delta I_D = 0.455 - 0.5 = -0.045$ mA
which is $-0.045/0.5 = -9\%$ change




Drain-to-Gate Feedback Resistor

- ▶ Simple and effective biasing arrangement
- ▶ large feedback resistance R_G (usually in the megohm range) forces the dc voltage at the gate to be equal to that at the drain (because $I_G = 0$)
 - ▶ $V_{GS} = V_{DS} = V_{DD} - R_D I_D \rightarrow V_{DD} = V_{GS} + R_D I_D$
 - ▶ The last term is the feedback effect
- ▶ if I_D increases $\rightarrow V_{GS}$ must decrease $\rightarrow I_D$ decrease again [a change that is opposite in direction to the one originally assumed]
- ▶ Thus the negative feedback or degeneration provided by R_G works to keep the value of I_D as constant as possible.

 


Circuit with two supplies

 - ▶ Two voltage sources
- ▶ $V_G + V_{GS} + I_D R_D - V_{SS} = 0$
- ▶ But $V_G = 0 \rightarrow V_{GS} = V_{SS} - I_D R_D$
- ▶ Same negative feedback or degeneration provided by R_G works to keep the value of I_D as constant as possible



Using a Constant-Current Source

 - ▶ most effective scheme
- ▶ R_G (usually in the mega ohm range)
 - ▶ establishes a dc ground at the gate
 - ▶ presents a large resistance to an input signal source that can be capacitively coupled to the gate.
- ▶ Resistor R_D establishes an appropriate dc voltage at the drain to allow for the required output signal swing while ensuring that the transistor always remains in the saturation region



(a)

Using a Constant-Current Source

 


Figure 5.55 (a) Biasing the MOSFET using a constant-current source I . (b) Implementation of the constant-current source I using a current mirror.

Using a Constant-Current Source

- ▶ A circuit for implementing the constant-current source I is shown in (b).

$$I_{D1} = \frac{1}{2}k'_n \left(\frac{W}{L}\right)_1 (V_{GS} - V_t)^2$$

$$I_{D1} = I_{\text{REF}} = \frac{V_{DD} + V_{SS} - V_{GS}}{R}$$

$$I = I_{D2} = \frac{1}{2}k'_n \left(\frac{W}{L}\right)_2 (V_{GS} - V_t)^2$$

$$I = I_{\text{REF}} \frac{(W/L)_2}{(W/L)_1}$$

- ▶ I is related to I_{REF} by the ratio of the aspect ratios of Q_1 and Q_2 .
- ▶ Current mirror is very popular in the design of IC MOS amplifiers

Thank you !