

Name: SOLUTION ID#: _____



SCHOOL OF ENGINEERING
Department of Electrical and Computer Engineering

ELE 302 – Electrical Circuits II Midterm Exam I – Fall 2013

Duration: 1 hour 30 mins
Start Time: 7:00 pm

Date: 06/11/2013
Dr. Dani Tannir


INSTRUCTIONS:

- Answer each of the following questions in the space provided.
- This is a closed-book exam.
- If something is not clear, state your assumptions.
- Programmable calculators are not allowed.
- The number of marks for each question is specified next to it.
- The total number of marks is 100.


1	2	3	4	Total
20/20	20/20	30/30	30/30	100

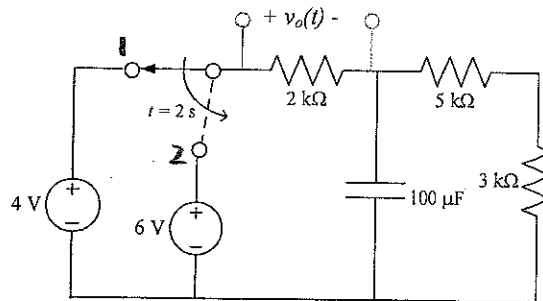Question 1 [20 marks]


In the following circuit, the switch was in position 1 for a long time before switching to position 2 at $t = 2$ s



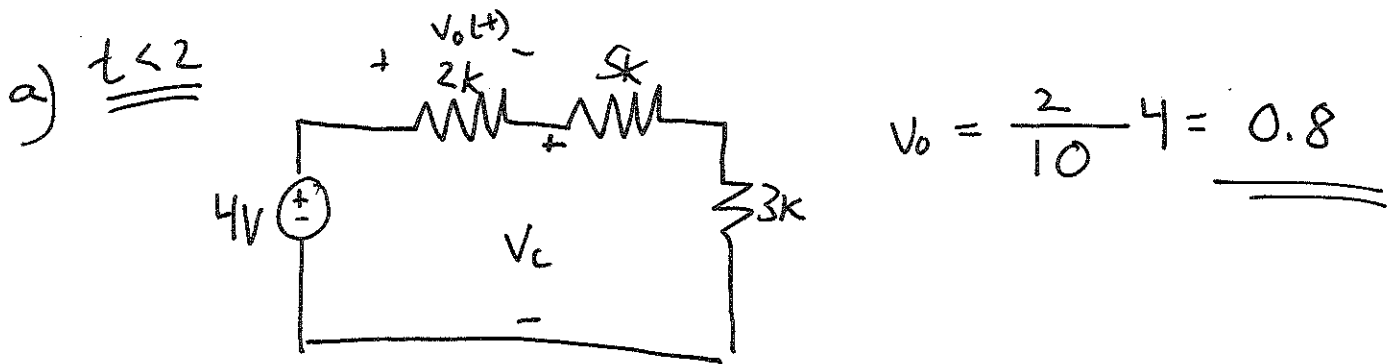
- ④ a. Determine $v_o(t)$ $t < 2$ s
- ⑫ b. Determine $v_o(t)$ $t > 2$ s
- ④ c. Sketch $v_o(t)$ for $t > 0$



b) $t = 2^-$ $V_c(2^-) = 3.2V$

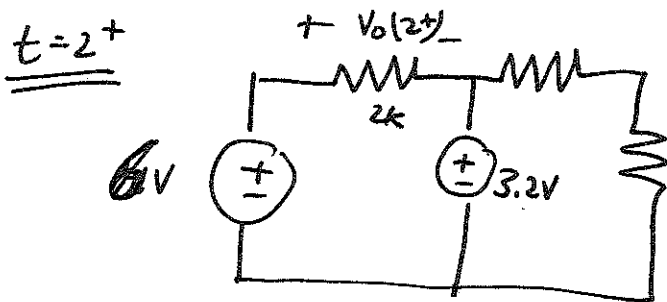


$$V_o(2^+) = 6 - 3.2 = 2.8V$$

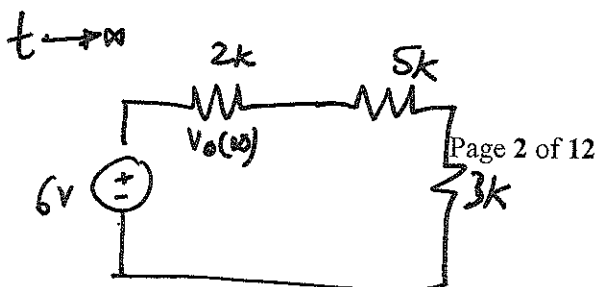

$$V_o(\infty) = \frac{2}{10} (6) = 1.2V$$

$$\tau = R_{th} C$$

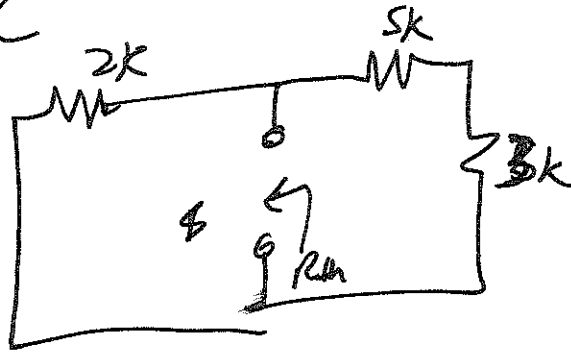

$$R_{th} = 2k \parallel (3k + 5k)$$


$$= 1.6k$$

$$\tau = (1.6k)(0.1m) = 0.16s$$

$$V_o(t) = V_o(\infty) + [V_o(2^+) - V_o(\infty)] e^{-\frac{(t-2)}{\tau}}$$

$$= 1.2 + [2.8 - 1.2] e^{-\frac{(t-2)}{0.16}}$$


$$= 1.2 + 1.6 e^{-\frac{(t-2)}{0.16}}$$

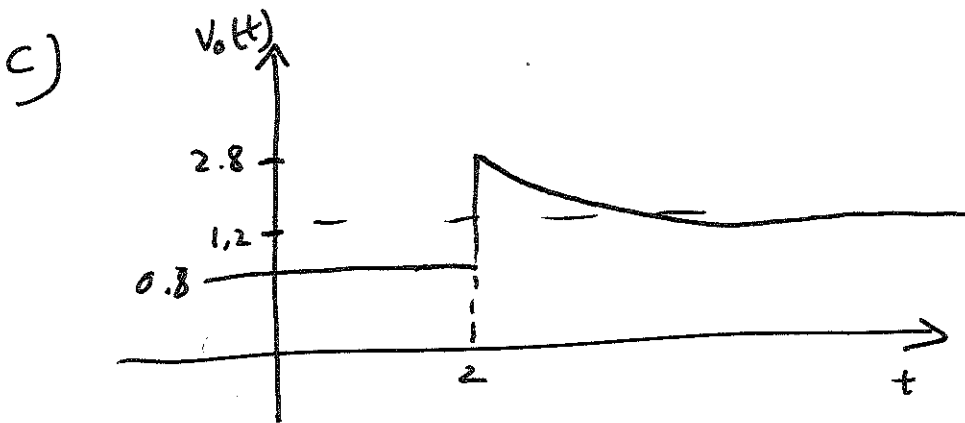

Question 2 [20 marks]

Determine the output voltage $v(t)$ in the following circuit.

Hint: Use phasors

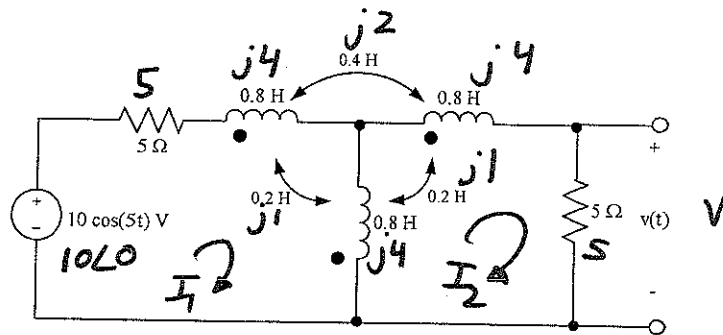

Mesh ①

$$10\angle 0 = 5I_1 + j4I_1 + j2I_2 - j1(I_1 - I_2) + j4(I_1 - I_2) - j1I_1 - j1I_2$$

$$10\angle 0 = (5 + j4 - j1 + j4 - j1)I_1 + (j2 + j1 - j4 - j1)I_2$$

$$\Rightarrow \boxed{10\angle 0 = (5 + j6)I_1 + (-j2)I_2} \quad \text{①}$$

Mesh ②

$$5I_2 + j4(I_2 - I_1) + j1I_2 + j1I_1 + j4I_2 + j2I_1 + j1(I_2 - I_1) = 0$$

$$(-j4 + j1 + j2 - j1)I_1 + (5 + j4 + j1 + j4 + j1)I_2 = 0$$

$$\boxed{-j2I_1 + (5 + j10)I_2 = 0} \quad \text{②}$$

$$I_1 = \frac{5 + j10}{j2} I_2 = (5 - j2.5)I_2$$

$$\Rightarrow 10\angle 0 = (40 + j17.5)I_2 - j2I_2$$

$$\Rightarrow I_2 = 0.23\angle -21.2^\circ$$


Page 5 of 12

$$\Rightarrow V = 1.165\angle -21.2^\circ$$

$$\Rightarrow v(t) = 1.165 \cos(st - 21.2^\circ) \text{ V}$$

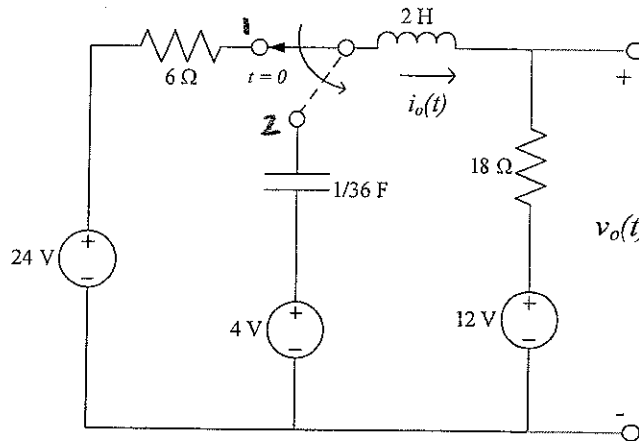Question 3 [30 marks]


The switch in the given network was in position 1 for a long time before moving to position 2 at $t = 0$.



- a) $i_L(0^-) \rightarrow 3$
 $v_L(0^-) \rightarrow 3$
 D.E. $\rightarrow 6$
 Roots $\rightarrow 3$
 expression $\rightarrow i_L(t) \rightarrow 2$
 $\rightarrow v_o(t) \rightarrow 3$
 $K_1, K_2, K_3 \rightarrow 6$


- a. Find $v_o(t)$ for $t > 0$
 b. Determine how much energy is stored in the inductor at $t = 50\text{ms}$?

b) 4

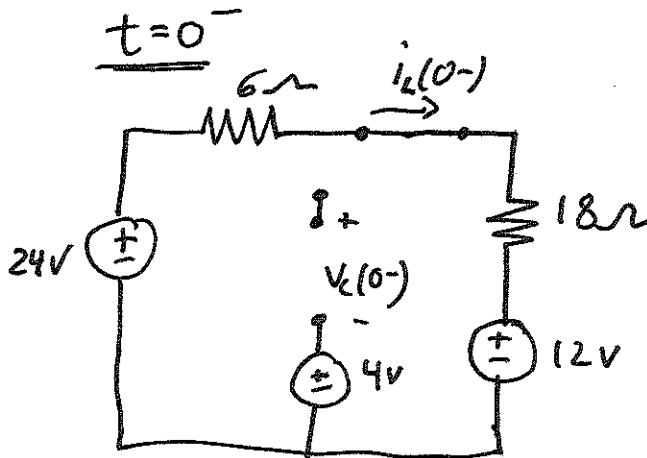

$$i_L(0^-) = \frac{24 - 12}{24} = 0.5\text{A}$$

$$v_L(0^-) = 0\text{V}$$

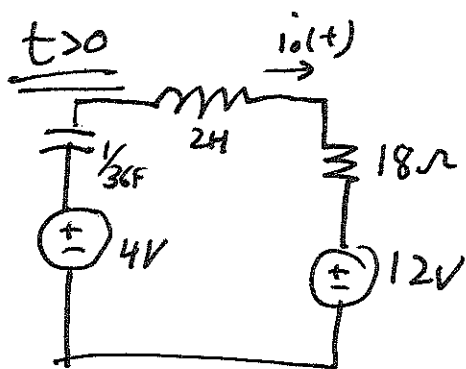


$$Ri_o + L \frac{di_o}{dt} + \frac{1}{C} \int i_o(t) dt = -8$$

$$18i_o + 2 \frac{di_o}{dt} + 36 \int i_o dt = -8$$

$$18 \frac{di_o}{dt} + 2 \frac{d^2 i_o}{dt^2} + 36 i_o = 0$$

$$\frac{d^2 i_o}{dt^2} + 9 \frac{di_o}{dt} + 18 i_o = 0$$

Page 7 of 12

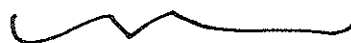

$$s^2 + 9s + 18$$

$s_1 = -3$
 $s_2 = -6$ } Real unequal roots
 over damped

$$i_0(t) = K_1 e^{-3t} + K_2 e^{-6t} + K_3$$

$$K_3 = i_0(0) = 0$$

$$i_0(0+) = K_1 + K_2$$

$$\frac{di_0(0+)}{dt} = -3K_1 - 6K_2$$

$$0,5 = K_1 + K_2$$

$$\begin{aligned} \frac{di_0(0+)}{dt} &= \frac{-8 - V_c(0+) - 18i_0(0+)}{2} \\ &= \frac{-8 - 0 - 9}{2} = -\frac{17}{2} \end{aligned}$$

$$0,5 = K_1 + K_2$$

$$-\frac{17}{2} = -3K_1 - 6K_2$$

$$K_1 = -1,833 \quad \left(-\frac{11}{6}\right)$$

$$K_2 = 2,333 \quad \left(\frac{14}{6}\right)$$

$$i_0(t) = -\frac{11}{6} e^{-3t} + \frac{14}{6} e^{-6t} \text{ A}$$

$$V_0(t) = 12 + 18i_0(t) = 12 - 33e^{-3t} + 42e^{-6t}$$

$$b) E = \frac{1}{2} L i_0^2$$

$$i_0(50\text{ms}) =$$

$$-1,577 + 1,729$$

$$0,151$$


ge 8 of 12

$$E = 0,0228 \text{ J}$$

Question 4 [30 marks]

The magnitude of the line-to-neutral voltage at the terminals of the balanced 3-phase load in the circuit shown below is **1200V**. At this voltage, the load is absorbing 500 kVA at 0.96 pf lag.

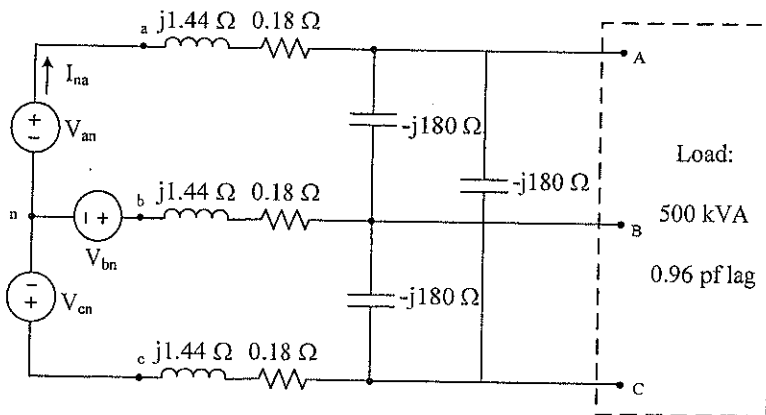
- (20) a. Use V_{AN} as the reference (i.e. phase angle of $V_{AN} = 0$) to compute the current I_{na} as labeled (express your answer in polar form).
 (10) b. Calculate the total complex power supplied by the ideal three-phase source.



Note (if required):

$|I_{line}| = \sqrt{3} |I_p|$
 $\theta_{line} = \theta_p - 30^\circ$

Line-phase current Relationship for Δ

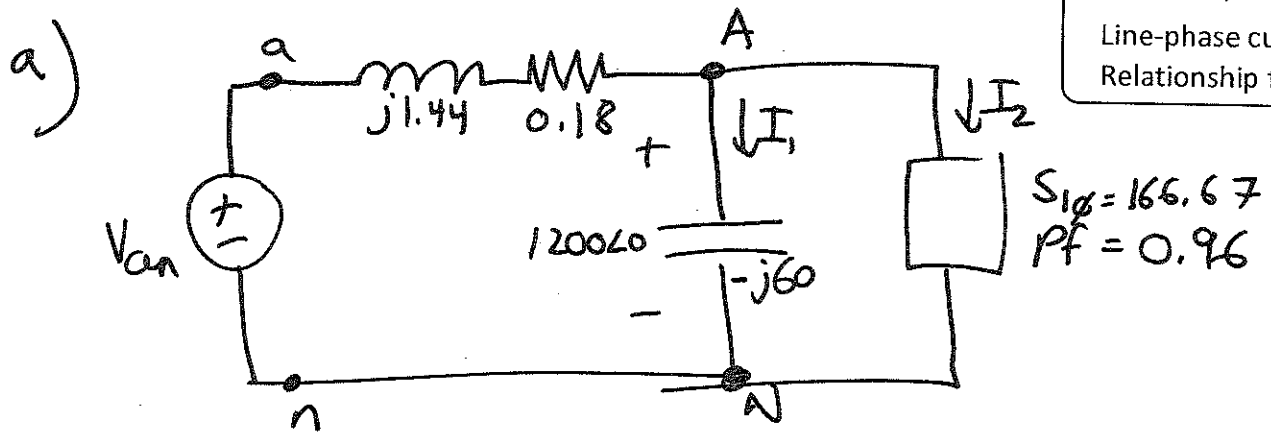

$$S = V_{rms} I_{rms}^* = 166.67 \angle 16.26 \text{ KVA}$$

$$I_2 = \left(\frac{166.67 \text{ K} \angle 16.26}{1200 \angle 0} \right)^*$$

$$= 133.3 - j38.89 \quad (138.8 \angle -16.3)$$

$$I_1 = \frac{V_{AN}}{-j60}$$

$$= \frac{1200 \angle 0}{-j60} = j20$$

$$I_{na} = I_1 + I_2 = 133.34 - j18.89$$

$$= 134.7 \angle -8.06^\circ \text{ A}$$

$$\begin{aligned}
 b) \quad S_{\text{supplied}} &= S_{TL} + S_L + S_C \\
 &= I_{na}^2 (0.18 + j1.44) + 166.67k \angle 16.26 \\
 &\quad + -j \left(\frac{1200^2}{60} \right) \\
 &= (134.7)^2 (0.18 + j1.44) + 166.67k \angle 16.26 - j24k \\
 &= 3265 + j26127.5 + \\
 &= 163270 + j48800 \\
 &= 163.3 + j48.8 \text{ kVA}
 \end{aligned}$$

$$\begin{aligned}
 &170.4 \text{ kVA} \angle 16.6^\circ \\
 S_{\text{total}} = 3 S_{\text{supplied}} &= \boxed{511.2 \text{ kVA} \angle 16.6^\circ}
 \end{aligned}$$