

Name: _____

ID#: _____



LEBANESE AMERICAN UNIVERSITY
Department of Electrical and Computer Engineering

ELE 302 – Electrical Circuits II
Midterm Exam 1


Duration: 1 hour
Start Time: 11:00 am

Date: 2/11/2011
Prepared by: Dr. Dani TANNIR

-
- **Answer each of the following questions in the space provided.**
 - **This is a closed-book exam.**
 - **Programmable Calculators are not allowed.**
 - **The number of marks for each question is indicated next to the question number.**
-

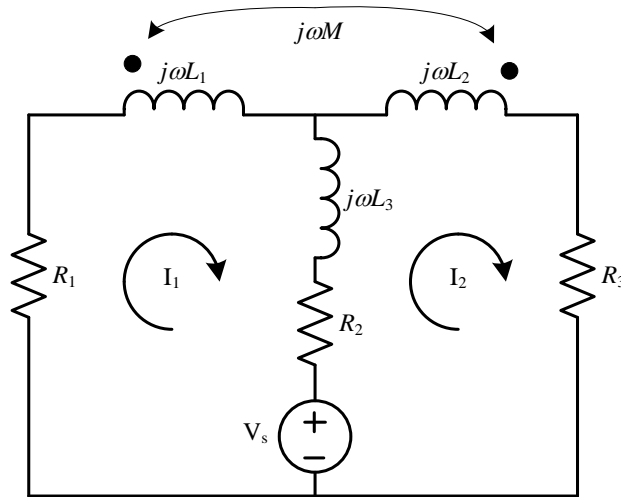
Question 1 (3 marks)

Write the mesh equations for the assigned mesh currents. Group the coefficients of each current variable together (Example: $K_1I_1 + K_2I_1 \rightarrow (K_1 + K_2)I_1$)



Question 2 (4 marks)


Consider the following Circuit

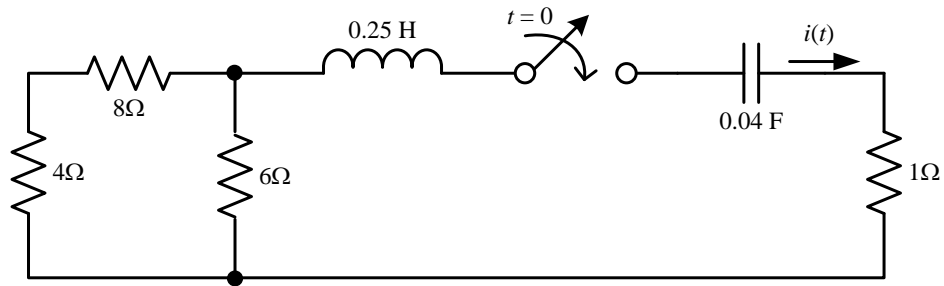

- Determine the Characteristic Equation in $i(t)$ for $t > 0$
- Determine the roots of the Characteristic Equation
- What type of damping does this circuit exhibit?

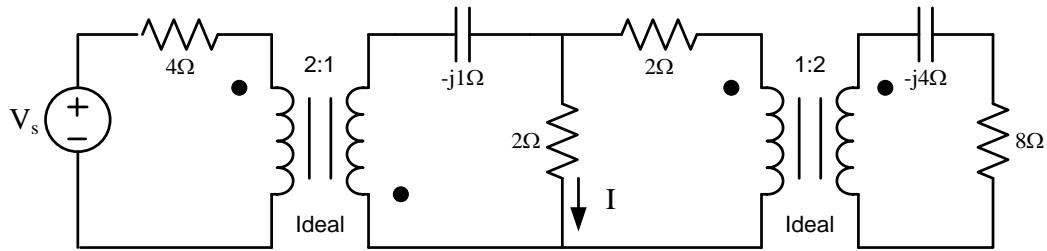Question 3 (6 marks)

In the following circuit, if $I = 4\angle 30^\circ$ A, Determine the value of V_s




Note The relations for an ideal transformer are as follows

$$V_1 = \pm \frac{V_2}{n}; I_1 = \pm nI_2; Z_1 = \frac{Z_2}{n^2}; n = \frac{N_2}{N_1}$$

Question 4 (7 marks)

Consider the following circuit

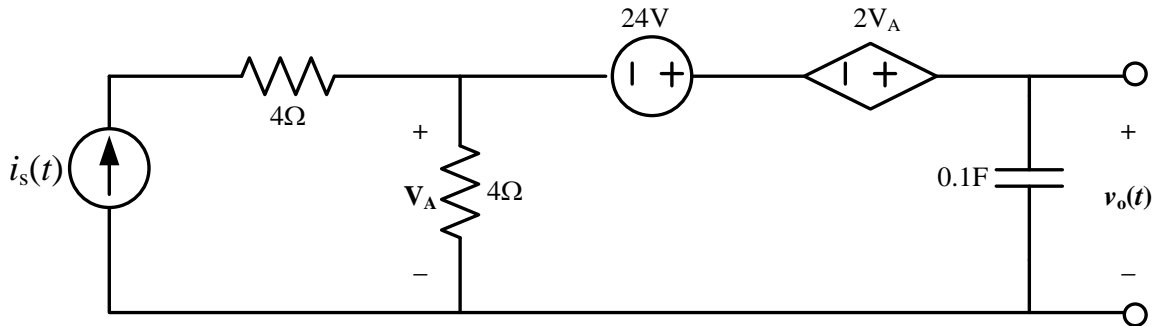

If $i_s(t)$ is defined as $i_s(t) = 3 - 3u(t-1)$, then

- Sketch $i_s(t)$ as defined
- Determine the general expression for the output voltage $v_o(t)$
- Sketch $v_o(t)$ as determined in part (b)

