

ELE 305: Introduction to Electrical Engineering Exam 1 – Spring 2018

Duration: **1 hour 30 minutes**
Start Time: 6:30 pm
Date: 13/3/2018

Dr. Jihad Fahs

Name: _____ ID#: _____



INSTRUCTIONS:

- Answer each of the following questions in the space provided. You can use both sides of each sheet for answers.
- This is a closed-book exam.
- If something is not clear, state your assumptions.
- Programmable calculators and smart devices are not allowed.
- The number of points for each question is specified next to it.
- The total number of points is 100.

1	2	3	4	5	6	Total
14	12	22	16	24	12	100

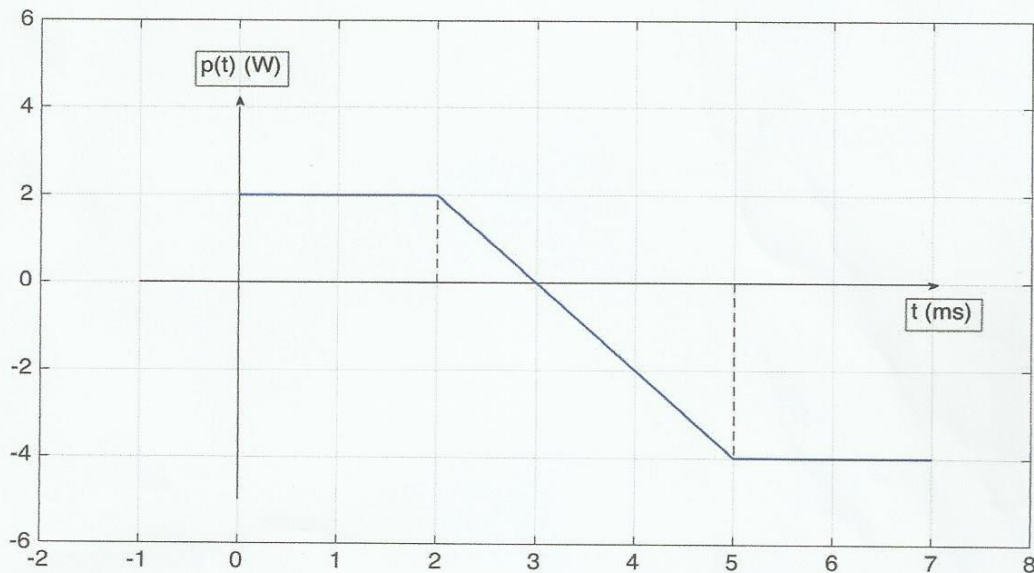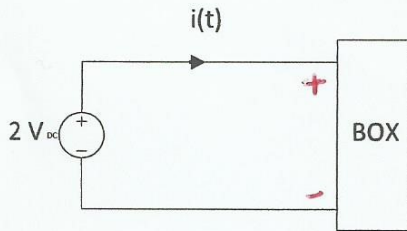Question 1 [14 points]

The power absorbed by the box is shown in Figure 1. Find and sketch the charge $q(t)$ that enters the box in the time interval $0 < t < 7$ ms.




$$P(t) = v(t) \times i(t) \Rightarrow i(t) = \frac{1}{2} P(t) = \begin{cases} 1 & 0 < t \leq 2 \\ -t + 3 & 2 < t \leq 5 \\ -4 & 5 < t \leq 7 \end{cases}$$

$$q(t) = \int_{t_0}^t i(t) dt + q(t_0)$$

$$\underline{0 < t \leq 2:} \quad q(t) = \int_0^t 1 dt + q(0) = t \quad \text{at } t=2 \Rightarrow q(2) = 2$$


$$\underline{2 < t \leq 5:} \quad q(t) = \int_2^t (-t + 3) dt + q(2) \\ = -\frac{t^2}{2} + 3t \Big|_2^t + 2 \\ = -\frac{t^2}{2} + 3t + \frac{4}{2} - 6 + 2 \\ = -\frac{1}{2}t^2 + 3t - 2 \\ \underline{\text{at } t=5:} \quad q(5) = -\frac{1}{2} \times 25 + 15 - 2 \\ = \frac{1}{2}$$
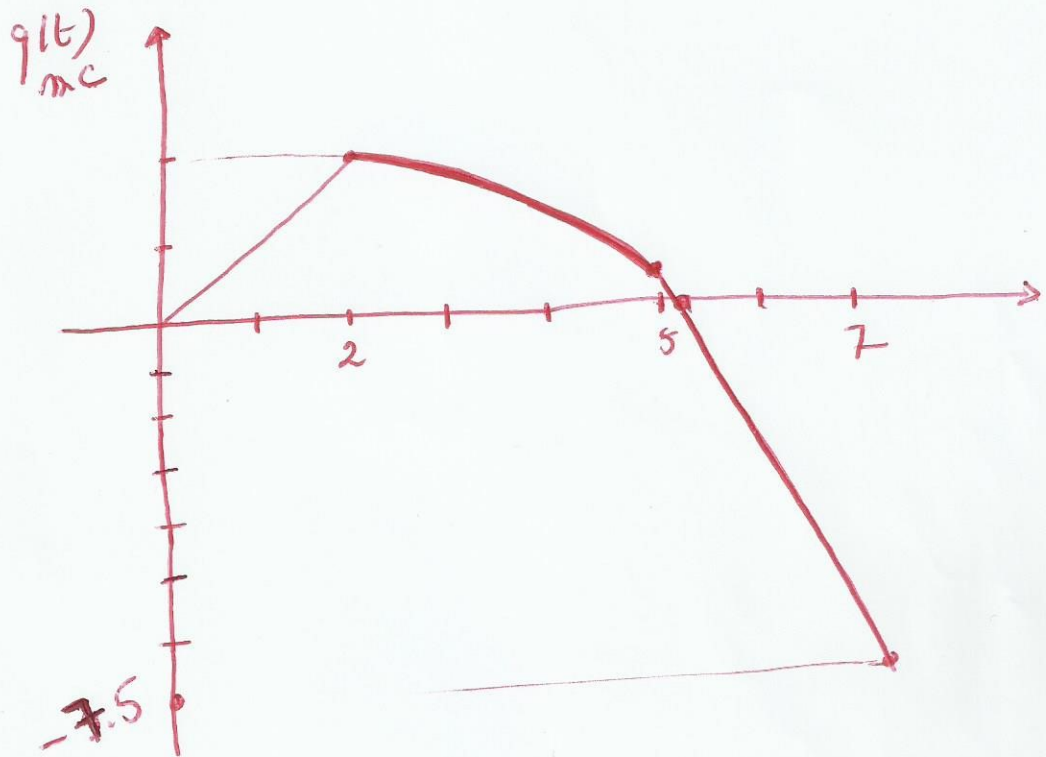
$$\begin{aligned}
 \underline{5 < t \leq 7}: q(t) &= \int_5^t i(t) dt + q(5) = \int_5^t -4 dt + \frac{1}{2} \\
 &= -4t/5 + \frac{1}{2} = -4t + 20 + \frac{1}{2} \\
 &= -4t + 20.5
 \end{aligned}$$




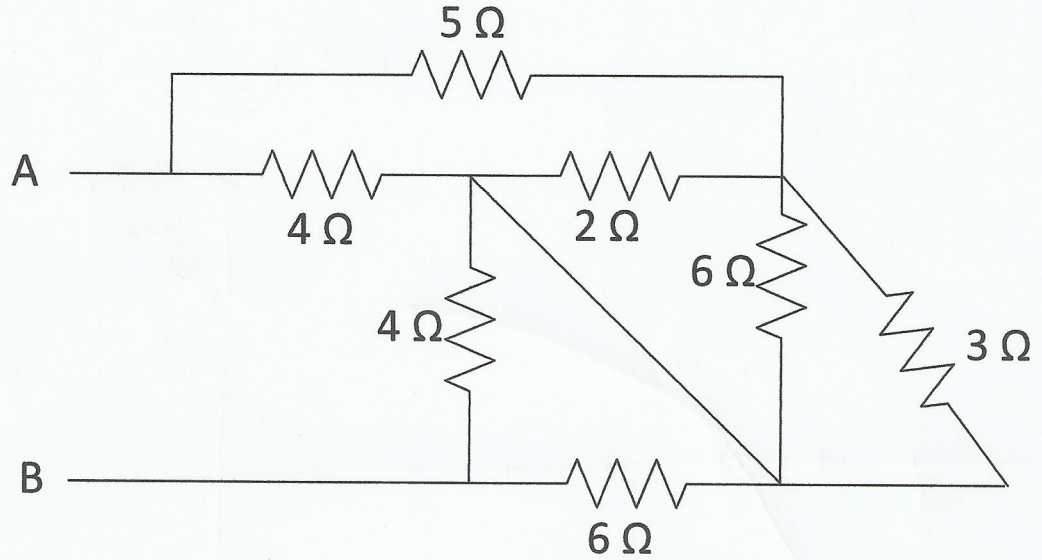Question 2 [12 points]

Find R_{AB} in the network in the below figure.




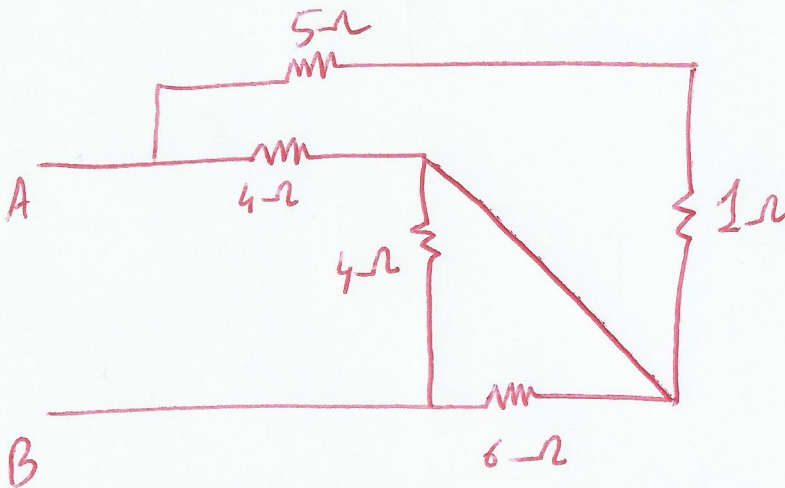$3 \parallel 6 \parallel 2 \rightarrow 1 \Omega$




$5 \parallel 1$ in series $\rightarrow 6 \Omega$

$4 \parallel 6 \rightarrow 2.4 \Omega$

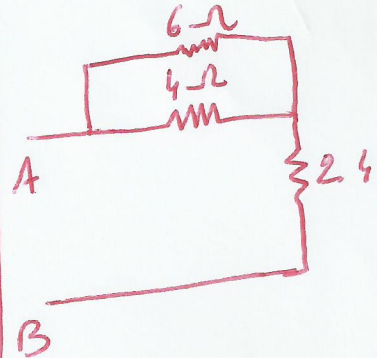


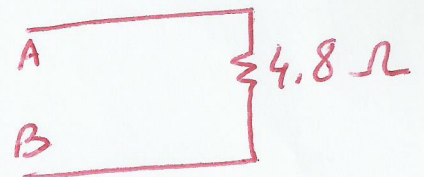$6 \parallel 4$ series $2.4 \rightarrow 4.8$



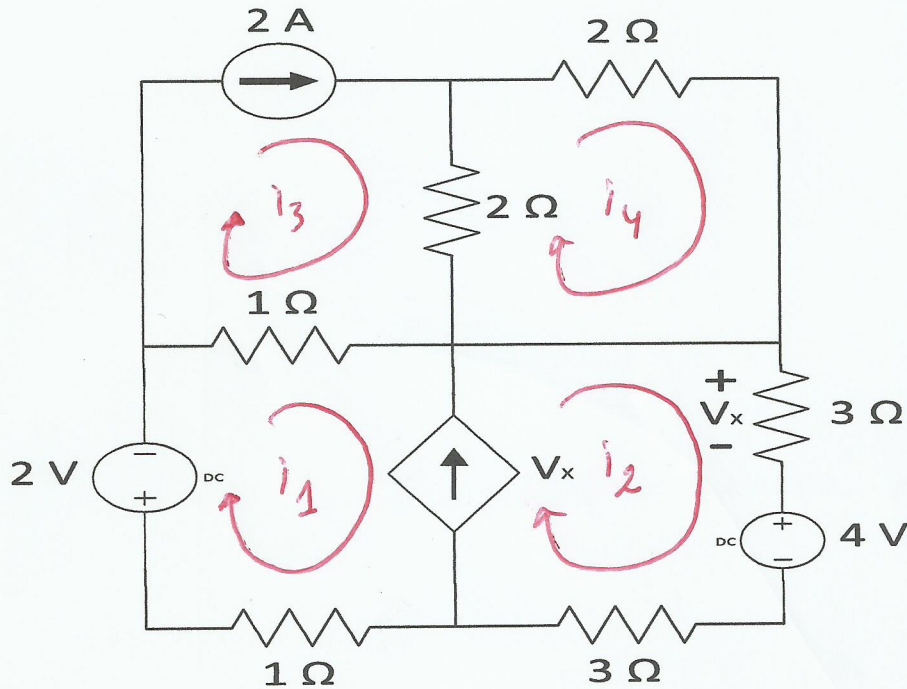Question 3 [22 points]

Use mesh analysis to calculate the power delivered by the 4V source in the network shown in the below figure.



Super-Mesh: $2 + 1(i_1 - i_3) + 3i_2 + 4 + 3i_2 + 1i_1 = 0$ ①

loop 3: $i_3 = 2A$

loop 4: $2(i_4 - i_3) + 2i_4 = 0 \Rightarrow 4i_4 = 2i_3 = 4 \Rightarrow i_4 = 1A$

Current Source: $i_2 - i_1 = V_x$
Controlling Variable: $V_x = 3i_2$
 $\Rightarrow i_1 = -2i_2$


① $\Rightarrow 2 + (i_1 - 2) + 6i_2 + 4 + 1 = 0$
 $\Rightarrow 2i_1 + 6i_2 + 4 = 0 \Rightarrow 2(-2i_2) + 6i_2 = -4 \Rightarrow$
 $2i_2 = -4 \Rightarrow i_2 = -2A$

and $i_1 = -2i_2 = 4A$


$P_{4V} = 4 \times i_2 = -8W$ (delivering 8W)

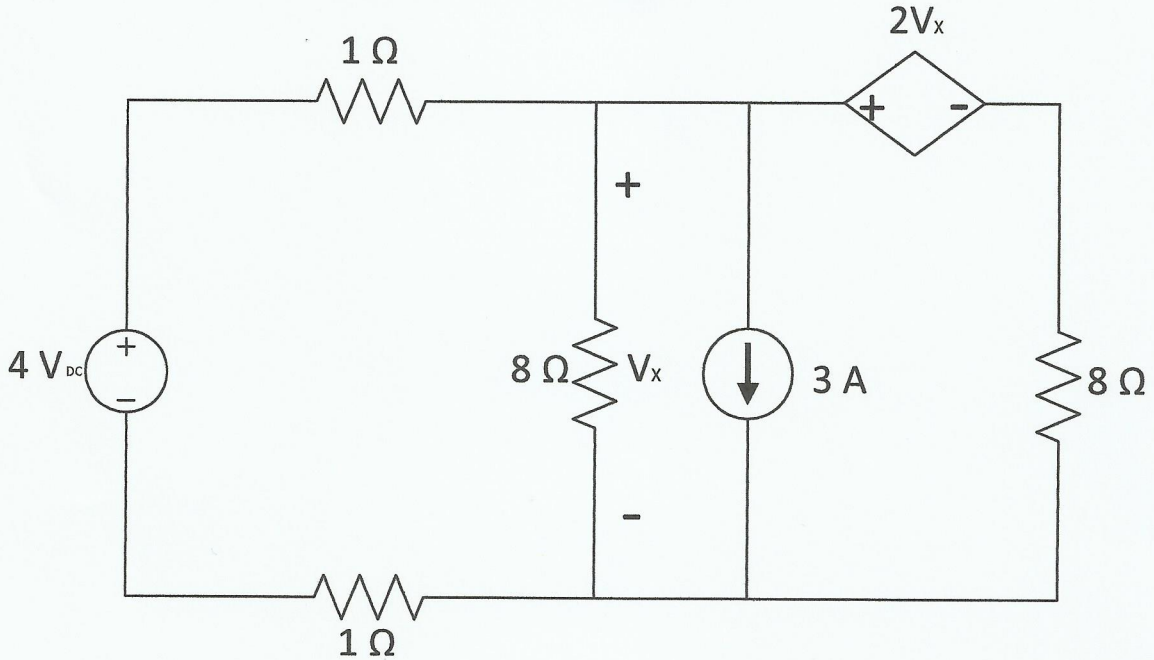Question 4 [16 points]

Consider the circuit shown below. Use superposition to find V_x .



4V ON, 3A OFF


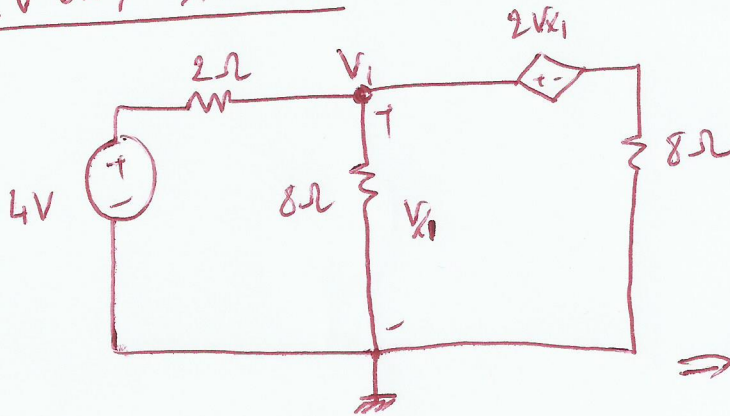


$$\left\{ \begin{aligned} \frac{V_1 - 4}{2} + \frac{V_1}{8} + \frac{V_1 - 2V_{x1}}{8} &= 0 \\ \text{Control variable: } V_1 &= V_{x1} \end{aligned} \right.$$

$$\Rightarrow \frac{V_1}{2} + \frac{V_1}{8} + \frac{V_1 - 2V_1}{8} = 2 \Rightarrow$$

$$\boxed{V_1 = 4V = V_{x1}}$$

4V OFF, 3A ON

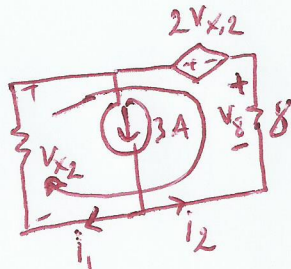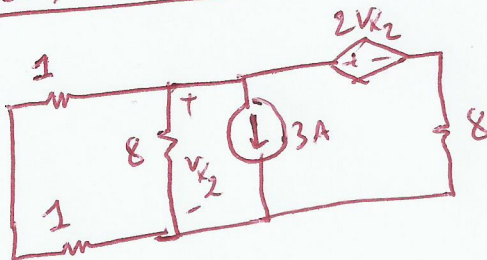

KVL: $-V_{x2} + 2V_{x2} + V_8 = 0$

$$\Rightarrow V_8 = -V_{x2} \quad (1)$$

KCL: $i_1 + i_2 = 3 \quad (2)$

Ohm's law: $V_{x2} = -1.6i_1$

$$V_8 = -8i_2$$

$$(1) \Rightarrow -8i_2 - 1.6i_1 = 0 \Rightarrow$$

$$i_2 = -\frac{1.6}{8}i_1 = -0.2i_1$$

$$(2) \Rightarrow i_1 - 0.2i_1 = 3 \Rightarrow i_1 = \frac{3}{0.8} = 3.75 \text{ A}$$


$$\Rightarrow V_{x2} = -1.6 \times 3.75 = -6V$$

Finally $V_x = V_{x1} + V_{x2} = 4 - 6 = -2V$

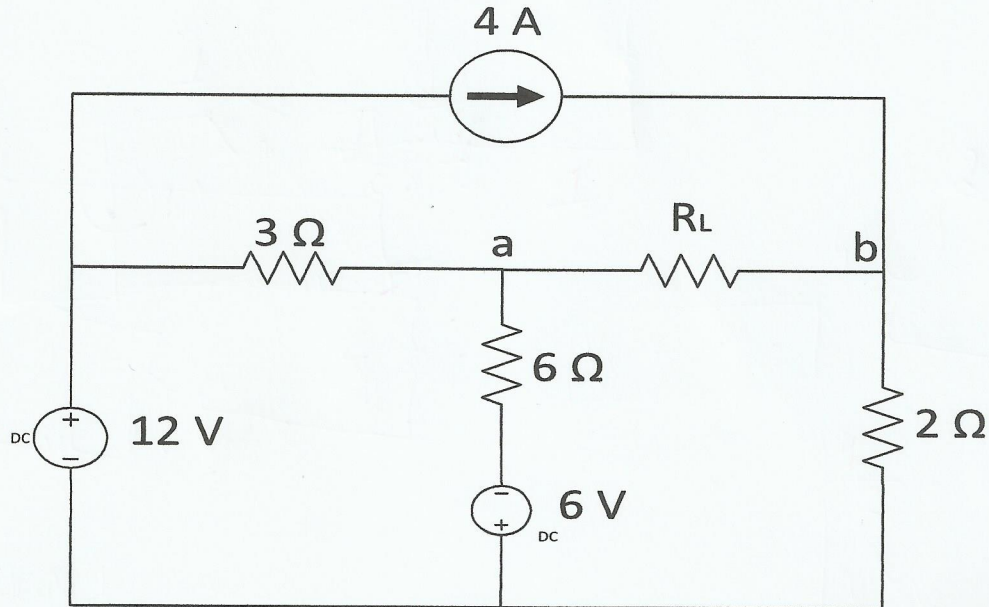
Question 5 [22 points]

Consider the network in the figure below.

- Find the Thevenin equivalent of the circuit between nodes a and b as seen by the resistance R_L .
- The resistance R_L absorbs 80% of the maximum power transfer. Find R_L .



Removing R_L :

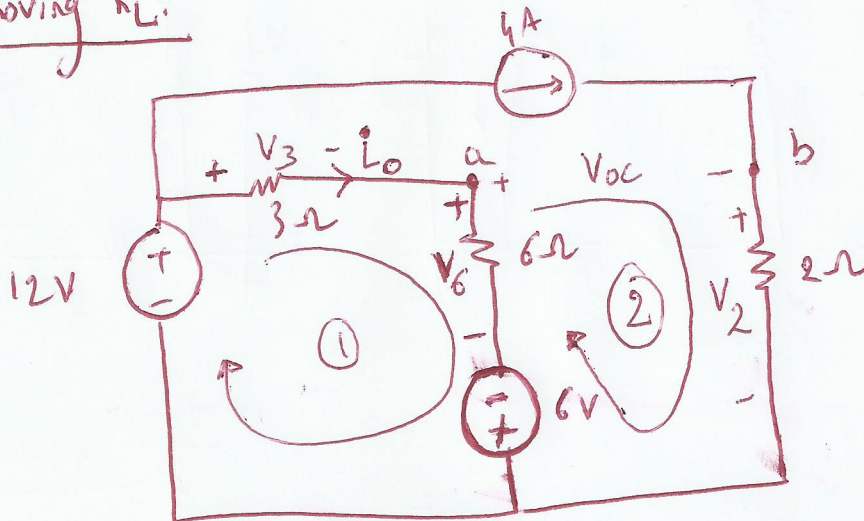

Finding V_{Th} : $V_{Th} = V_{oc} = V_{ab}$


kVL in ①: $-12 + 3i_o + 6i_o - 6 = 0 \Rightarrow 9i_o = 18 \Rightarrow i_o = 2A$

KVL in ②: $+6 - V_6 + V_{OC} + V_2 = 0$


$$\begin{aligned} \Rightarrow V_{OC} &= V_6 - V_2 - 6 \\ &= 6i_0 - 2 \times 4 - 6 \\ &= 6 \times 2 - 2 \times 4 - 6 \\ &= -2V \end{aligned}$$

Finding R_{Th} : Turning off the sources
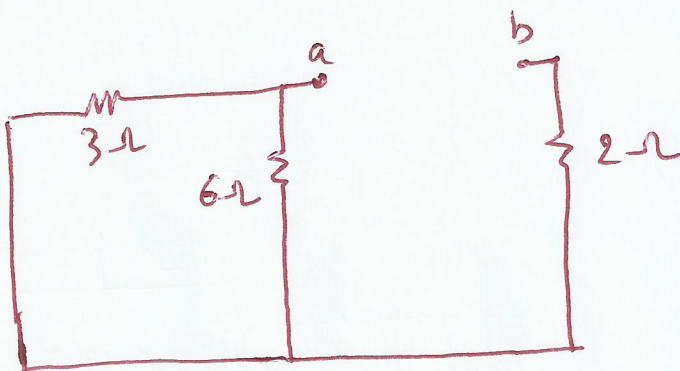
$$R_{Th} = R_{ab} = R_{eq} = 3 \parallel 6 + 2 = 4 \Omega$$




\Rightarrow the equivalent circuit

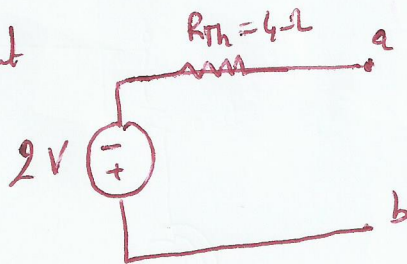

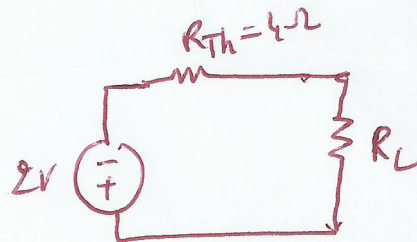b. We know that

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{4}{4 \times 4} = \frac{1}{4} \text{ W}$$

$$P_{RL} = \frac{V_{RL}^2}{R_L} = \left(\frac{2 \times R_L}{R_L + R_{Th}} \right)^2 \times \frac{1}{R_L}$$






$$\Rightarrow P_{RL} = 80\% P_{max} \Rightarrow$$

$$= 4 \frac{R_L^2}{(R_L + 4)^2} \times \frac{1}{R_L} = \frac{4 R_L}{(R_L + 4)^2}$$

$$\begin{aligned} \frac{4 R_L}{(R_L + 4)^2} &= 0.8 \times \frac{1}{4} \Rightarrow 20 R_L = (R_L + 4)^2 \\ \Rightarrow R_L^2 + 8 R_L + 16 &= 20 R_L \Rightarrow \begin{cases} R_L = 6 \sqrt{2} \Omega \\ \text{or} \\ R_L = 6 + \sqrt{2} \Omega \end{cases} \end{aligned}$$

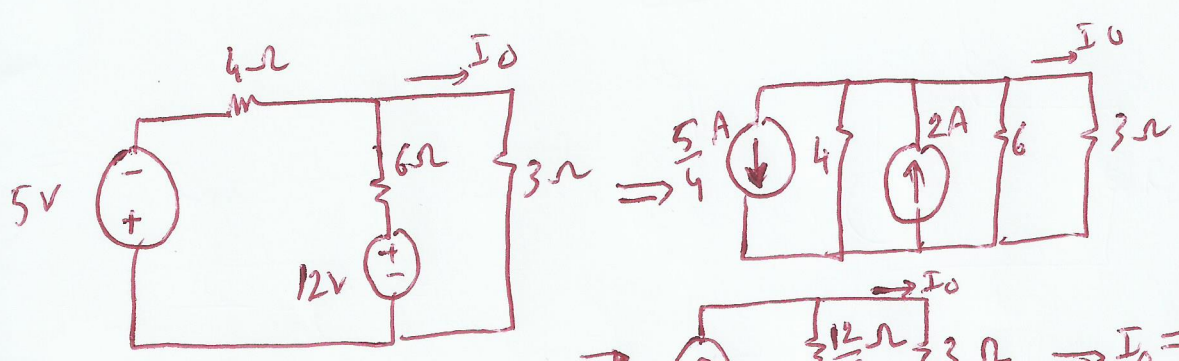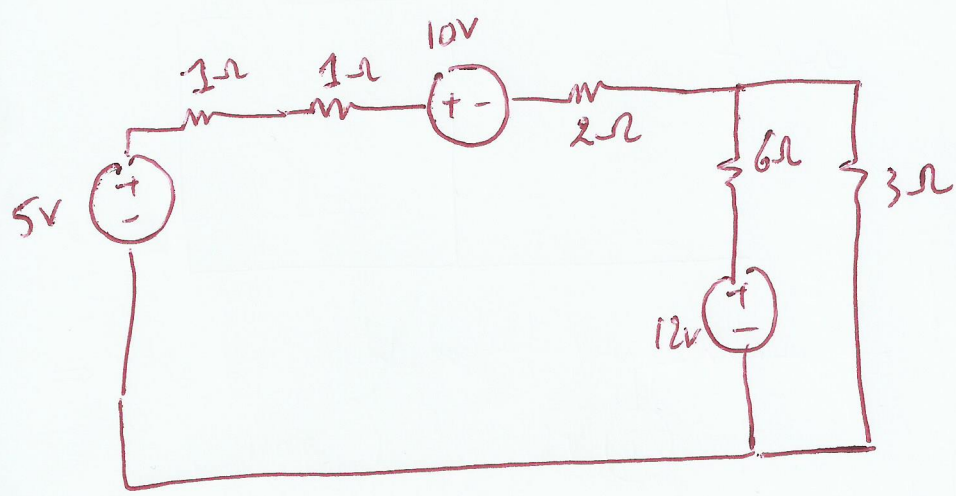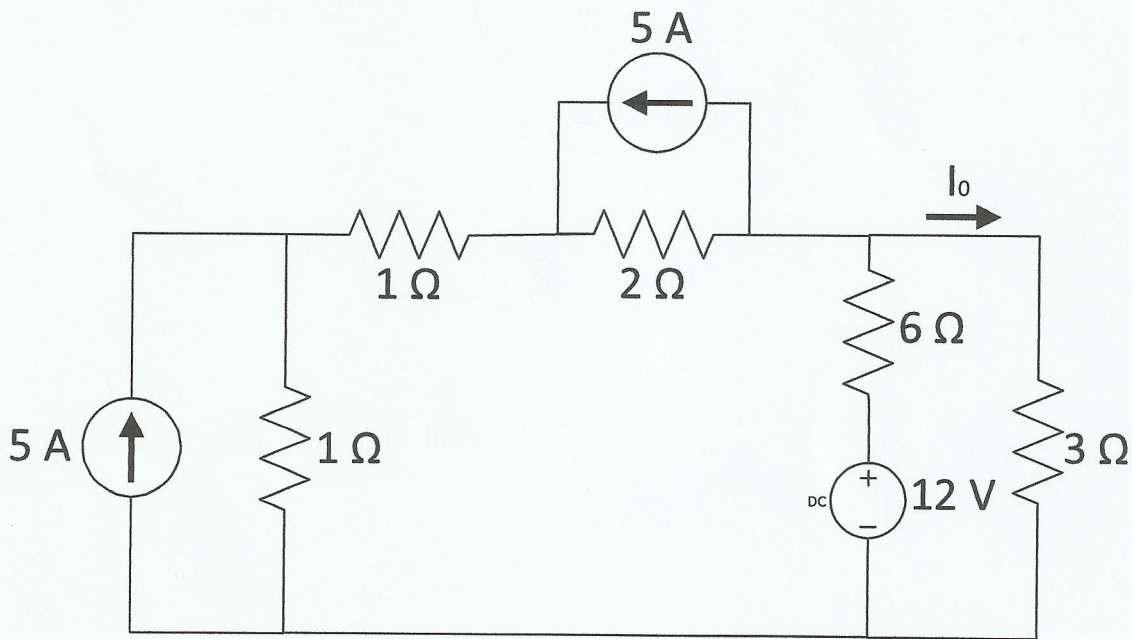Question 6 [19 points]

Use source transformation to find I_0 in the network in the below figure.



$$\Rightarrow \frac{3}{4} \text{ A} \uparrow \parallel \frac{12}{5} \Omega \parallel 3 \Omega \Rightarrow I_0 = \frac{3}{4} \times \frac{\frac{12}{5}}{\frac{12}{5} + 3}$$

$$= \frac{3}{4} \times \frac{12}{27} = \frac{1}{3} \text{ A}$$