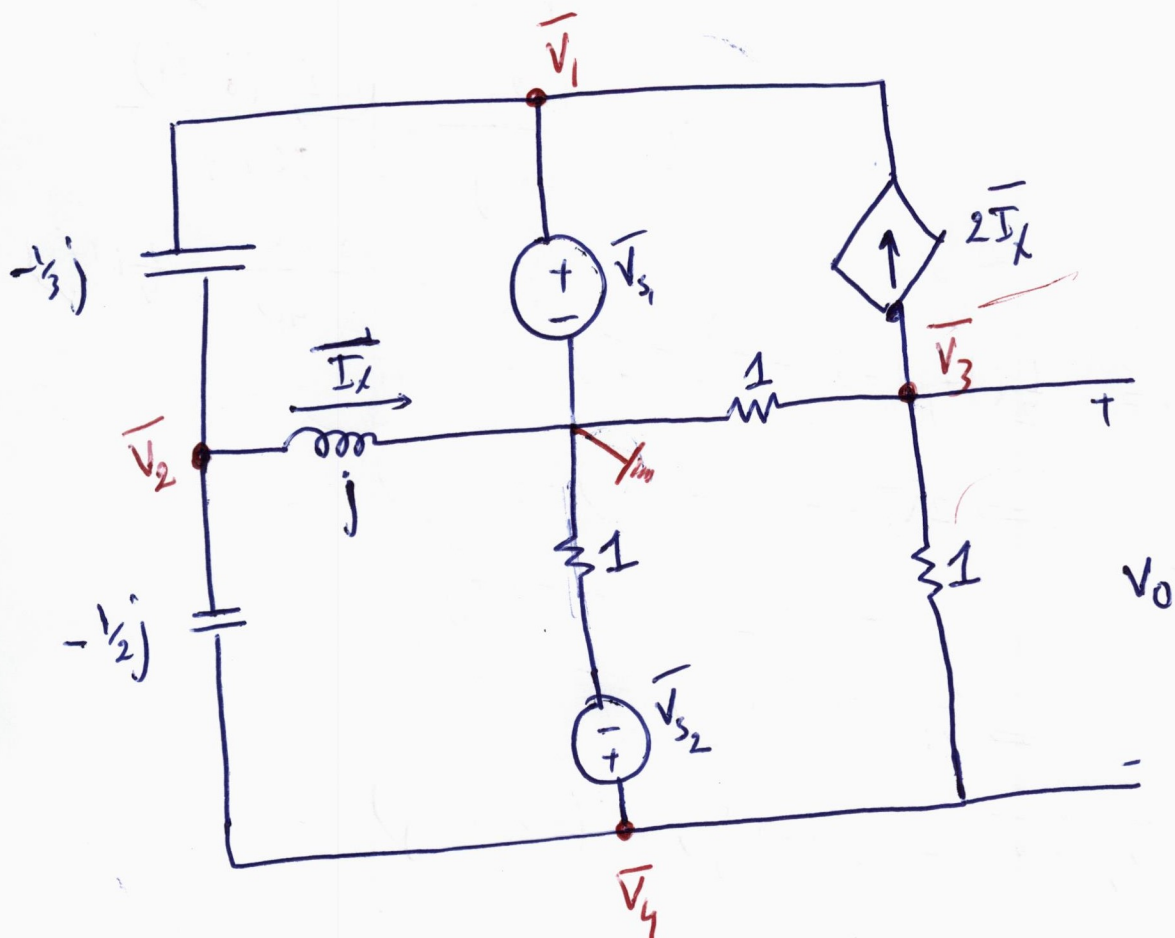


p2 Use Nodal analysis to Find \bar{V}_o .

$$\bar{V}_{s_1} = \frac{2}{3} \angle 0 \quad , \quad \bar{V}_{s_2} = \sqrt{2} \angle -35$$



node 1: $\bar{V}_1 = \bar{V}_{s_1} = \frac{2}{3} \angle 0$

node 2: $\frac{\bar{V}_2 - \bar{V}_1}{-\frac{1}{3}j} + \frac{\bar{V}_2}{j} + \frac{\bar{V}_2 - \bar{V}_4}{-\frac{1}{2}j} = 0 \Rightarrow 4j\bar{V}_2 - 2j\bar{V}_4 = 2j$

$$\boxed{\bar{V}_4 = 2\bar{V}_2 - 1} \quad (1)$$

node 3: $\frac{\bar{V}_3}{1} + \frac{\bar{V}_3 - \bar{V}_4}{1} + 2\bar{I}_x = 0$

$$\left. \begin{array}{l} \bar{I}_x = \frac{\bar{V}_2}{j} \\ \Rightarrow 2\bar{V}_3 - \bar{V}_4 - 2j\bar{V}_2 = 0 \end{array} \right\} \Rightarrow \boxed{2\bar{V}_3 - 2(1+j)\bar{V}_2 = -1} \quad (2)$$

node 4: $\frac{\bar{V}_4 - \bar{V}_2}{-\frac{1}{2}j} + \frac{\bar{V}_4 - \bar{V}_3}{1} + \frac{\bar{V}_4 - \bar{V}_{s_2}}{1} = 0 \Rightarrow (2+2j)\bar{V}_4 - 2j\bar{V}_2 - \bar{V}_3 = -1-j$

$$\boxed{(4+2j)\bar{V}_2 - \bar{V}_3 = 1+j} \quad (3)$$

$$\left. \begin{aligned} 2\bar{V}_3 - 2(1+j)\bar{V}_2 &= -1 \\ (4+2j)\bar{V}_2 - \bar{V}_3 &= 1+j \end{aligned} \right\} \Rightarrow \begin{aligned} (8+4j - 2-2j)\bar{V}_2 &= -1+2+2j \\ (6+2j)\bar{V}_2 &= 1+2j \end{aligned}$$

$$\begin{aligned} \bar{V}_2 &= \frac{1+2j}{6+2j} = \frac{(1+2j)(6-2j)}{36+4} \\ &= \frac{10+10j}{40} = \frac{1}{4}(1+j) \end{aligned}$$

$$\bar{V}_4 = 2\bar{V}_2 - 1 = \frac{1}{2}(1+j) - 1 = -\frac{1}{2} + \frac{1}{2}j$$

$$2\bar{V}_3 - 2(1+j)\bar{V}_2 = -1 \Rightarrow 2\bar{V}_3 = -1 + 2(1+j) \times \frac{1}{4}(1+j)$$


$$= -1 + \frac{1}{2} \times 2j = -1 + j$$

$$\Rightarrow \bar{V}_3 = \frac{1}{2}(-1+j)$$


$$\begin{aligned} \text{Finally } \bar{V}_0 &= \bar{V}_3 - \bar{V}_4 = \frac{1}{2}(-1+j) - \left(-\frac{1}{2} + \frac{1}{2}j\right) \\ &= 0 \text{ V} \end{aligned}$$

P4: a) Find the Norton equivalent of the circuit between the nodes A and B as seen by the impedance Z_L

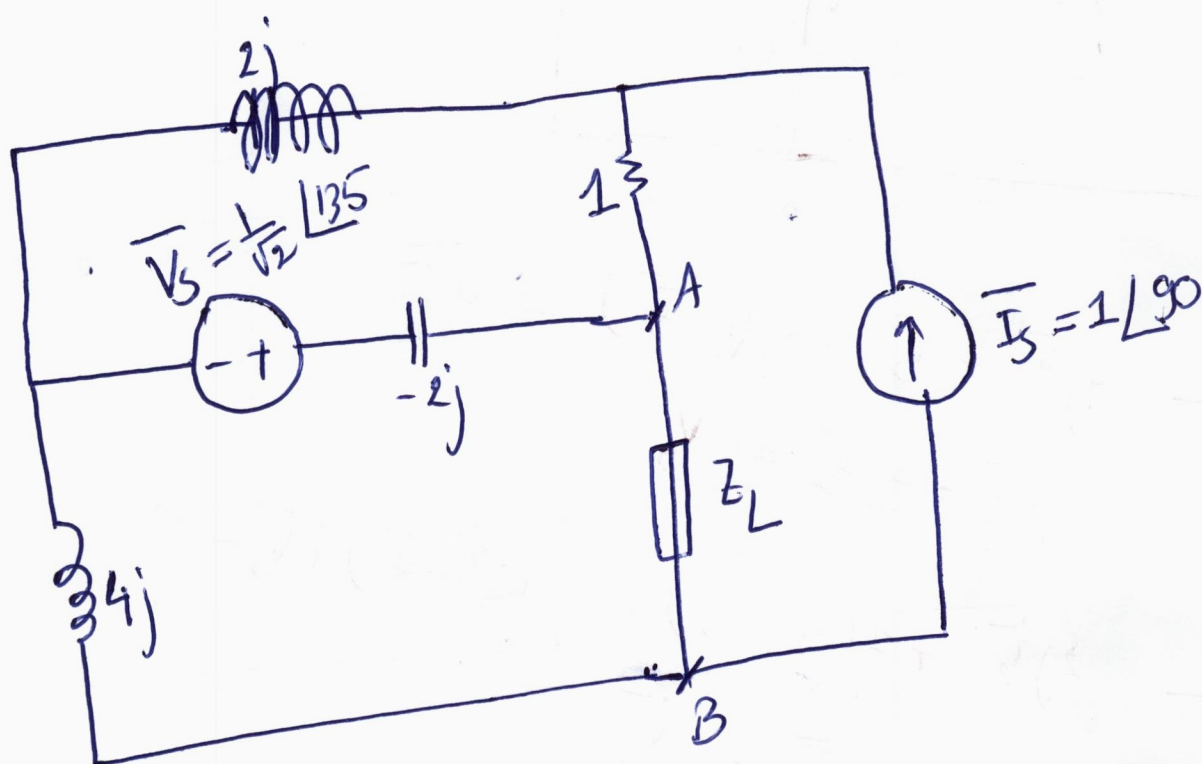b) The load Z_L consumes zero reactive power. Find the value of Z_L that would ensure a maximum power transfer




a)

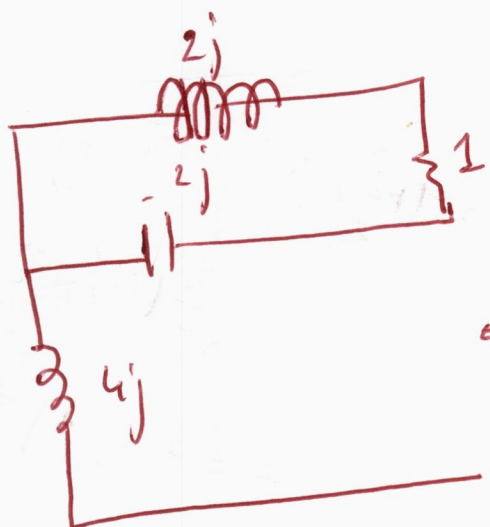

$$Z_T = Z_{eq} = \frac{(1+2j) \times (-2j)}{1} + 4j$$

$$= 4 + 2j$$

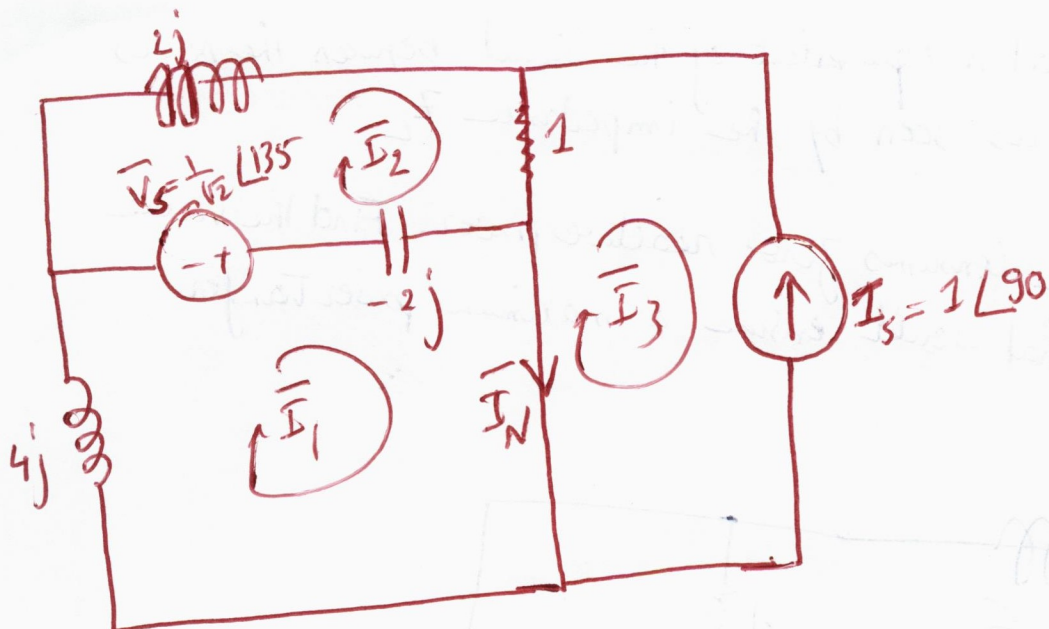

Mesh 1: $4j\bar{I}_1 + \bar{V}_S - 2j(\bar{I}_1 - \bar{I}_2) = 0$

$$2j\bar{I}_1 + 2j\bar{I}_2 = \bar{V}_S$$

Mesh 2: $2j\bar{I}_2 + 1(\bar{I}_2 - \bar{I}_3) - 2j(\bar{I}_2 - \bar{I}_1) + \bar{V}_S = 0$

$$\bar{I}_2 + 2j\bar{I}_1 - \bar{I}_3 = -\bar{V}_S$$

Mesh 3: $\bar{I}_3 = -\bar{I}_S = -j$

Now

$$\begin{cases} 2j\bar{I}_1 + 2j\bar{I}_2 = \bar{V}_S \\ 2j\bar{I}_1 + \bar{I}_2 = -\bar{V}_S + \bar{I}_3 = -\bar{V}_S - j \end{cases} \Rightarrow (1+2j)\bar{I}_2 = 2\bar{V}_S + j$$

$$= \frac{2}{\sqrt{2}} \left(\frac{-\sqrt{2}}{2} + \frac{\sqrt{2}}{2}j \right) + j$$

$$= -1 + j + j = -1 + 2j$$

$$\Rightarrow \bar{I}_2 = 1 \angle 0$$


$$2j\bar{I}_1 + 2j\bar{I}_2 = \bar{V}_S \Rightarrow 2j\bar{I}_1 = \bar{V}_S - 2j\bar{I}_2 = \frac{1}{\sqrt{2}} \left(\frac{-\sqrt{2}}{2} + \frac{\sqrt{2}}{2}j \right) - 2j$$

$$= -\frac{1}{2} + \frac{1}{2}j - 2j = -\frac{1}{2} - \frac{3}{2}j$$

$$\Rightarrow \boxed{\bar{I}_1 = \frac{1}{4}j - \frac{3}{4}}$$

Finally $\bar{I}_N = \bar{I}_1 - \bar{I}_3$

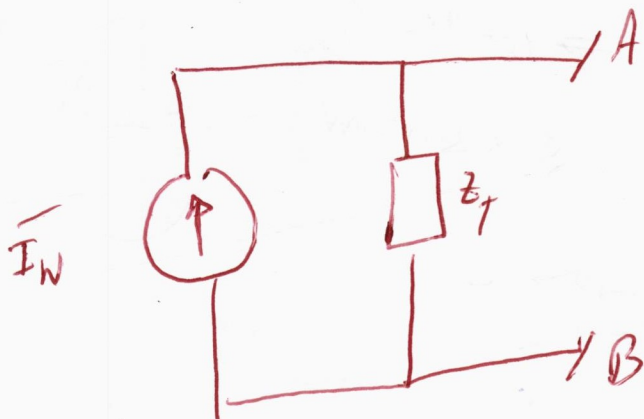
$$= \frac{1}{4}j - \frac{3}{4} - (-j) = -\frac{3}{4} + \frac{5}{4}j$$



b) This reactive power \Rightarrow resistance

$$R_L = |Z_T| = \sqrt{16 + 4} = \sqrt{20} \Omega$$

P.1

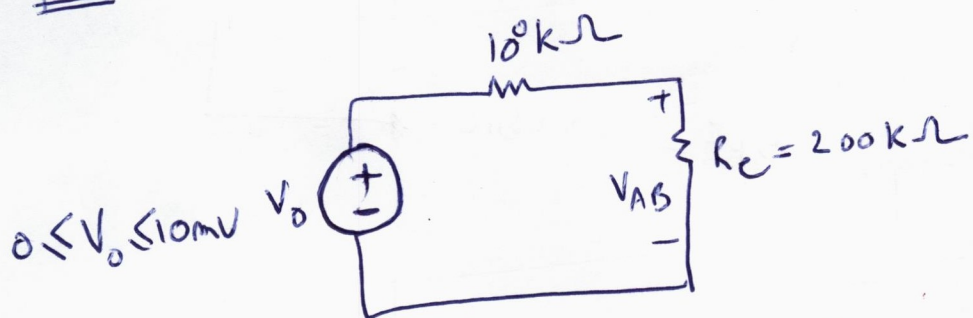

a. voltage divider: $V_{AB} = V_0 \times \frac{R_L}{R_L + R} = V_0 \times \frac{200}{300} = \frac{2}{3} V_0$

$$0 \leq V_{AB} \leq \frac{20}{3} \text{ mV}$$

$$b. \begin{cases} i_+ = i_- = 0 \\ v_+ = v_- \end{cases}$$

Drop voltage on $R=0 \Rightarrow v_+ = v_o \Rightarrow v_- = v_o$

$$\text{KCL @ } - : \frac{v_o}{R_1} + \frac{v_o - v_s}{R_2} = 0 \Rightarrow \frac{v_o}{R_1} + \frac{v_o}{R_2} = \frac{v_s}{R_2}$$

$$\Rightarrow \frac{v_s}{v_o} = \left(1 + \frac{R_2}{R_1}\right) = 1 + 10 = 11$$


c. add R_c KCL @ - : $\frac{v_o}{R_1} + \frac{v_o - v_s}{R_2} = 0 \Rightarrow$

$$\frac{v_s}{v_o} = 11 \Rightarrow v_s = 11v_o$$

$$0 \leq v_s \leq 110\text{mV}$$

d.) No drop voltage across $R=100\text{ k}\Omega$
 voltage gain

P2: a. $C_{eq}?$

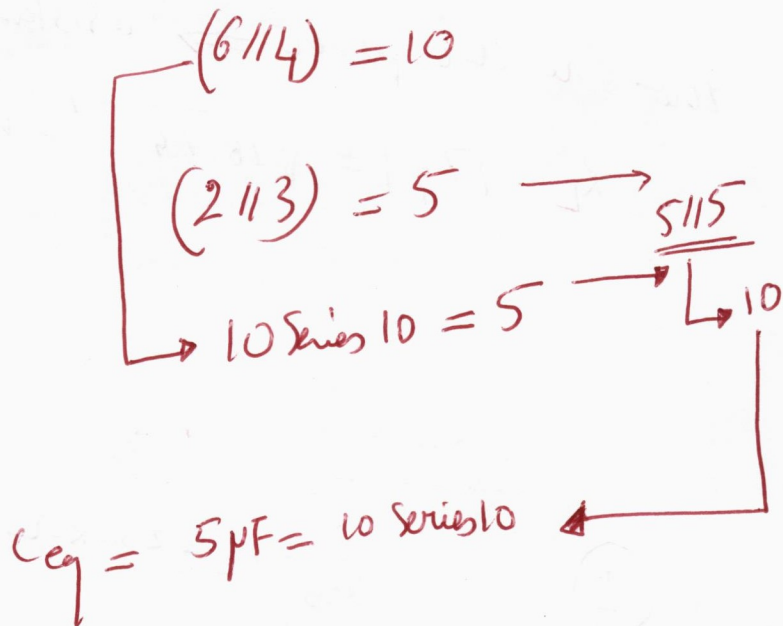

b. $w(t) = \frac{1}{2} C v^2(t)$

We will use $C_{eq} = 10 \text{ pF}$

$$i(t) = C \frac{dv(t)}{dt} \Rightarrow v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt + v(t_0)$$

$$0 \leq t \leq 2 : i(t) = 5t \text{ mA}, \text{ ~~10t~~}$$

$$2 \leq t \leq 4 : i(t) = 10 \text{ mA}, \text{ ~~10t~~}$$

$$4 \leq t \leq 6 : i(t) = (-10t + 50) \text{ mA}, \text{ ~~10t~~}$$

Now, let us find $v(t)$ in Volts

~~0 ≤ t ≤ 2~~
$$0 \leq t \leq 2 : v(t) = \frac{1}{10} \int_0^t 5z dz + v(0)$$

$$= \frac{1}{10} \times 5 \times \frac{t^2}{2} = \frac{t^2}{4} \quad (1)$$

$$2 \leq t \leq 4 : v(t) = \frac{1}{10} \int_2^t 10 dz + v(2)$$

$$\text{But } v(2) = \frac{2^2}{4} = 1 \text{ V (From eq. (1))}$$

$$\Rightarrow v(t) = \frac{1}{10} \times 10 \times (t-2) + 1 = t-1 \quad (2)$$

$$4 \leq t \leq 6 : v(t) = \frac{1}{10} \int_4^t (-10z + 50) dz + v(4)$$

$$\text{But } v(4) = 4-1 = 3 \text{ V (From eq. (2))}$$

$$v(t) = \frac{1}{10} (-5z^2 + 50z) \Big|_4^t + 3$$

$$= \frac{1}{10} (-5t^2 + 50t + 5 \times 16 - 50 \times 4) + 3$$

$$= -\frac{1}{2}t^2 + 5t + 8 - 20 + 3 = -\frac{1}{2}t^2 + 5t - 9 \quad (3)$$

$$V(t) = \begin{cases} \frac{t^2}{4} & 0 \leq t \leq 2 \\ t-1 & 2 \leq t \leq 4 \\ -\frac{1}{2}t^2 + 5t - 9 & 4 \leq t \leq 6 \end{cases}$$

$$\text{@ } t=1.3 \Rightarrow V(1.3) = \frac{(1.3)^2}{4} = 0.4225 \text{ V} \Rightarrow W(1.3) = \frac{1}{2} \times 10 \times (0.4225)^2 = \boxed{0.89 \mu\text{J}}$$

$$\text{@ } t=2.4 \Rightarrow V(2.4) = 2.4 - 1 = 1.4 \text{ V} \Rightarrow W(2.4) = \frac{1}{2} \times 10 \times (1.4)^2 = \boxed{9.8 \mu\text{J}}$$

$$\text{@ } t=5.5 \text{ ms} \Rightarrow V(5.5) = -\frac{1}{2}(5.5)^2 + 5 \times 5.5 - 9 = 3.375 \text{ V}$$

$$\Rightarrow W(5.5) = \frac{1}{2} \times 10 \times (3.375)^2 = \boxed{56.95 \mu\text{J}}$$

A Second Method:

$$V(t) = \frac{1}{C_{eq}} \int_{t_0}^t i(z) dz + V(t_0)$$

$$t_0 = 0 \Rightarrow V(t) = \frac{1}{C_{eq}} \int_0^t i(z) dz$$

$$V(1.3) = \frac{1}{10} \int_0^{1.3} i(z) dz = \frac{1}{10} \times \text{area under the curve of } i \text{ from } 0 \text{ to } 1.3$$

$$= \frac{1}{10} \times \frac{1.3 \times (1.3) \times 5}{2} = 0.4225 \text{ V}$$

$$V(2.4) = \frac{1}{10} \times \text{area under the curve from } 0 \text{ to } 2.4$$


$$= \frac{1}{10} \left(\frac{2 \times 10}{2} + 0.4 \times 10 \right) = 1 + 0.4 = 1.4 \text{ V}$$

$$V(5.5) = \frac{1}{10} \left(\frac{2 \times 10}{2} + 2 \times 10 + 1 \times \frac{10}{2} + \frac{0.5 \times (-5)}{2} \right)$$


$$= 1 + 2 + 0.5 - 0.125 = 3.375 \text{ V}$$

Then Find $W(1.3)$, $W(2.4)$ and $W(5.5)$

Question 5:

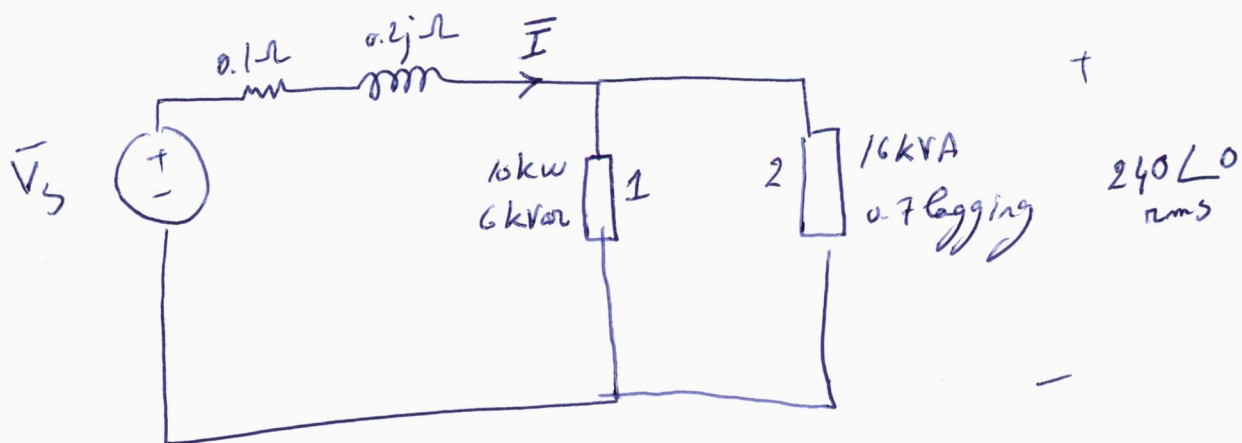

a) power triangle for load 2:

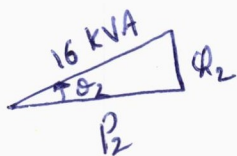

$$\cos \theta_2 = 0.7 \Rightarrow P_2 = 16 \times \cos \theta_2 = 16 \times 0.7 = 11.2 \text{ kW}$$

$$Q_2 = + \sqrt{(16)^2 - (11.2)^2} = 11.43 \text{ kVAR}$$

As for Load 1: it is given that $P_1 = 10 \text{ kW}$ and $Q_1 = 6 \text{ kVAR}$

Thus the total power absorbed by loads 1 & 2 is $P_T = 11.2 + 10 = 21.2 \text{ kW}$
 the total reactive power of the loads 1 & 2 is $Q_T = 11.43 + 6 = 17.43 \text{ kVAR}$

$$\text{Hence } \tan \theta_T = \frac{Q_T}{P_T} = \frac{17.43}{21.2} = 0.822 \Rightarrow \theta_T = 39.42^\circ$$

↳ this $\theta_V - \theta_I$ for the equivalent load of 1 & 2

To find I_{rms} , we have

$$P_T = V_{\text{rms}} I_{\text{rms}} \cos \theta_T \Rightarrow I_{\text{rms}} = \frac{21.2 \times 10^3}{240 \times \cos(39.42)} = 114.34 \text{ A}$$

$$\Rightarrow \bar{I} = I_{\text{rms}} \angle \theta_I = 114.34 \angle -39.42 \text{ A}$$

Since we have \bar{I} : we find P_R and Q_L
 $(Q_R=0)$ $(P_L=0)$

$$P_R = R I_{rms}^2 = 0.1 \times (114.34)^2 = 1.307 \text{ kW}$$

$$Q_L = X_L I_{rms}^2 = 0.2 \times (114.34)^2 = 2.614 \text{ KVAR}$$

Finally $P_{source} = P_L + P_R = 21.2 + 2.614 = 23.814 \text{ kW}$

$$Q_{source} = Q_L + Q_C = 17.43 + 2.614 = 20.044 \text{ KVAR}$$

b) $\cos \theta_2 = 0.9$ in this case. Using the same approach,

$$P_2 = 16 \times \cos \theta_2 = 16 \times 0.9 = 14.4 \text{ kW}$$

$$Q_2 = \sqrt{16^2 - (14.4)^2} = 6.97 \text{ KVAR}$$

$$P_L = P_1 + P_2 = 10 + 14.4 = 24.4 \text{ kW}$$

$$Q_L = Q_1 + Q_2 = 6 + 6.97 = 12.97 \text{ KVAR}$$

$$\text{Hence } \tan \theta_L = \frac{12.97}{24.4} = 0.53 \Rightarrow \theta_L = 28^\circ \Rightarrow \theta_V - \theta_I = 28^\circ \Rightarrow$$

$$0 - \theta_I = 28^\circ \Rightarrow \theta_I = -28^\circ$$

$$P_L = V_{rms} I_{rms} \cos \theta_L \Rightarrow I_{rms} = \frac{24.4 \times 10^3}{240 \times \cos(28)} = 115.14 \text{ A}$$

$$\Rightarrow \bar{I} = 115.14 \angle -28$$

$$P_R = R I_{rms}^2 = 0.1 \times (115.14)^2 = 1.325 \text{ kW}$$

$$Q_L = X_L I_{rms}^2 = 0.2 \times (115.14)^2 = 2.651 \text{ KVAR}$$

Finally $P_{source} = P_L + P_R = 24.4 + 1.325 = 25.725 \text{ kW}$

$$Q_{source} = Q_L + Q_C = 12.97 + 2.651 = 15.621 \text{ KVAR}$$

c) part a) The % loss of average power = $\frac{P_R}{P_{\text{source}}} \times 100 = \frac{1.307}{23.814} \times 100 = 5.488\%$

part b) The % loss of average power = $\frac{P_R}{P_{\text{source}}} \times 100 = \frac{1.325}{25.725} \times 100$
5.15%

↳ smaller loss
⇒ Better