



Department of Electrical  
and Computer Engineering

## ELE 305: Introduction to Electrical Engineering Exam 2 – Spring 2017

Duration: **1 hour 30 minutes**  
Date: 12/04/2016  
Start Time: 5:00 pm

Dr. Elie Abou Diwan  
Dr. Jihad Jawad Fahs  
Dr. Harag Margossian

**Name:** \_\_\_\_\_ **ID#:** \_\_\_\_\_


**INSTRUCTIONS:**

- Answer each of the following questions in the space provided.
- You can use both sides of the sheets for answers.
- Solutions written outside this booklet will not be graded.
- This is a closed-book exam
- Programmable calculators and smart devices are not allowed.
- The number of points for each question is specified next to it.
- The total number of points is 100.

1	2	3	4	5	Total
/24	/16	/20	/20	/20	/100


**Question 1 (24 pts)**

Consider a sensor modeled by a voltage source  $V_0$  ( $V_0$  is between 0 and 10 mV) in series with its internal resistance  $R = 100\text{ k}\Omega$  (see Figure 1). The accessible output voltage of this sensor is  $V_{AB}$ .  $V_{AB}$  is measured using a voltmeter that is modeled as a resistance  $R_e = 200\text{ k}\Omega$  connected between A and B.

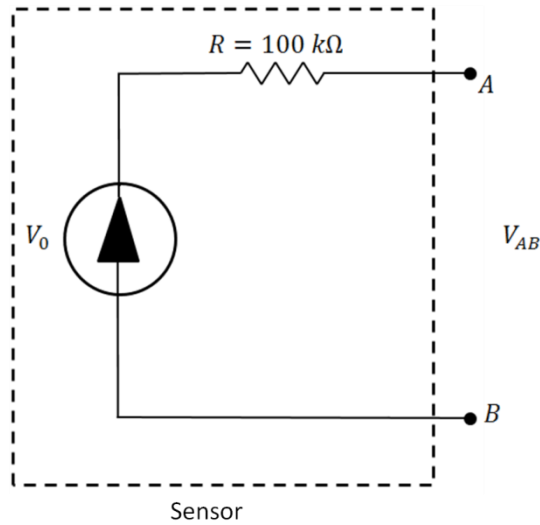

**Figure 1**

- What is the range of voltages measured by the voltmeter?
- The configuration below (see Figure 2) is used to amplify the monitored measurement. The operational amplifier is considered ideal. Calculate the gain of this circuit.
- If the voltmeter is added between  $V_S$  and the ground, what is the range of voltages measured in this case?
- What is the advantage of using the opAmp circuit in part c over the setup in part a?

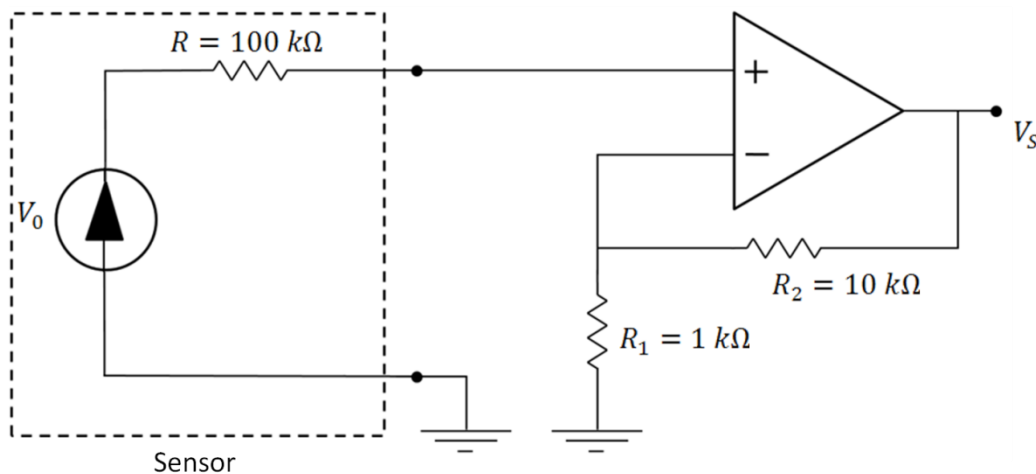


**Figure 2**




**Question 2 (16 pts)**

- a. Find the equivalent capacitance  $C_{eq}$  between the terminals A and B in the circuit of Figure 3. Values of all capacitance are in  $\mu F$ .

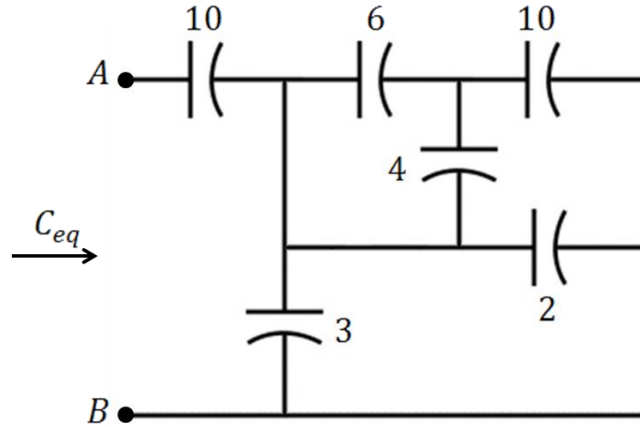


**Figure 3**

- b. Consider the circuit in Figure 4.a. The current flowing through the capacitor is shown in Figure 4.b. Find the energy stored in the capacitor at  $t = 1.3 \text{ ms}$ ,  $t = 2.4 \text{ ms}$  and  $t = 5.5 \text{ ms}$ . *Hint: if you could not solve part (a), use  $C_{eq} = 10 \mu F$ .*

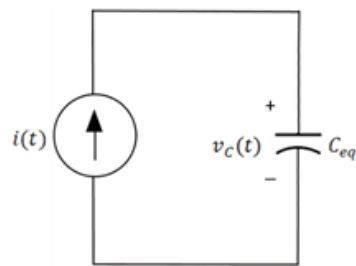

**Figure 4.a**

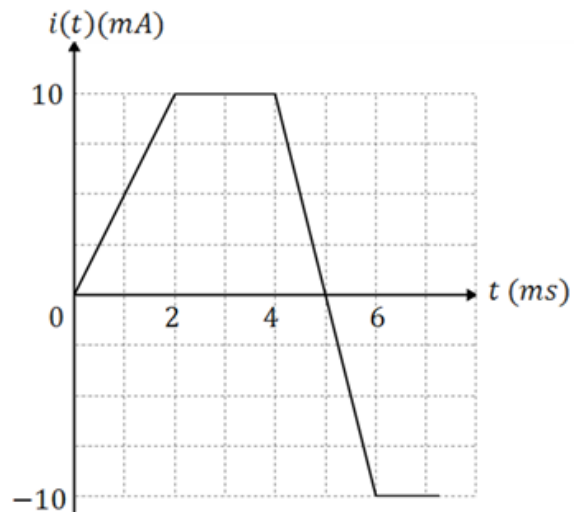


**Figure 4.b**

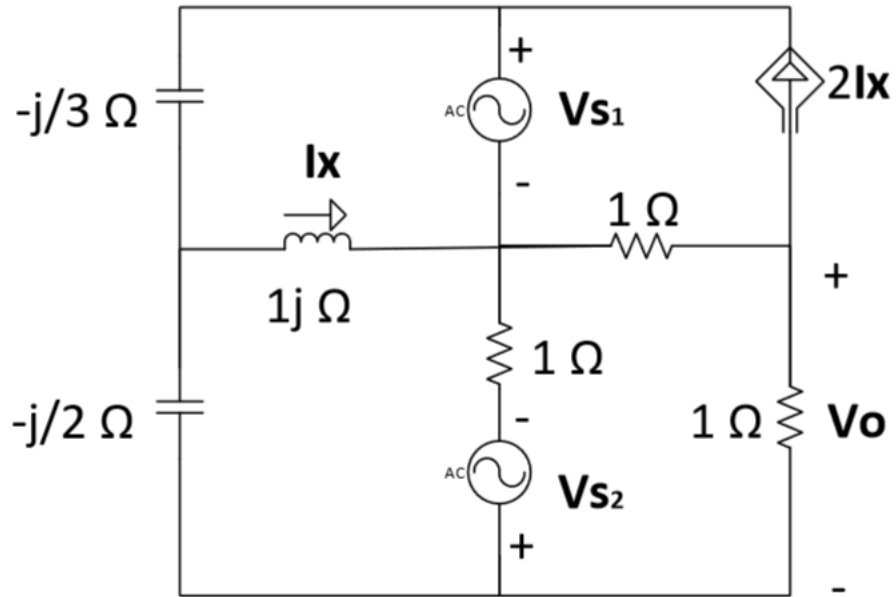

**Question 3 (20 pts)**

Use nodal analysis to find  $V_o$ .  $V_{s_1} = \frac{2}{3} \angle 0^\circ$  and  $V_{s_2} = \sqrt{2} \angle -135^\circ$ .




**Figure 5**



**Question 4 (20 pts)**

Consider the circuit below. You are given  $V_s = \frac{1}{\sqrt{2}} \angle 135^\circ$  and  $I_s = 1 \angle 90^\circ$

- Find the Norton equivalent of the circuit between the nodes A and B as seen by the impedance  $\bar{Z}_L$ .
- If the reactive power of  $\bar{Z}_L$  must be zero, what value of  $\bar{Z}_L$  should be used to ensure maximum power transfer?

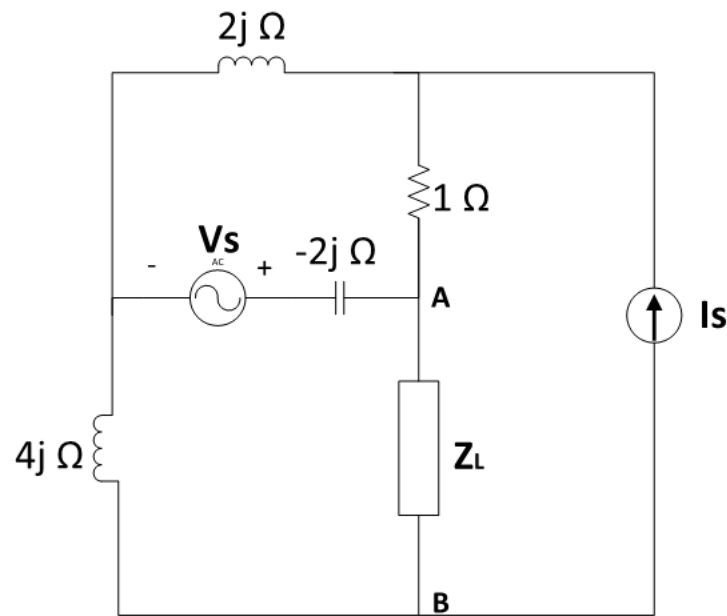**Figure 6**






**Question 5 (20 pts)**

Consider the power system shown below. The loads are connected at 240 V rms.

- Calculate the real and reactive power supplied by the source.
- Repeat the calculation with the power factor of load 2 being 0.9 lagging instead of 0.7 lagging.
- Which of the two power factors is better? Explain why.

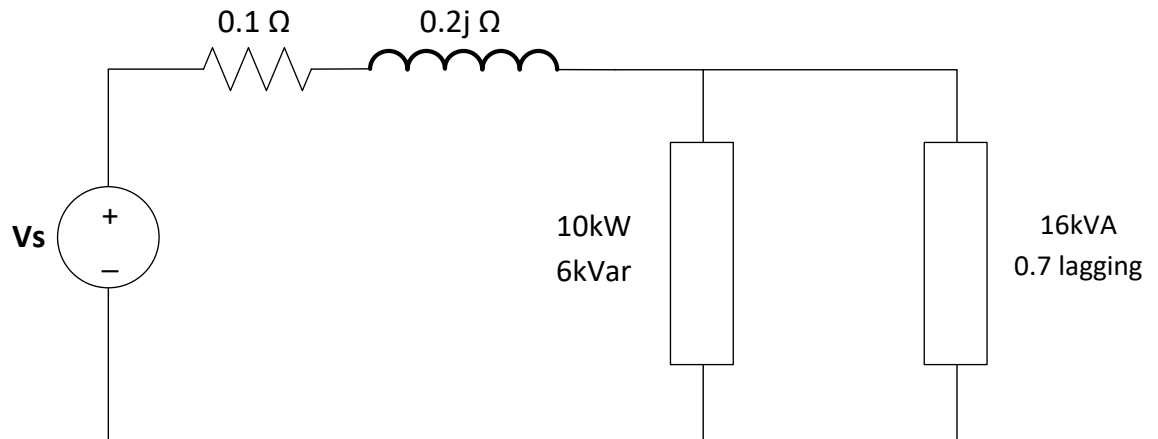

**Figure 7**

