

# problem 1:

a)  $3\Omega$  OC  $\rightarrow$  removed  
 $5\Omega$  series with  $3\Omega = 8\Omega$ , short circuited  $\rightarrow$  remove

$$3\Omega \parallel 2\Omega \parallel 6\Omega = 1\Omega$$


$$12\Omega \parallel 4\Omega = 3\Omega$$

$$4\Omega \parallel 8\Omega = \frac{8}{3}\Omega$$

$$3\Omega \text{ series with } 1\Omega = 4\Omega$$

$$4\Omega \parallel \left(\frac{8}{3}\right)\Omega = \frac{8}{5}\Omega$$

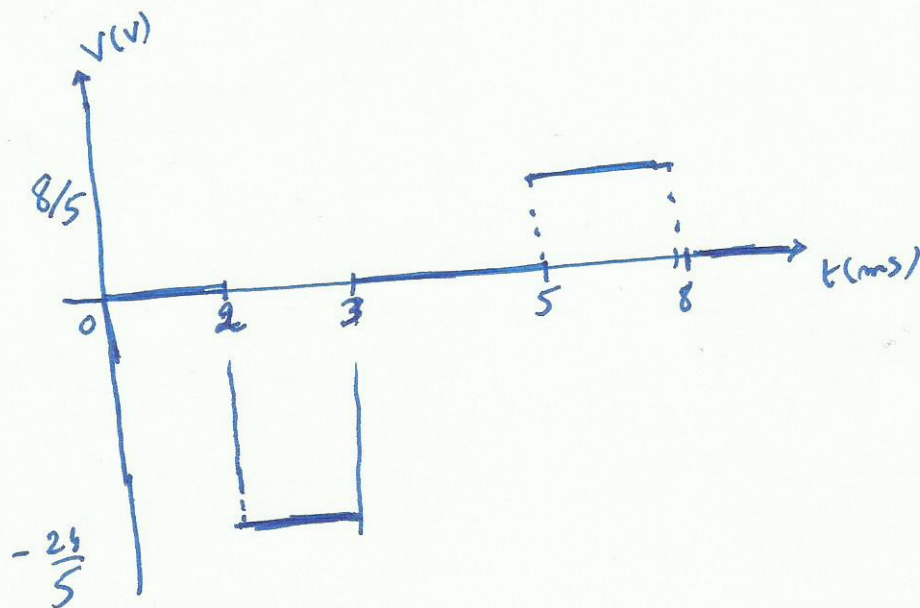b)  $t=2$  to  $3$        $i = \frac{dq}{dt} = -3A \Rightarrow v = \cancel{\frac{12}{8}} - 3 \times \frac{8}{5} = -\frac{24}{5}V$   
 $t=5$  to  $8$        $i = 1A \Rightarrow v = \frac{8}{5}V$



## Question 2

Use mesh analysis to calculate the power delivered by the 3mA source in the network shown in Figure 3.


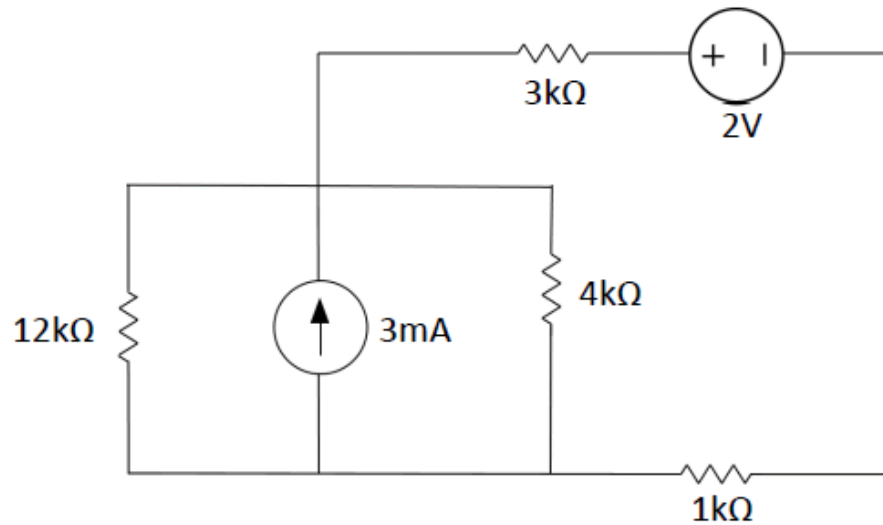


Figure 3

## Solution

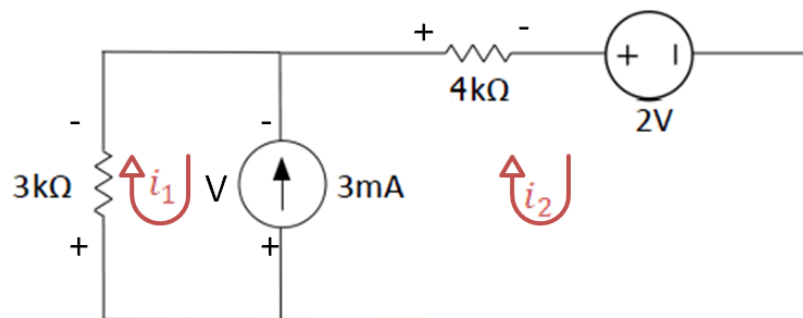

$$\begin{cases} 3ki_1 + 4ki_2 + 2 = 0 \\ i_2 - i_1 = \frac{3}{k} \end{cases} \Rightarrow i_1 = -2mA$$

Or:

$$V = 3k \times i_1 = -6V$$

And:

$$P = V \times 3mA = -18mW$$

### Question 3

Use superposition to find  $V_o$  in the network in Figure 4.


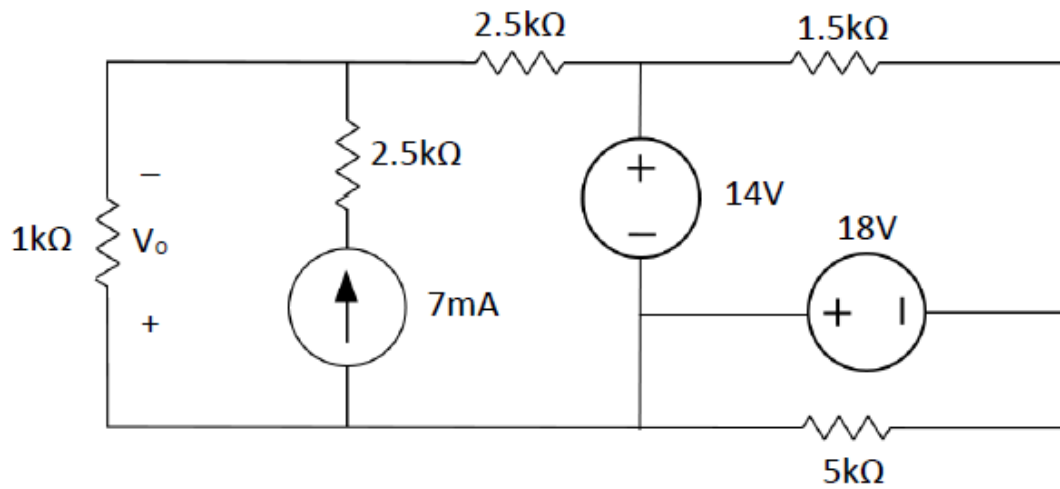


Figure 4

### Solution

Short circuit 14V and 18V sources:

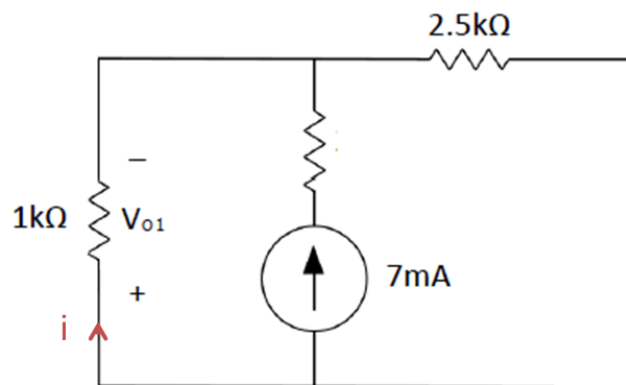


$$i = \frac{-2.5k}{2.5k + 1k} \times 7 \times 10^{-3} = -5mA$$

Therefore:

$$V_{o1} = 1k \times i = -5V$$

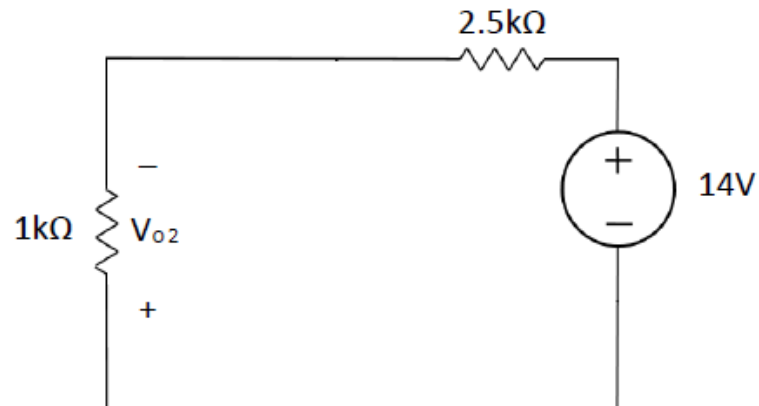Short circuit 18V and open circuit 7mA sources:



$$V_{02} = \frac{-1k}{2.5k + 1k} \times 14 = -4V$$




Short circuit 14V and open circuit 7mA sources:

$$V_{03} = 0$$

Finally:


$$V_0 = V_{01} + V_{02} + V_{03} = -5 - 4 + 0 = -9V$$

Question 4:

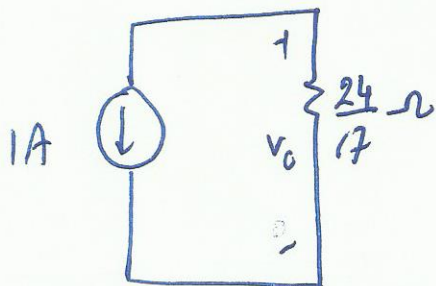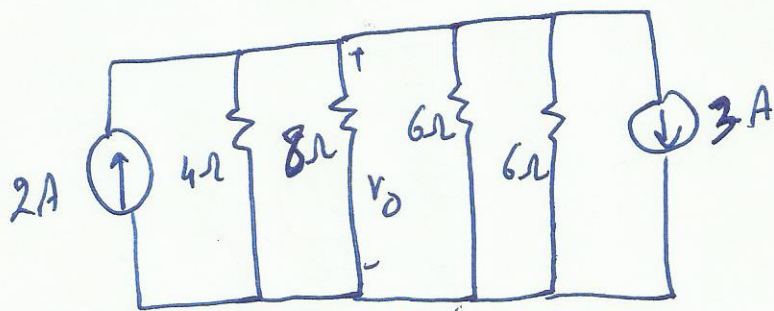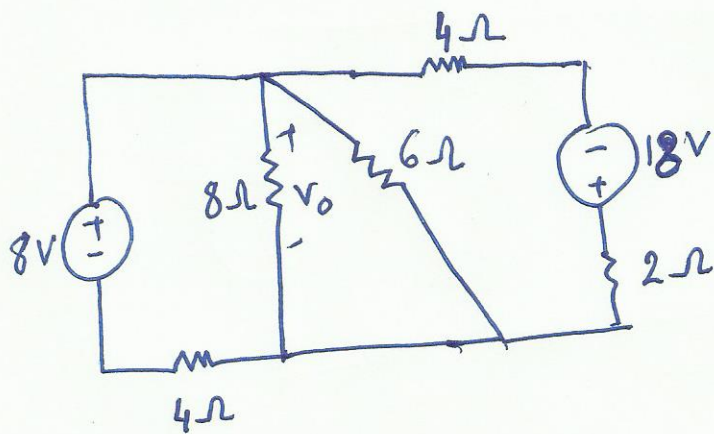

$$\Rightarrow v_o = -\frac{24}{17} \text{ V}$$

## Questions

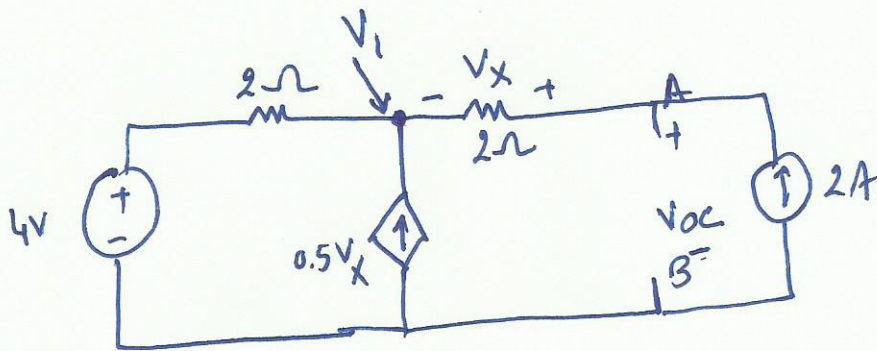

To Find  $V_{OC}$ , use node-voltage analysis:

KCL @ node 1  $\Rightarrow$


$$\frac{V_1 - 4}{2} = 0.5V_x + 2 \quad \Rightarrow V_1 = 12V$$

and

$$V_x = 2 \times 2 = 4V$$

$$\text{Now } V_{OC} = V_x + V_1 = 4 + 12 = 16V$$

$$V_{Th} = V_{OC} = 16V$$

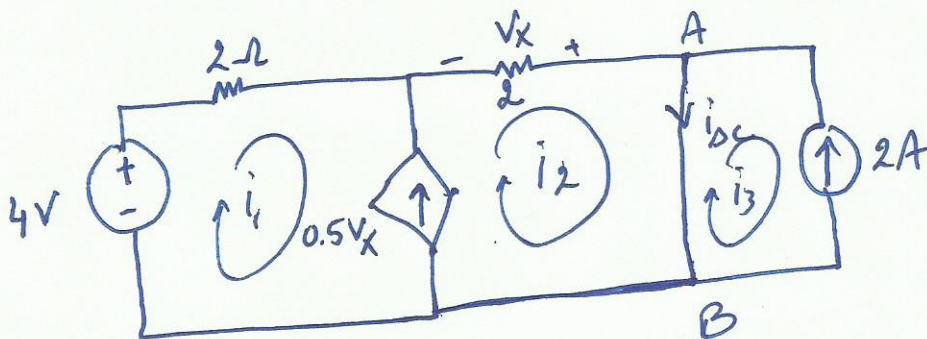

Use mesh analysis:

$$\begin{aligned} \text{Super mesh 1 and 2} &\Rightarrow -4 + 2i_1 - V_x = 0 \\ \text{mesh 3} &\Rightarrow i_3 = -2A \\ \text{and } 0.5V_x &= i_2 - i_1, \quad V_x = -2i_2 \end{aligned} \quad \Rightarrow \begin{cases} 2i_1 + 2i_2 = 4 \\ i_1 - 2i_2 = 0 \\ i_3 = -2A \end{cases}$$




Then  $i_1 = \frac{4}{3} A$ ,  $i_2 = \frac{2}{3} A$ ,  $i_3 = -2 A$


$$i_{sc} = i_2 - i_3 = \frac{2}{3} + 2 = \frac{8}{3} A$$

Therefore  $R_{Th} = \frac{V_{oc}}{i_{sc}} = \frac{16}{\frac{8}{3}} = 6 \Omega$

The Thevenin equivalent is

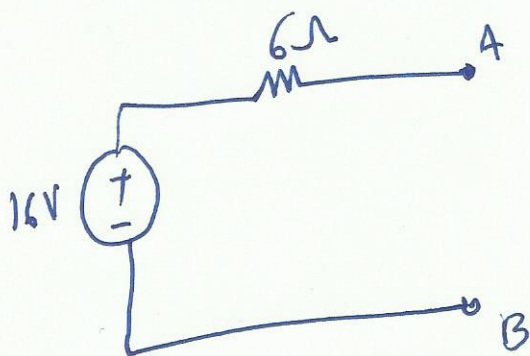

b)

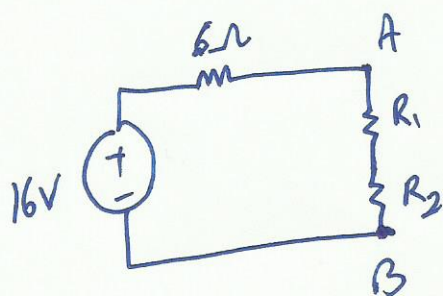

In order to ensure a maximum power transfer to  $R_2$ , we need to find the  $R_{Th}$  of the Thevenin equivalent as seen by the resistance  $R_2$ . This gives

$$R'_{Th} = R_1 + 6$$

For maximum power transfer to  $R_2$ , we must have

$$R_2 = R'_{Th} = R_1 + 6$$