



Department of Electrical
and Computer Engineering

ELE 305: Introduction to Electrical Engineering

Exam 1 – Fall 2016

Duration: **1 hour 30 minutes**

Dr. Harag Margossian

Date: 8/10/2016

Start Time: 2:00 pm

Name: _____ ID#: _____

INSTRUCTIONS:

- Answer each of the following questions in the space provided.
- You can use both sides of the sheets for answers.
- Solutions written outside this booklet will not be graded.
- This is a closed-book exam
- Programmable calculators and smart devices are not allowed.
- The number of points for each question is specified next to it.
- The total number of points is 100.

1	2	3	4	5	Total
/10	/15	/20	/25	/30	/100

Question 1 (10 points)

The current entering an element is shown in Figure 1. Find the charge that enters the element in the time interval $0 < t < 30$ s

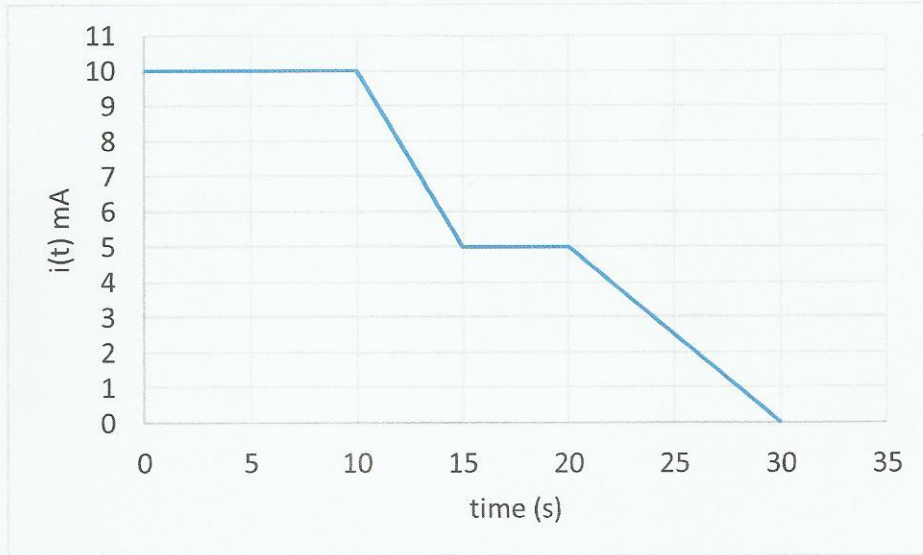


Figure 1

According to the figure:

$$i(t) \text{ (mA)} = \begin{cases} 10 & 0 \leq t \leq 10 \\ -t+20 & 10 \leq t \leq 15 \\ 5 & 15 \leq t \leq 20 \\ -\frac{t}{2}+15 & 20 \leq t \leq 30 \end{cases}$$

$$i(t) = \frac{dq(t)}{dt} \Rightarrow q(t) = \int_{t_0}^t i(t) dt + q(t_0)$$

• $0 \leq t \leq 10$: $q(t) = \int_0^t i(t) dt + q(0) = \int_0^t 10 dt + 0 = 10t$

• $10 \leq t \leq 15$: $q(t) = \int_{10}^t i(t) dt + q(10) = \int_{10}^t (-t+20) dt + q(10) = \left[-\frac{t^2}{2} + 20t \right]_{10}^t + q(10)$

$q(10) = 10 \times 10 = 100 \text{ mC}$

$\Rightarrow q(t) = -\frac{t^2}{2} + 20t + 50 - 200 + 100 = -\frac{t^2}{2} + 20t - 50$

• $15 \leq t \leq 20$: $q(t) = \int_{15}^t i(t) dt + q(15) = [5t]_{15}^t + q(15) = 5t - 75 + \frac{225}{2}$

$q(15) = \frac{-(15)^2}{2} + 20 \times 15 - 50 = -\frac{225}{2} + 300 - 50 = \frac{225}{2}$

• $20 \leq t \leq 30$: $q(t) = \int_{20}^t i(t) dt + q(20) = \int_{20}^t \left(-\frac{t}{2} + 15\right) dt + q(20) = \left(-\frac{t^2}{4} + 15t\right)_{20}^t + q(20)$

$q(20) = 5 \times 20 - 75 = \frac{275}{2}$

Question 2 (15 points)

Find R_{AB} in the network in Figure 2.



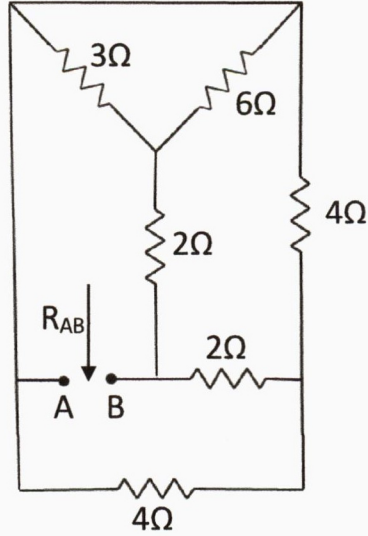
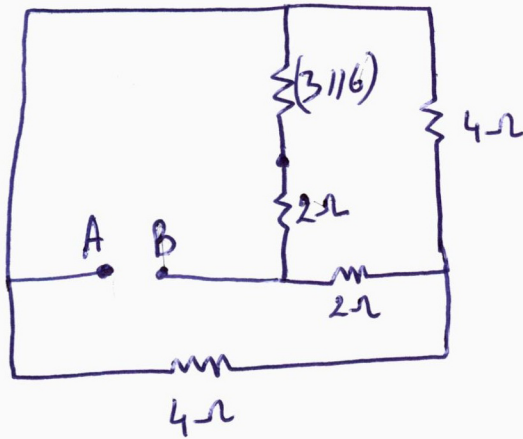
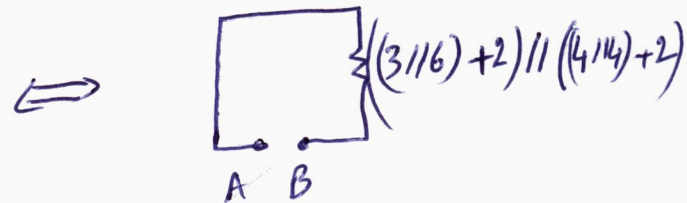


Figure 2

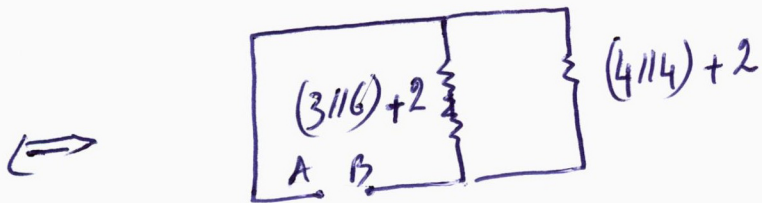

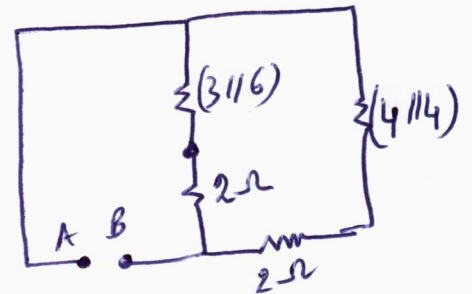The two (4Ω) resistances are in \parallel



$$R_{AB} = (2+2) \parallel (2+2) = 4 \parallel 4 = 2 \Omega$$

Question 3 (20 points)

Use superposition to find V_o in the network in Figure 3.


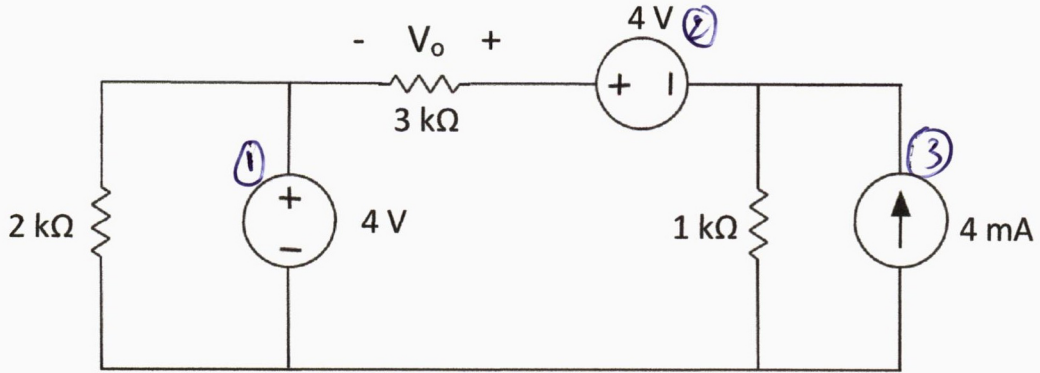


Figure 3

Phase I

① ON , ② OFF, ③ OFF

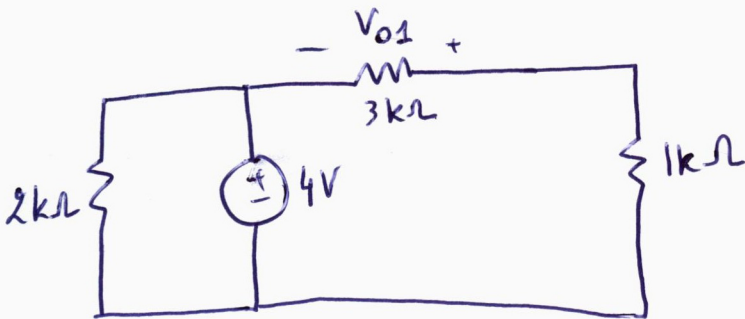


Voltage divider \Rightarrow

$$V_{o1} = -4 \times \frac{3}{3+1} = -4 \times \frac{3}{4} = -3V$$


The ratio in here is $\frac{k\Omega}{k\Omega}$, so no problem

Phase II

① OFF , ② ON , ③ OFF

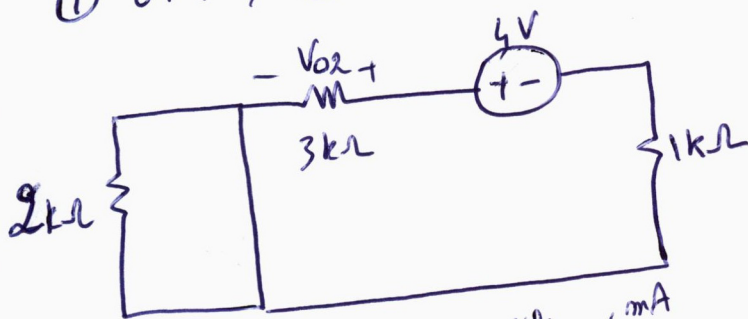

\Rightarrow

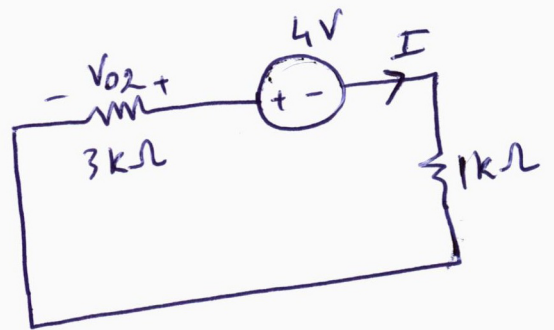

KVL \Rightarrow $1 \times I - V_{o2} + 4 = 0$



But $V_{o2} = -3 \times I$

$$\begin{cases} \Rightarrow I + 3I + 4 = 0 \\ \Rightarrow 4I = -4 \Rightarrow I = -1 \text{ mA} \end{cases}$$

Then $V_{o2} = -3 \times I = -3 \times (-1) = 3V$

Phase III

① OFF, ② OFF, ③ ON

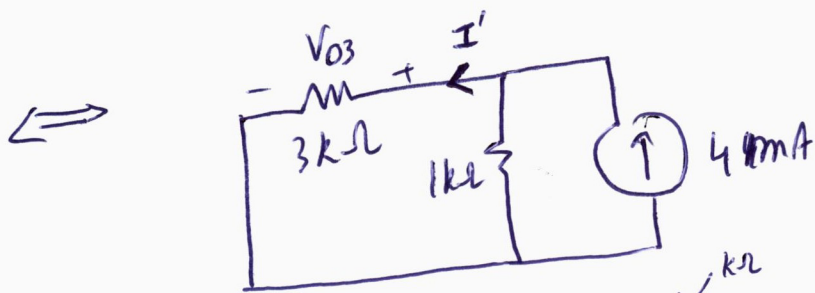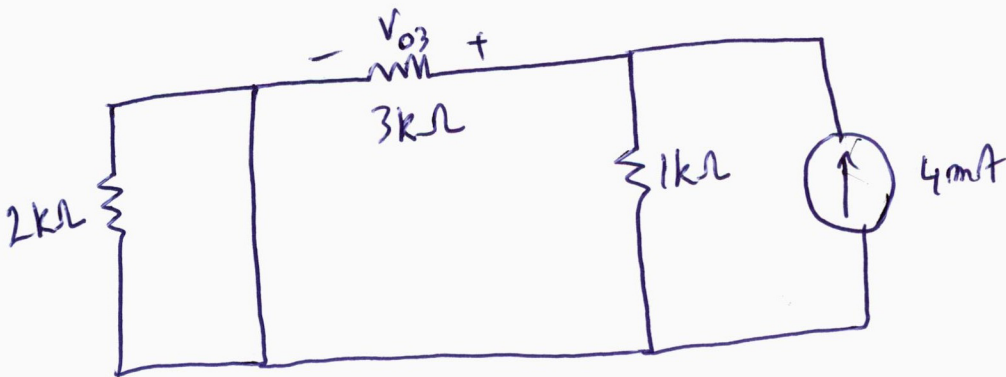

Current divider: $I' = 4 \times \frac{1 \text{ k}\Omega}{3 + 1 \text{ k}\Omega} = 1 \text{ mA}$

$$V_{03} = + 3 \times I' = 3 \times 1 = 3 \text{ V}$$

Finally, $V_0 = V_{01} + V_{02} + V_{03} = -3 + 3 + 3 = 3 \text{ V}$

Question 4 (25 points)

Use source transformation to find I_o in the network in Figure 4.



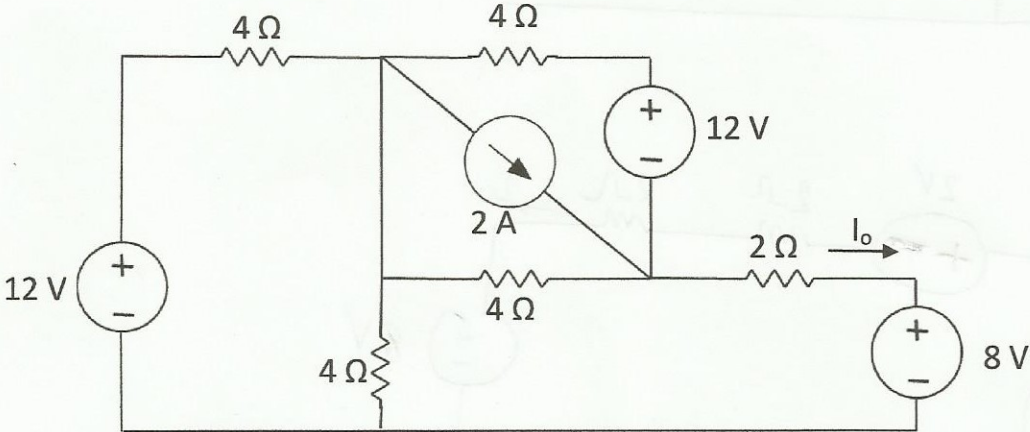
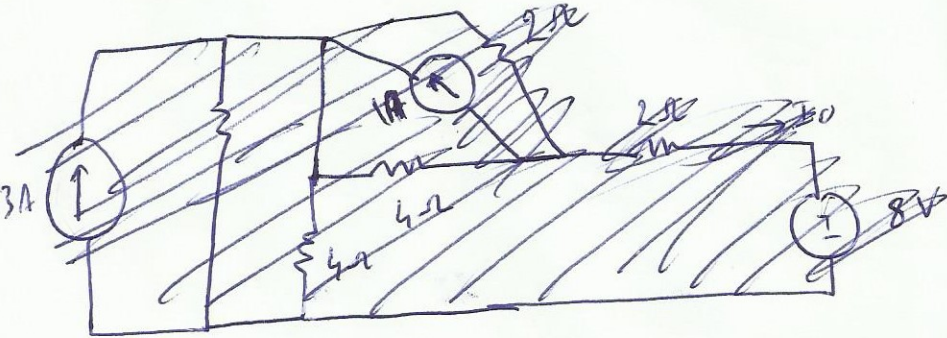
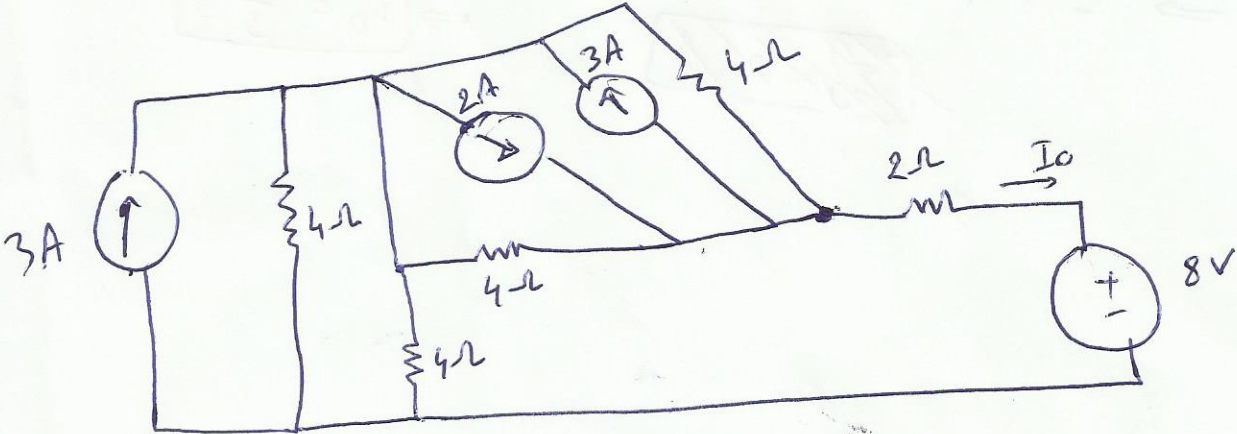


Figure 4

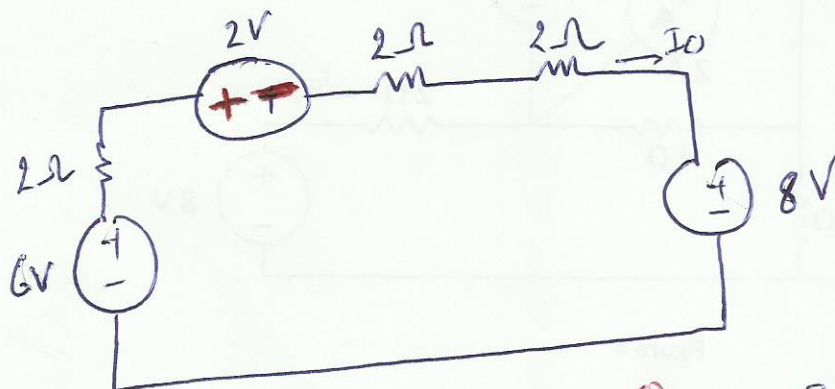

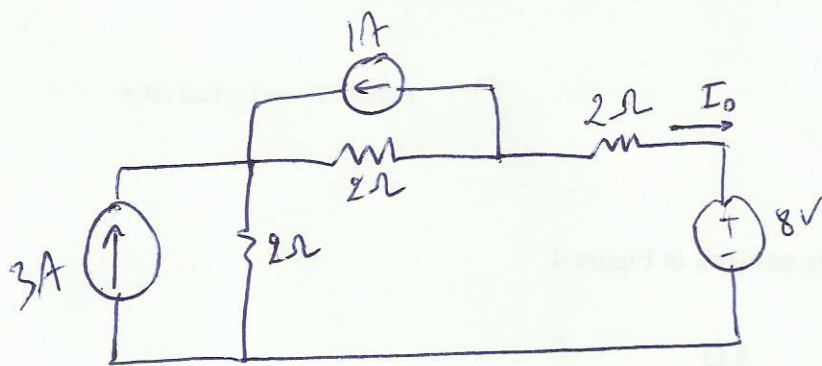

$$\text{KVL} \Rightarrow -6 + 6I_0 + 2 + 8 = 0 \Rightarrow 6I_0 = -4$$

$$\Rightarrow I_0 = -\frac{2}{3} \text{ A}$$

~~$$I_0 = 0 \text{ A}$$~~

Question 5 (30 points)

Consider the network in Figure 5.

- Find the thevenin equivalent of Circuit A as seen by the rest of the network.
- Calculate the maximum power that can be transferred to R_L and the value of R_L for which this happens.



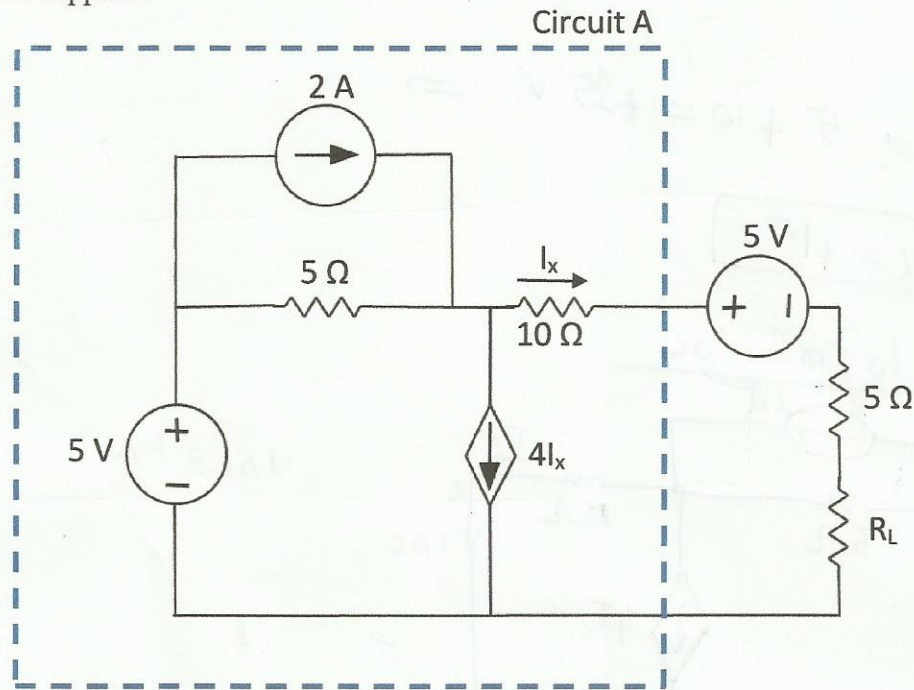


Figure 5

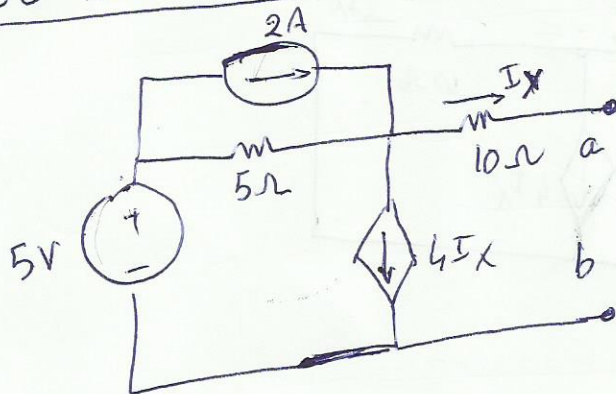We cut circuit A: (we remove the remaining part from the circuit)



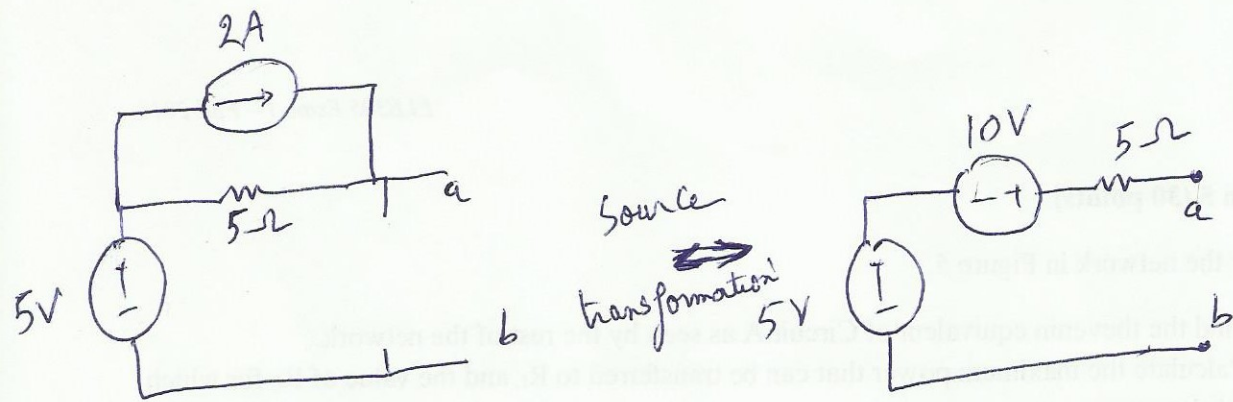
$V_{Th} = V_{ab} = V_{oc}$
 since open circuit $\Rightarrow I_x = 0 \text{ A} \Rightarrow 4I_x = 0 \text{ A} \Rightarrow$ we can open the
 branch of the $(4I_x)$
 dependent current source
 and remove the 10Ω
 resistance




(KVL) $V_{ab} = 5 + 10 = +15 \text{ V} \Rightarrow$

$V_{Th} = +15 \text{ V}$

Now, we need to find i_{sc} :

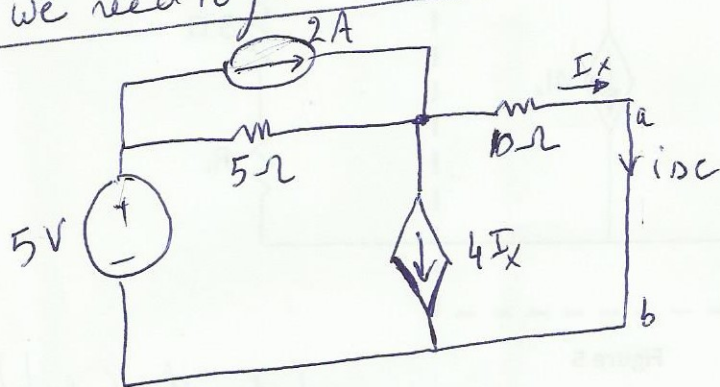

Let us find I_x :

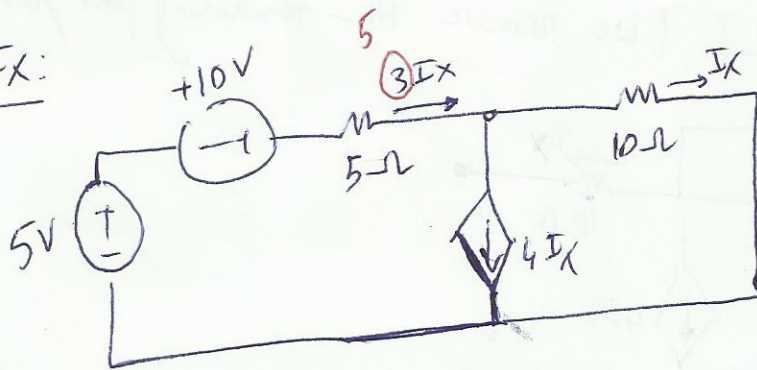


Apply KVL to the outer loop:

$$-5 - 10 + 5 \times 3I_x + 10 I_x = 0 \Rightarrow$$


$$35 I_x = 15 \Rightarrow I_x = \frac{15}{35} = \frac{3}{7} \text{ A} \Rightarrow i_{sc} = \frac{3}{7} \text{ A}$$

Then $R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{15 \text{ V}}{\frac{3}{7}} = 35 \Omega$

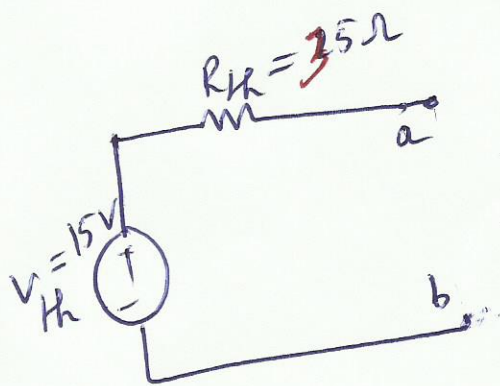
The Thevenin Equivalent of the circuit (A) as seen by the remaining elements is:



b. the equivalent circuit looks like

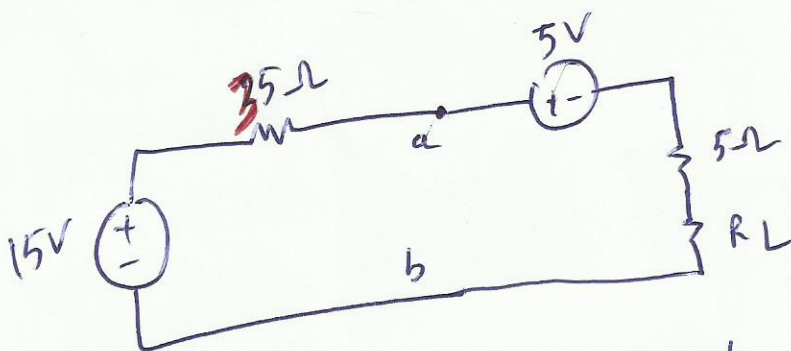

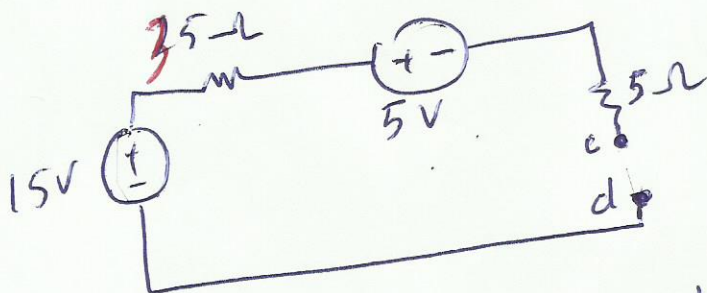In order to ensure a max power transfer to R_L , we need to find the ~~Req~~ R_{Th} of the Thevenin equivalent circuit as seen by R_L !



→ $V_{Th} = V_{cd} = V_{oc} = 20V$ (we do not need it)

→ to find R_{Th} , zero the voltage sources and find $R_{eq} = R_{cd}$. For a max power transfer to R_L

we obtain $R_{cd} = \frac{40}{30} \Omega = R_{eq} = R'_{Th}$. Then $R_L = 40 \Omega$