
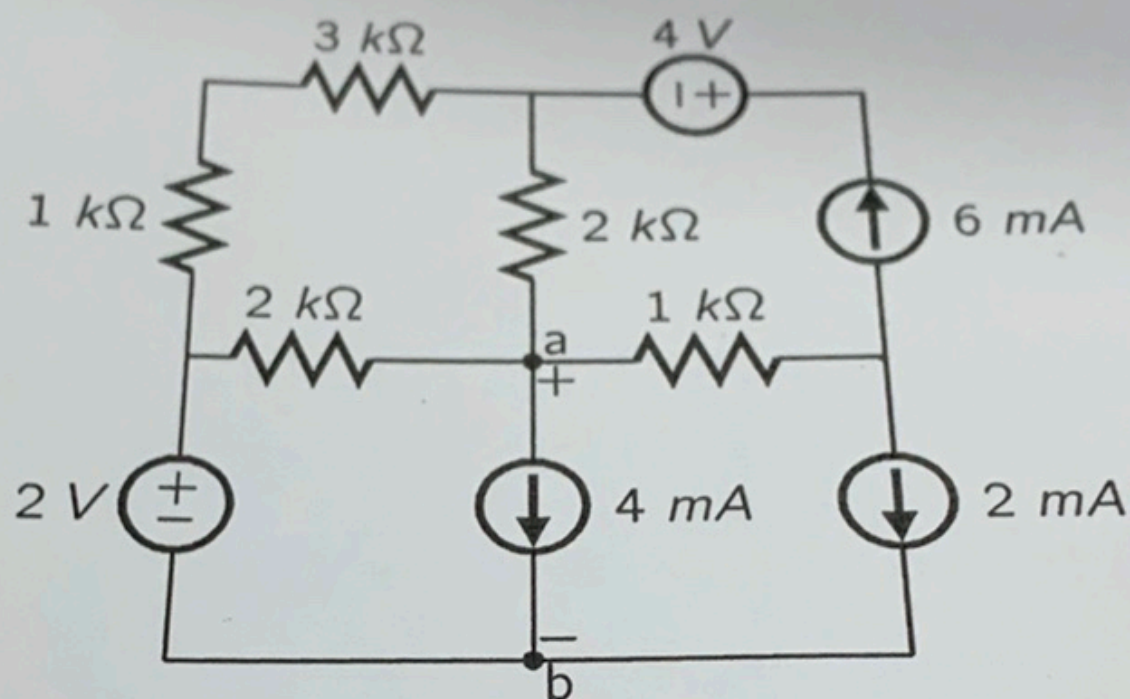


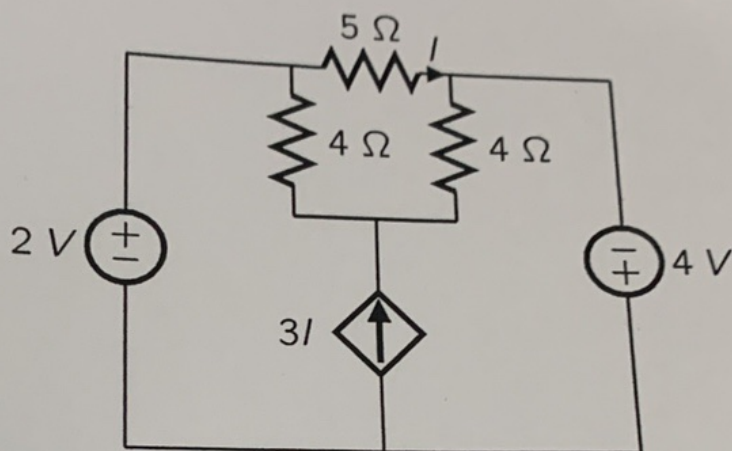1. (30 points) **Thévenin Equivalent Circuit.**
Consider the following circuit.



- a. [15 points] Find R_{TH} between the terminals $a - b$.
- b. [10 points] Find V_{TH} between the terminals $a - b$. Remove the 4 mA source.
- c. [5 points] Deduce the power delivered by the 4 mA current source.


3. (30 points) **Mesh Current Analysis.**
Consider the following circuit





- a. [15 points] Using the mesh current technique, find the current I .
- b. [15 points] Using the mesh current technique, find R_{TH} between the terminals of the

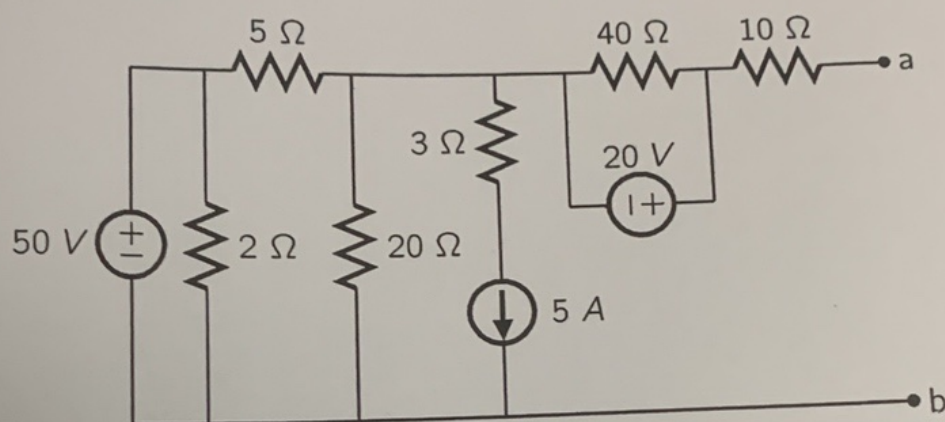4. (20 points) **Thévenin Equivalent.**

Using source transformation, find the Thévenin equivalent voltage V_{TH} between the terminals a and b in the following circuit.



Exon 2 Correction

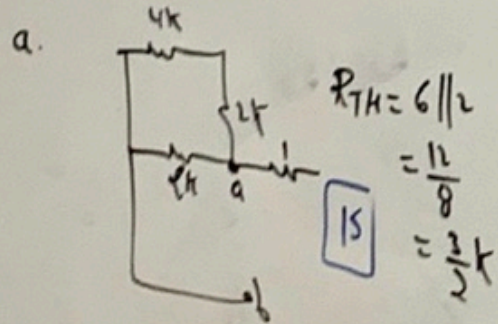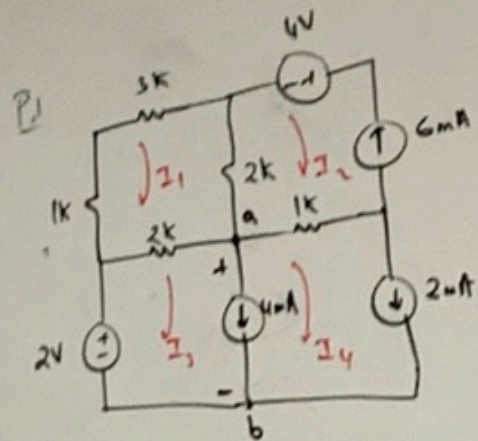

b.

$$I_2 = -6mA$$

$$I_4 = 2mA$$


$$I_3 = 2mA$$

$$4I_1 + 2(I_1 + 6) + 2(I_1 - 2) = 0$$

$$\Rightarrow I_1 = -1mA$$

10
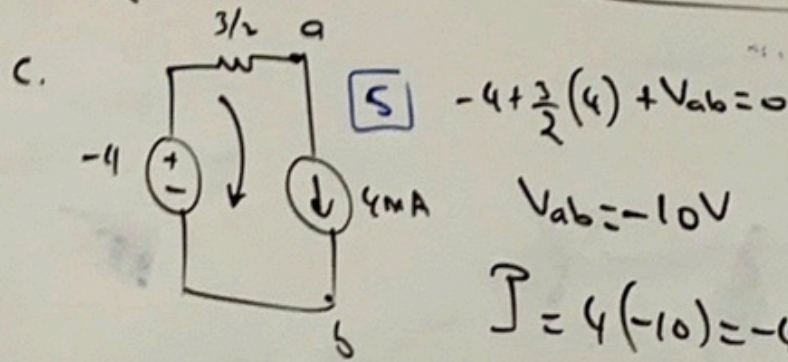
$$2(2+1) + V_{oc} - 2 = 0 \Rightarrow \underline{\underline{V_{oc} = -4V = V_{TH}}}$$



$$V_{ab} = -10V$$

$$P = 4(-10) = \underline{\underline{-40mW}}$$

Correction

b. $\sum P = 1$


$$P = \frac{V_a}{1} + \frac{V_b}{2} + \frac{V_c}{1} + \frac{V_d}{2} + \frac{(V_b - V_d)}{2}$$

$$+ \frac{(V_a - 5 - V_d)}{1}$$

$$= \underline{\underline{1350W}} \quad (10)$$

2

P2

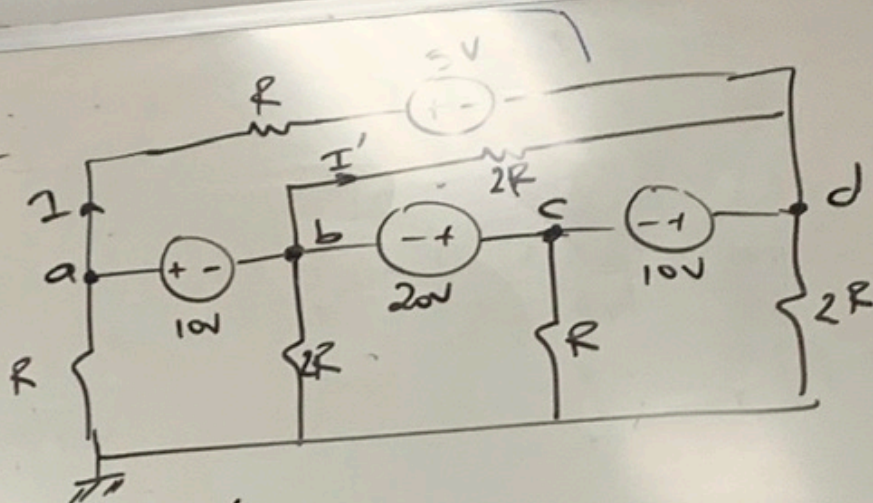

a) $\frac{V_a}{R} + \cancel{I} + \frac{V_b}{2R} + \cancel{I'} + \frac{V_c}{R} + \frac{V_d}{2R} - \cancel{I'} - \cancel{I} = 0$

(10)


$$\boxed{V_a + \frac{V_b}{2} + V_c + \frac{V_d}{2} = 0}$$

$$\begin{aligned} V_a - V_b &= 10 \Rightarrow V_b = V_a - 10 = \underline{\underline{-15V}} \\ V_c - V_b &= 20 \Rightarrow V_c = V_a + 10 = \underline{\underline{5V}} \\ V_d - V_c &= 10 \Rightarrow V_d = V_a + 20 = \underline{\underline{15V}} \end{aligned}$$

$$V_a + \frac{V_a - 10}{2} + V_a + 10 + \frac{V_a + 20}{2} = 0 \Rightarrow \boxed{V_a = -5V}$$

Exon 2 Correction

P.3

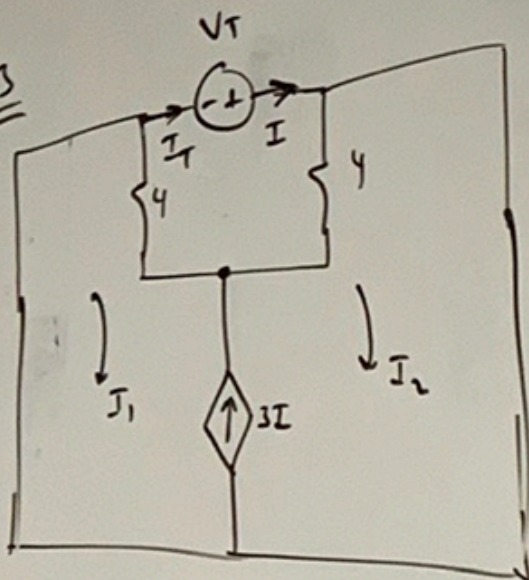

b. $I = I_T$

$$\begin{cases} -V_T + 4(I - I_2) + 4(I - I_1) = 0 \\ 4(I_1 - I) + 4(I_2 - I) = 0 \\ I_2 - I_1 = 3I \end{cases}$$

$$\begin{cases} V_T = 8I_T - 4I_2 - 4I_1 = 0 \\ 4I_1 + 4I_2 = 8I_T \end{cases}$$

15

$$\frac{V_T}{I_T} = 0 = R_{TH}$$

a. $5I + 4(I - I_1) + 4(I - I_2) = 0$

$$4(I_1 - I) - 4 + 4(I_2 - I) = 0$$

$$I_2 - I_1 = 3I$$

15

$$\therefore I = \frac{6}{5} A$$

3

P.4

