

### Homework 13

**P11.1.15** The switch in Figure P11.1.15 is moved to position 'b' at  $t = 0$  after being in position 'a' for a long time. Determine,

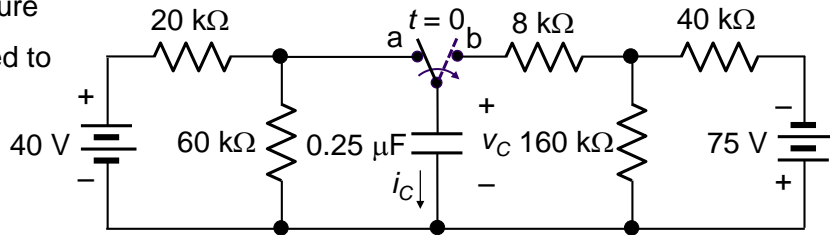


Figure P11.1.15

for  $t \geq 0^+$ : (a)  $v_C(t)$  (b)  $i_C(t)$  from initial and final values as well as from the  $v-i$  relation for the capacitor.

**Solution:** (a)  $v_C(0^-) = 40 \times 60 / 80 = 30$  V; after the switch is moved to position 'b',  $v_C(\infty) = -75 \times 160 / 200 = -60$  V; the resistance seen by C is:

$$8 + 160 \parallel 40 = 8 + 32 = 40 \text{ k}\Omega; \tau_C = 40 \times 10^{-3} \times 0.25 \times 10^{-6} = 10 \times 10^{-3}; 1/\tau_C = 100/\text{s};$$

$$v_C(t) = -60 + (30 + 60) e^{-100t} = -60 + 90 e^{-100t} \text{ V, } t \text{ is in s.}$$

(b) The circuit at  $t = 0^+$  is a two-essential-node

$$\text{circuit. From KCL, } \frac{V_a - 30}{8} + \frac{V_a}{160} + \frac{V_a + 75}{40} =$$

$$0; \text{ this gives } V_a = 12 \text{ V, } i_C(0^+) = (12 - 30)/8 =$$

$$-2.25 \text{ mA. } i_C(\infty) = 0, \text{ so that}$$

$$i_C(t) = -2.25 e^{-100t} \text{ mA. From the } v-i$$

$$\text{relation for the capacitor } i_C(t) = C \frac{dv_C}{dt} = 0.25 \times 10^{-6} (-9000 e^{-100t}) = -2.25 e^{-100t} \text{ mA.}$$

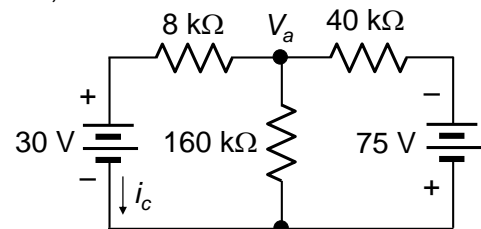


Figure P11.1.15-1

**P11.1.23** The switch in Figure P11.1.23 is moved to position 'b' at  $t = 0$ , after being in position 'a' for a long time. Determine, for  $t \geq 0^+$ , (a)  $v_L(t)$ ; (b)  $i_L(t)$ . A make-before-break switch is used to avoid open-circuiting the source.

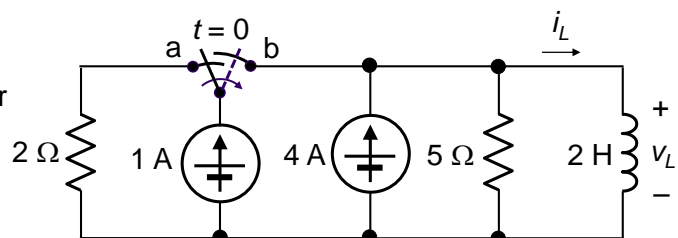


Figure P11.1.23

**Solution:** (a) Just before the switch is moved,  $i_{L0} = 4$  A. Just after the switch is moved,  $i_L$  remains the same and the 1 A source current flows through the 5 Ω resistance, so  $V_{L0} = 5$  V;  $V_{LF} = 0$ , and the time constant is  $2/5 = 0.4$  s. Hence,  $v_L = 0 + (5 - 0) e^{-2.5t} = 5e^{-2.5t}$  V.

(b)  $I_{L0} = 4$  A and  $I_{LF} = 5$  A. Hence,  $i_L = 5 - (4 - 5)e^{-2.5t} = 5 - e^{-2.5t}$  A.

**P11.1.27** The switch in Figure P11.1.27 is opened at  $t = 0$  after being closed for a long time. Determine  $i_L(t)$  for  $t \geq 0^+$ .

**Solution:** After the switch has been closed for a long time, the inductor behaves as a short circuit, so that the voltage across it is zero. This means that there will be a current  $i_L$  flowing downwards through the  $2\ \Omega$  resistor. KCL at the upper node gives  $4 = 2I_{L0}$ , so that  $I_{L0} = 2$  A. The final value of  $i_L$  is zero.

When the inductor is replaced by a test source, the circuit becomes as shown. The dependent source is equivalent to a  $2\ \Omega$  resistor. It follows that  $V_T/I_T = 4\ \Omega$  and  $\tau = 0.5/4 = 1/8$  s.

Hence,  $i_L(t) = 2e^{-8t}$  V,  $t$  is in s.

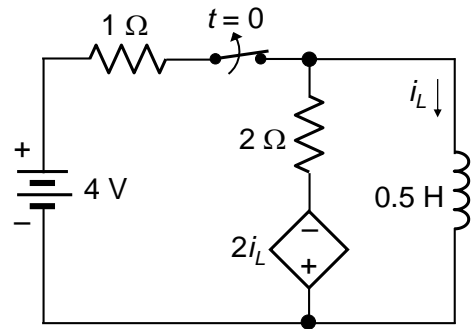


Figure P11.1.27

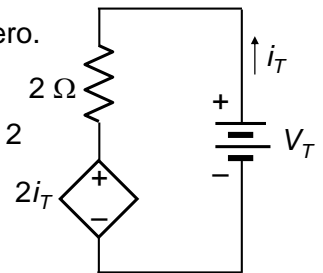


Figure P11.1.27-1

**P11.1.29** The switch in Figure P11.1.29, is closed at  $t = 0$  after being open for a long time. Determine  $v_O(t)$  for  $t \geq 0^+$ .

**Solution:** When the switch has been open for a long time, the capacitor current is zero, so that

$V_A = 4 \times 3 = 12$  V, and  $v_O(0^-) = 3V_A + 24 = 60$  V. As

$t \rightarrow \infty$ ,  $V_A = 0$  and  $V_{OF} = 24$  V. To find the effective resistance across C, a test source  $V_T$  is applied in place of C, as shown. It

is seen that  $V_T = 3V_A$ , where  $V_A = 2I_T$ ; hence,  $\frac{V_T}{I_T} = 6\ \text{k}\Omega$ ,

and  $\tau = 6 \times 20 = 120$  ms. It follows that  $v_O(t) = 24 + 48e^{-t/0.12}$  V, where  $t$  is in s.

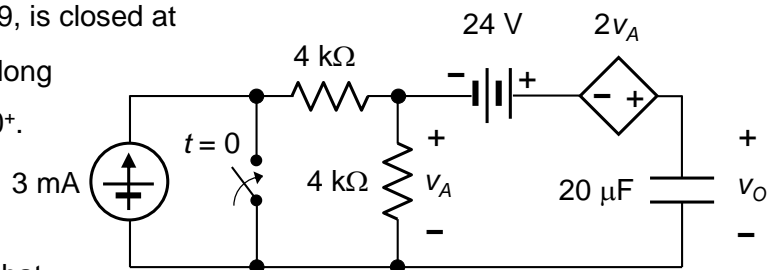


Figure P11.1.29

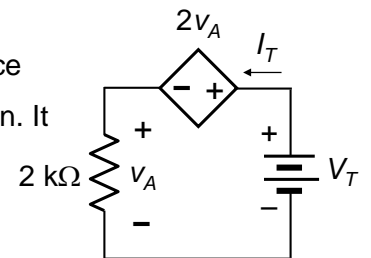


Figure P11.1.29-1

**P11.2.5** The switch in Figure P11.2.5 is moved to position 'b' at  $t = 0$  after having been in position 'a' for a long time.

Determine  $v_o(t)$  for  $t \geq 0^+$ .

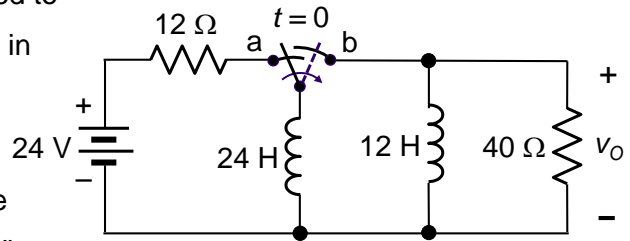


Figure P11.2.5

**Solution:** When the switch is in position 'a', the current in the 24 H inductor is 2 A. When

the switch is moved to position 'b', this current initially flows in the 40 Ω resistor, producing an initial value of  $v_o$  that is  $-2 \times 40 = -80$  V. The final value of  $v_o$  is zero.

The effective inductance is  $\frac{12 \times 24}{36} = 8$  H. The time constant is  $\frac{8}{40} = \frac{1}{5}$  Ω. It

follows that:  $v_o(t) = -80e^{-5t}$  V.

**P11.2.9**  $RC = 1$  ms in Figure P11.2.9. Before the switch is closed, the circuit is in a steady state, with a total energy storage of 1 J. If the switch is closed at  $t = 0$ , determine the total energy stored at  $t = 1$  ms.

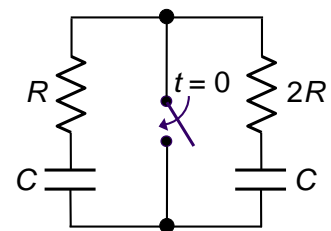


Figure P11.2.9

**Solution:** When the switch is open, the capacitor voltages are equal, each capacitor storing 0.5 J. If the voltage across each capacitor is  $V_{C0}$ , then  $0.5CV_{C0}^2 = 0.5$  J.

After the switch is closed, the voltage across the capacitor on the LHS is  $V_{C0}e^{-t/RC}$  and the voltage across the capacitor on the RHS is  $V_{C0}e^{-t/2RC}$ . At  $t = 1$  ms, these voltages are  $V_{C0}e^{-1}$  and  $V_{C0}e^{-1/2}$ . The stored energy is  $0.5CV_{C0}^2e^{-2} + 0.5CV_{C0}^2e^{-1}$ . Substituting  $0.5CV_{C0}^2 = 0.5$ , the total energy is  $0.5(e^{-2} + e^{-1}) = 0.25$  J.

**P11.2.16** The switch in Figure P11.2.16 is moved at  $t = 0$  from position 'a' to position 'b', after being in position 'a' for a long time. Determine for  $t \geq 0^+$ : (a)  $i_O(t)$ ; (b)  $v_O(t)$ .

**Solution:**  $L_{eq} = 0.2 + 0.4 - 0.2 = 0.4$  H. After the switch has been in position 'a' for a long time, the inductors behave as a short circuit, so that  $I_O = 12$  A. The circuit for  $t \geq 0^+$  is as shown, where  $I_{O0} = 12$  A; so that  $V_{O0} = 24 - 4(12 + 8) = -56$  V. In the steady state,  $V_{OF} = 0$ , and  $2I_{OF} - 4(I_{OF} + 8) = 0$ , so that  $I_{OF} = -16$  A. The resistance seen by the inductor is obtained by applying a test source, with the independent source set to zero.  $V_T + 2I_T = 4I_T$ , which gives  $R_{eff} = 2 \Omega$ . It follows that:  $i_O(t) = -16 + (12 + 16)e^{-5t} = -16 + 28e^{-5t}$  A, and  $v_O(t) = -56e^{-5t}$  V. As a check,  $L di_O/dt = 0.4 \times (28)(-5)e^{-5t} = -56e^{-5t}$ .

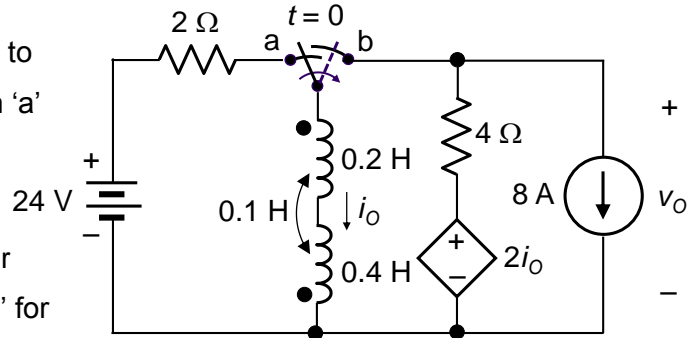


Figure P11.2.16

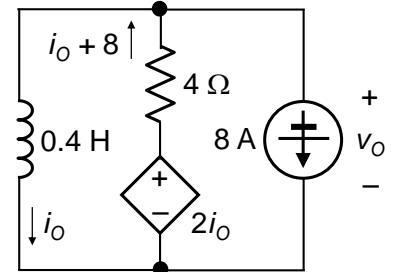


Figure P11.2.16-1

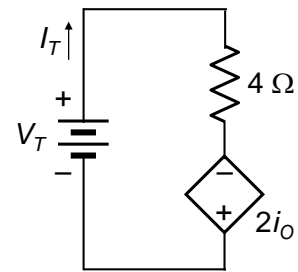


Figure P11.2.16-2

**P11.2.17** The switch in Figure P11.2.17 is opened at  $t = 0$  with no energy initially stored in the circuit.

Determine  $v_s(t)$ ,  $t \geq 0^+$ .

**Solution:** After the switch is opened, the current source partitions the circuit into two;  $v_C(t)$  is that of an  $RC$  parallel circuit charged by a 1 A source.  $v_C(0^+) = 0$ ,  $V_{CF} = 5$  V, and  $\tau = 0.5$  s. It follows that  $v_C(t) = 5(1 - e^{-2t})$

V;

$v_L(t)$  is that of an  $RL$  parallel circuit charged by a 1 A source.  $v_L(0^+) = 5$  V,  $V_{LF} = 0$ , and  $\tau = 2.5/5 = 0.5$

follows that  $v_L(t) = 5e^{-2t}$  V; hence,

$$v_s(t) = v_C(t) + v_L(t) = 5 \text{ V.}$$

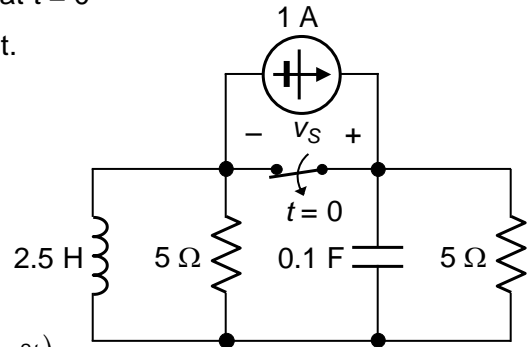


Figure P11.2.17

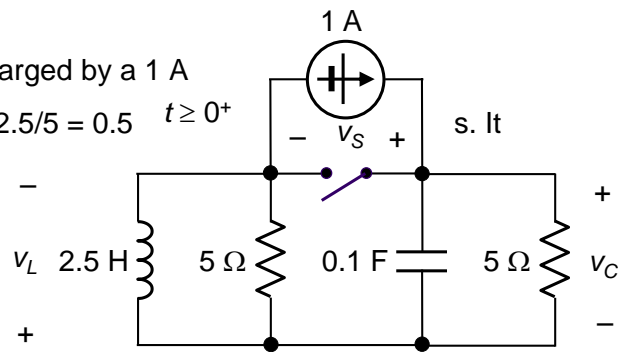


Figure P11.2.17-1