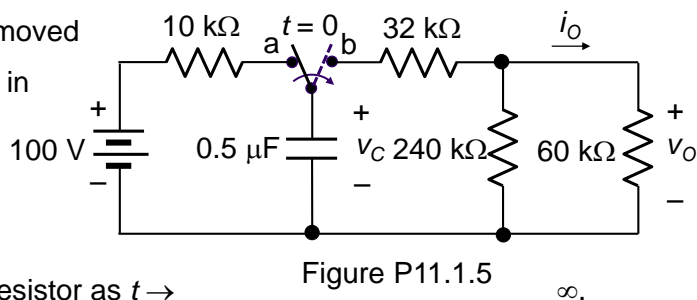


## Homework 12

**P11.1.5** The switch in Figure P11.1.5 is moved to position 'b' at  $t = 0$  after being in position 'a' for a long time.

Determine, for  $t \geq 0^+$ : (a)  $v_C(t)$ ; (b)  $v_O(t)$ ; (c)  $i_O(t)$ ; (d) the total energy dissipated in the  $60 \text{ k}\Omega$  resistor as  $t \rightarrow \infty$ .




**Solution:** (a)  $v(0^+) = 100 \text{ V}$ ;  $V_F = 0$ ; the resistance seen by  $C$  is:  $32 + 240 \parallel 60 = 32 + 48 = 80 \text{ k}\Omega$ ;  $\tau = 0.5 \times 10^{-6} \times 80 \times 10^3 = 0.04 \text{ s}$ ; it follows that  $v_C(t) = 100 e^{-25t} \text{ V}$ ,  $t$  is in s.  
 (b) From voltage division,  $v_O(t) = (48/80)v_C(t) = 60e^{-25t} \text{ V}$ .  
 (c)  $i_O(t) = v_O(t)/60 = e^{-25t} \text{ mA}$ .

(d) The total energy dissipated in the  $60 \text{ k}\Omega$  resistor is  $60 \times 10^3 \int_0^\infty i_O^2(t) dt =$

$60 \times 10^{-3} \int_0^\infty e^{-50t} dt = \frac{60}{50} \times 10^{-3} \approx 1.2 \text{ mJ}$ . Alternatively, The initial energy stored in the capacitor is  $0.5 \times 0.5 \times 10^{-6} \times 10^4 \approx 2.5 \text{ mJ}$ ; the energy dissipated in the  $48 \text{ k}\Omega$  resistor in series with the  $32 \text{ k}\Omega$  resistor is  $2.5 \times 48/80 = 1.5 \text{ mJ}$ ; this energy is dissipated in  $60 \text{ k}\Omega$  in parallel with  $240 \text{ k}\Omega$ , and divides in proportion to the conductances. The energy dissipated in the  $60 \text{ k}\Omega$  resistor is therefore

$$\frac{1/60}{1/60 + 1/240} \times 1.5 = \frac{4}{5} \times 1.5 = 1.2 \text{ mJ}.$$

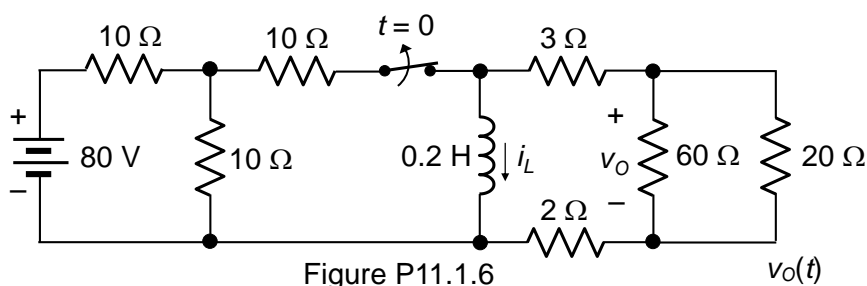**P11.1.6** The switch in Figure P11.1.6 is opened at  $t = 0$  after being closed for a long time. Determine for  $t \geq 0^+$ .



**Solution:** Before the switch is opened, the inductor behaves as a short circuit; the source current is  $80/15 = 16/3 \text{ A}$ , so that  $i_L(0^+) = (16/3)/2 = 8/3 \text{ A}$ ;  $i_{LF} = 0$ ; the resistance seen by inductor is  $5 + 60 \parallel 20 = 20 \Omega$ ;  $\tau = 0.2/20 = 0.01 \text{ s}$ . It follows that

$i_L(t) = (8/3)e^{-100t} \text{ A}$ ,  $t$  is in s; from current division,  $v_O(t) = -15i_L(t) = -40e^{-100t} \text{ V}$ ,  $t$  is in s.

**P11.1.10** The switch in Figure P11.1.10 is opened at  $t = 0$  after being closed for a long time. Determine  $i_X(t)$ ,  $t \geq 0^+$ .

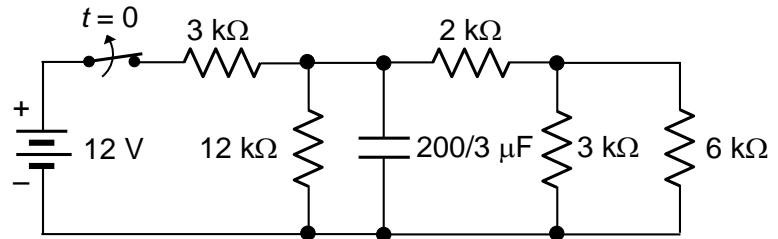


Figure P11.1.10

**Solution:** After the switch has been

closed for a long time, the capacitor behaves as an open circuit;  $6||3 = 2 \text{ k}\Omega$ ; in series with  $2 \text{ k}\Omega$ , this is  $4 \text{ k}\Omega$ ; in parallel with  $12 \text{ k}\Omega$ , this is  $3 \text{ k}\Omega$ ; from voltage division, the initial voltage on the capacitor is  $6 \text{ V}$ ; the current through the  $2 \text{ k}\Omega$  resistor is  $6/4 = 1.5 \text{ mA}$ , the voltage across the parallel combination is  $3 \text{ V}$ , and  $i_X = 1 \text{ mA}$ . When the switch is opened the capacitor voltage does not change at this instant, so  $i_X$  does not change. Hence,  $i_X(0^+) = 1 \text{ mA}$ ;  $i_{XF} = 0$ ; the resistance seen by the capacitor after the switch is opened is  $3 \text{ k}\Omega$ ;  $\tau = (200/3) \times 10^{-6} \times 3 \times 10^3 = 0.2 \text{ s}$ . It follows that  $i_X(t) = e^{-5t} \text{ mA}$ ,  $t$  is in s.

**P11.1.12** Both switches in Figure P11.1.12 have been closed for a long time. The first switch opens at  $t = 0$  and the second switch opens at  $t = 35 \text{ ms}$ .

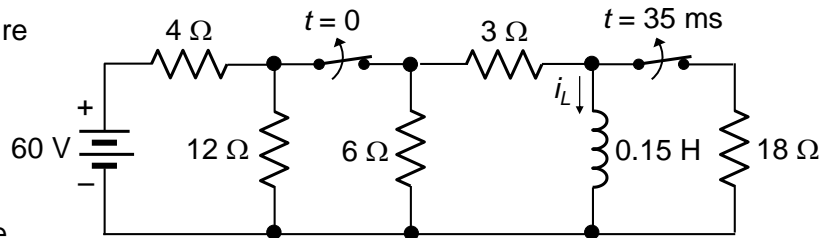


Figure P11.1.12

Determine: (a)  $i_L(t)$  for  $0 \leq t \leq 35 \text{ ms}$ ; (b)  $i_L(t)$  for  $t \geq 35 \text{ ms}$ ; (c) the percentage of the energy initially stored in the inductor that is dissipated in the  $18 \Omega$  resistor.

**Solution:** (a) When the switches have been closed for a long time, the inductor behaves as a short circuit. To determine the initial value of  $i_L$ , the voltage source in series with  $4 \Omega$  can be transformed to a current source of  $15 \text{ A}$  in parallel with  $4 \Omega$ . It

follows from current division that  $i_L(0^+) = 15 \frac{1/3}{1/4 + 1/12 + 1/6 + 1/3} = 6$ .

Between  $t = 0$  and  $t = 35 \text{ ms}$ , the resistance seen by the inductor is  $18||9 = 6 \Omega$ ; hence,  $\tau = 0.15/6 = 0.025 \text{ s} \equiv 25 \text{ ms}$ . It follows that  $i_L(t) = 6e^{-t/25} \text{ A}$ ,  $0 \leq t \leq 35 \text{ ms}$

(b) At  $t = 35 \text{ ms}$ ,  $i_L(35) = 6e^{-35/25} = 1.48 \text{ A}$ ; the resistance seen by the inductor after both switches are open is  $9 \Omega$ , so that  $\tau = 0.15 \times 9 \equiv 50/3 \text{ ms}$ . It follows that  $i_L = 1.48e^{-3(t-35)/50}$ ,  $t \geq 35 \text{ ms}$

(c) For  $0 \leq t \leq 35 \text{ ms}$ , the current in the  $18 \Omega$  resistor is  $i_L/3 = 2e^{-t/0.025} \text{ A}$ ,  $t$  is in s;

the energy dissipated during this period is  $18 \times 4 \int_0^{0.035} e^{-2t/0.025} dt = 0.8453 \text{ J}$ .

The initial energy stored in the inductor is  $0.5 \times 0.15 \times (6)^2 = 2.7 \text{ J}$ .

The percentage is  $(0.8435/2.7) \times 100 = 31.31\%$ .

**P11.1.13** The switch in Figure P11.1.13 is moved to position 'b' at  $t = 0$ , after being in position 'a' for a long time. Determine  $v_C(t)$  for  $t \geq 0^+$ .

**Solution:** Just before the switch is moved,  $V_{C0} = -30 \text{ V}$ ;  $V_{CF} = -20 \text{ V}$ ;  $\tau = 50 \times 10^3 \times 2 \times 10^{-6} = 0.1 \text{ s}$ . Hence,

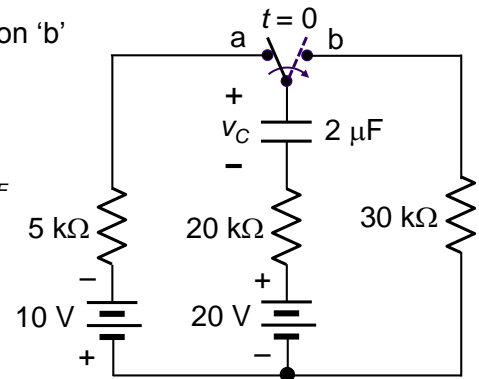


Figure P11.1.13