

Homework 11

P10.1.3 Determine I_o in Figure P10.1.3.

Solution: A current of $j5$ A leaves the marked terminal on the primary side. It follows that a positive current of $j10$ A leaves the unmarked terminal on the secondary side. From current division, $I_o = j10(-j2)/(-j2 + j4) = -j10$ A.

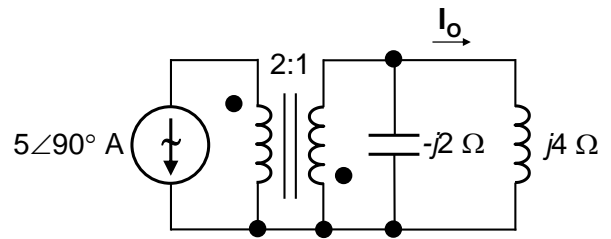


Figure P10.1.3

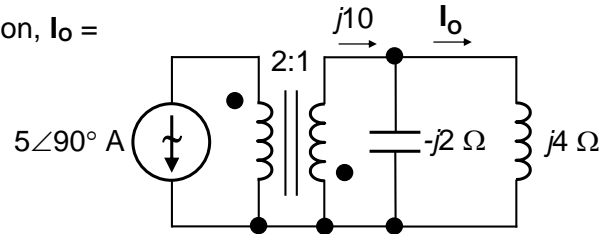


Figure P10.1.3-1

P10.1.11 Determine V_o in Figure P10.1.11.

Solution: The problem will be solved by applying KVL and KCL starting from the output and working backwards toward the source. The current through the $20\ \Omega$ resistor at the output is $V_o/20$ A.

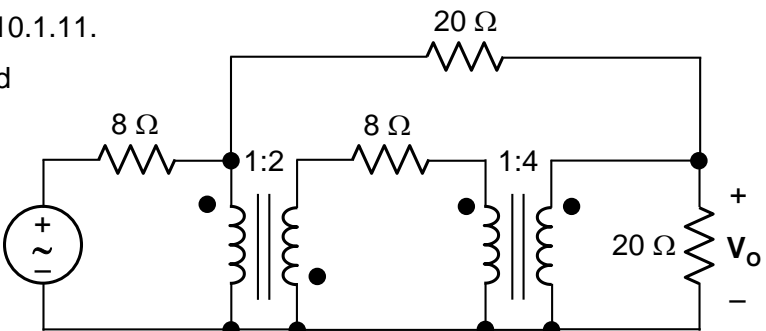


Figure P10.1.11

Denoting the secondary current of the transformer on the RHS by I , the primary $120\angle 0^\circ$ V current is $4I$, the current in the upper $20\ \Omega$ resistor is

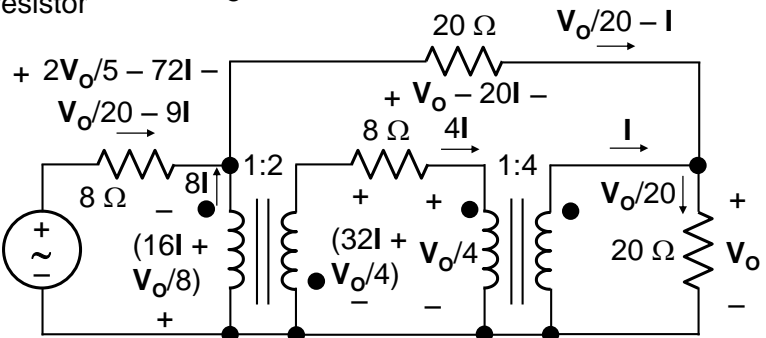


Figure P10.1.11-1

$(V_o/20 - I)$, and the voltage across this resistor is $(V_o - 20I)$. The secondary voltage of the transformer on the LHS is $(32I + V_o/4)$ of the polarity indicated. The primary voltage of this transformer is $(16I + V_o/8)$ and the primary current is $8I$, both of the polarity indicated. The current in the $8\ \Omega$ resistor is $(V_o/20 - 9I)$. From KVL around the mesh on the LHS is: $120 = (2V_o/5 - 72I - V_o/8 - 16I) = (11V_o/40 - 88I)$. KVL around the primary voltage, the $20\ \Omega$ resistor and the output is: $(-16I - V_o/8 - V_o + 20I - V_o) = 0$, which gives $I = 17V_o/32$. Substituting for I gives $V_o = -4800/1859 = 2.58\angle 180^\circ$.

P10.1.20 Determine V_L in Figure

P10.1.20.

Solution: TEC as seen from the primary winding will be derived.

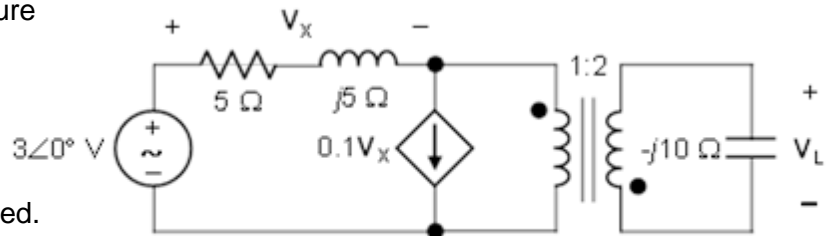


Figure P10.1.20

It is seen that $V_x = 0.1V_x(5 + j5)$,

which makes

$V_x = 0$ and V_{Th}

$= 3$ V. On

short

circuit, $V_x = 3$

V, so that $0.1V_x$

$= 0.3$ V; from

KCL, $3/(5 +$

$j5) = 0.3 +$

I_{sc} , which

$I_{sc} =$

$-j0.3$ A, so that $Z_{Th} =$

$3/(-j0.3) = j10 \Omega$. TEC becomes as shown. Reflecting this to the secondary, it

follows from voltage division that $V_L = -(-j10/j30) \times 6 = 2$ V.

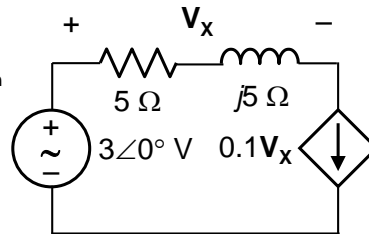


Figure P10.1.20-1

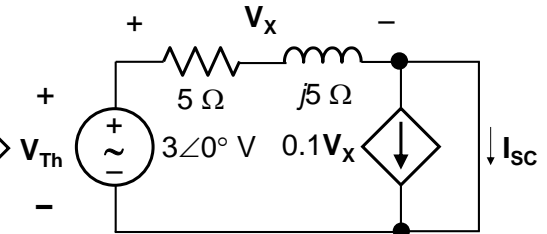


Figure P10.1.20-2

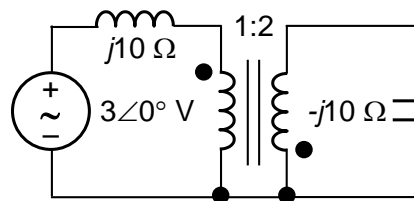


Figure P10.1.20-3

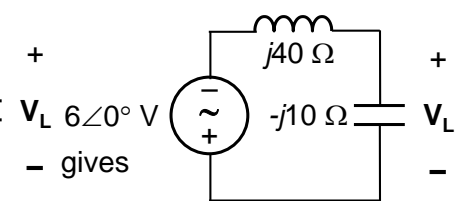


Figure P10.1.20-4

P10.1.30 Determine I_{SRC} in Figure P10.1.30.

Solution: The voltages and currents of the ideal autotransformer may be assigned as shown. From KVL in the mesh involving R , C , and the autotransformer, $2I_2 + 2V_1 + V_1 - (-j2I_2) = 0$, or $3V_1 = -2(1 + j)I_2$. From KVL in the upper mesh, $2I_2 + 2V_1 = 1\angle 0^\circ$. Substituting for V_1 , $2I_2 - (4/3)(1 + j)I_2 = 1\angle 0^\circ = (2/3)(1 - j)I_2$, which gives, $I_2 = \frac{1.5}{1 - j2}$. Since $I_{\text{SRC}} = 3I_2$,

$$I_{\text{SRC}} = \frac{4.5}{1 - j2} = 0.9(1 + j2) = 2.01\angle 63.4^\circ \text{ A.}$$

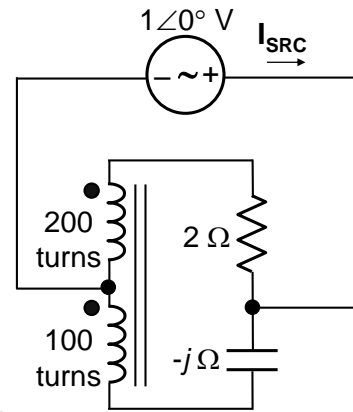


Figure P10.1.30

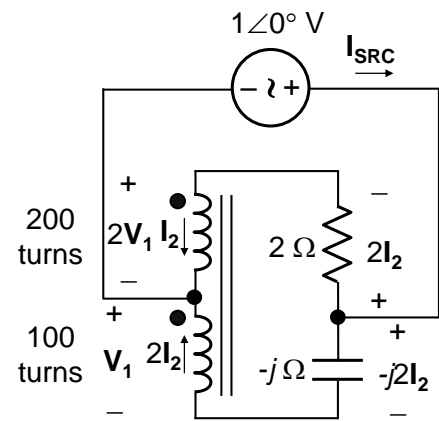


Figure P10.1.30-1

P10.1.36 Derive TEC looking into terminals 'ab' in Figure P10.1.36.

Solution: On open circuit, the equations for the transformer are:

$$\frac{V_2}{V_1} = \frac{300 + 200}{200} = 2.5; V_2 = 10 - 50I_2$$

$$I_2 = \frac{V_1}{-j8} + I_1; 300I_2 + 200I_1 = 0.$$

Substituting V_1 , $I_2 = \frac{V_2}{-j8} + I_1$.

Substituting I_1 , $I_2 = \frac{V_2}{-j8} - \frac{3}{2}I_2$, or $50I_2 = jV_2$.




Substituting $50I_2$, $V_2 = 10 - jV_2$, or

$$V_2 = \frac{10}{1+j} = 5(1-j) \text{ V, and } V_{Th} = 2V_2 =$$

$$10(1-j) \text{ V.}$$

When a test source V_T is applied, with the independent source set to zero, $V_T = 2V_2 = 100I_2$. $V_1 = V_T/5 = -j8I_1$, or $I_1 = jV_T/40$. The mmf equation is: $500I_T + 300(I_T - I_2) + 200(I_T - I_2 - I_1) = 0$, or $10I_T - 5I_2 - 2I_1 = 0$. Substituting I_1 and I_2 in terms of V_T gives:
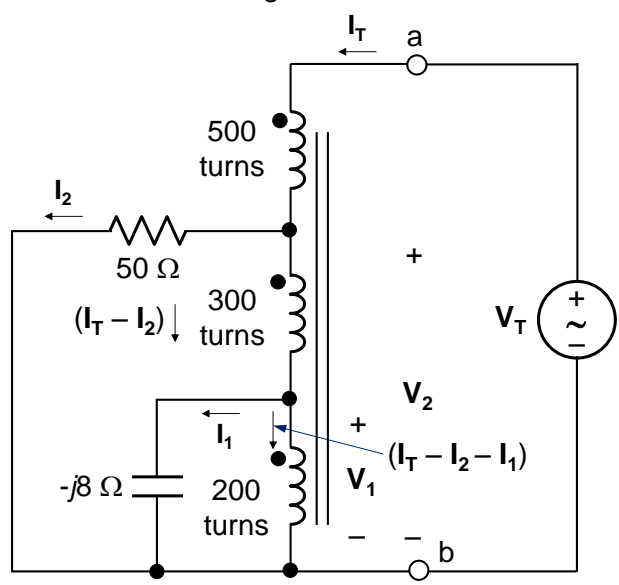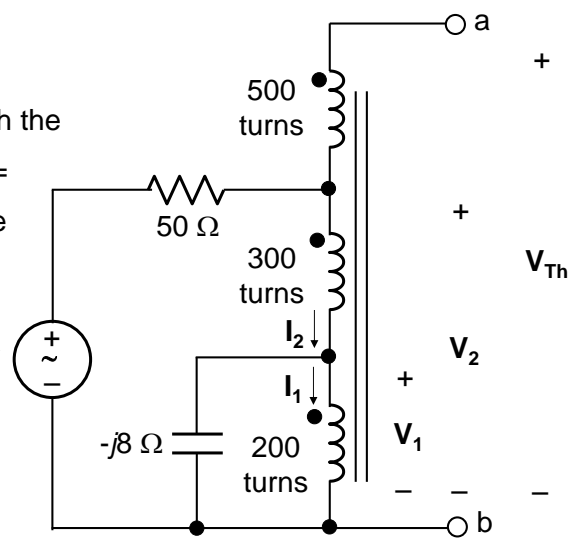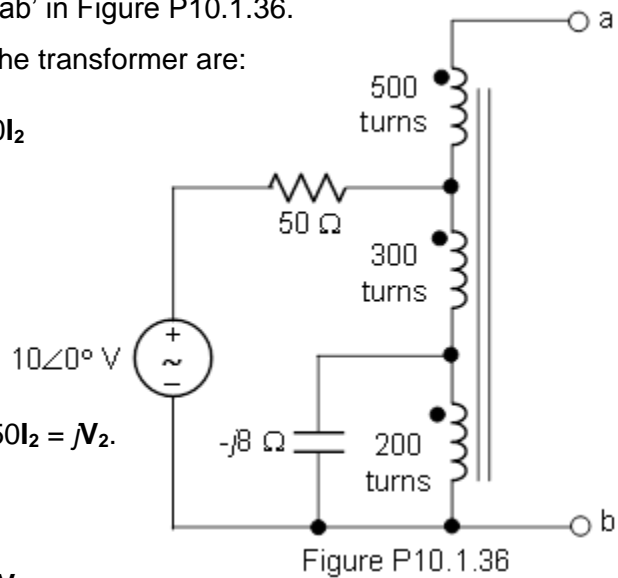
$$\frac{V_T}{I_T} = \frac{200}{1+j} = 100(1-j) \Omega = Z_{Th}.$$



P10.1.40 Derive TEC looking into terminal 'ab' in Figure P10.1.40.

Solution: $V_2 = j50I_1$, $V_{Th} = -j40(-2I_1)$, $50 = 50I_1 + 0.5V_2 - 2V_{Th}$. Substituting for I_1 and V_2 in terms of V_{Th} gives: $50 = -j\frac{5}{8}V_{Th} + \frac{5}{16}V_{Th} - 2V_{Th}$; or, $50 = -\left(\frac{27}{16} + j\frac{5}{8}\right)V_{Th}$, or, $V_{Th} = -26.1 + j9.65$ V.

Let a test voltage source be applied between terminals 'ab'. The $j100 \Omega$ impedance reflected to the primary side is $j25 \Omega$.

$$I_1 = \frac{2V_T}{50 + j25}; I_T = I_c + 2I_1$$

$$2I_1 = V_T \left(\frac{4}{50 + j25} - \frac{1}{j40} \right). \text{ It}$$

$$\text{follows that } \frac{V_T}{I_T} = \left(\frac{1}{\frac{4}{50 + j25} - \frac{1}{j40}} \right) =$$

$$\left(\frac{j40(50 + j25)}{-50 + j135} \right) = 15.44 + j1.69 \Omega.$$



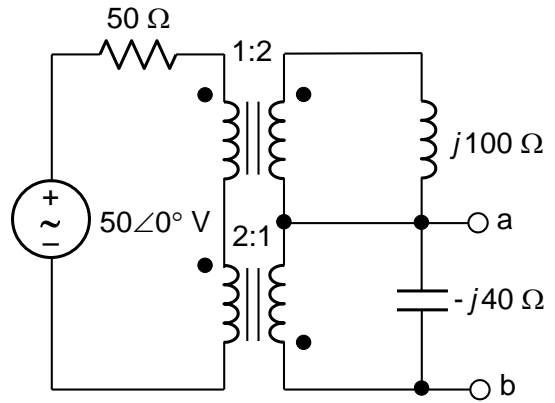


Figure P10.1.40

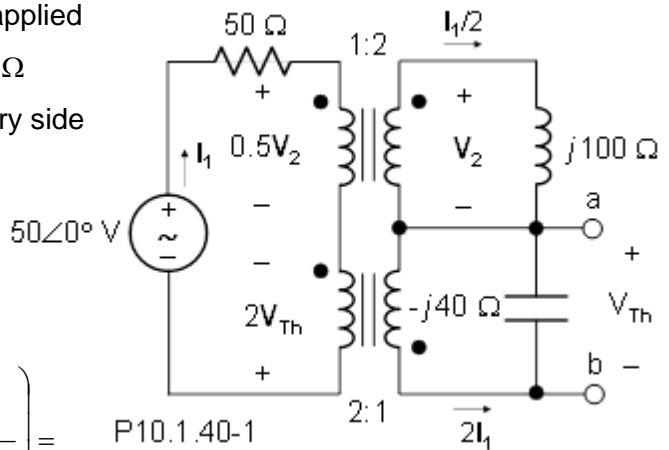

P10.1.40-1

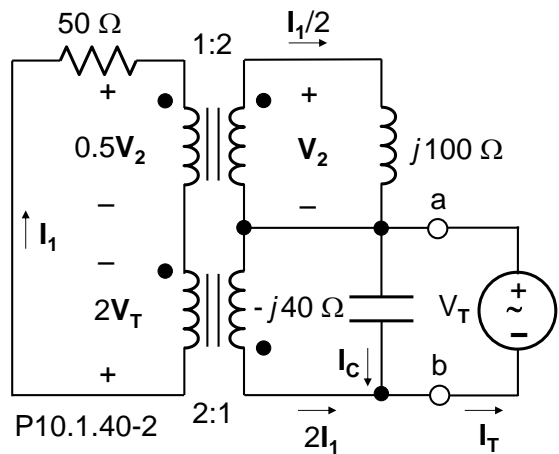

P10.1.40-2

P10.2.5 Determine L_{eq} in Figure P10.2.5.

Solution: It is seen from the current relations for the ideal transformer that $I/2 = (I_T - I)$, or $I = 2I_T/3$. From KVL for each of the two branches:

$$j\omega 6I + j\omega 4.5(I_T - I) + V = V_T \text{ and}$$

$$j\omega 12(I_T - I) + j\omega 4.5I - 2V = V_T$$

Eliminating V and I between these equations

gives $j\omega 6I_T = V_T$, so that $L_{eq} = V_T/j\omega I_T = 6 \text{ H}$.

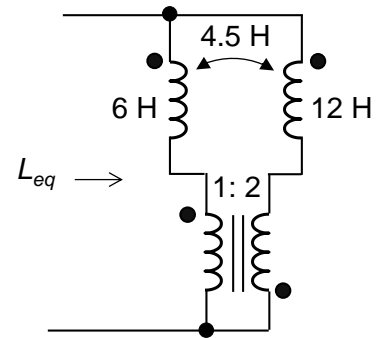


Figure P10.2.5

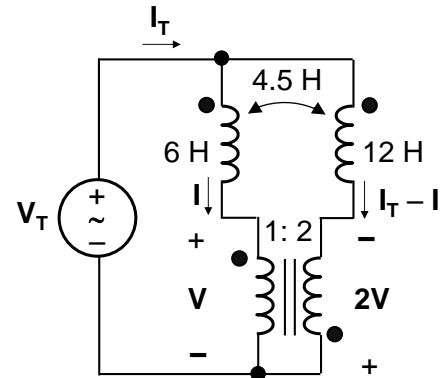


Figure P10.2.5-1

P10.2.7 Determine a in Figure P10.2.7 so that

$Y_{in} = 0$, assuming $\omega = 1$ Mrad/s

Solution: The two coupled coils have $L_{eq} =$

$6 + 4 - 2 \times 3 = 4 \mu\text{H}$, and an impedance of

$j\omega L_{eq} = j4 \Omega$; $1/j\omega C = 1/(j10^6 \times 0.25 \times 10^{-6})$

$= -j4 \Omega$.

When a test source \mathbf{V}_T is applied, the test current \mathbf{I}_T should be zero. The voltage across

$j\omega L_{eq}$ is $(\mathbf{V}_T - a\mathbf{V}_T)$, so that $\mathbf{I} = (1 - a)\mathbf{V}_T/(j4)$.

From KCL at the upper node, $a\mathbf{I} = \mathbf{I} +$

$\mathbf{V}_T/(-j4)$, or $\mathbf{I} = \mathbf{V}_T/[(j4)(1 - a)]$. Equating the

two expressions of \mathbf{I} : $\frac{1 - a}{j4} = \frac{1}{j4(1 - a)}$, or,

$(1 - a)^2 = 1$, $a = 1 \pm 1$, or $a = 2$.

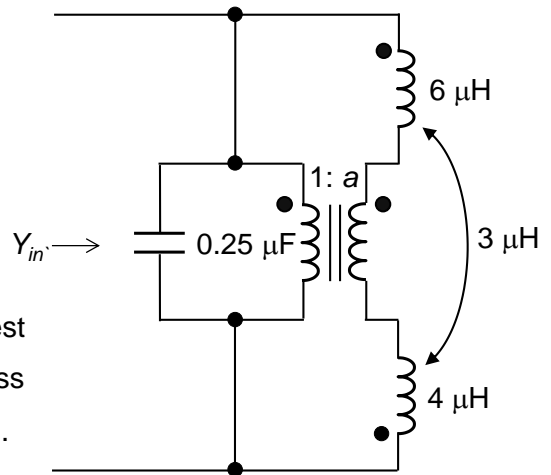


Figure P10.2.7

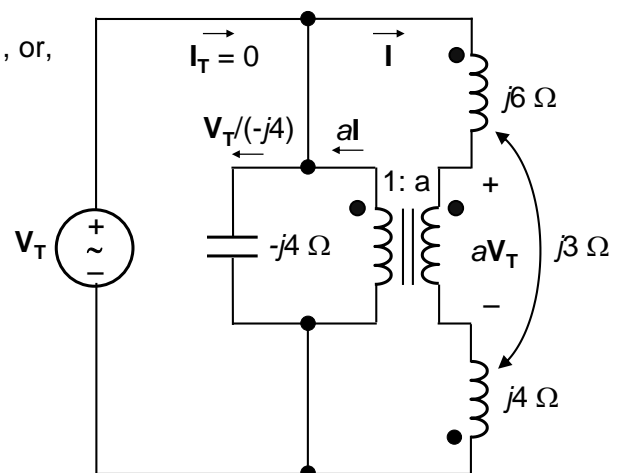


Figure P10.2.7-1