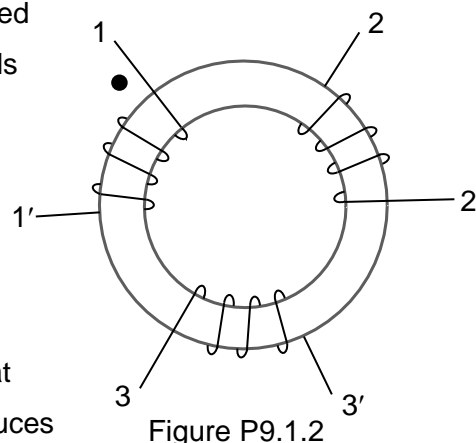


Homework 10


- P9.1.2** The terminal of one coil in Figure P9.1.2 is marked with a dot. (a) Mark one terminal of the other coils with a dot; (b) connect the coils in series for maximum total inductance; (c) determine the inductances of coils 2 and 3, assuming $L_1 = 40$ mH; $M_{12} = M_{23} = 20$ mH, and $k_{12} = k_{23} = 1/\sqrt{2}$; (d) determine M_{13} , assuming $k_{13} = 0.5$.



Solution: (a) The dots on the windings should be such that current entering at the dotted terminals produces flux in the same direction in the core.

(b) To produce maximum inductance, the coils have to be connected so that fluxes are additive.

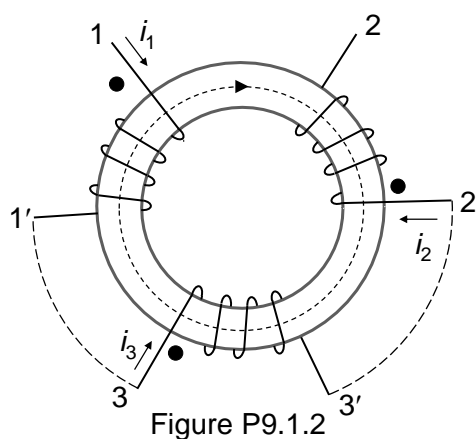- (c) $M_{12} = k_{12}\sqrt{L_1L_2}$, or, $20 = \sqrt{40L_2} / \sqrt{2}$,
 which gives $L_2 = 800/40 = 20$ mH;
 $20 = \sqrt{20L_3} / \sqrt{2}$, which gives $L_3 =$
 $800/20 = 40$ mH;
 $M_{13} = 0.5\sqrt{40 \times 40} = 20$ mH.



- P9.1.20** Determine $v_1(t)$ and $v_2(t)$ in Figure P9.1.20, assuming $i_1(t) = (64t + 50)$ A and $i_2(t) = 15t$ A.


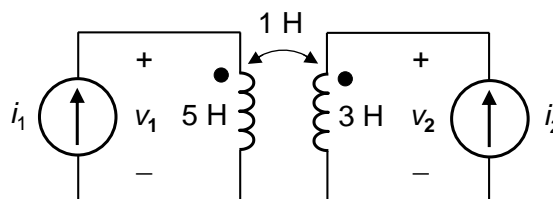
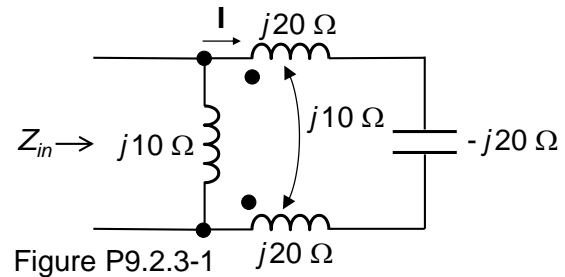


Figure P9.1.20

Solution: $v_1 = L_1 di_1/dt + M di_2/dt = 5 \times 64 + 15 = 335$ V; $v_2 = L_2 di_2/dt + M di_1/dt = 3 \times 15 + 64 = 109$ V.

P9.2.3 Determine Z_{in} in Figure P9.2.3.

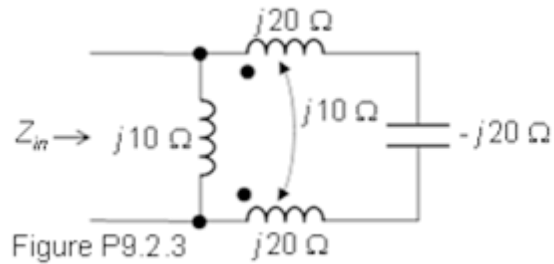Solution: The impedance encountered by the current \mathbf{I} is: $j\omega L_1 + j\omega L_2 - j2\omega M - j/\omega C = j20 + j20 - j20 - j20 = 0$.
Hence, $Z_{in} = 0$.



P9.2.7 By substituting the T-equivalent circuit of either Figure 9.4.1b or Figure 9.4.1d for the linear transformer in Figure P9.2.7, show that the input impedance $\mathbf{V}_1/\mathbf{I}_1$ can be

$$\text{expressed as: } Z_{in} = \frac{\mathbf{V}_1}{\mathbf{I}_1} = j\omega L_1 + \frac{\omega^2 M^2}{j\omega L_2 + Z_L}.$$

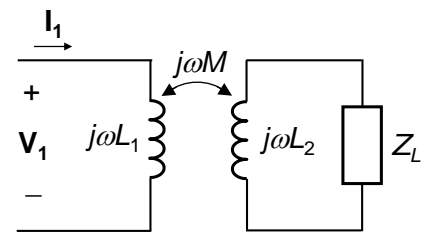


Figure P9.2.7

Note that because M is squared in this expression, Z_{in} is independent of the dot markings.

Solution: Assuming the dot markings of Figure 9.4.1a,

$$\begin{aligned} Z_{in} &= j\omega(L_1 - M) + \frac{j\omega M(j\omega(L_2 - M) + Z_L)}{j\omega L_2 + Z_L} = \\ &= j\omega L_1 + \frac{\omega^2 M L_2 - j\omega M Z_L - \omega^2 M L_2 + \omega^2 M^2 + j\omega M Z_L}{j\omega L_2 + Z_L} \\ &= j\omega L_1 + \frac{\omega^2 M^2}{j\omega L_2 + Z_L} \end{aligned}$$

Since M is squared, this result is independent of the dot markings.

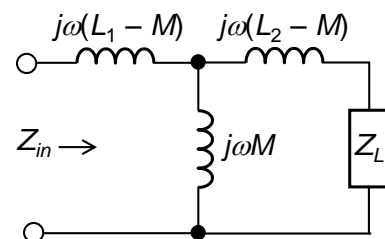


Figure P9.2.7-1

P9.2.11 Using the result of Problem P9.2.7, determine k in Figure P9.2.10 so that: (a) the input impedance Z_{in} is purely resistive; (b) I_1 is maximum.

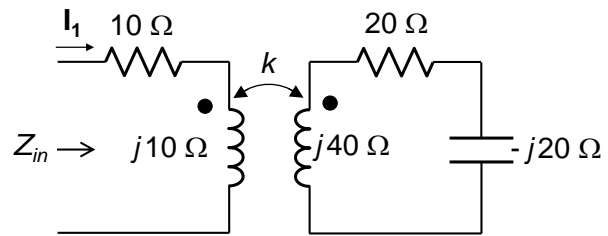


Figure P9.2.11

Solution: Input impedance = $10 + j10 +$

$$\frac{10 \times 40k^2}{j40 + 20 - j20} = 10 + j10 +$$

$$\frac{400k^2}{20 + j20} = 10 + j10 + \frac{20k^2(1 - j)}{2} =$$

$$10(1 + k^2) + j10(1 - k^2).$$

(a) The impedance is purely resistive when $k = 1$.

(b) $|Z_{in}|^2 = 100[(1 + k^2)^2 + (1 - k^2)^2]$; current is maximum when bracketed quantity is minimum. Bracketed quantity is: $2 + 2k^4$ and is a minimum when $k = 0$.

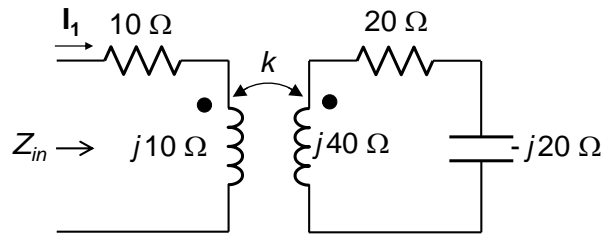


Figure P9.2.11

P9.2.18 Determine the stored energy in the circuit of Figure P9.2.18 in the dc steady state, assuming $M = 1$ H.

Solution: No current flows in the dc state through the 4 H inductor because of the series capacitor. L_{eq} of the 2 H and 3 H inductors is $2 + 3 + 2 \times 1 = 7$ H. This inductor acts as a

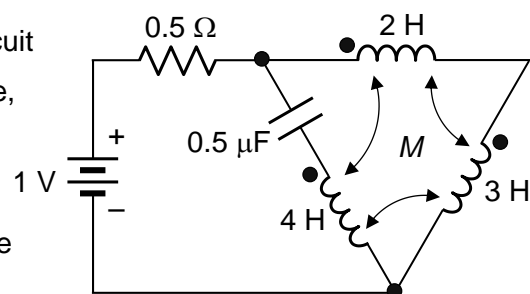


Figure P9.2.18

short circuit, so that the current through it is $1/0.5 = 2$ A, and the voltage the capacitor is zero. The energy stored in the circuit is $0.5 \times 7 \times 4 = 14$ J.

P9.2.27 Derive TEC between terminals 'ab' in Figure P9.2.27.

Solution: With terminals ab open circuited, the equivalent inductance in mesh 1 is $j50 + j40 + 2 \times j30 = j150 \Omega$. Hence,

$$I_1 = \frac{200}{50 + j150 - j100} =$$

$$\frac{4}{1+j} = 2(1-j) \text{ A. } V_{Th} =$$

$$(j40 - j100 + j40 + j30 + j20)I_1 =$$

$$j60(1-j) = 60(1+j) \text{ V.}$$

With terminals ab short circuited,

$$200 = (50 + j50 + j40 - j100)I_1 -$$

$$(j40 - j100)I_2 + j30I_1 +$$

$$j30(I_1 - I_2) - j40I_2 - j20I_2, \quad 200 \angle 0^\circ \text{ V}$$

$$\text{or } (50 + j50)I_1 - j30I_2 = 200. \text{ For}$$

$$\text{mesh 2: } (j80 + j40 - j100)I_2 - (j40 -$$

$$j100)I_1 + j20I_2 + j20(I_2 - I_1) - j30I_1 - j40I_1 =$$

$$0, \text{ or } -j30I_1 + j60I_2 = 0, \text{ or } I_1 = 2I_2.$$

$$\text{Substituting, } I_{sc} = I_2 = \frac{20}{10 + j7} \text{ A.}$$

$$Z_{Th} = \frac{60(1+j)(10+j7)}{20} =$$

$$3(3 + j17) \Omega.$$

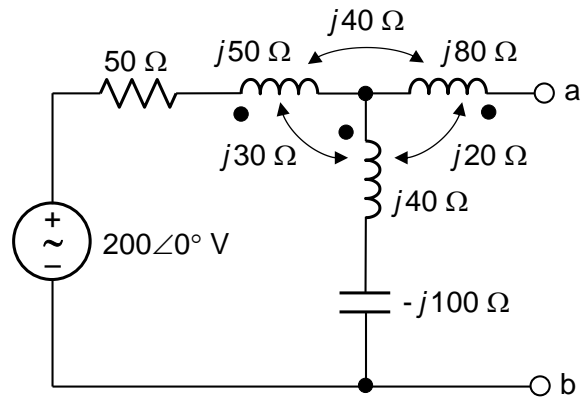


Figure P9.2.27

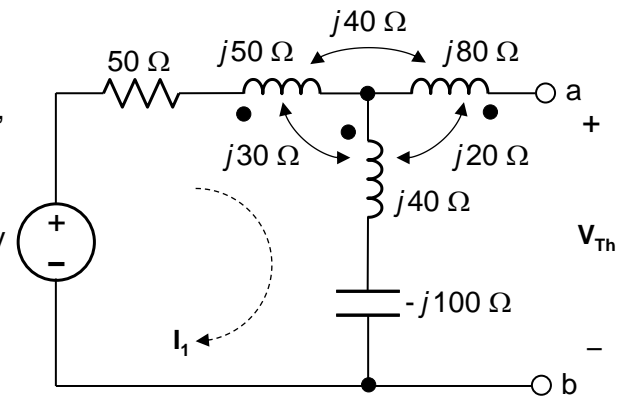


Figure P9.2.27-1

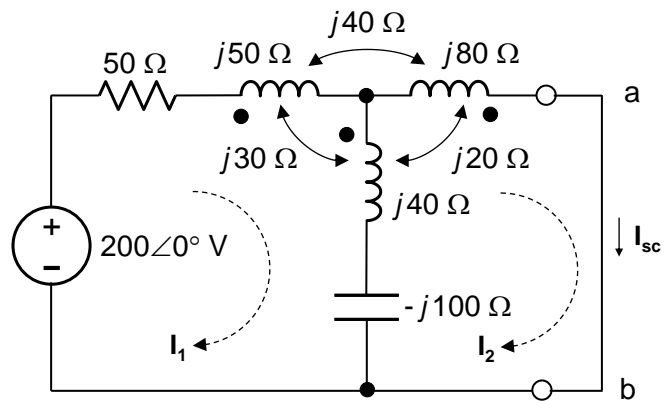


Figure P9.2.27-2

P9.2.38 For the circuit of Figure P9.2.38, (a) Derive the mesh-current equations; (b) determine V_{ab} .

P9.2.38 The mesh-current equations are:
 Mesh 1: $j20I_1 + j10I_2 - j10I_4 = V_Y$,
 where V_Y is a voltage rise across the dependent source in the direction of I_1

Mesh 2: $j10I_1 + (j10 - j10)I_2 + -(-j10I_3)$
 $= -V_Y$

Adding these two equations,

$$j30I_1 + j10I_2 + j10I_3 - j10I_4 = 0$$

Substituting $I_4 = -j$ and $I_3 = 1$ and dividing by $j10$

gives: $3I_1 + I_2 = -1 - j$. Moreover,

$V_x = I_2 - I_1$, where $V_x = 3(1 + j)$.

Substituting for I_2 : $-4I_1 = (1 + j) + 3(1 + j) = 4(1 + j)$, or $-I_1 = (1 + j)$.

$V_{ab} = j10(I_4 - I_1) = j10(-j + 1 + j) = j10 \text{ V}$.

