

Homework 9

P8.1.6 Given $\mathbf{A} = 3 + j5$, $\mathbf{B} = 10 - j8$, and $\mathbf{C} = j12$. Determine the phasors resulting from the following operations: (a) $\mathbf{A}*\mathbf{B}*\mathbf{C}$; (b) $(\mathbf{A}*\mathbf{B})/\mathbf{C}$; (c) $(\mathbf{A}/\mathbf{B})*\mathbf{C}$; and (d) $\mathbf{A}/\mathbf{B}/\mathbf{C}$. Express the result in rectangular and polar forms.

Solution: $\mathbf{A} = 3 + j5 = 5.83\angle 59.04^\circ$
 $\mathbf{B} = 10 - j8 = 12.81\angle -38.66^\circ$
 $\mathbf{C} = j12 = 12\angle 90^\circ$
 (a) $\mathbf{A}*\mathbf{B}*\mathbf{C} = 896.1\angle 110.4^\circ \equiv -312 + j840$
 (b) $(\mathbf{A}*\mathbf{B})/\mathbf{C} = 6.22\angle -69.62^\circ \equiv 2.17 - j5.83$
 (c) $(\mathbf{A}/\mathbf{B})*\mathbf{C} = 5.46\angle 187.7^\circ \equiv -5.41 - j0.73$
 (d) $\mathbf{A}/\mathbf{B}/\mathbf{C} = 0.0376 + j0.0051, 0.0379\angle 7.696^\circ$

P8.2.20 Determine Z_{Th} looking into terminals 'ab' in Figure P8.2.20.

Solution: The admittance of L in parallel with C $-j/20 + j/10 = j0.05$ S. It follows that $\mathbf{V}_x = 2\mathbf{V}_x \times j0.05$, so that $\mathbf{V}_x = 0$. Hence, $Z_{Th} = 1/j0.05 = -j20 \Omega$.

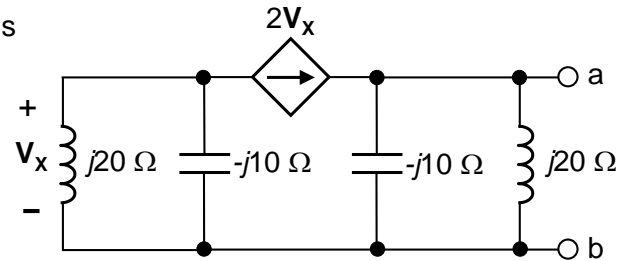


Figure P8.2.20

P8.3.12 Determine \mathbf{V}_x in Figure P8.3.12.

Solution: The $j2 \Omega$ in series with $-j2 \Omega$ is a short circuit. It follows that $\mathbf{V}_x = 20\angle 60^\circ \frac{2}{2 + j2} = 10\angle 60^\circ (1 - j) = 10\sqrt{2}\angle 15^\circ$ V.

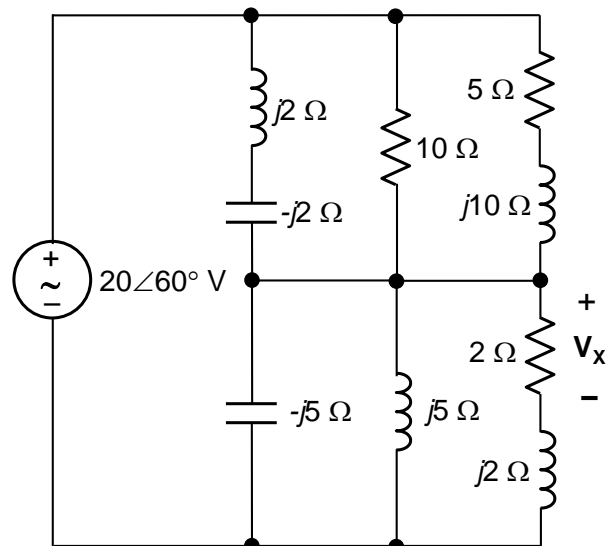


Figure P8.3.12

P8.3.26 Determine $i_C(t)$ in Figure P8.2.26, assuming $v_{SRC}(t) = \sin(1000t + 30^\circ)$ V.


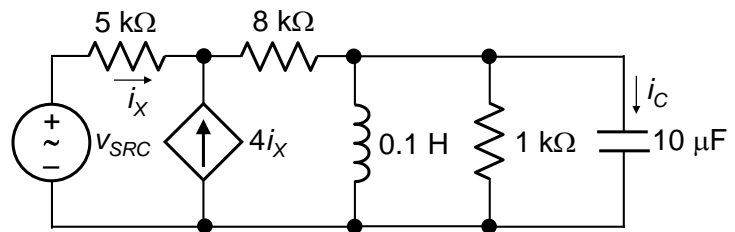


Figure P8.3.26

Solution: $j\omega L = j1000 \times 0.1 = j100 \Omega$; $-j/\omega C = -j/(1000 \times 10^{-5}) = -j100 \Omega$; it follows that the parallel impedance of L and C is infinite. The circuit reduces to that shown in the frequency domain. From KVL, $\mathbf{V}_{SRC} = 5\mathbf{I}_x + 5(8 + 1)\mathbf{I}_x = 50\mathbf{I}_x$; $\mathbf{I}_x = \mathbf{V}_{SRC}/50$ mA; $\mathbf{V}_C = 1(5\mathbf{I}_x) = \mathbf{V}_{SRC}/10$ V; $\mathbf{I}_C = j\omega C \mathbf{V}_C = j\mathbf{V}_C/100$ A $\equiv j\mathbf{V}_{SRC}$ mA = $j \times 1 \angle 30^\circ = 1 \angle 120^\circ$ mA. Hence, $i_C(t) = \sin(1000t + 120^\circ)$ mA.

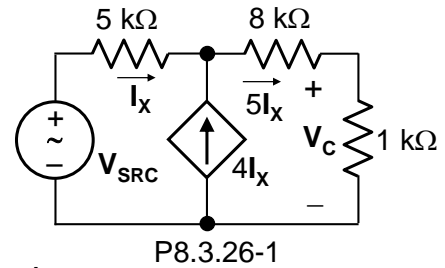

P8.4.10 Determine Z in figure P8.4.10

so that $\mathbf{V}_o = 1 \angle -90^\circ \text{ A}$.

Solution: When terminals 'ab' are open circuited,

$\mathbf{V}_{Th} = \mathbf{V}_{bc} - \mathbf{V}_{ac}$; from current division,

$$\mathbf{I}_{ac} = \frac{(4 - j3)}{8}, \text{ and}$$

$$\mathbf{V}_{ac} = \frac{j3(4 - j3)}{8}; \mathbf{I}_{bc} = \frac{(4 + j3)}{8}, \text{ and}$$

$$\mathbf{V}_{bc} = \frac{4(4 + j3)}{8}; \text{ it follows that } \mathbf{V}_{Th} =$$

$$\mathbf{V}_{ba} = \frac{4(4 + j3)}{8} - \frac{j3(4 - j3)}{8} = \frac{7}{8} \text{ V.}$$

The impedance looking into terminals 'ab',

with the current source set to zero, is $(4 - j3) \parallel (4 + j3) = 25/8 \Omega$. The circuit

reduces to that shown. When $\mathbf{V}_o = 1 \angle -90^\circ = -j$

V, it follows from voltage division that $\mathbf{V}_o = -j =$

$$\frac{7}{8} \frac{Z}{Z + 25/8}, \text{ Solving for } Z \text{ gives: } Z =$$

$$-\frac{25(8 + j7)}{113} \Omega.$$

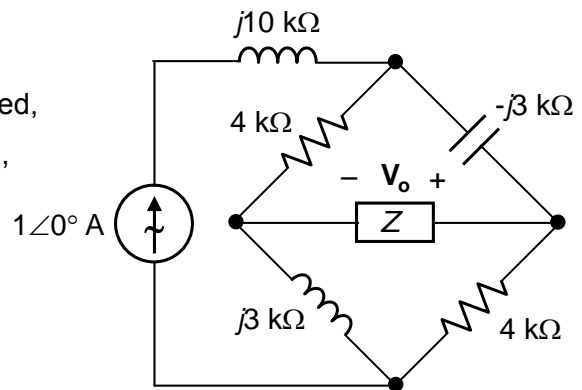


Figure P8.4.10

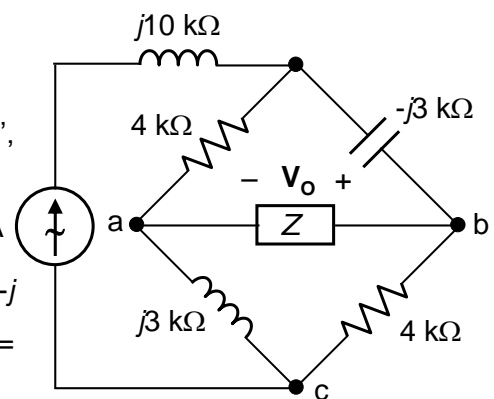


Figure P8.4.10-1

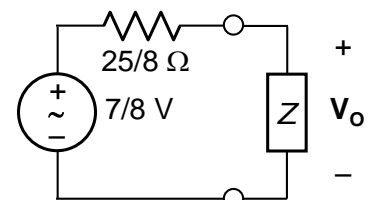


Figure P8.4.10-2

P8.4.11 Derive NEC looking into terminals 'ab' in Figure P8.4.11.

Solution: KCL at the right node:

$$\frac{V_o - 4V_o}{-j250} + I_x + 100\angle 0^\circ V = 0$$

$$\frac{V_o}{50} = 0, \text{ where } I_x = \frac{100 - V_o}{1000}.$$

Substituting, $\frac{3V_o}{j250} + \frac{100 - 4V_o}{1000} + \frac{V_o}{50} = 0.$

This gives $V_o = -4 - j3 \text{ V}.$

When terminals 'ab' are short-circuited, the dependent voltage source is set to zero, which makes $I_x = 0.1 \text{ A}.$ No current flows in the capacitor or in the 50Ω resistor. It follows that $I_N = -I_\phi = -0.1 \text{ A}.$ Hence, $Y_N = \frac{0.1}{4 + j3} = \frac{1}{250} (4 - j3) \text{ S}.$

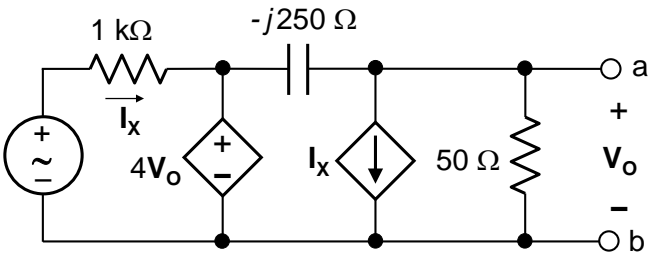


Figure P8.4.11

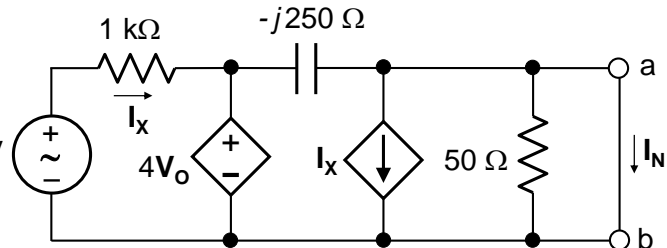


Figure P8.4.11-1

P8.5.6 Determine I_o in Figure P8.5.6 using the mesh-current method.

Solution: The mesh-current equations are:

Mesh 1: $(2 + j2)I_1 - j2I_2 - 2I_3 = j10$

Mesh 2: $-j2I_1 + (4 + j2)I_2 = V_y$

Mesh 3: $-2I_1 + (2 - j4)I_3 = -V_y.$

Adding:

$$-(2 + j2)I_1 + (4 + j2)I_2 + (2 - j4)I_3 = 0.$$

For the current source, $I_2 - I_3 = 5.$ Solving these equations gives $I_o = I_1 - I_3 = 5 + j5 \text{ A}.$

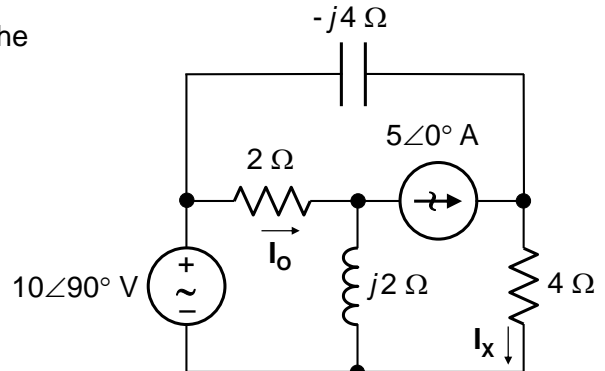


Figure P8.5.6

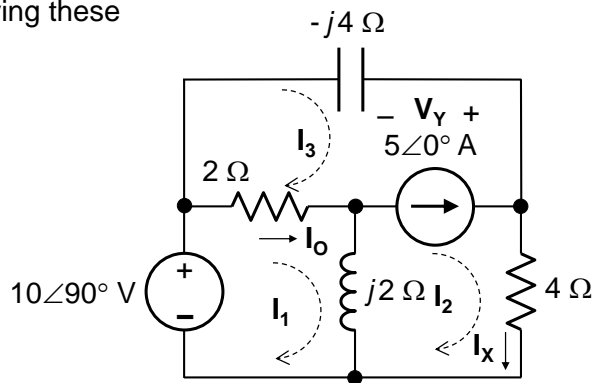


Figure P8.5.6-1

P8.5.7 Determine $v_c(t)$ in Figure P8.5.7 using the node-voltage method.

Solution: $\omega L = 2 \times 10^3 \times 2 \times 10^{-3} = 4 \Omega$; $1/\omega C =$
 $1/2 \times 10^3 \times 100 \times 10^{-4} = 5 \Omega$; the circuit

in the frequency domain becomes as shown. The node-voltage equations are:

Node 'a': $V_a = 10$

Node 'b': $V_c - j5 + (V_c - 10)/j4 + (V_c - V_c)/j4 = 0$

Node 'c': $(V_c - V_c)/j4 + (V_c - 10)/3 = 5I_x =$

$(10 - V_c)/j4$. Solving these equations

gives: $V_c = 11.98 + j1.44 =$

$12.1 \angle 6.86^\circ$, so that $v(t) =$

$12.1 \sin(2000t + 6.86^\circ) \text{ V}$.

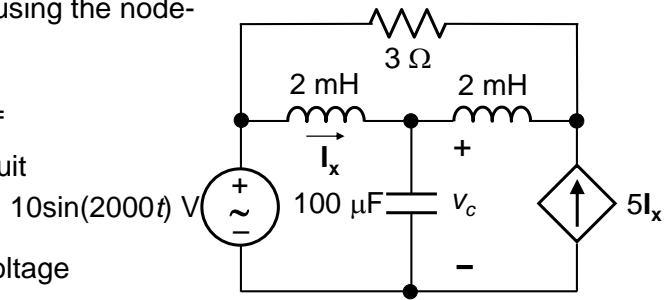


Figure P8.5.7

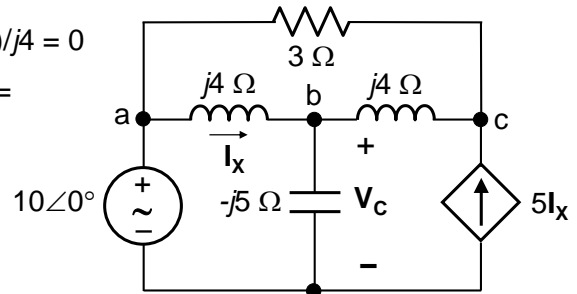


Figure P8.5.7-1