

Homework 7

P6.2.8 Determine V_O in Figure P6.2.8.

Solution: The linear-output current source is transformed to its equivalent voltage source. The mesh current equations are:

$$\text{Mesh 1: } 7I_1 - I_2 - 2I_3 = 80$$

$$\text{Mesh 2: } -I_1 + 7I_2 - 2I_3 = 0$$

$$\text{Mesh 3: } -2I_1 - 2I_2 + 4I_3 = 40$$

Solving these equations gives $I_1 =$

20 A, $I_2 = 10$ A, and $I_3 = 25$ A. It follows that

$$V_O = 4I_2 = 40 \text{ V.}$$

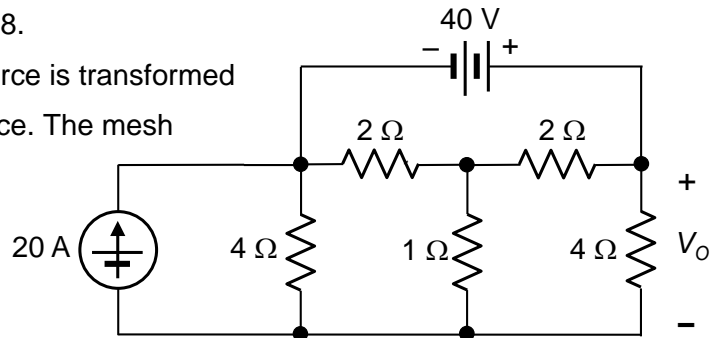


Figure P6.2.8

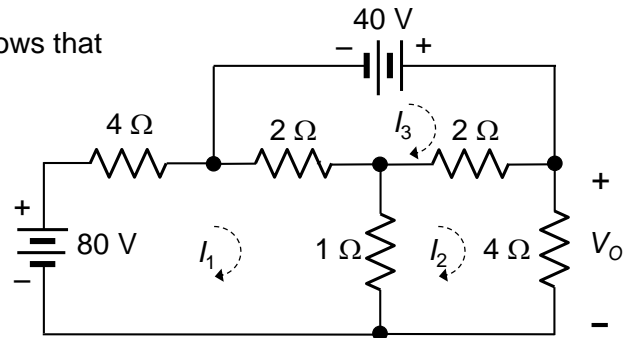


Figure P6.2.8-1

P6.2.12 Determine V_O in Figure P6.2.12.

Solution: The mesh-current equations are:

$$\text{Mesh 1: } 30I_1 - 10I_2 - 20I_3 = 40$$

$$\text{Mesh 2: } -10I_1 + 20I_2 = -20$$

$$\text{Mesh 3: } I_3 = 0.5I_O = 0.5(I_1 - I_2)$$

Solving these equations gives $I_1 = 2$ A,

$I_2 = 0$, and $I_3 = 1$ A. It follows that

$$V_O = 10I_O = 20 \text{ V.}$$

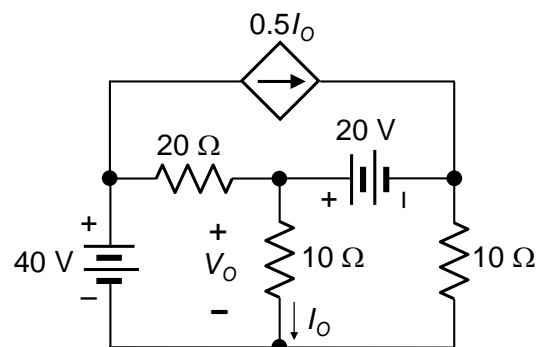


Figure P6.2.12

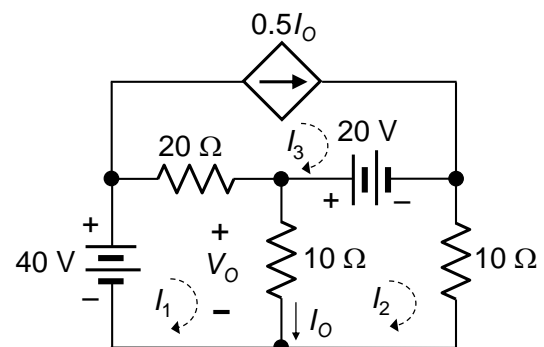


Figure P6.2.12-1

P6.2.22 Determine V_O in Figure P6.2.22, assuming all resistances are $2\ \Omega$.

$$I_X = I_3 - I_1 = -0.5\text{ A and } V_Y = 20I_2 = -10\text{ V.}$$

Solution: The redundant resistor in series with the 5 A current source is removed, and the CCVS is replaced by a $0.5\ \Omega$ resistor. Moreover, it is necessary to remove the “hidden mesh” involving the two grounds. To do so, it is noted that the two bottom $2\ \Omega$ resistors are in parallel, so they form a $1\ \Omega$ resistor in series with the $2\ \Omega$ resistor, the circuit becoming as shown.

The mesh-current equations are:



$$\text{Mesh 1: } I_1 = 5$$

$$\text{Mesh 2: } 4.5I_2 - 2I_4 = 10$$

$$\text{Mesh 3: } -2I_1 + 7I_3 - 3I_4 = 0$$

$$\text{Mesh 4: } I_4 = -0.5I_X = -0.5(I_1 - I_2), \text{ or, } 0.5I_1 - 0.5I_2 + I_4 = 0$$

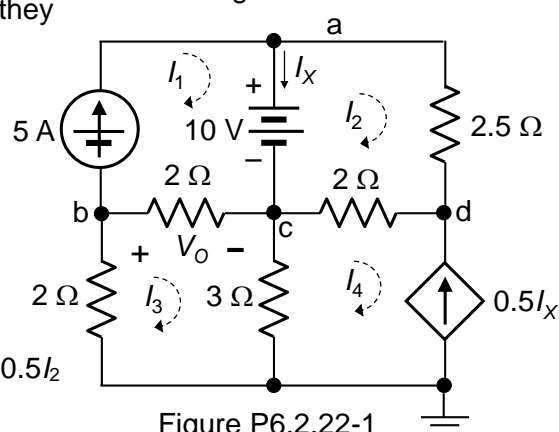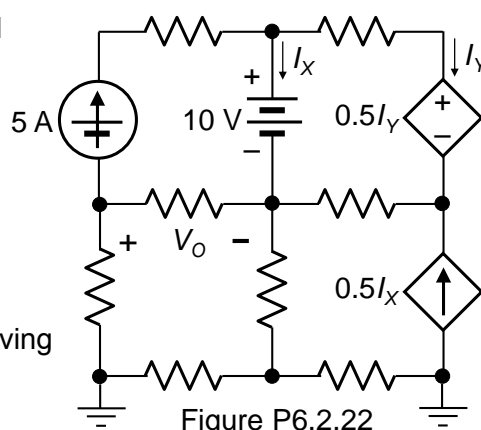Solving these equations gives $I_2 = 10/7\text{ A}$, $I_3 = 65/98\text{ A}$, and $I_4 = -25/14\text{ A}$. It follows that $V_O = 2(I_3 - I_1) = -425/49 = -8.67\text{ V}$.



P6.2.23 Determine V_X in Figure P6.2.23.

Solution: The mesh-current equations are:

$$\text{Mesh 1: } 60I_1 - 40I_2 = V_Y$$

$$\text{Mesh 3: } 10I_3 = -V_Y - 5I_{\phi}, \text{ where } I_{\phi} = I_2.$$

Adding these two equations and substituting for I_{ϕ} :

$$60I_1 - 35I_2 + 10I_3 = 0$$

For the 5 A source, $I_1 - I_3 = 5$

$$\text{Mesh 2: } -40I_1 + 50I_2 = V_X$$

Mesh 4: $20I_4 = 5I_{\phi} - V_X$. Adding these two equations and substituting for I_{ϕ} :

$$-40I_1 + 45I_2 + 20I_4 = 0$$

For the dependent current source,

$$2I_X = I_4 - I_2, \text{ where } I_X = I_1, \text{ or, } 2I_1 + I_2 - I_4 = 0.$$

Solving these equations gives $I_1 =$

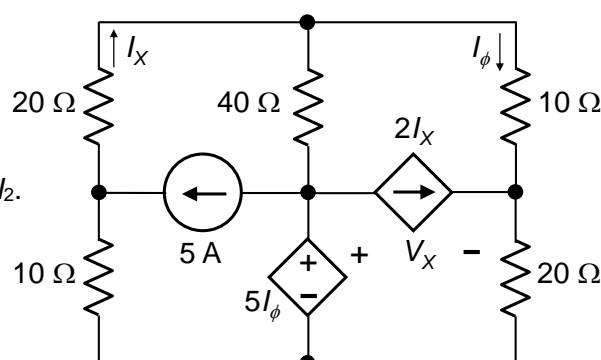


Figure P6.2.23

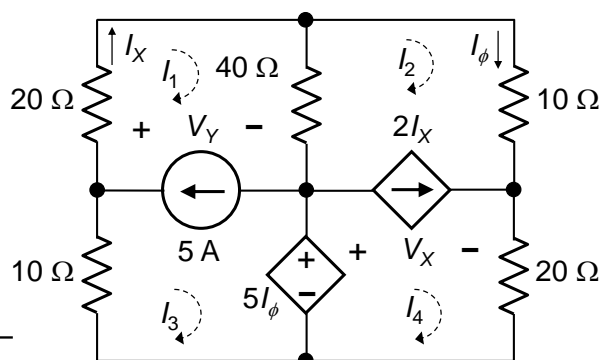


Figure P6.2.23-1

$5/7$ A, $i_2 = 0$, $i_3 = -30/7$, and $i_4 = 10/7$. It follows that $V_X = 40(i_2 - i_1) + 10i_2 = -40i_1 = -200/7 = -28.57$ V.

P7.1.8 The voltage waveform shown in Figure

P7.1.8 is applied to a $1\text{ }\mu\text{F}$ capacitor. Determine the value of the current through the capacitor.

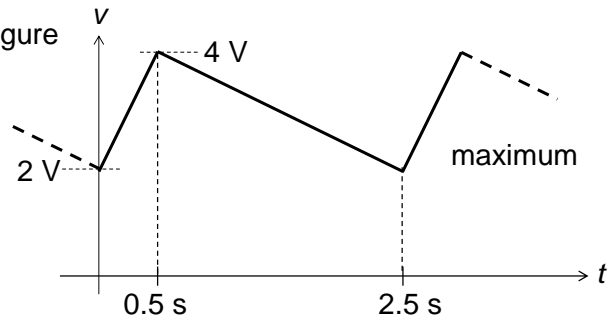


Figure P7.1.8

Solution: The maximum capacitor current occurs on the steeper region of the voltage waveform. $i = Cdv/dt = 10^{-6} \times (2\text{ V}/0.5\text{ s}) = 4\text{ }\mu\text{A}$.

P7.1.10 When the switch is closed in Figure P7.1.10, a current i flows that charges the capacitor. After a sufficiently long time, the capacitor is fully charged to 2 V. Determine, when the capacitor is fully charged: (a) the energy stored in the capacitor; (b) the total energy delivered by the battery, by considering the total charge delivered by the battery.

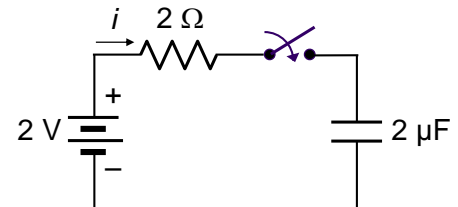


Figure P7.1.10

Soution: (a) When the final voltage is 2 V, the energy stored in the capacitor is $(1/2) \times 2 \times 10^{-6} \times 4 = 4\text{ }\mu\text{J}$.

(b) The total energy supplied by the battery is $w(\infty) =$

$$\int_0^\infty 2i dt = 2 \int_0^\infty i dt = 2q(\infty) = 2 \times 2 \times 10^{-6} \times 2 =$$

$8\text{ }\mu\text{J}$.


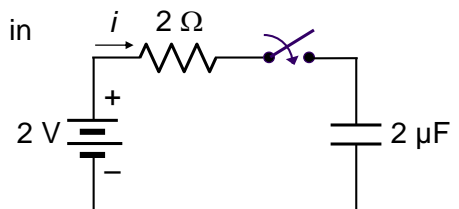


Figure P7.1.10

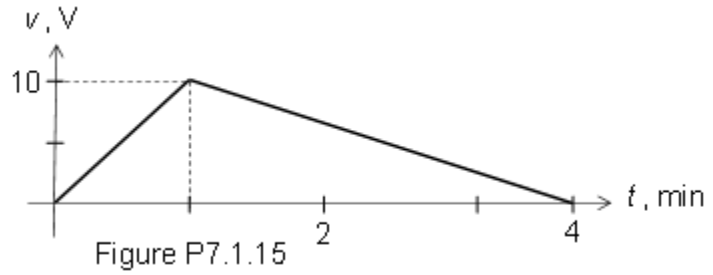P7.1.15 The triangular voltage pulse of Figure P7.1.15 is applied to an initially-uncharged $0.1 \mu\text{F}$



capacitor. Plot as functions of time: (a) the charge on the capacitor; (b) the energy stored in the capacitor, (c) the instantaneous power input to the capacitor.

Solution: $v(t) = \frac{t}{6} \text{ V}, 0 \leq t \leq 60 \text{ s}; v(t) = -\frac{t}{18} + \frac{40}{3} \text{ V}, 60 \leq t \leq 240 \text{ s}; v(t) = 0, t \geq 240 \text{ s}.$

(a) $q(t) = \frac{t}{60} \mu\text{C},$

$0 \leq t \leq 60 \text{ s};$

$q(t) = -\frac{t}{180} + \frac{4}{3} \mu\text{C},$

$60 \leq t \leq 240 \text{ s}; q(t) = 0,$

s.

(b) $w(t) = \frac{1}{2} qv = \frac{t^2}{720} \mu\text{J},$

$0 \leq t \leq 60 \text{ s}; w(t) =$

$= \frac{1}{180} \left(\frac{t^2}{36} - \frac{40t}{3} + 1600 \right)$




$\mu\text{J},$

$60 \leq t \leq 240 \text{ s}; w(t) = 0, t \geq 240 \text{ s}.$

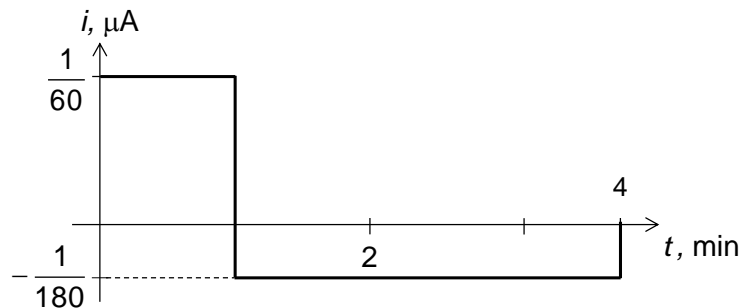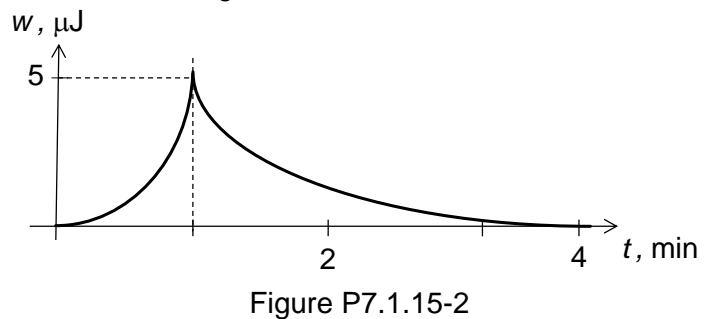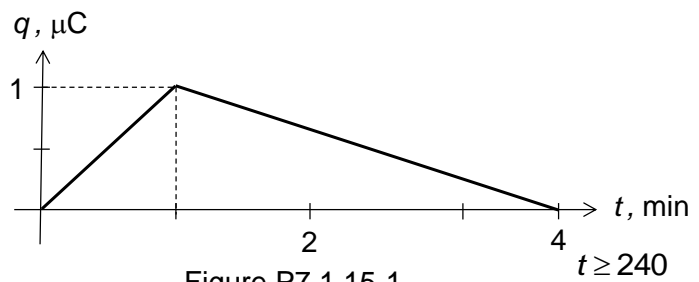(c) $i(t) = \frac{dq}{dt} = \frac{1}{60} \mu\text{A},$

$0 < t < 60 \text{ s}; i(t)$

$= -\frac{1}{180} \mu\text{A}, 60 < t < 240 \text{ s};$



$i(t) = 0$, $t > 240$ s, where $\frac{1}{60}$ μ A may also be expressed as 1 μ C/min.

(d) $p(t) = vi = \frac{t}{360} \mu$ W,

$0 \leq t \leq 60$ s; $p(t) =$

$\frac{1}{180} \left(\frac{t}{18} - \frac{40}{3} \right) \mu$ W,

$60 \leq t \leq 240$ s; $p(t) = 0$,

$t \geq 240$ s, where $\frac{1}{6}$ μ W may

expressed as 10 μ J/min.

It is seen that $w(t) = \int p dt$. Thus $\int_0^t \frac{t}{360} dt = \frac{t^2}{720} \mu$ J, $0 \leq t \leq 60$ s. At $t = 60$ s,

$w(t) = 5 \mu$ J. For $60 \leq t \leq 240$ s $w(t) = \int_{60}^t \frac{1}{180} \left(\frac{t}{18} - \frac{40}{3} \right) dt + 5$

$= \frac{1}{180} \left(\frac{t^2}{36} - \frac{40t}{3} + 1600 \right) \mu$ J.

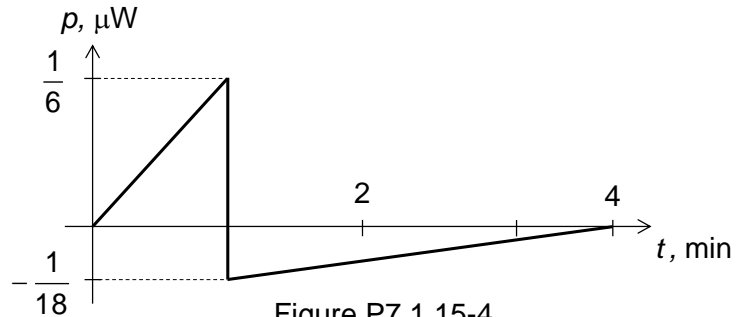


Figure P7.1.15-4

also be

P7.1.16 The current waveform of Figure P7.1.16 is applied to an initially-uncharged 0.5 μ F capacitor. (a) Derive expressions,

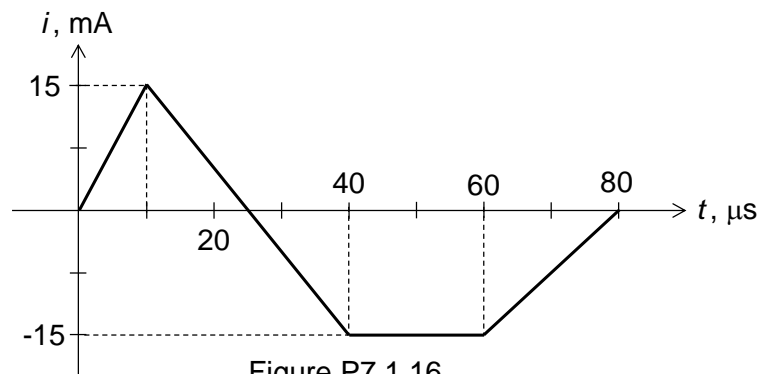


Figure P7.1.16

as functions of time, for the voltage across the capacitor during the time intervals:

$0 \leq t \leq 10 \mu$ s, $10 \leq t \leq 40 \mu$ s, $40 \leq t \leq 60 \mu$ s, $60 \leq t \leq 80 \mu$ s, and $t > 80 \mu$ s. (b)

What is the charge on the capacitor at $t = 10 \mu$ s and at $t = 50 \mu$ s? Check the final value of voltage against the final charge. (c) What is the energy stored in the capacitor at $t = 80 \mu$ s? (d) How do the expressions for the voltage across the capacitor derived in (a) above change if the capacitor was initially charged to 0.5 V?

Solution: $v(t) = \frac{1}{C} \int_{t_0}^t i dt + V(t_0)$

(a) $0 \leq t \leq 10 \mu\text{s}$:

$$v(t) = \frac{1}{0.5} \int_0^t 1.5t dt =$$

$1.5t^2 \text{ mV}$, where t is in μs . At $t = 10 \mu\text{s}$, $v(t) = 150 \text{ mV}$.

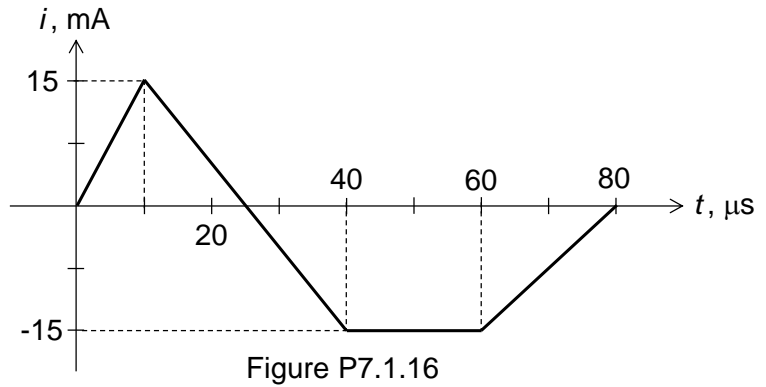


Figure P7.1.16

$10 \leq t \leq 40 \mu\text{s}$: $v(t) = \frac{1}{0.5} \int_{10}^t (-t + 25) dt + 150$

$$= \left[-\frac{1}{2}t^2 + 50t \right]_{10}^t + 150 = -\frac{1}{2}t^2 + 50t - 250 \text{ mV. At } t = 40 \mu\text{s}, v(t) = 150 \text{ mV.}$$

$40 \leq t \leq 60 \mu\text{s}$: $v(t) = \frac{1}{0.5} \int_{40}^t -15 dt + 150 = \left[-30t \right]_{40}^t + 150 = -30t + 1350 \text{ mV.}$

At $t = 60 \mu\text{s}$, $v(t) = -450 \text{ mV}$.

$60 \leq t \leq 80 \mu\text{s}$: $v(t) = \frac{1}{0.5} \int_{60}^t (0.75t - 60) dt - 450 = \left[0.375t^2 - 120t \right]_{60}^t - 450 =$

$0.75t^2 - 120t + 4050 \text{ mV. At } t = 80 \mu\text{s}, v(t) = -750 \text{ mV.}$

$t \geq 80 \mu\text{s}$: $v = -750 \text{ mV}$.

Check: Total area = $0.5 \times 15 \times 10 + 0.5 \times 15 \times 15 - 0.5 \times 15 \times 15 - 15 \times 20 -$

$0.5 \times 15 \times 20 = -375 \text{ nC. Hence } v = \frac{-375}{0.5} = -750 \text{ mV.}$

(b) At $t = 10 \mu\text{s}$, $v(t) = 150 \text{ mV}$, so $q = CV = 75 \text{ nC}$.

At $t = 50 \mu\text{s}$, $v(t) = -150 \text{ mV}$, so $q = CV = -75 \text{ nC}$.

(c) At $t = 80 \mu\text{s}$, $v(t) = -750 \text{ mV}$, so $w = \frac{1}{2} C v^2 = 0.14 \mu\text{J}$.

(d) All the expressions derived above for the voltage are increased by 0.5 V .