

## Homework 5

**P4.1.50** Derive NEC between terminals 'ab' in Figure P4.1.50, assuming all resistances are  $2\ \Omega$ .

**Solution: Initialize.** All given values and the required  $I_N$  are entered. The nodes are labeled.

**Simplify.** The circuit is in a simple enough form.

**Deduce.** The branches 'ha' and 'hcb' are in parallel, so that by current division,  $I_{cb} = 1/3\ \text{A}$ . It follows that  $I_{bd} = I_N + 4/3$ . Since the voltage across the branch 'bdf' is the same as the  $V_{af}$ ,

then  $I_{af} = 2(I_N + 4/3)$  and  $I_{fg} = 3(I_N + 4/3) = 3I_N + 4$ ;

From KCL at node 'g',  $I_{ga} = 3I_N + 3$ . From KVL

around the mesh 'afga',  $2 \times 2(I_N + 4/3)$

$4(3I_N + 4) + 2(3I_N + 3) = 0$ , which gives

$I_N = -41/33\ \text{A}$ .

When the current sources are set to zero,  $R_{af} = 2 \parallel 6 = 1.5\ \Omega$ ;  $R_{fb} = 4\ \Omega$ ;  $R$  of the branch on the RHS is  $6\ \Omega$ ; it follows

that  $R_N = (6 \times 5.5) / 11.5 = 66/23\ \Omega$ .

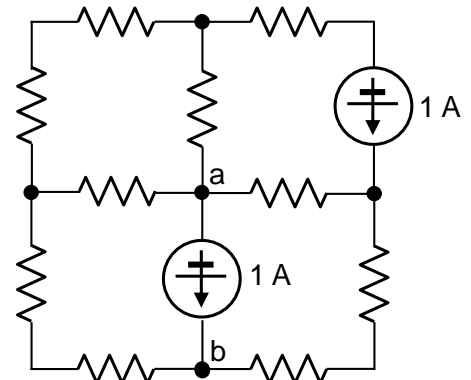


Figure P4.1.50



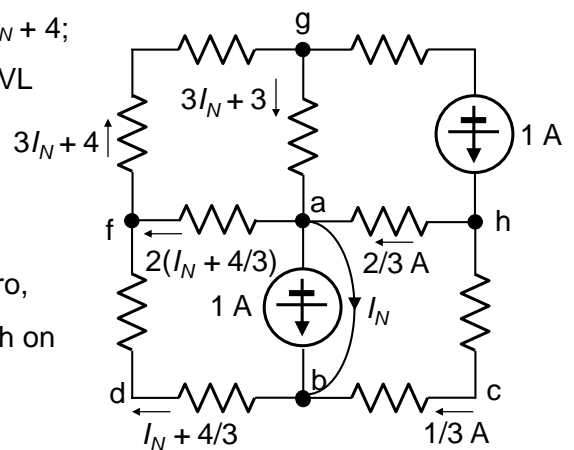


Figure P4.1.50-1

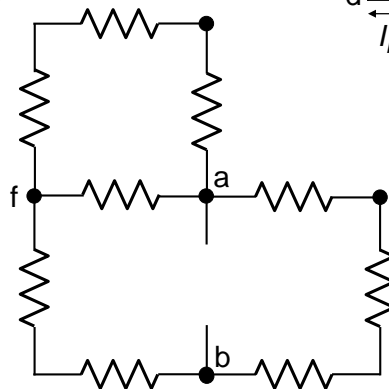

(a)

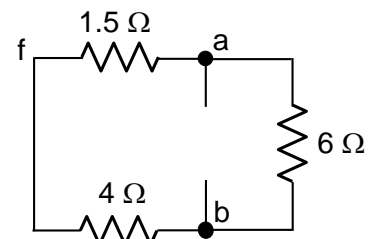

(b)

Figure P4.1.50-2

**P4.2.2** Determine  $V_X$  in Figure P4.2.2 by using the substitution theorem, where  $N_A$  is an unspecified circuit that passes a current of 0.5 A.

**Solution:**  $N_A$  is replaced by a 0.5 A current source.

The current in the 7.5  $\Omega$  resistor is  $V_X/7.5$  A. The current in the 10  $\Omega$  resistor is  $(V_X/7.5 - 0.5)$ . From KVL around the mesh on the LHS,  $30 - V_X - 10(V_X/7.5 - 0.5) = 0$ , which gives  $I_X = 2$  A, so that  $V_X = 15$  V.

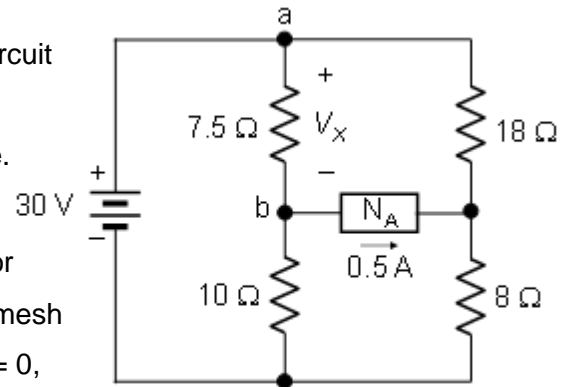


Figure P4.2.2

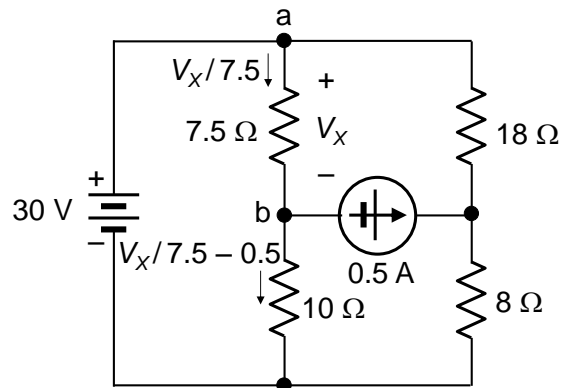


Figure P4.2.2-1

**P4.2.10** Determine  $R_{in}$  in Figure P4.2.10 by applying the source absorption theorem.

**Solution:** The voltage across the 2  $\Omega$  resistor is  $4 V_O$ , so that the current in the middle branch is  $2 V_O$  in the direction of a voltage rise across the VCVS. This source is equivalent to a

resistance of  $-2.5 \Omega$ . In series with  $2 \Omega$ , the resistance of this branch is  $-0.5 \Omega$ , which cancels out the  $0.5 \Omega$  resistance of the branch on the RHS. The current in the branch on the LHS is  $V_A$  A in the direction of a voltage drop through the VCVS, so that this source is equivalent to

a resistance of  $0.25 \Omega$ . Added to  $1 \Omega$ , this gives  $R_{in} = 1.25 \Omega$ .

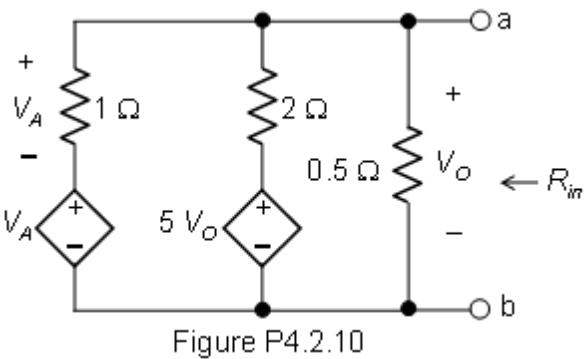


Figure P4.2.10

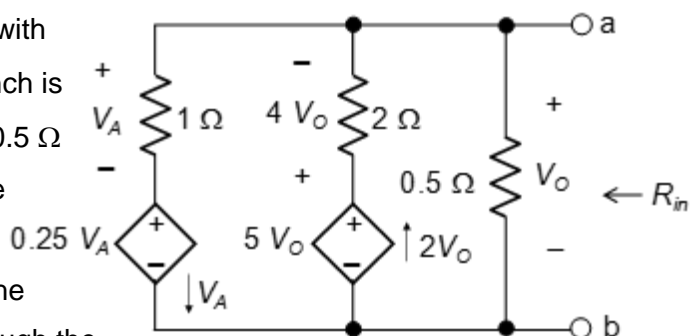


Figure P4.2.10-1

**P5.1.10** Determine  $I_x$  in Figure P5.1.10.

**Solution:** The sources can be split in two resulting in two half circuits as shown. These two half circuits are symmetrical about the midline, so they have the same currents at symmetrical nodes. Thus, if a current  $I$  enters node 'a', then an equal current  $I$  enters node 'a'. this means that  $I = -I$ , so that  $I$  is zero. Similarly, no current flows between nodes 'b' and 'b' and between nodes 'c' and 'c'. the two half circuits can therefore be separated. It follows that  $I_x = 0.5$  A.

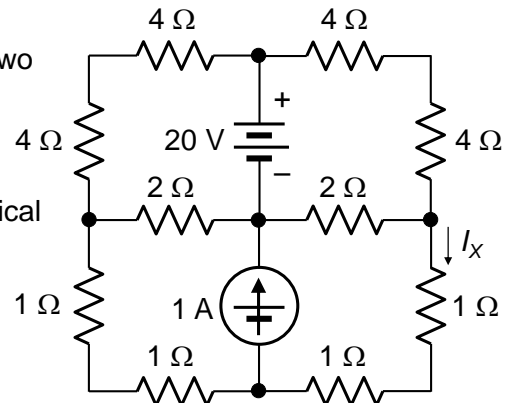


Figure P5.1.10

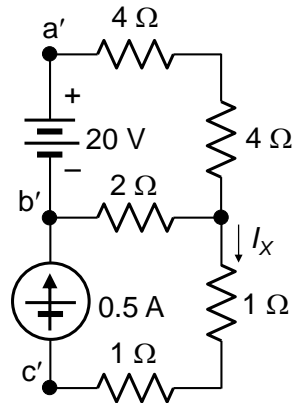


Figure P5.1.10-2

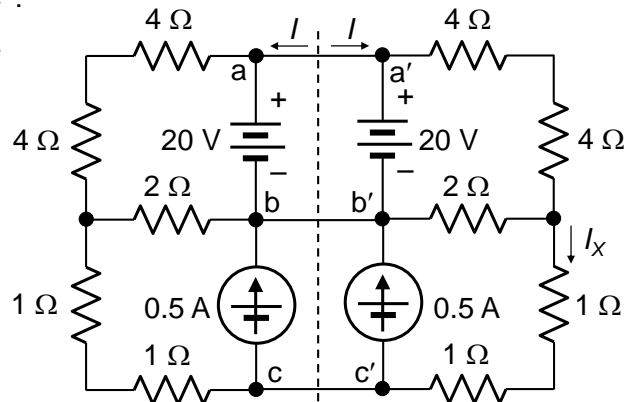


Figure P5.1.10-1

**P5.1.15** Determine  $I_x$  in Figure P5.1.15. Note that  $I_x$  is independent of the  $10\ \Omega$  resistor and the dependent source because the  $5$  A source partitions the circuit into two subcircuits. The upper subcircuit is independent of the lower subcircuit, but the lower subcircuit depends on the upper subcircuit through  $I_x$ .

**Solution:** The current in the diagonal branch is, from KCL,  $I_x - 5$ . From KVL around the mesh on the RHS,  $10 + 5I_x + 5(I_x - 5) = 0$ , or  $10I_x = 15$ , so that  $I_x = 1.5$  A.

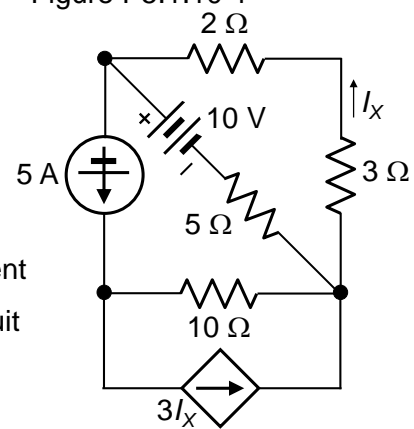


Figure P5.1.15

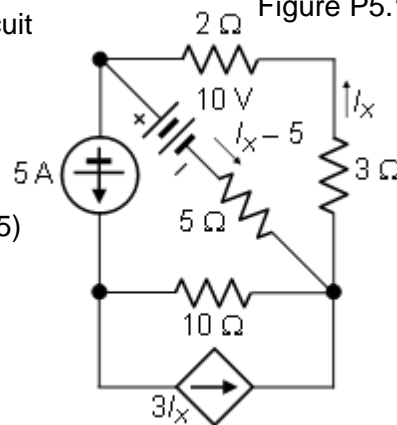


Figure P5.1.15

**P5.1.22** Determine  $I_x$  in Figure P5.1.22.

**Solution:**  $V_o = -5 \times 5 = -25$  V, so that the dependent source is replaced with an independent voltage source of 5 V, and of reversed polarity, as shown. When either voltage source is applied alone, with the current source replaced by an open circuit, the components are zero. When the current source is applied

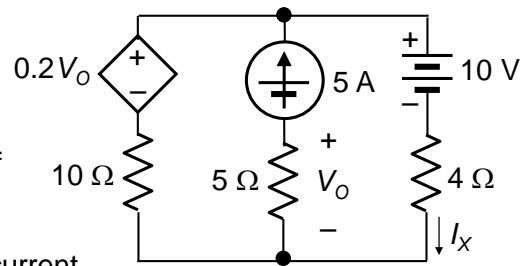


Figure P5.1.22 of  $V_o$

alone,  $V_o = -25$  V. From KCL at the upper node, the current in the left branch is  $(5 - I_x)$  A. From KVL around the outer loop, starting with the lower node and moving CW:  $10(5 - I_x) - 5 - 10 - 4I_x = 0$ , or,  $-14I_x + 35 = 0$ , which gives  $I_x = 2.5$  A.

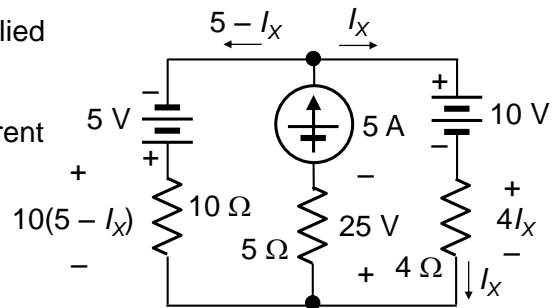


Figure P5.1.22-1

**P5.1.25** Determine  $I_x$  in Figure P5.1.25.

**Solution:** The dependent source is replaced by an independent source  $V_Y$ . If the 10 V source is applied alone, with the other sources set to zero, the component of  $I_x$  due to this source is zero. If the 12 V source is applied alone, the 12 V appears across  $10 \Omega$  in series with a parallel combination of 3 and  $6 \Omega$ . The source current is  $12 \text{ V} / 12 \Omega = 1$  A. From current division,  $I_{x1} = -1/3$  A. When  $V_Y$  is applied alone, the source current is  $V_Y / 12$ . From current division,  $I_{x2} = V_Y / 36$ . By superposition, and substituting  $V_Y = 6I_x$ ,  $I_x = -1/3 + I_x / 6$ . This gives  $I_x = -0.4$  A.

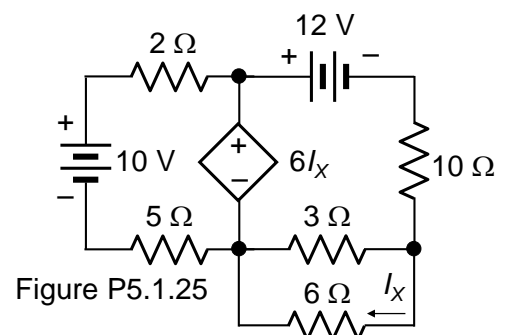


Figure P5.1.25

**P5.1.29** Determine in Figure P5.1.29: (a)  $V_O$ , and (b) the power delivered or absorbed by the 1 A source.

**P5.1.29**

(a) The  $8\ \Omega$  resistor is redundant as far as  $I_X$  and  $V_O$  are concerned. If the 1 A source is applied alone,  $I_{X1} = 1$  A. If the  $5I_X$  source is replaced by an independent source  $I_Y$  and applied alone,  $I_{X2} = -I_Y$ . If the 3 V source is applied alone,  $I_{X3} = -3/2$ . If the  $10I_X$  source is replaced by an independent source  $V_Y$  and applied alone,  $I_{X4} = V_Y/2$ . By superposition, and substituting  $I_Y = 5I_X$  and  $V_Y = 10I_X$ ,  $I_X = 1 - 5I_X - 3/2 + 10I_X/2$ , or  $I_X = -0.5$  A. From the original circuit,  $V_O = 3 - 2(1 - 6I_X) = 3 - 2(1 + 3) = -5$  V.

(b) The current in the  $4\ \Omega$  resistor is  $(1 - 5I_X) = 3.5$  A; hence, the voltage across the 1 A source is  $3 + 4 \times 3.5 + 8 = 25$  V. The power delivered by the source is  $P = 25$  W.

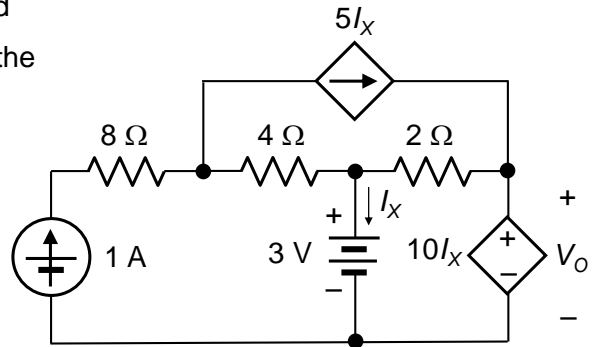


Figure P5.1.29

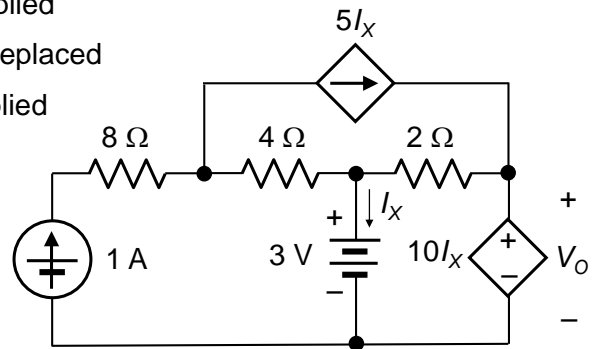


Figure P5.1.29

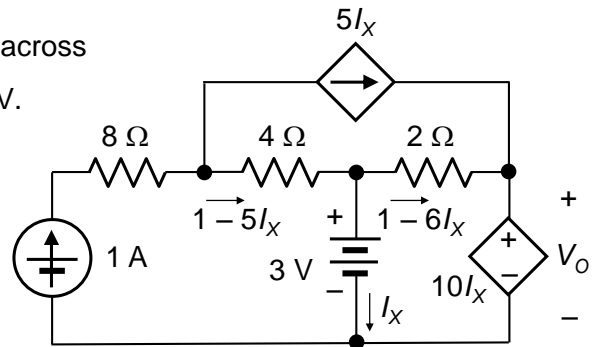


Figure P5.1.29-1