

## Homework 2

**P2.1.4** The voltage shown in Figure P2.1.4 is applied across a  $5\ \Omega$  resistor. Determine: (a) the resistor current.; (b)  $p(t)$ ,  $0 \leq t \leq 1$  min;

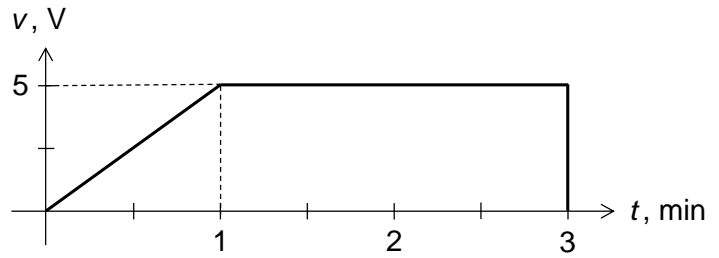


Figure P2.1.4

(c) the energy dissipated in the resistor at  $t = 3$  min.

**Solution:** 
$$v(V) = \begin{cases} t/12 & 0 \leq t \leq 60 \text{ s} \\ 5 & 60 \leq t < 180 \text{ s} \\ 0 & t > 180 \text{ s} \end{cases}$$

(a)  $i = v/R$ ;  $i = t/60$  A,  $0 \leq t \leq 60$  s;  $i = 1$  A,  $60 \leq t < 180$  s;  $i = 0$ ,  $t > 80$  s.

(b)  $0 \leq t \leq 60$  s;  $p(t) = \frac{v^2}{R} = \frac{1}{5} \left( \frac{t}{12} \right)^2 = \frac{t^2}{720}$  W, where  $t$  is in s.


(c)  $w = \int_0^{180} p dt = \int_0^{60} \frac{t^2}{720} dt + \int_{60}^{180} \frac{25}{5} dt = 700$  J.

- P2.1.5** A voltage  $v(t) = 10 \cos 100\pi t$  V is applied across a  $10 \Omega$  resistor. (a) Sketch  $p(t)$ .  
 (b) Determine the average power dissipated in the resistor and the energy dissipated during half a cycle of  $v(t)$ .

**Solution:**  $v(t) = 10 \cos 100\pi t = 10 \cos \omega t$ , where  $\omega = 100\pi$  rad/s, and so that the supply

frequency is  $\frac{100\pi}{2\pi} = 50$  Hz, and the

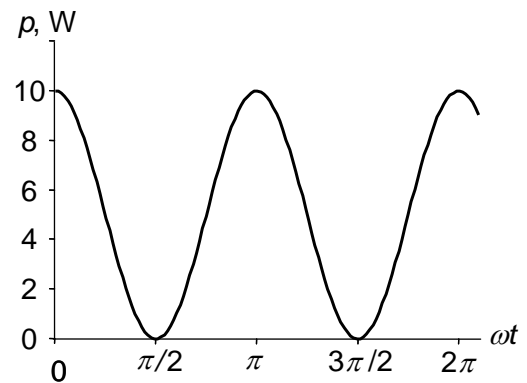supply period is  $\frac{1}{50} = 20$  ms.



$$f = \frac{\omega}{2\pi} \text{ where } f \text{ is in Hz and } \omega \text{ is in } \frac{\text{rad}}{2\pi}$$

(a)  $p = \frac{v^2}{R} = \frac{(10 \cos 100\pi t)^2}{10} \cos^2 \alpha = (1 + \cos 2\alpha + \frac{1}{2}) = 10 \cos^2 100\pi t = 5(1 + \cos 2\omega t)$  W, as shown.

(b)  $\frac{5}{2\pi} \int_0^{2\pi} (1 + \cos 2\omega t) d(\omega t) = \frac{10}{2\pi} \times \frac{2\pi}{2} = 5$  W

$$w = \int_0^{0.01} p dt = \int_0^{0.01} 10 \cos^2 100\pi t dt = 5 \int_0^{0.01} (1 + \cos 200\pi t) dt$$

$$= 5 \left[ t + \frac{\sin 200\pi t}{200\pi} \right]_0^{0.01} = 0.05 \text{ J. Since the average power dissipated is 5 W,}$$

the energy dissipated during one half cycle is  $5(\text{W}) \times 0.01(\text{s}) = 0.05 \text{ J}$ . Note that the average power, i.e., average energy per unit time, is independent of the time scale, but the energy is the integral of instantaneous power with respect to time.

**P2.2.6** Determine in Figure P2.2.6 the voltage across each current source, the current through each voltage source, and the power delivered or absorbed by each source.

**Solution:**  $V_{ab} = 20\text{ V}$ ,  $I_x = 0.8V_{ab} = 16\text{ A}$ . From KCL at node 'a', net current flowing away from this node is  $16 - 10 = 6\text{ A}$ . Hence, 6A must flow into node 'a' from the 20 V source.

Voltage drop across the CCVS =  $0.5I_x = 8\text{ V}$ ;

let the voltage drop across the VCCS be  $V_x$ .

From KVL the voltage drop  $V_{ab}$  is the same whether going through the 20 V source or the two dependent sources. Hence  $20 = V_x + 8$ , which gives  $V_x = 12\text{ V}$ .

The 20 V source delivers  $20 \times 6 = 120\text{ W}$ ;

the 10 A source delivers  $20 \times 10 = 200\text{ W}$ ;

VCCS absorbs  $12 \times 16 = 192\text{ W}$ ; and CCVS

absorbs  $8 \times 16 = 128\text{ W}$ . Total power delivered =  $320\text{ W}$  = total power absorbed.

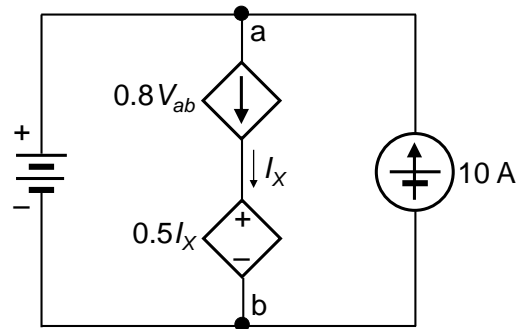


Figure P2.2.6

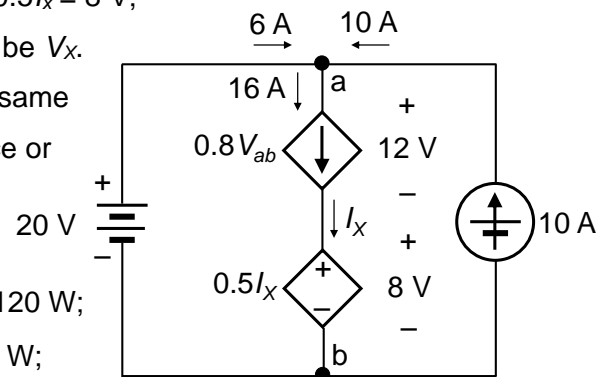


Figure P2.2.6-1

**P2.2.7** Determine the total power delivered or absorbed by each source in Figure P2.2.7, assuming the voltage sources are 1 V each,  $I_1 = 2$  A,  $I_2 = 1$  A, and  $I_3 = 1$  A.

**Solution:** The current leaving node 'a' through  $V_1$  is  $I_2 + I_3 = 1 + 1 = 2$  A. The source  $V_1$  absorbs  $1 \times 2 = 2$  W.

The current leaving node 'b' through  $V_2$  is  $I_1 - I_3 = 2 - 1 = 1$  A. The source  $V_2$  delivers  $1 \times 1 = 1$  W.

The current entering node 'c' through  $V_3$  is  $I_1 + I_2 = 3$  A.  $V_3$  absorbs  $1 \times 3 = 3$  W.

From KVL,  $V_{ab} = 2$  V,  $V_{ac} = 2$  V, and  $V_{bc} = 0$ . The source  $I_1$  neither absorbs nor delivers power; the source  $I_2$  delivers 2 W; the source  $I_3$  delivers 2 W.

Total power delivered = 5 W = total power absorbed.

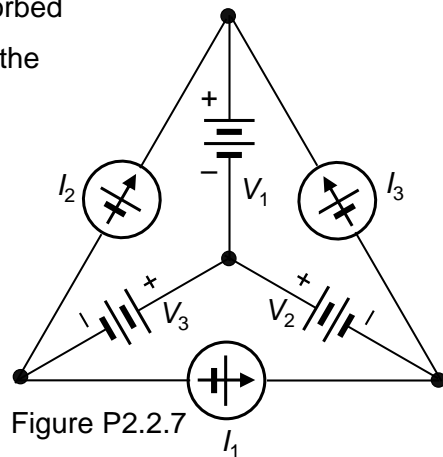


Figure P2.2.7

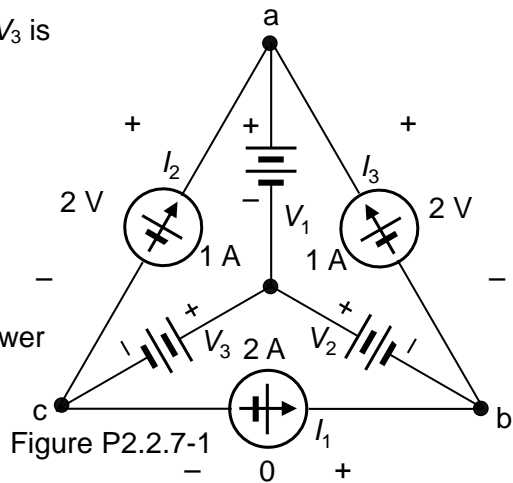


Figure P2.2.7-1

**P2.2.8** Determine in Figure P2.2.8 the voltage across each current source, the current through each voltage source, and the power delivered or absorbed by each source.

**Solution:** From KCL at node 'd':  $10 = 5 + I_{\Delta}$ , so  $I_{\Delta} = 5$  A. From KCL at node 'b':  $I_Y = 10 + 3 = 13$  A. From KCL at node 'a':  $3 + 5 = 8$  A =  $I_X$ . As a check, KCL at node 'c' is:  $13 = 8 + 5$  A.

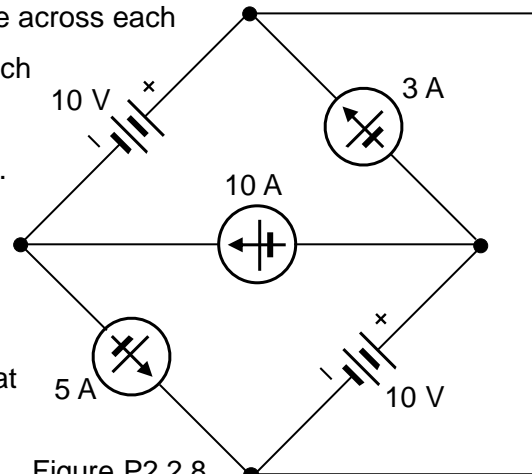


Figure P2.2.8

From KVL around the outer loop:  $-V_{cd} + 10 = 0$ , so that  $V_{cd} = 10$  V. From KVL around the mesh on the RHS:  $10 - V_{ba} = 0$ , so that  $V_{ba} = 10$  V. From KVL around the mesh 'abda':  $-V_{ba} - 10 + V_{bd} = 0$ , so that  $V_{bd} = 20$  V.

As a check, KVL around the mesh 'bcdcb' gives:  $-10 - V_{cd} + V_{bd} = -10 - 10 + 20 = 0$ . Upper 10 V source delivers 50 W; lower 10 V source delivers 130 W; 5 A source delivers 50 W; 10 A source absorbs 200 W; 3 A source absorbs 30 W. Total power

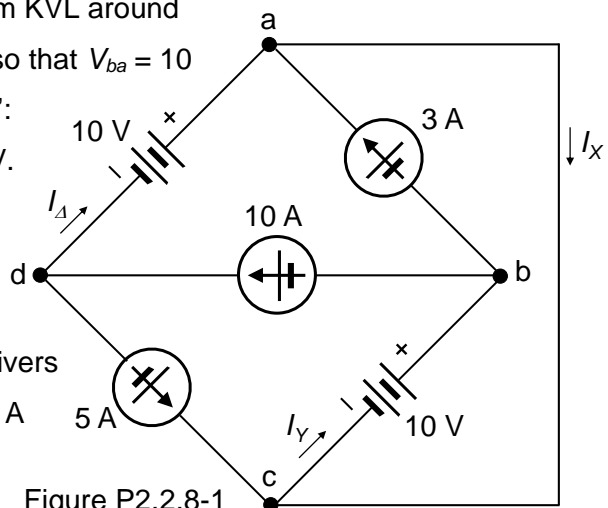


Figure P2.2.8-1

delivered = 230 W = total power absorbed.

**P2.3.23** Determine the power delivered or absorbed by the dependent source in Figure P2.3.23.

**Solution: Initialize.** The circuit is marked with given values. To determine the power delivered or absorbed by the dependent source, the voltage  $V_x$  should be determined.

**Simplify.** The circuit is in a simple enough form, although the two batteries can be combined in one 15 V battery.

**Deduce.** From KCL around a surface enclosing the dependent source and the two batteries, the

current through the lower  $10\ \Omega$  resistor is 100 mA in the direction shown. From Ohm's law,  $V_x = 10 \times 0.1 = 1\ \text{V}$ . The source current of the dependent source is 2 A. Since the voltage across the source is 15 V, and the 2 A is in the direction of a 15 V drop across the source, the source absorbs  $15 \times 2 = 30\ \text{W}$ .

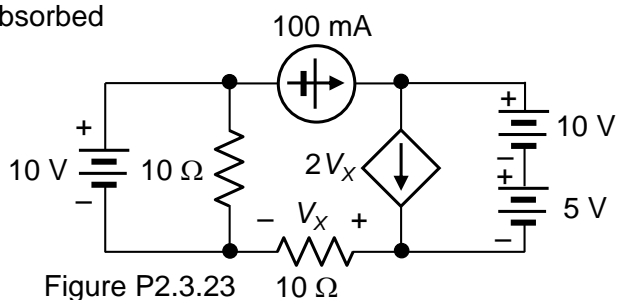


Figure P2.3.23

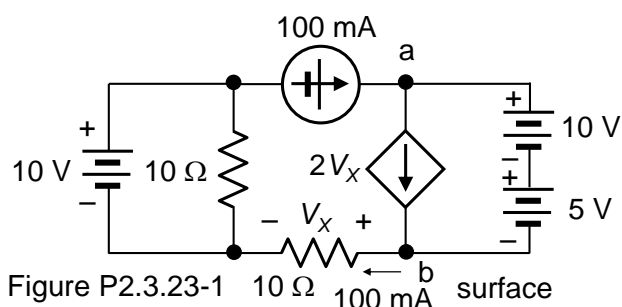


Figure P2.3.23-1

**P2.3.31** Determine  $R$ ,  $V_x$ , and  $V_y$  in Figure P2.3.31, given that the current in the top connection is zero.

**Solution: Initialize.** The circuit is marked with given values. The nodes are labeled. To determine  $R$ , the voltage across it and the current through it should be determined.  $V_x$  and  $V_y$  are determined from KVL around a mesh.

**Simplify.** The circuit is in a simple enough form.

**Deduce.** From KCL at node 'b',  $I_{be} = 5$  A; from KCL at node 'e',  $I_{de} = 5$  A; from KCL at node 'c',  $I_{ca} = 15$  A; from KCL at node 'a',  $I_{ad} = 15$  A; as a check, KCL is satisfied at node 'd'. From Ohm's law,  $V_{be} = 30$  V,  $V_{ad} = 15$  V, and  $V_{de} = 5R$ . From KVL in the outer loop,  $5R + 15 - 30 = 0$ , which gives  $R = 3 \Omega$ . From KVL around the mesh 'abca',  $-V_1 + 20 = 0$ , or  $V_1 = 20$  V; from KVL around the mesh 'cbec',  $V_1 - 30 + V_x = 0$ , or  $V_x = 10$  V. From KVL around the mesh 'acda',  $-20 - V_y + 15 = 0$ , or  $V_y = -5$  V.

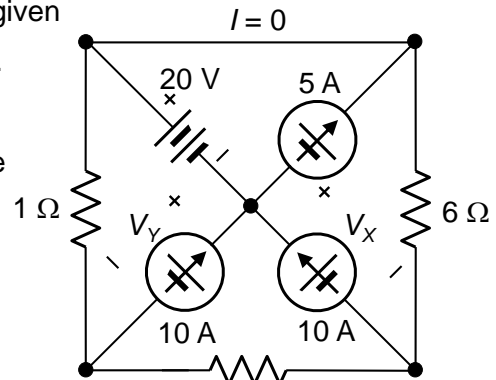


Figure P2.3.31

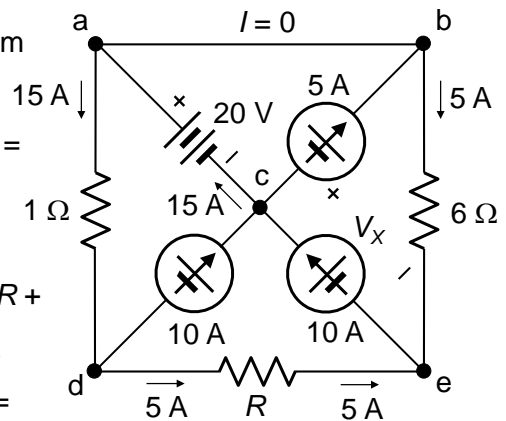


Figure P2.3.31-1

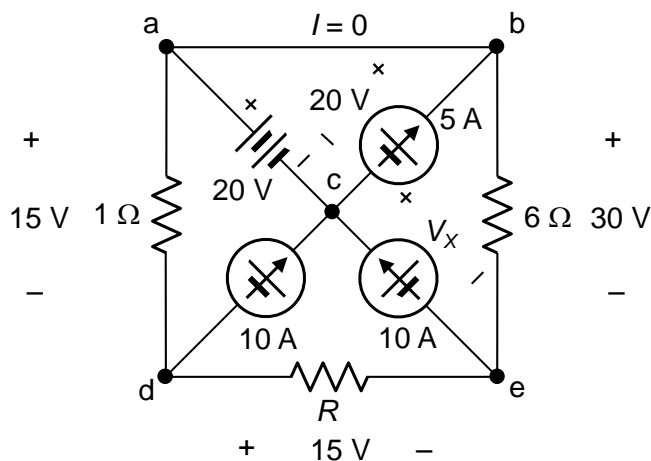


Figure P2.3.31-2

**P2.3.32** Determine  $I_o$  in Figure P2.3.32.

**Solution: Initialize.** The circuit is marked with given values. The nodes are labeled.

**Simplify.** The circuit is in a simple enough form.

**Deduce.**  $V_{ab} = 2I_o$ , so that the current in the  $2\ \Omega$  resistor is  $I_o$ . From KCL at node 'a',  $I_{da} = 3I_o$ . From KCL at node 'b',  $I_{bc} = 0$ . From KVL around the mesh 'abcd',  $-2I_o + 0 + 5 - 3I_o = 0$ , which gives  $I_o = 1\ \text{A}$ .

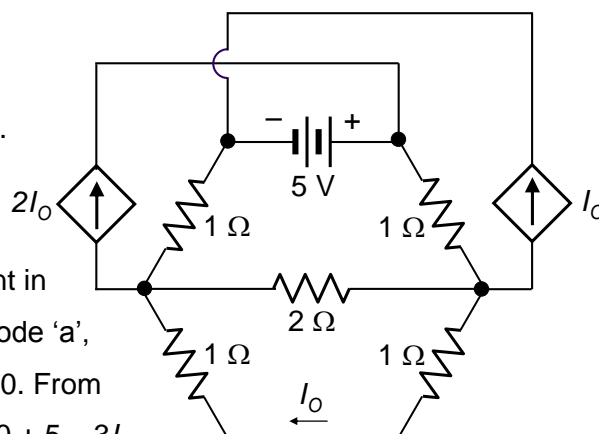


Figure P2.3.32

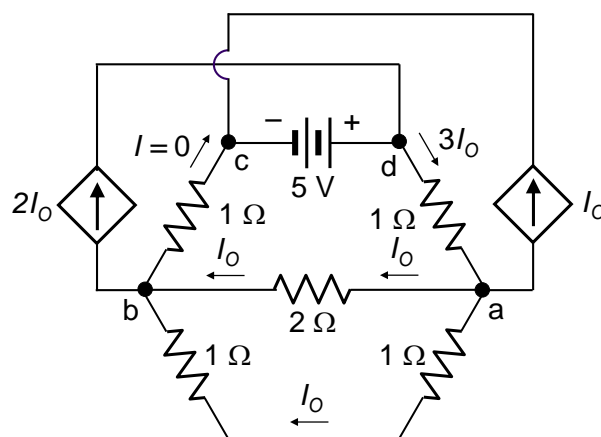


Figure P2.3.32-1