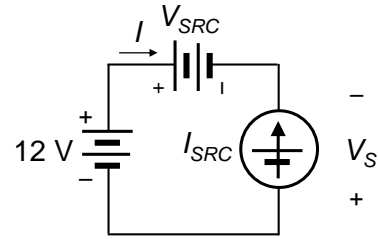


EECE 210 – Quiz 1
September 28, 2015

4%

A. Determine I and V_S , assuming $V_{SRC} = 2$ V and $I_{SRC} = 1$ A.



Solution: From KCL at the upper node of I_{SRC} , $I + I_{SRC} = 0$, or $I = -I_{SRC}$; from KVL around the mesh, starting from

the bottom node and going clockwise, $12 - V_{SRC} + V_S = 0$, or $V_S = -12 + V_{SRC}$

Version 1: $V_{SRC} = 2$ V, $I_{SRC} = 1$ A; $I = -1$ A, $V_S = -10$ V

Version 2: $V_{SRC} = 3$ V, $I_{SRC} = 2$ A; $I = -2$ A, $V_S = -9$ V

Version 3: $V_{SRC} = 4$ V, $I_{SRC} = 3$ A; $I = -3$ A, $V_S = -8$ V

Version 4: $V_{SRC} = 5$ V, $I_{SRC} = 4$ A; $I = -4$ A, $V_S = -7$ V

Version 5: $V_{SRC} = 6$ V, $I_{SRC} = 5$ A; $I = -5$ A, $V_S = -6$ V

4%

B. Determine the power actually delivered or absorbed by each source in the preceding problem.

Solution: Power absorbed by $I_{SRC} = V_S I_{SRC}$; power delivered by 12 V source is $12I$; power absorbed by V_{SRC} is $V_{SRC} I$.

Version 1: $V_{SRC} = 2$ V, $I_{SRC} = 1$ A, $I = -1$ A, $V_S = -10$ V; power absorbed by $I_{SRC} = V_S I_{SRC} = -10$ W, source actually delivers 10 W, power delivered by 12 V source is $12I = -12$ W, source actually absorbs 12 W; power absorbed by V_{SRC} is $V_{SRC} I = -2$ W, source actually delivers 2 W.

Version 2: $V_{SRC} = 3$ V, $I_{SRC} = 2$ A, $I = -2$ A, $V_S = -9$ V; power absorbed by $I_{SRC} = V_S I_{SRC} = -18$ W, source actually delivers 18 W, power delivered by 12 V source is $12I = -24$ W, source actually absorbs 24 W; power absorbed by V_{SRC} is $V_{SRC} I = -6$ W, source actually delivers 6 W.

Version 3: $V_{SRC} = 4$ V, $I_{SRC} = 3$ A, $I = -3$ A, $V_S = -8$ V; power absorbed by $I_{SRC} = V_S I_{SRC} = -24$ W, source actually delivers 24 W, power delivered by 12 V source is $12I = -36$ W, source actually absorbs 36 W; power absorbed by V_{SRC} is $V_{SRC} I = -12$ W, source actually delivers 12 W.

Version 4: $V_{SRC} = 5$ V, $I_{SRC} = 4$ A, $I = -4$ A, $V_S = -7$ V; power absorbed by $I_{SRC} = V_S I_{SRC} = -28$ W, source actually delivers 28, power delivered by 12 V source is $12I = -48$ W, source actually absorbs 48 W; power absorbed by V_{SRC} is $V_{SRC} I = -20$ W, source actually delivers 20 W.

Version 5: $V_{SRC} = 6$ V, $I_{SRC} = 5$ A, $I = -5$ A, $V_S = -6$ V; power absorbed by $I_{SRC} = V_S I_{SRC} = -30$ W, source actually delivers 30, power delivered by 12 V source is $12I = -60$ W, source actually absorbs 60 W; power absorbed by V_{SRC} is $V_{SRC} I = -30$ W, source actually delivers 30 W.

4%

C. Determine the current I_S and the power dissipated in the $20\ \Omega$ resistor, assuming $V_{SRC} = 20\text{ V}$.

Solution: $20\parallel 80 = 20 \times 80 / (20 + 80) = 16\ \Omega$;

$40\parallel 60 = 40 \times 60 / (40 + 60) = 24\ \Omega$; $16 + 24 = 40\ \Omega$;

$I_S = V_{SRC} / 40\text{ A}$; I_S divides between the $20\ \Omega$ and $80\ \Omega$

resistors in the ratio of 4:1. Hence, the current in the $20\ \Omega$ resistor is $4I_S/5 = \text{A}$, and the power dissipated is $20(4I_S/5)^2 = 12.8 I_S^2\text{ W}$.


Version 1: $V_{SRC} = 20\text{ V}$; $I_S = 20/40 = 0.5\text{ A}$, $P_{20\Omega} = 12.8 I_S^2 = 3.2\text{ W}$

Version 2: $V_{SRC} = 30\text{ V}$; $I_S = 30/40 = 0.75\text{ A}$, $P_{20\Omega} = 12.8 I_S^2 = 7.2\text{ W}$

Version 3: $V_{SRC} = 40\text{ V}$; $I_S = 40/40 = 1\text{ A}$, $P_{20\Omega} = 12.8 I_S^2 = 12.8\text{ W}$

Version 4: $V_{SRC} = 50\text{ V}$; $I_S = 50/40 = 1.25\text{ A}$, $P_{20\Omega} = 12.8 I_S^2 = 20\text{ W}$

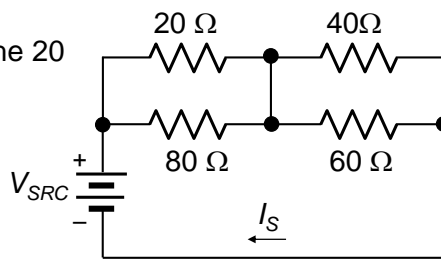Version 5: $V_{SRC} = 60\text{ V}$; $I_S = 60/40 = 1.5\text{ A}$, $P_{20\Omega} = 12.8 I_S^2 = 28.8\text{ W}$.



4%

D. Determine the current I by transforming both linear-output current sources to their equivalent linear-output voltage sources,

assuming $R = 5\ \Omega$.

Solution: The transformed sources are as shown. It follows that $I = 50 / (R + 5)\text{ A}$.


Version 1: $R = 5\ \Omega$; $I = 50 / (R + 5) = 5\text{ A}$

Version 2: $R = 10\ \Omega$; $I = 50 / (R + 5) = 10/3\text{ A}$

Version 3: $R = 15\ \Omega$; $I = 50 / (R + 5) = 2.5\text{ A}$

Version 4: $R = 20\ \Omega$; $I = 50 / (R + 5) = 2\text{ A}$

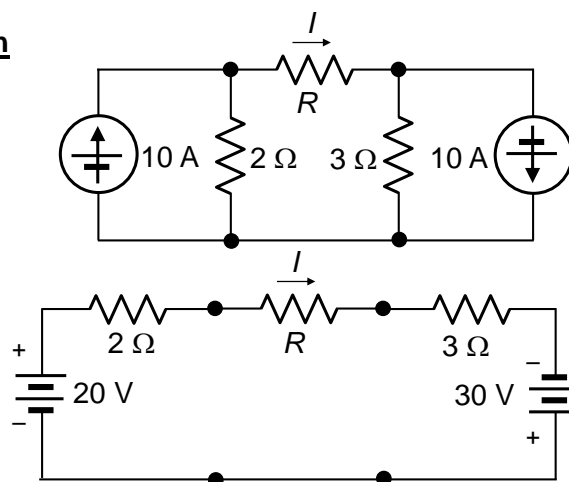Version 5: $R = 25\ \Omega$; $I = 50 / (R + 5) = 5/3\text{ A}$.




4%

1. The voltage v across a device and the current i through the device are as shown. Determine the largest value of the magnitude of the energy absorbed or delivered by the device during the interval $0 < t < 3\text{ s}$, assuming $V_0 = 1\text{ V}$.

Solution: The largest magnitude of the energy absorbed occurs at $t = 2\text{ s}$, and is $w(2) = (1/2)(V_0 \times 2)(-1) = -V_0\text{ J}$.

Version 1: $V_0 = 1\text{ V}$; $w(2) = -V_0 = 1\text{ J}$ delivered

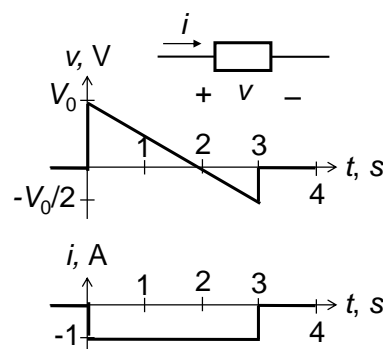

Version 2: $V_0 = 2 \text{ V}$; $w(2) = -V_0 \equiv 2 \text{ J}$ delivered

Version 3: $V_0 = 3 \text{ V}$; $w(2) = -V_0 \equiv 3 \text{ J}$ delivered

Version 4: $V_0 = 4 \text{ V}$; $w(2) = -V_0 \equiv 4 \text{ J}$ delivered

Version 5: $V_0 = 5 \text{ V}$; $w(2) = -V_0 \equiv 5 \text{ J}$ delivered.

4%

2. Element 'A' absorbs 4 W when $I_{SRC} = 3 \text{ A}$. Determine the power delivered or absorbed by the 2 A source.

Solution: The current through 'A' is $(I_{SRC} - 2) \text{ A}$; $V_A = 4/(I_{SRC} - 2) \text{ V}$; the power absorbed by the 2 A source is $P_{2A} = 8/(I_{SRC} - 2) \text{ W}$.



Version 1: $I_{SRC} = 3 \text{ A}$; $P_{2A} = 8/(I_{SRC} - 2) = 8 \text{ W}$ absorbed

Version 2: $I_{SRC} = 4 \text{ A}$; $P_{2A} = 8/(I_{SRC} - 2) = 4 \text{ W}$ absorbed

Version 3: $I_{SRC} = 5 \text{ A}$; $P_{2A} = 8/(I_{SRC} - 2) = 2.67 \text{ W}$ absorbed

Version 4: $I_{SRC} = 6 \text{ A}$; $P_{2A} = 8/(I_{SRC} - 2) = 2 \text{ W}$ absorbed

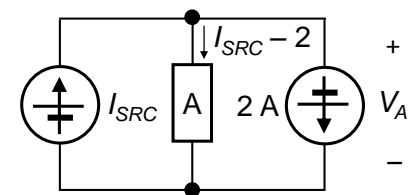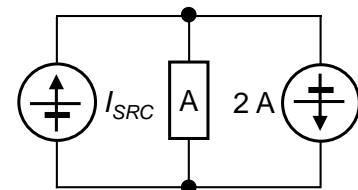Version 5: $I_{SRC} = 7 \text{ A}$; $P_{2A} = 8/(I_{SRC} - 2) = 1.6 \text{ W}$ absorbed.



4%

3. Determine I_{SRC} given that $V_X = 5 \text{ V}$.

Solution: $6 \parallel 12 = 72/18 = 4 \text{ k}\Omega$; from current division, $I_X = 3I_{SRC}/(3 + 9) = I_{SRC}/4 \text{ mA}$; $V_X = -5I_X = -5I_{SRC}/4 \text{ V}$; hence, $I_{SRC} = -4V_X/5$.



Version 1: $V_X = 5 \text{ V}$; $I_{SRC} = -4 \text{ mA}$

Version 2: $V_X = 10 \text{ V}$; $I_{SRC} = -8 \text{ mA}$

Version 3: $V_X = 15 \text{ V}$; $I_{SRC} = -12 \text{ mA}$

Version 4: $V_X = 20 \text{ V}$; $I_{SRC} = -16 \text{ mA}$

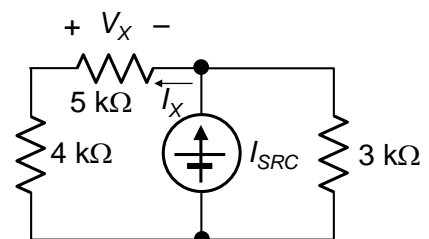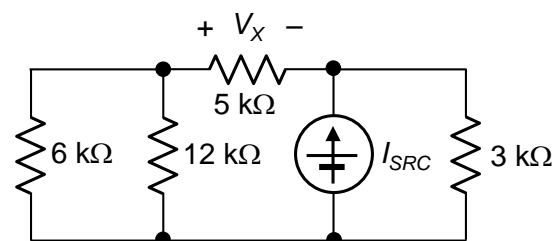Version 5: $V_X = 25 \text{ V}$; $I_{SRC} = -20 \text{ mA}$.



4%


4. Determine the power delivered or absorbed by the independent source, assuming $I_{SRC} = 1 \text{ A}$.

Solution: From KVL on the RHS mesh, $I_a \times 1 + V_X - 2I_a = 0$, or $V_X = I_a \text{ V}$; from KCL at the upper node, with I_a replaced by V_X , $3V_X = V_X + I_{SRC}$, which gives $V_X = I_{SRC}/2 \text{ V}$; independent source delivers a power $P = (I_{SRC})^2/2 \text{ W}$.

Version 1: $I_{SRC} = 1 \text{ A}$; $P = 1/2 = 0.5 \text{ W}$ delivered

Version 2: $I_{SRC} = 2 \text{ A}$; $P = 4/2 = 2 \text{ W}$ delivered

Version 3: $I_{SRC} = 3 \text{ A}$; $P = 9/2 = 4.5 \text{ W}$ delivered

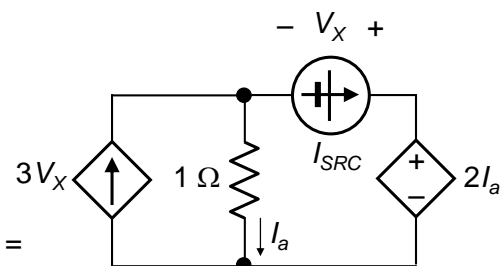

Version 4: $I_{SRC} = 4 \text{ A}$; $P = 16/2 = 8 \text{ W}$ delivered

Version 5: $I_{SRC} = 5 \text{ A}$; $P = 25/2 = 12.5 \text{ W}$ delivered.

4%

5. Determine I_S , assuming $V_{SRC} = 6 \text{ V}$.

Solution: The 10Ω resistor is short-circuited, and the 4Ω and 5Ω resistors are in series, the series combination being in parallel with the 3Ω resistor. This gives an equivalent resistance of $9 \times 3/12 = 9/4 = 2.25 \Omega$. In series with 1.75Ω , this gives 4Ω . In parallel with 4Ω and in series with 1Ω , the resistance seen by the source becomes 3Ω . It follows that $I_S = V_{SRC}/3 \text{ A}$.


Version 1: $V_{SRC} = 6 \text{ V}$; $I_S = 2 \text{ A}$

Version 2: $V_{SRC} = 9 \text{ V}$; $I_S = 3 \text{ A}$

Version 3: $V_{SRC} = 12 \text{ V}$; $I_S = 4 \text{ A}$

Version 4: $V_{SRC} = 15 \text{ V}$; $I_S = 5 \text{ A}$

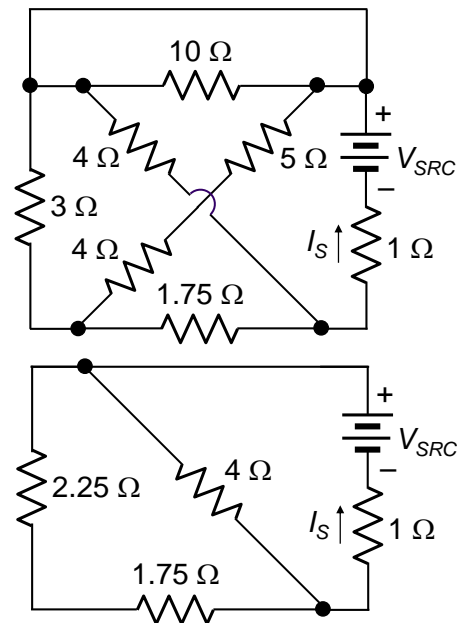Version 5: $V_{SRC} = 18 \text{ V}$; $I_S = 6 \text{ A}$.



4%

6. Determine I_S , assuming $V_{SRC} = 5 \text{ V}$.

Solution: The three 1Ω resistors in Y are transformed to three 3Ω resistors in Δ . The voltage across the 1Ω resistor is $2I_X \text{ V}$. It follows from KVL around the outer loop that $V_{SRC} = 4I_X$, so that the voltage of the rightmost node with respect to the bottom node is $V_{SRC}/2$. From

KCL at the bottom node, $I_S = \frac{V_{SRC}}{2} + \frac{V_{SRC}}{6} + \frac{V_{SRC}}{3} =$

$V_{SRC} \text{ A}$.


Version 1: $V_{SRC} = 5 \text{ V}$; $I_S = 5 \text{ A}$

Version 2: $V_{SRC} = 10 \text{ V}$; $I_S = 10 \text{ A}$

Version 3: $V_{SRC} = 15 \text{ V}$; $I_S = 15 \text{ A}$


Version 4: $V_{SRC} = 20 \text{ V}$; $I_S = 20 \text{ A}$

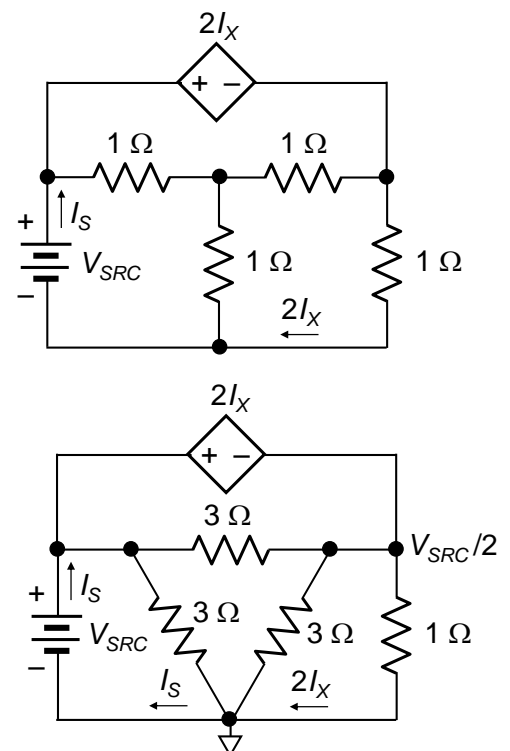Version 5: $V_{SRC} = 25 \text{ V}$; $I_S = 25 \text{ A}$.



20%

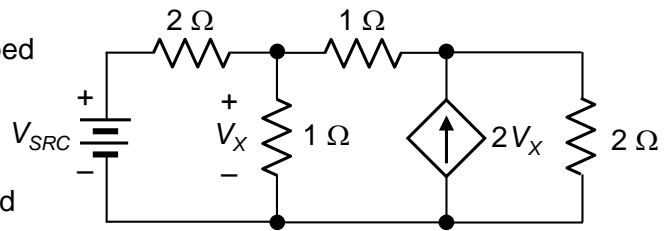
7. Determine the power delivered or absorbed by the dependent source, assuming $V_{SRC} = 1 \text{ V}$.



Solution: Initialize: All given parameters and variables are entered. The nodes are labelled.

Simplify: The circuit is already in a simple enough form.

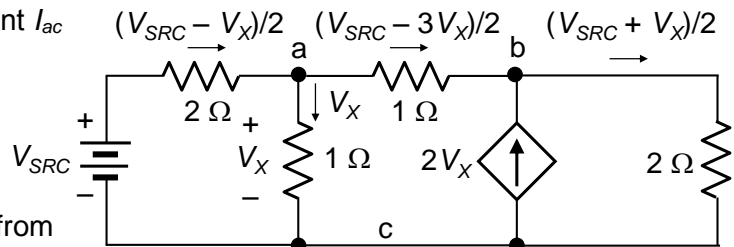Deduce: From Ohm's law, the current I_{ac} is $V_X/1 = V_X \text{ A}$; from KVL around the mesh on the LHS, the voltage drop across the 2Ω resistor is



$(V_{SRC} - V_X)$, and the current flowing from V_{SRC} to node 'a' is $(V_{SRC} - V_X)/2$. From KCL at node 'a',

$I_{ab} = (V_{SRC} - V_X)/2 - V_X = (V_{SRC} - 3V_X)/2$. From KCL at node 'b', the current through the 2Ω resistor on the RHS is $I_{bc} = (V_{SRC} - 3V_X)/2 + 2V_X = (V_{SRC} + V_X)/2$. From KVL around the outer loop $V_X - 1 \times (V_{SRC} - 3V_X)/2 - 2 \times (V_{SRC} + V_X)/2 = 0$, or $2V_X - V_{SRC} + 3V_X - 2V_{SRC} - 2V_X = 0$, which gives $V_X = V_{SRC}$. Hence, $V_{bc} = 2 \times (V_{SRC} + V_X)/2 = 2V_{SRC}$. The power delivered by the dependent source is $P = 2V_{SRC}I_a = 4(V_{SRC})^2 \text{ W}$.

Version 1: $V_{SRC} = 1 \text{ V}$; $P = 4 \text{ W}$

Version 2: $V_{SRC} = 2 \text{ V}$; $P = 16 \text{ W}$


Version 3: $V_{SRC} = 3 \text{ V}$; $P = 36 \text{ W}$

Version 4: $V_{SRC} = 4 \text{ V}$; $P = 64 \text{ W}$

Version 5: $V_{SRC} = 5 \text{ V}$; $P = 100 \text{ W}$.

20%

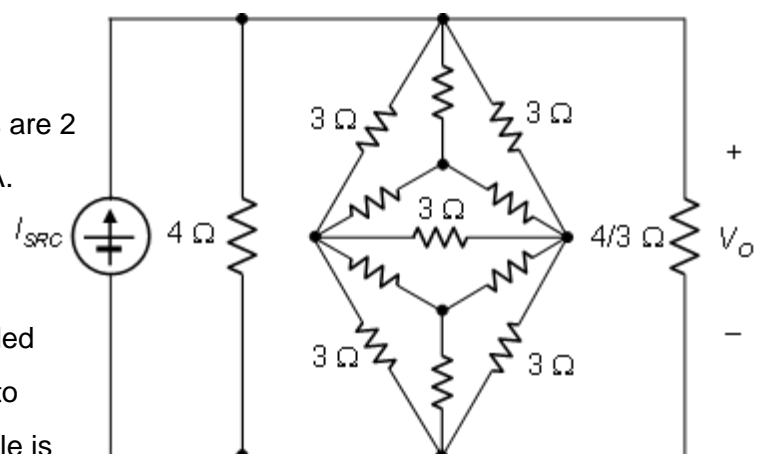
8. Determine V_O , given that the six, unmarked Y-connected resistors are 2Ω each, and assuming $I_{SRC} = 3 \text{ A}$.



Solution: The 2Ω , Y-connected resistors are transformed to 6Ω , Δ -connected resistors. 6Ω are paralleled with each of the outer 3Ω resistors to give 2Ω . The resistance in the middle is

$6||6||3 = 1.5 \Omega$. The resistive circuit in the middle becomes as shown. The upper delta is transformed to a Y-connection as shown. $3/5.5 \Omega$ in series with 2Ω is $14/5.5 \Omega$. The two $14/5.5 \Omega$ in parallel are $7/5.5 \Omega$. In series with $4/5.5 \Omega$, this gives 2Ω . The resistors reduce to 2Ω in parallel with 4Ω and $4/3 \Omega$; 2Ω in parallel with 4Ω is $4/3 \Omega$; in parallel with $4/3 \Omega$ this gives $2/3 \Omega$. It follows that $V_O = 2I_{SRC}/3 \text{ V}$.




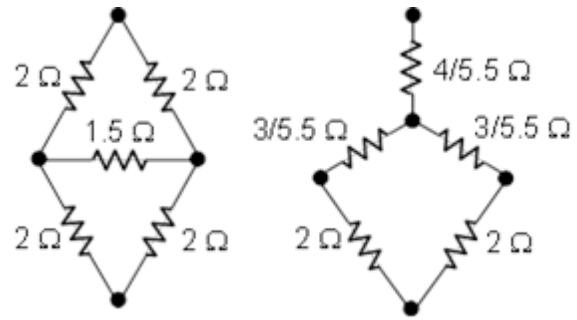
- Version 1:** $I_{SRC} = 3 \text{ A}$; $V_O = 2 \text{ V}$
- Version 2:** $I_{SRC} = 6 \text{ A}$; $V_O = 4 \text{ V}$
- Version 3:** $I_{SRC} = 9 \text{ A}$; $V_O = 6 \text{ V}$
- Version 4:** $I_{SRC} = 12 \text{ A}$; $V_O = 8 \text{ V}$
- Version 5:** $I_{SRC} = 15 \text{ A}$; $V_O = 10 \text{ V}$.



20%

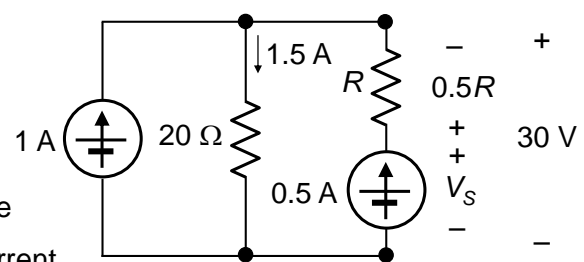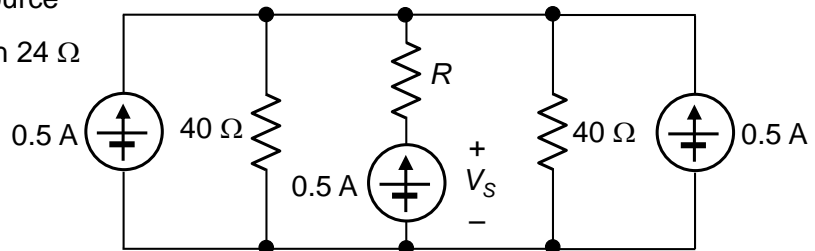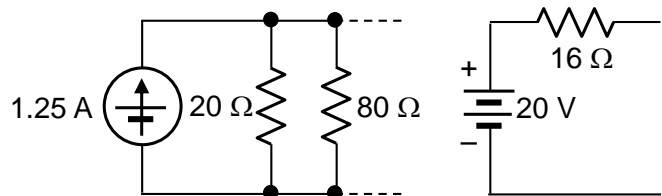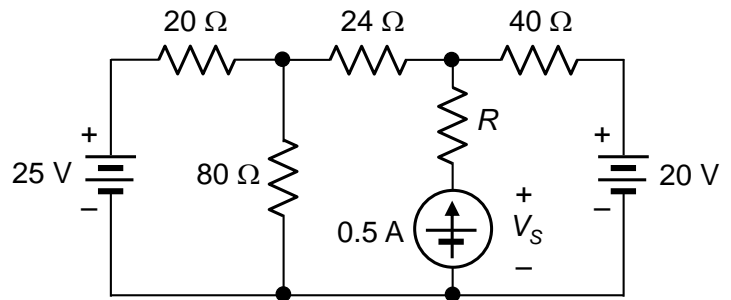9. Determine V_S , assuming $R = 10 \Omega$.

Solution: Successive source transformations are applied to reduce the circuit to a simple enough form. The 25 V source in series with 20Ω is transformed to a 1.25 A current source in parallel with 20Ω . In parallel with 80Ω the resistance is 16Ω . The 1.25 A current source in parallel with 16Ω is transformed to a 20 V source in series with 16Ω . In series with 24Ω the resistance is 40Ω . The 20 V source in series with 40Ω is transformed to a 0.5 A source in parallel with 40Ω . In the same manner,



the 20 V source in series with 40Ω on the RHS is transformed to a 0.5 A source in parallel with 40Ω , as shown. The two 40Ω resistors in parallel give a resistance of 20Ω and the two 0.5 A source add to a 1 A source, as shown. From KCL, the current in the 20Ω resistor is 1.5 A, and the voltage across the paralleled elements is 30 V. It follows that $V_S = 30 + 0.5R \text{ V}$.

- Version 1:** $R = 10 \Omega$; $V_S = 35 \text{ V}$
- Version 2:** $R = 20 \Omega$; $V_S = 40 \text{ V}$
- Version 3:** $R = 30 \Omega$; $V_S = 45 \text{ V}$
- Version 4:** $R = 40 \Omega$; $V_S = 50 \text{ V}$
- Version 5:** $R = 50 \Omega$; $V_S = 55 \text{ V}$.