

American University of Beirut
Department of Electrical and Computer Engineering
EECE 210 - Electric Circuits
Quiz 2
Closed Book - No Programmable Calculators - 90 minutes

April 17, 2015

Name: _____

ID: _____

Solve the following problems;

Provide your answers on the attached Scantron card;

This question sheet must be returned with the Scantron card;

There is No penalty;

Mark with a *pencil* your LAST NAME, your First name Initial (FI) and your Middle name Initial (MI);

Mark your AUB ID Number in the box titled "ID NUMBER";

Write the name of your course instructor on the Scantron card;

Use a pencil for marking your answers ;

When using an eraser, make sure that you have erased well.

This exam has 9 pages.

Course Instructors: L. Hamandi, S. Khaddaj, Y. Nasser, and R. Jabr.

1. In the circuit shown in Fig. 1, $I_S = 3$ A and each of the resistances is equal to $5\ \Omega$. Find I_X .

- (a) 0.25 A
- (b) 0.5 A
- (c) 0.75 A
- (d) 1 A
- (e) None of the above

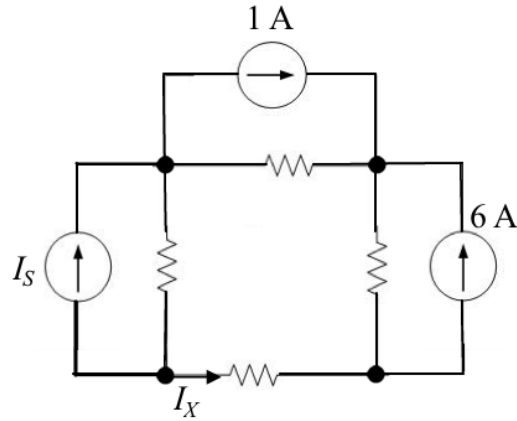


Fig. 1: Circuit for Problem 1

2. If $R = 30\ \Omega$ in the circuit shown in Fig. 2, find the Thévenin voltage between terminals a, b .

- (a) 10 V
- (b) 20 V
- (c) 30 V
- (d) 40 V
- (e) None of the above

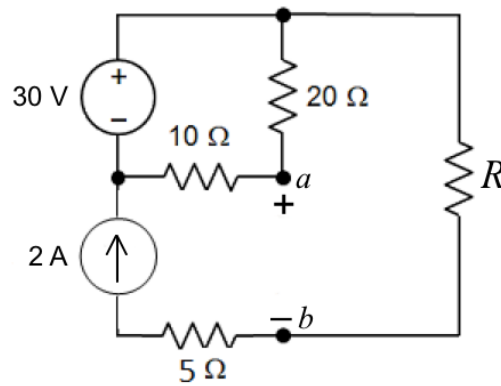


Fig. 2: Circuit for Problem 2

3. If $I_S = 5$ A in the circuit shown in Fig. 3, find the Thévenin voltage between terminals a, b .

- (a) 18 V
- (b) 12 V
- (c) 14 V
- (d) 16 V
- (e) None of the above

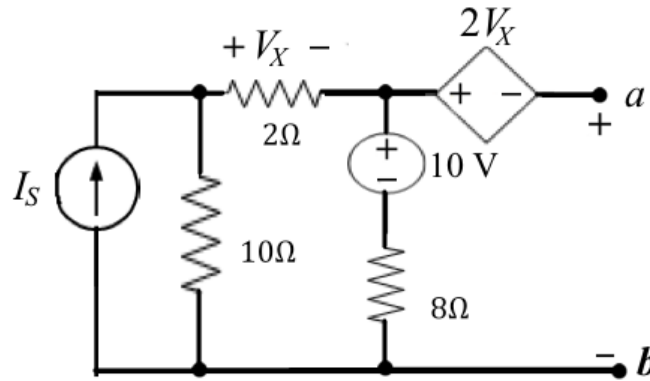


Fig. 3: Circuit of Problem 3

4. In the circuit shown in Fig. 4, $R_a = 3$ Ω. Find the value of R_L that results in maximum power being transferred to R_L .

- (a) 15 Ω
- (b) 16 Ω
- (c) 17 Ω
- (d) 18 Ω
- (e) None of the above

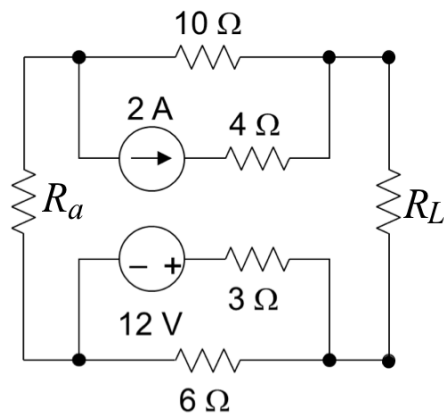


Fig. 4: Circuit of Problem 4

5. If $V_S = 120$ V in the circuit shown in Fig. 5, find the maximum power that can be delivered to R_L .

- (a) 329.14 W
- (b) 302.29 W
- (c) 228.57 W
- (d) 96.57 W
- (e) None of the above

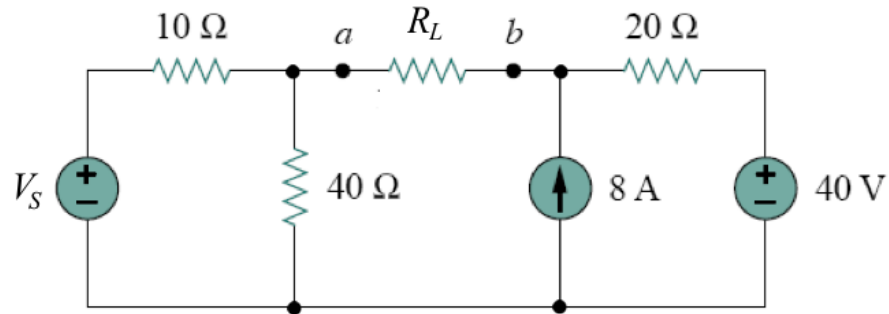


Fig. 5: Circuit of Problem 5

6. In the circuit shown in Fig. 6, $V_T = 120$ V. Find the component of I_S resulting from the V_T voltage source acting alone, with all the other voltage and current sources deactivated.

- (a) 1 A
- (b) 2 A
- (c) 3 A
- (d) 4 A
- (e) None of the above

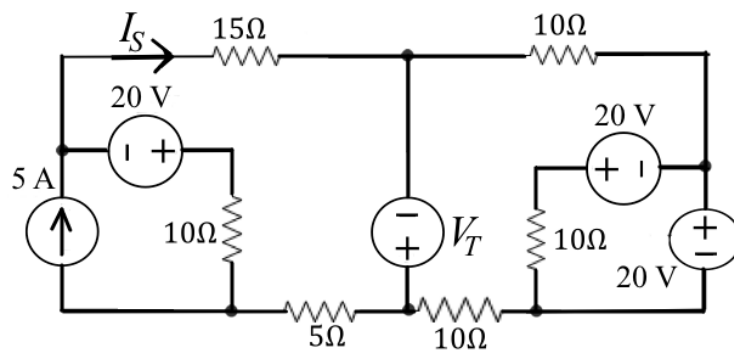


Fig. 6: Circuit of Problem 6

7. In the circuit shown in Fig. 7, $V_{CC} = 2.5$ V. Find the maximum value of R_X that can be used such that the op-amp operates in its linear region.

- (a) $15\ \Omega$
- (b) $30\ \Omega$
- (c) $45\ \Omega$
- (d) $60\ \Omega$
- (e) None of the above

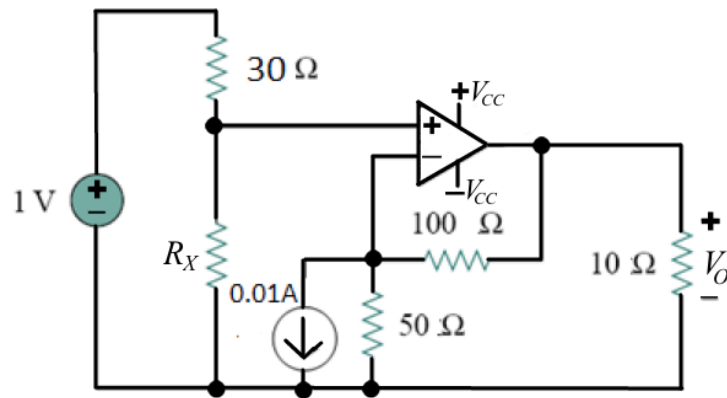


Fig. 7: Circuit of Problem 7

8. Each op-amp shown in Fig. 8 is operating in the linear region, and each of the resistances is equal to $10\ \Omega$. If $V_S = 6$ V and $V_T = 24$ V, find the current I_O .

- (a) 0.5 A
- (b) 0.6 A
- (c) 0.7 A
- (d) 0.8 A
- (e) None of the above

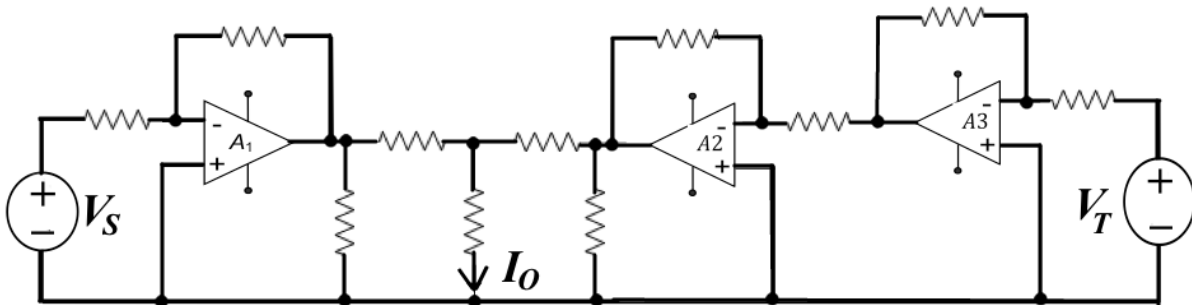


Fig. 8: Circuit of Problem 8

9. The op-amp shown in Fig. 9 is operating in the linear region. $V_{SRC} = 1\text{ V}$, $R_1 = 4\text{ k}\Omega$, $R_2 = 40\text{ k}\Omega$, $R_3 = 4\text{ k}\Omega$, and $R_L = 10\text{ k}\Omega$. Find I_L .

- (a) 1.75 mA
- (b) 2.375 mA
- (c) 3 mA
- (d) 4.25 mA
- (e) None of the above

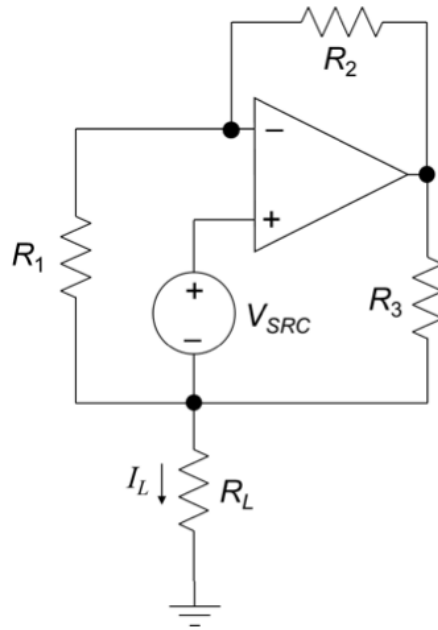


Fig. 9: Circuit of Problem 9

10. If $C = 11\text{ }\mu\text{F}$ in the network shown in Fig. 10, find the equivalent capacitance with respect to the terminals a, b .

- (a) $0.8\text{ }\mu\text{F}$
- (b) $2\text{ }\mu\text{F}$
- (c) $2.4\text{ }\mu\text{F}$
- (d) $3\text{ }\mu\text{F}$
- (e) None of the above

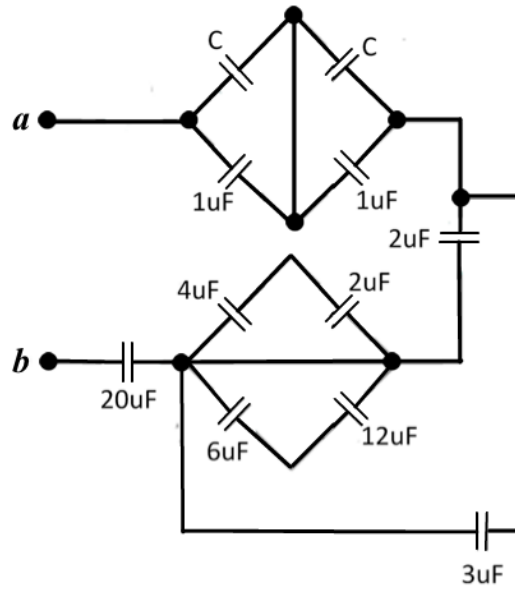


Fig. 10: Circuit of Problem 10

11. In the circuit shown in Fig. 11, $L_1 = 4 \text{ H}$, $L_2 = 4 \text{ H}$, and $M = 2 \text{ H}$. Write the mesh-current equation around mesh 2 (corresponding to mesh-current i_2).

- (a) $6(di_1/dt) - 13(di_2/dt) - 14i_2 = 0$
- (b) $6(di_1/dt) - 12(di_2/dt) - 14i_2 = 0$
- (c) $6(di_1/dt) - 11(di_2/dt) - 14i_2 = 0$
- (d) $6(di_1/dt) - 10(di_2/dt) - 14i_2 = 0$
- (e) None of the above

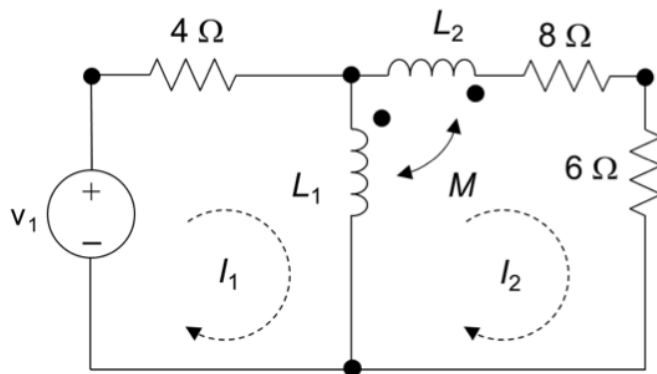


Fig. 11: Circuit of Problem 11

12. In the circuit shown in Fig. 12, $V_S = 75$ V. The switch has been closed for a long time, and is opened at $t = 0$. How much energy is delivered to the $5\ \Omega$ resistor in the time interval $0 \leq t < \infty$?

- (a) 0.3 J
- (b) 1.2 J
- (c) 2.7 J
- (d) 4.8 J
- (e) None of the above

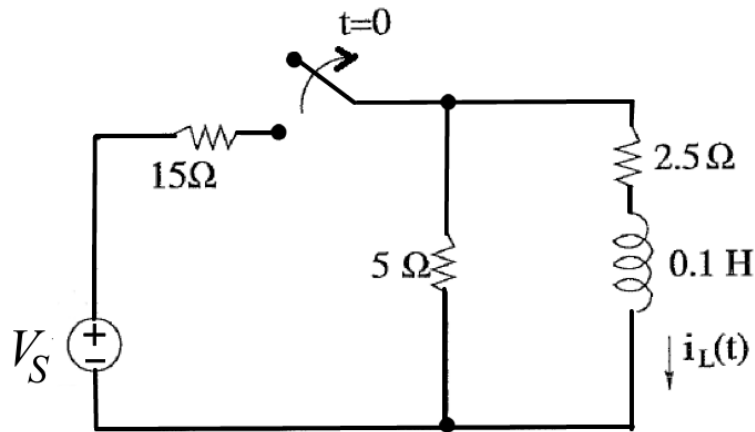


Fig. 12: Circuit of Problem 12

13. In the circuit shown in Fig. 13, the initial currents in inductors L_1 and L_2 (10 A upward and 4 A downward) have been established by sources not shown. The switch is opened at $t = 0$. Find the value of $i_2(t)$ at $t = 0.82$ s.

- (a) -5.00 A
- (b) -4.80 A
- (c) -4.60 A
- (d) -4.40 A
- (e) None of the above

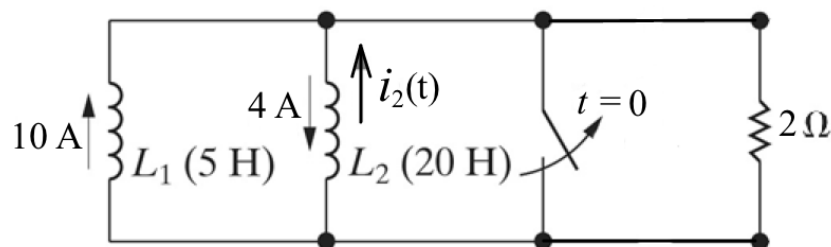


Fig. 13: Circuit of Problem 13

14. In the circuit shown in Fig. 14, $V_S = 180$ V. The two switches operate simultaneously. Switch 1 ($SW1$) has been in position a and switch 2 ($SW2$) has been in position c for a long time. At $t = 0$, $SW1$ moves to position b and $SW2$ moves to position d . Find $V_o(0^+)$.

- (a) 10 V
- (b) 20 V
- (c) 30 V
- (d) 40 V
- (e) None of the above

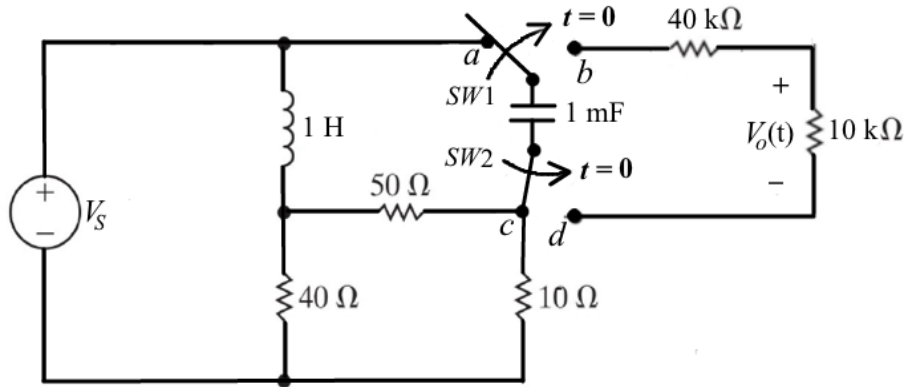


Fig. 14: Circuit of Problem 14

15. In the circuit shown in Fig. 15, the initial capacitor voltages are $v_1(0) = 10$ V and $v_2(0) = 5$ V. Find the value of $v_2(t)$ as $t \rightarrow \infty$.

- (a) 9 V
- (b) 13 V
- (c) 17 V
- (d) 21 V
- (e) None of the above

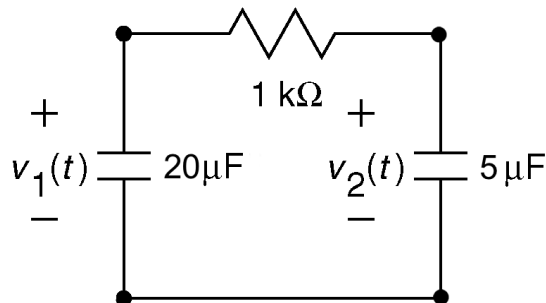


Fig. 15: Circuit of Problem 15