

American University of Beirut
Department of Electrical and Computer Engineering
EECE 210 - Electric Circuits
Quiz 1
Closed Book - No Programmable Calculators - 90 minutes

March 6, 2015

Name: SOLUTION

ID: _____

Solve the following problems;

Provide your answers on the attached Scantron card;

This question sheet must be returned with the Scantron card;

There is No penalty;

Mark with a *pencil* your LAST NAME, your First name Initial (FI) and your Middle name Initial (MI);

Mark your AUB ID Number in the box titled "ID NUMBER";

Write the name of your course instructor on the Scantron card;

Use a pencil for marking your answers ;


When using an eraser, make sure that you have erased well.

This exam has 9 pages.

Course Instructors: L. Hamandi, S. Khaddaj, Y. Nasser, and R. Jabr.

1. In the circuit shown in Fig. 1, $V_S = 30\text{ V}$. Find the power supplied by the independent voltage source.

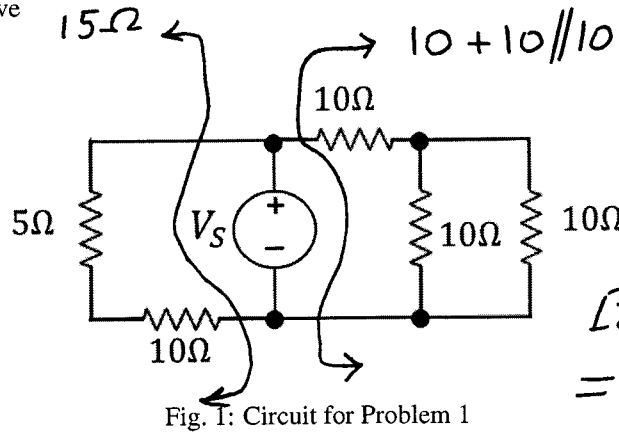- (a) 4.8 W
- (b) 7.5 W
- (c) 30 W
- (d) 120 W**
- (e) None of the above



$$R_{eq} = 15 \parallel 15 = 7.5 \Omega$$

$$\text{Power supplied by } V_S = P_{Req} = \frac{30^2}{7.5} = 120 \text{ W}$$

Fig. 1: Circuit for Problem 1

2. In the circuit shown in Fig. 2, $R = 30 \Omega$. Find the equivalent resistance R_{eq} seen across terminals ab.

- (a) 15 Ω**
- (b) 18.75 Ω
- (c) 20 Ω
- (d) 21 Ω
- (e) None of the above

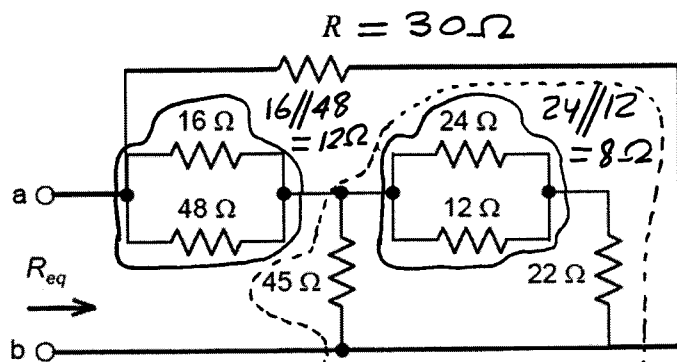


Fig. 2: Circuit for Problem 2

$$45 \parallel (8 + 22) = 18 \Omega$$

$$R_{eq} = (12 + 18) \parallel 30 = 15 \Omega$$

3. If $I_S = 3 \text{ A}$ in the circuit shown in Fig. 3, find the current I_O .

- (a) 4.11 A
- (b) 6.17 A
- (c) 8.23 A
- (d) 10.29 A
- (e) None of the above

$$I_O = \frac{3V_x}{2+3}$$

$$= \frac{3}{5} \left(\frac{24}{7} \times 3 \right)$$

$$6 \parallel 8 = \frac{24}{7} \Omega = 6.17 \text{ A}$$

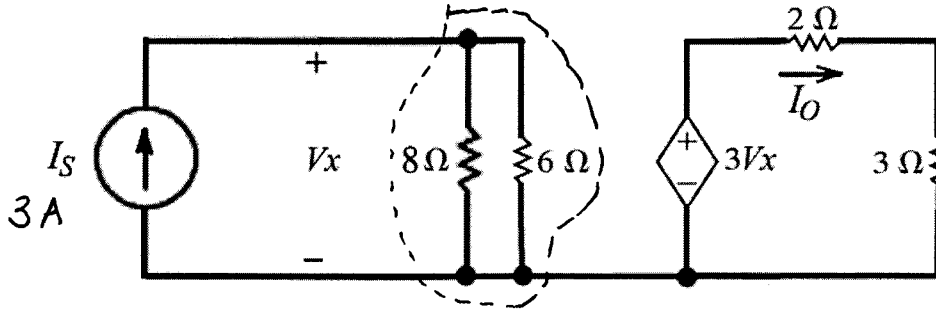


Fig. 3: Circuit of Problem 3

4. If $V_S = 180 \text{ V}$ in the circuit shown in Fig. 4, find the voltage V_O .

- (a) 6 V
- (b) 15 V
- (c) 25 V
- (d) 30 V
- (e) None of the above

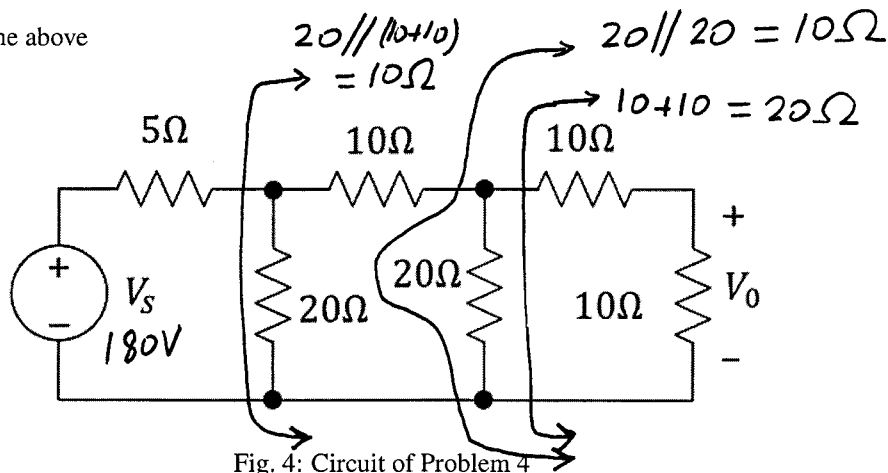


Fig. 4: Circuit of Problem 4


$$V_O = 180 \times \frac{10}{10+5} \times \frac{10}{10+10} \times \frac{10}{10+10}$$

$$= 30 \text{ V}$$

5. If $V_S = 7\text{ V}$ in the circuit shown in Fig. 5, find the voltage V_a .

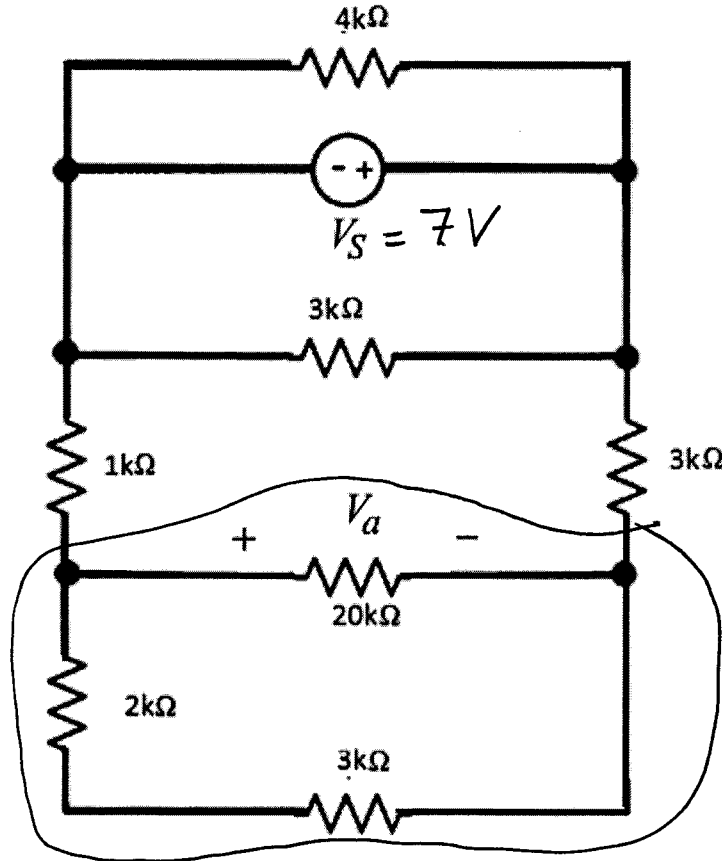- (a) -2 V
- (b) -2.5 V
- (c) -3 V
- (d) -3.5 V
- (e) None of the above

$$V_a = -7 \times \frac{4}{4+1+3} = -3.5\text{ V}$$



$$20 \parallel (2+3) = 4\text{ k}\Omega$$

Fig. 5: Circuit of Problem 5

6. Each of the resistances in the circuit shown in Fig. 6 is equal to $100\ \Omega$, and $I_S = 10\text{ A}$. Find the current I_1 .

- (a) 7.33 A
- (b) 8.07 A
- (c) 8.80 A
- (d) 9.53 A
- (e) None of the above

$$I_1 = 10 \times \frac{275}{100+275} = 7.33\text{ A}$$

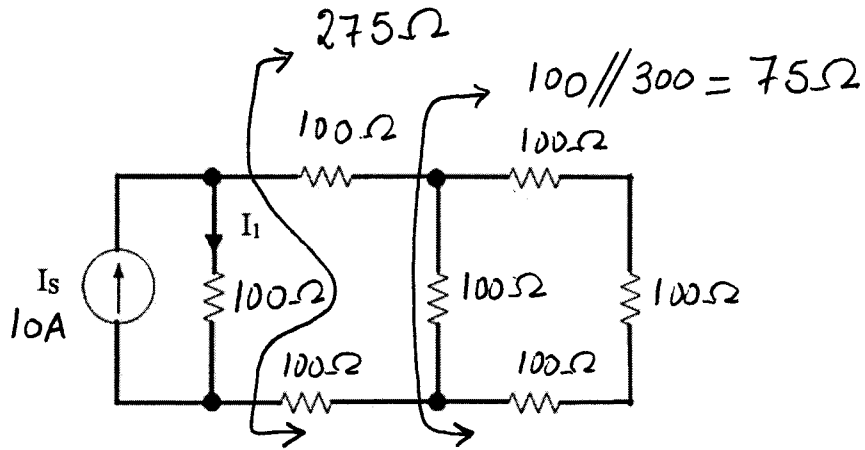


Fig. 6: Circuit of Problem 6

7. In the circuit shown in Fig. 7, $I_s = 5$ A. Find the power absorbed by the 5Ω resistor.

- (a) 0.8 W
- (b) 1.8 W
- (c) 3.2 W
- (d) 5 W
- (e) None of the above

$$I_{5\Omega} = \frac{2}{2+3+5} \cdot 5$$

$$= 1 \text{ A}$$

$$\Rightarrow P_{5\Omega} = 5 (1)^2 = 5 \text{ W}$$

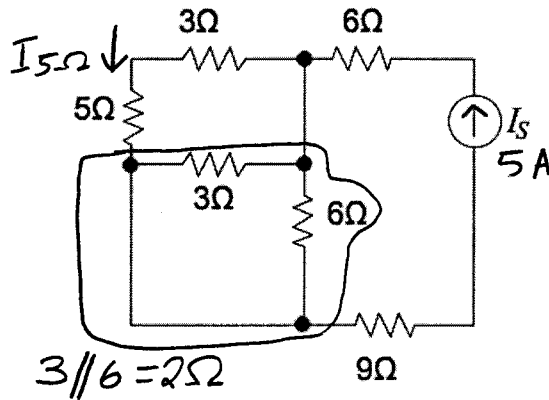


Fig. 7: Circuit of Problem 7

8. Find the voltage V_s in the circuit shown in Fig. 8 if $I_0 = 11$ A.

- (a) 83 V
- (b) 166 V
- (c) 332 V
- (d) 498 V
- (e) None of the above

$$I_0 = \frac{22}{22+12} I_s$$

$$\Rightarrow I_s = \frac{34}{22} \times 11 = 17 \text{ A}$$

$$V_s = 12 \times I_0 + 2 \times I_s$$

$$= 12 \times 11 + 2 \times 17$$

$$= 166 \text{ V}$$

10. In the circuit shown in Fig. 10, $I_s = 3$ A. The node-voltage equation at node a can be equivalently written as:

- (a) $3V_b - 7V_a = 8$
- (b) $3V_b - 7V_a = 2$
- (c) $7V_a - 3V_b = 4$
- (d) $7V_a - 3V_b = 10$
- (e) None of the above

$$\frac{V_a + 12}{3} + \frac{V_a - 5}{3} - 3 + \frac{V_a - V_b}{2} = 0$$

$$2V_a + 24 + 2V_a - 10 - 18 + 3V_a - 3V_b = 0$$

$$7V_a - 3V_b = 4$$

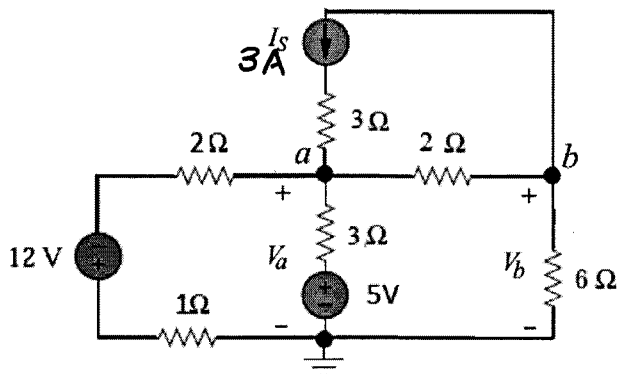


Fig. 10: Circuit of Problem 10

11. Find the voltage V_a in the circuit shown in Fig. 11 if $V_s = 12$ V. *hint: use the node-voltage method.*

- (a) 11 V
- (b) 9 V
- (c) 8 V
- (d) 7 V
- (e) None of the above

$$\frac{V_a}{4} + 5 + \frac{V_a - 24}{4} + \frac{(V_a + 12) - 24}{4} - 2 = 0$$

$$\frac{3}{4} V_a = 6 \Rightarrow V_a = 8V$$

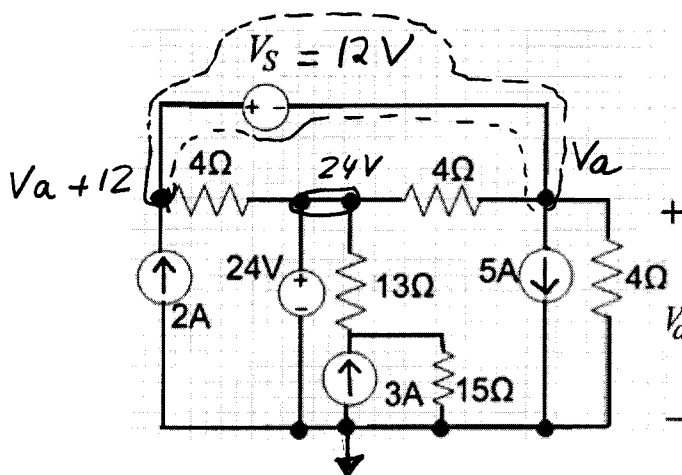


Fig. 11: Circuit of Problem 11

12. Find the current I_x in the circuit shown in Fig. 12 if $V_S = 12\text{ V}$ and $V_T = 20\text{ V}$.

- (a) -3.2 A
- (b) -2.8 A
- (c) -2.2 A
- (d) -3.8 A
- (e) None of the above

$$\textcircled{+} V_x : \frac{V_x - 12}{10} + \frac{V_x - 32}{10} + \frac{V_x + 6}{5} = 0$$

$$V_x = 8\text{ V}$$

$$I_x = \frac{-14}{5} = -2.8\text{ A}$$

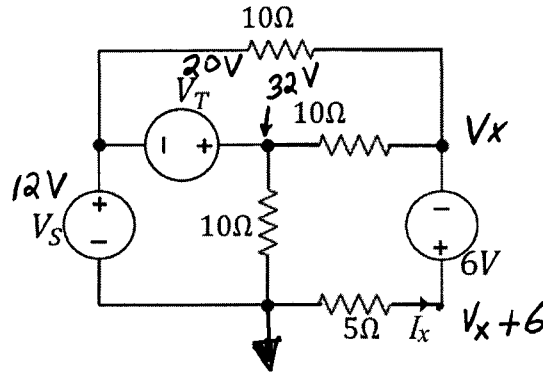


Fig. 12: Circuit of Problem 12

13. Find the current I_x in the circuit shown in Fig. 13 if $R = 5\ \Omega$. *hint: use the mesh-current method.*

- (a) 1 A
- (b) 1.3 A
- (c) 2 A
- (d) 2.66 A
- (e) None of the above

$$\textcircled{I_x} \quad 9I_x - 1 \cdot I_y - 5 \times 3 = 2$$

$$9I_x - I_y = 17$$

$$\textcircled{I_y} \quad 2I_y - 1 \cdot I_x - 1 \cdot 3 = -3$$

$$-I_x + 2I_y = 0$$

$$\Rightarrow I_x = 2\text{ A}$$

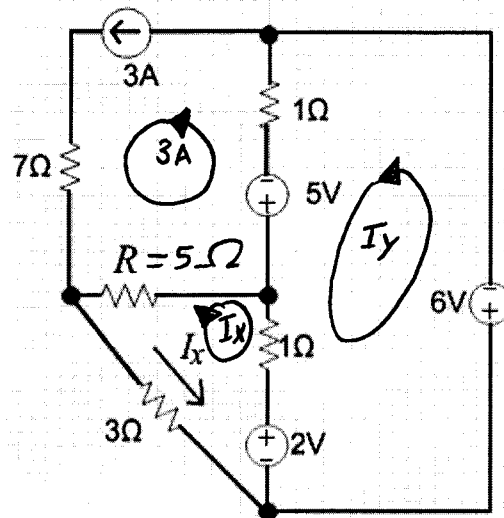


Fig. 13: Circuit of Problem 13

14. Each of the resistances in the circuit shown in Fig. 14 is equal to $10\text{ k}\Omega$, and $\beta = 2\text{ mA/V}$. Find the mesh current I_2 if $I_{SRC} = 23\text{ mA}$.

- (a) 1 mA
- (b) 2 mA
- (c) 3 mA
- (d) 4 mA
- (e) None of the above

$$\textcircled{I_2} : 10(I_2 - 23) + 10(I_2 + 20I_2) + 10I_2 = 0$$

$$I_2 = 1\text{ mA}$$

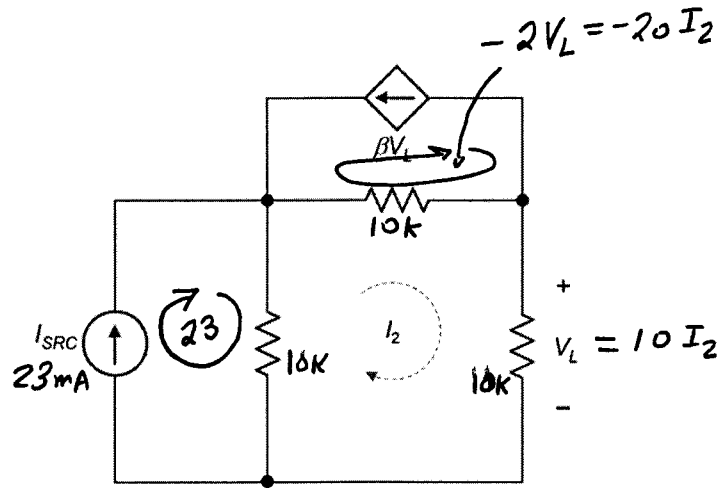


Fig. 14: Circuit of Problem 14

15. Find the current I_x in the circuit shown in Fig. 15 if $V_0 = 115\text{ V}$.

- (a) 2 A
- (b) 4 A
- (c) 6 A
- (d) 8 A
- (e) None of the above

supermesh $\Rightarrow 40I_1 - 20I_x + 40(I_1 + 0.25I_x) - 30I_x = 0$

$$80I_1 = 40I_x \Rightarrow I_1 = \frac{I_x}{2}$$

$$-115 + 90I_x - 20I_1 - 30(I_1 + 0.25I_x) = 0$$

$$90I_x - 20\frac{I_x}{2} - 30\left(\frac{I_x}{2} + 0.25I_x\right) = 115$$

$$\Rightarrow I_x = 2\text{ A}$$

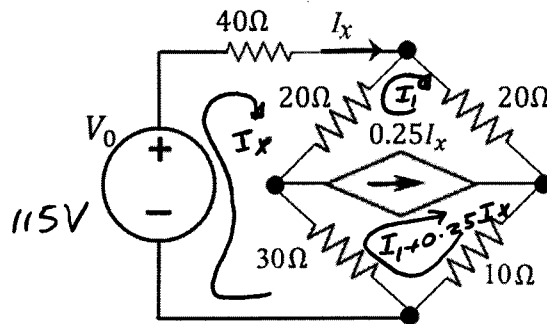


Fig. 15: Circuit of Problem 15