

3.6 Measuring Resistance: The Wheatstone Bridge

- The Wheatstone bridge is used to measure resistances in the range 1Ω to $1\text{M}\Omega$.
- Accuracies of the order of $\pm 0.1\%$ are possible commercially.
- The Wheatstone Bridge Circuit:

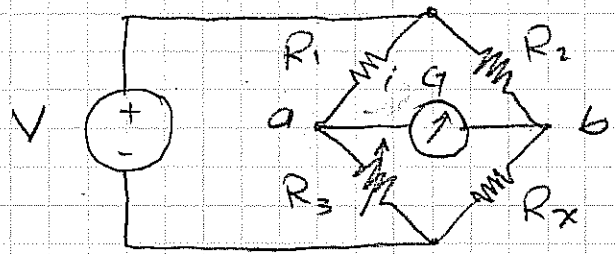


Fig. 3.26.

Adjust R_3 until there is no current in the galvanometer. R_x is given by:

$$R_x = \frac{R_2}{R_1} R_3 \quad (3.33)$$

When the bridge is balanced, the current in the galvanometer (G) is zero. So points a and b are at the same potential. So:

$$i_3 R_3 = i_x R_x \quad (3.36)$$

and $i_1 R_1 = i_2 R_2 \quad (3.37)$

Since current in G is zero, by KCL at nodes a and b we have:

$$i_1 = i_3 \quad \text{and} \quad i_2 = i_x$$

if we replace in 3.36 and 3.37 and divide the two equations we obtain:

$$\frac{R_3}{R_1} = \frac{R_x}{R_2} \Rightarrow R_x = \frac{R_2}{R_1} R_3$$

If the values of R_1 , R_2 and R_3 are known, we can determine R_x .

Assessment Problem 3.7:

For the bridge circuit shown in Fig. 3.26

$$R_1 = 100 \Omega, \quad R_2 = 1000 \Omega, \quad R_3 = 150 \Omega, \quad v = 5 \text{ V}$$

a) What is R_x ?

$$\frac{R_x}{R_2} = \frac{R_3}{R_1} \Rightarrow R_x = \frac{150}{100} \times 1000 = 1500 \Omega$$

b) Can the bridge be left in the balanced state without exceeding the power dissipation of the resistors given at 250 mW?

We need to calculate the currents i_1 and $i_2 (= i_x)$.

$$i_2 = i \frac{R_{eq}}{R_2 + R_x} \quad R_{eq} = v = 5 \text{ V} \Rightarrow$$

$$i_2 = \frac{5}{2500} = 2 \times 10^{-3} \text{ A} = 2 \text{ mA}$$

$$P_2 = R_2 i_2^2 = 1000 \times (2 \times 10^{-3})^2 = 4 \times 10^{-3} = 4 \text{ mW}$$

which is way below the 250 mW limit.

Similarly for other resistors:

$$P_x = R_x i_x^2 = 1500 \times (2 \times 10^{-3})^2 = 6 \text{ mW}$$

The power dissipation of R_1 and R_3 will be calculated using the voltage division rule.

$$v_1 = v \frac{R_1}{R_1 + R_3} = 5 \times \frac{100}{100 + 150} = 2 \text{ V}$$

$$v_2 = v \frac{R_2}{R_1 + R_3} = 5 \times \frac{150}{100 + 150} = 3 \text{ V}$$

(or $v_2 = v - v_1$ (KVL) !)


$$P_1 = \frac{v_1^2}{R_1} = \frac{4}{100} = 0.04 \text{ W} = 40 \text{ mW}$$

$$P_3 = \frac{v_2^2}{R_2} = \frac{9}{150} = 0.06 \text{ W} = 60 \text{ mW}$$


So the power dissipation in all resistors is $\ll 250 \text{ mW}$, and thus we can leave the bridge in the balanced state for an extended period of time.

3.7 Delta-to Wye (Δ -Y) or Pi-to-Tee (Π -T) Equivalent Circuits.

A Δ configuration can be viewed as a Π :

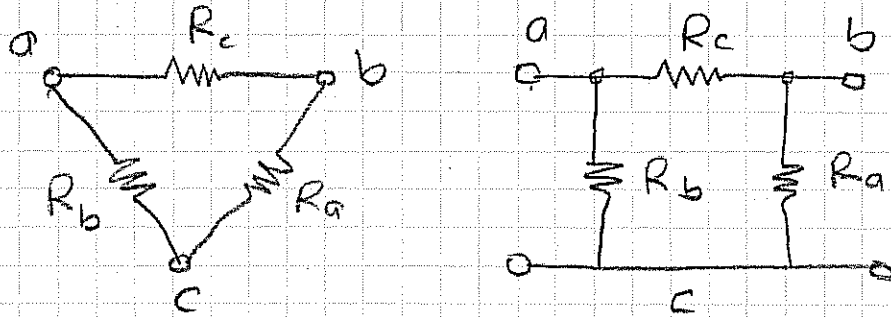

A Y configuration can be viewed as a T:

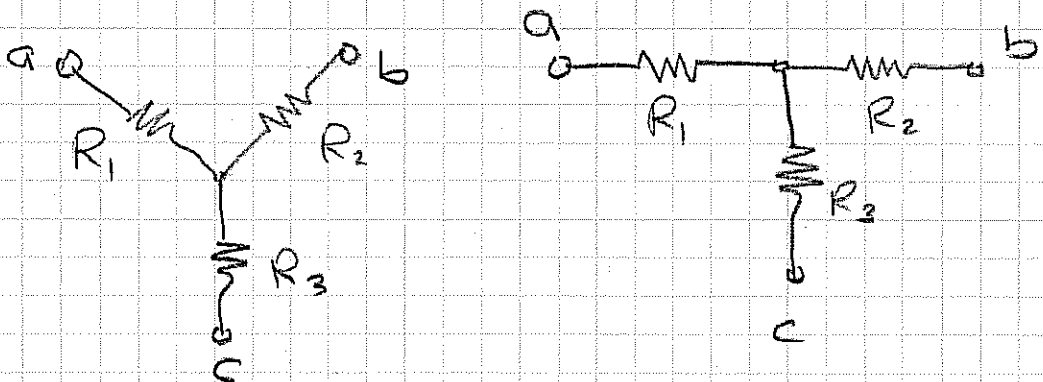

For a Δ (or Π) configuration to be equivalent to a Y (or T). The resistances seen (measured) between any two terminals on the Δ must be equivalent to the corresponding in the Y:

$$R_{ab}(\Delta) = R_{ab}(Y)$$

$$R_{ab}(\Delta) = R_c \parallel (R_a + R_b)$$

$$R_{ab}(Y) = R_1 + R_2$$

$$S_0 = \frac{R_c (R_a + R_b)}{R_a + R_b + R_c} = R_1 + R_2 \quad (3.41)$$

Similarly:

$$R_{bc} = \frac{R_a (R_b + R_c)}{R_a + R_b + R_c} = R_2 + R_3 \quad (3.42)$$

$$\text{and } R_{ca} = \frac{R_b (R_a + R_c)}{R_a + R_b + R_c} = R_1 + R_3 \quad (3.43)$$

Solve for R_1 , R_2 and R_3 in terms of R_a , R_b and R_c to obtain the equations of a Y- Δ transformation (T- Π):

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad (3.44)$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c} \quad (3.45)$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c} \quad (3.46)$$

For the Δ -Y transformation we solve 3.41 \rightarrow 3.43 for R_a , R_b , and R_c in terms of R_1 , R_2 and R_3 :


$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \quad (3.47)$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \quad (3.48)$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} \quad (3.49)$$

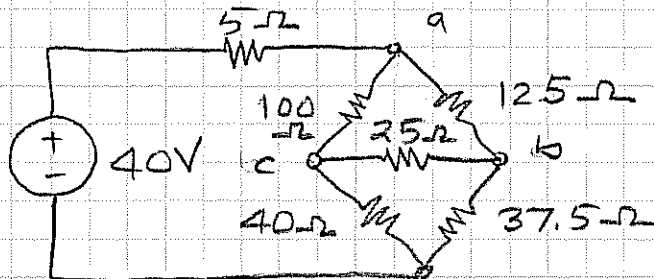Example 3.7:

Use a Δ -Y transformation to find the current and power supplied by the source in the following circuit:



Solution:


Use equations 3.44 to 3.46 to transform the top Δ to a Y =

$$R_1 = \frac{100 \times 125}{100 + 125 + 25} = 50 \Omega$$

$$R_2 = \frac{125 \times 25}{250} = 12.5$$

$$R_3 = \frac{100 \times 25}{250} = 10 \Omega$$

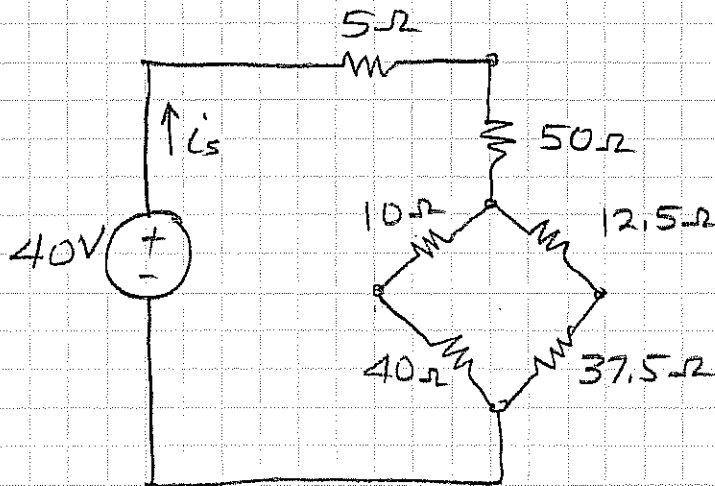The circuit following the transformation becomes:



R_{eq} "seen" by the source is:

$$R_{eq} = 5 + 50 + \frac{50 \times 50}{100} = 80 \Omega$$


$$I_s = \frac{40}{80} = 0.5 \text{ A}$$

$$P_s = 40 \times 0.5 = 20 \text{ W. is delivered}$$

to the circuit.

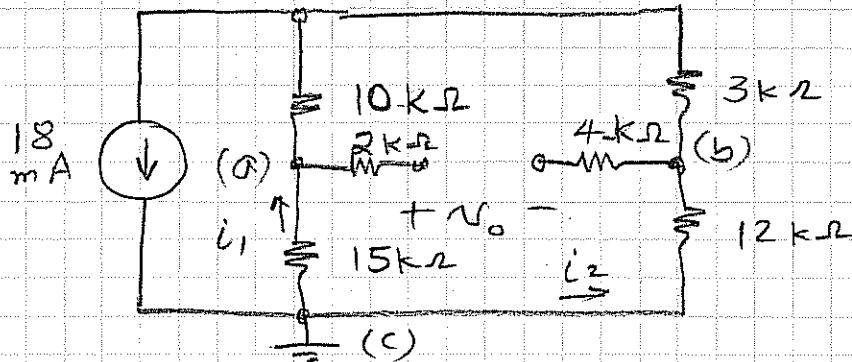Problem 3.26

Find voltage v_o in the following circuit:



Check whether bridge is balanced.

$$\frac{10}{15} = 0.667 \neq \frac{3}{12} = 0.25$$

The bridge is not balanced.

By KVL $v_o = v_{ac} - v_{bc}$, so let us calculate v_{ac} and v_{bc} . To do that we need to determine the current in each branch. We will do that using the current divider rule:

$$i_1 = 18 \times \frac{15}{15+25} = 6.75 \text{ mA}$$

$$i_2 = 18 \times \frac{25}{15+25} = 11.25 \text{ mA}$$


$$v_{ac} = -i_1 \times 15 = -6.75 \times 15 = -101.25 \text{ V}$$

$$v_{bc} = -i_2 \times 12 = -11.25 \times 12 = -135 \text{ V}$$

$$V_o = V_{ac} - V_{bc} = -101.25 + 135 = 33.75 \text{ V}$$

Problem 3.27

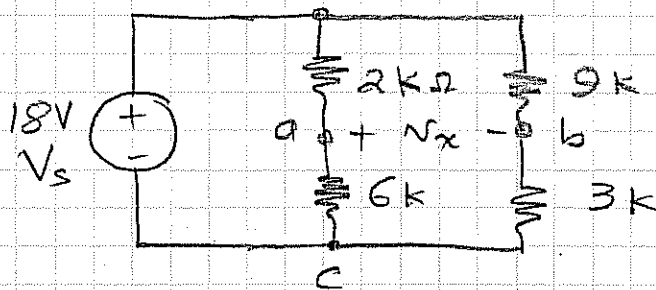a) Find the voltage V_x in the circuit shown below:



$$V_x = V_{ac} - V_{bc}$$

$$V_{ac} = 18 \times \frac{6}{18} = 6 \text{ V}$$

$$V_{bc} = 18 \times \frac{3}{12} = 4.5 \text{ V}$$

$$V_x = 6 - 4.5 = 1.5 \text{ V}$$

Note: Bridge is not balanced!

b) Find V_x as a function of V_s :


$$V_{ac} = V_s \times \frac{1}{3} \quad V_{bc} = V_s \times \frac{1}{4}$$

$$V_x = V_s \left(\frac{1}{3} - \frac{1}{4} \right) = \frac{V_s}{12}$$

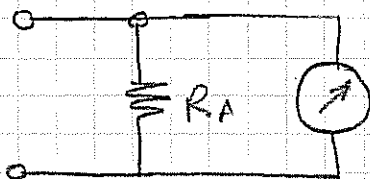3.39

50mV, 1mA d'Arsonval movement.

What is the largest full-scale reading if the shunt resistors available have a 0.5W rating?



At full scale the voltage drop across the ammeter is 50mV,

The power dissipated in R_A is:

$$P = \frac{(50 \times 10^{-3})^2}{R_A} = 0.5 \Rightarrow$$

$$R_A = \frac{(50 \times 10^{-3})^2}{0.5} = 5 \times 10^{-3} = 5 \text{ m}\Omega$$

Note that largest full-scale corresponds to the smallest R_A !


The current in the ammeter is the current in R_A (very nearly) because

$$R_A (= 5 \text{ m}\Omega) \ll R_{\text{mov}} = 50 \Omega$$


So the full scale reading is

$$I_{\text{FS}} = 50 \times 10^{-3} / (5 \times 10^{-3}) = 10 \text{ A.}$$

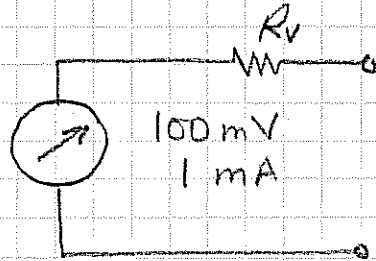Problem 3.40: The voltmeter shown has a Full-scale reading of 800V, the meter movement is rated at 100mV and 1mA.



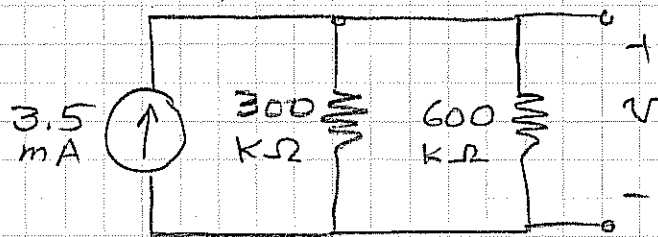What is the error if it is used to measure the voltage v in the following circuit?



The voltage is calculated as:

$$V = 3.5 \times \frac{300 \times 600}{300 + 600} = 3.5 \times 200$$

$$= 700 \text{ V}$$

The resistance of the meter is obtained from KVL applied on the meter at full scale:

$$800 = R_v \times 1 \times 10^{-3} + 100 \times 10^{-3} \Rightarrow$$

$$R_v \approx \frac{800}{1} = 800 \text{ k}\Omega$$

when inserted in parallel with the given circuit the measured voltage V_m would be read as:

$$V_m = 3.5 \times \frac{200 \times 800}{200 + 800} = 3.5 \times 160 \\ = 560 \text{ V}$$

The error is defined by:

$$\text{error} = \left(\frac{\text{measured}}{\text{true}} - 1 \right) \times 100\% \\ = \left(\frac{560}{700} - 1 \right) \times 100 = -20\%$$

Note:

Obviously, the meter is not appropriate to measure the voltage in the circuit.


It will be able to measure voltages across resistances that should be much smaller than $800 \text{ k}\Omega$. For example if the resistances were $30 \text{ k}\Omega$ and $60 \text{ k}\Omega$ and the current source 35 mA . The voltage V would still be 700 V .

But the measured voltage would be =

$$V_m = 35 \times \frac{20 \times 800}{820} = 682.9 \text{ V}$$

The error would then be -2.44% !

3.51

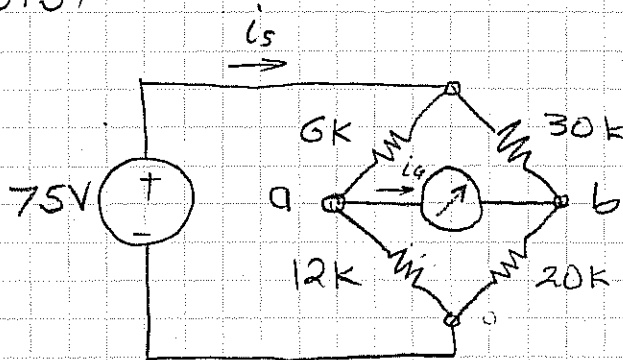

Find the detector current in the bridge (i_g) if the voltage drop across the detector (G) is negligible.

Solution:

Since $\frac{6}{12} = \frac{1}{2} \neq \frac{30}{20} = 1.5$, the bridge is not balanced. Nevertheless points a , and b are at the same potential because the voltage drop across the galvanometer is zero!


Since points a and b are at the same potential, I can short them! Then the equivalent resistance is obtained as follows:

$$R_{eq} = (6 \parallel 30) + (12 \parallel 20) \\ = 5 + 7.5 = 12.5 \text{ k}\Omega$$

The current from the source is-

$$i_s = \frac{75}{12.5} = 3 \text{ mA}$$

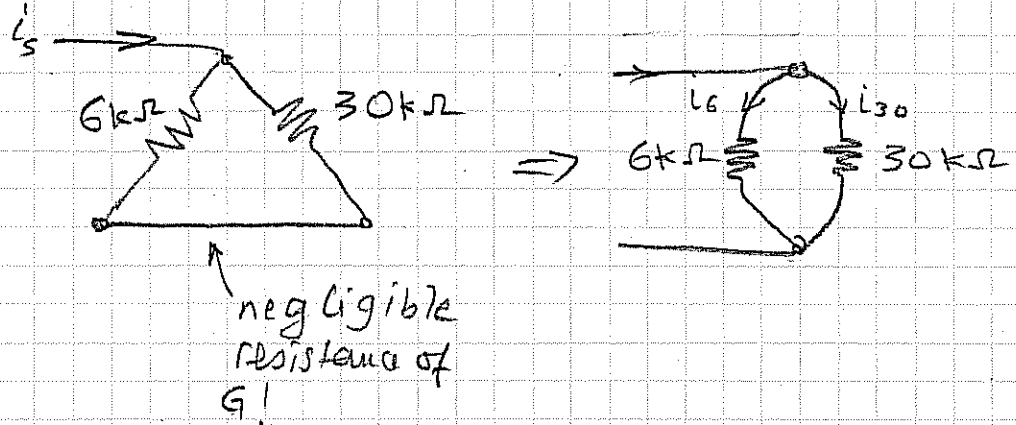
Since points a and b are at the same potential, then the currents in the 6 and 30 k Ω resistors can be found using the current divider rule



$$\text{So } I_6 = I_s \frac{30}{36} = 3 \times \frac{30}{36} = 2.5 \text{ mA}$$

$$I_{30} = 3 - 2.5 = 0.5 \text{ mA}$$

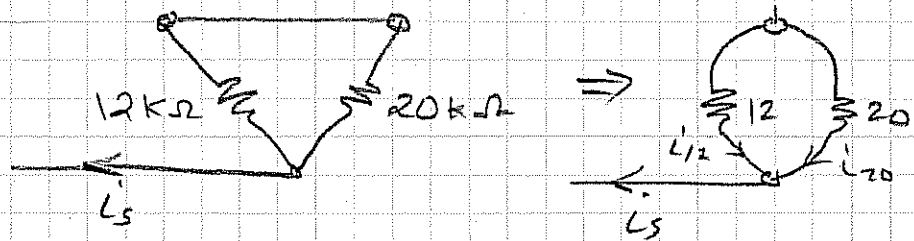
Similarly for 12 k Ω and 20 k Ω resistors:



$$I_{12} = I_s \frac{20}{32} = 3 \times \frac{20}{32} = 1.875 \text{ mA}$$

$$I_{20} = I_s \frac{12}{32} = 3 \times \frac{12}{32} = 1.125 \text{ mA}$$

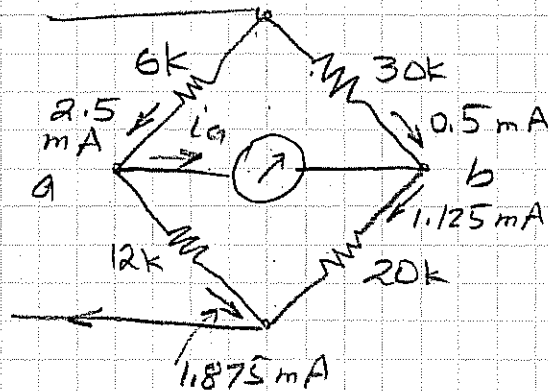Now if we go back to the original circuit:




i_g can be found from KCL at node a:

$$i_g + i_{12} = i_6 \Rightarrow$$

$$i_g = i_6 - i_{12} = 0.625 \text{ mA}$$


The same answer is obtained with KCL at node b.

Problem 3.56

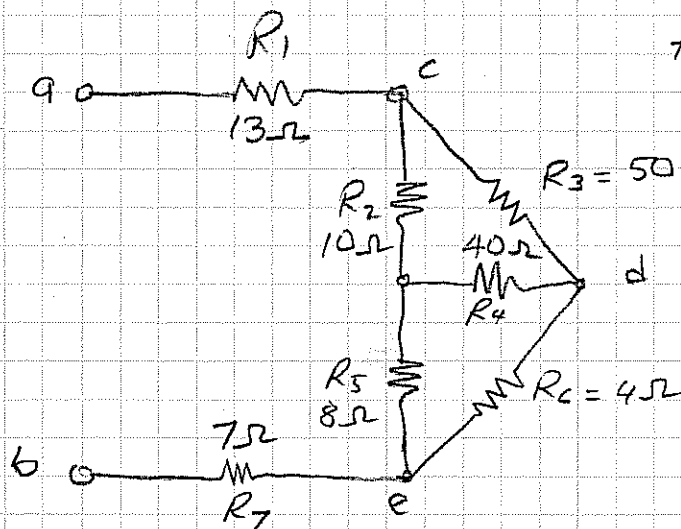

Find R_{ab} .

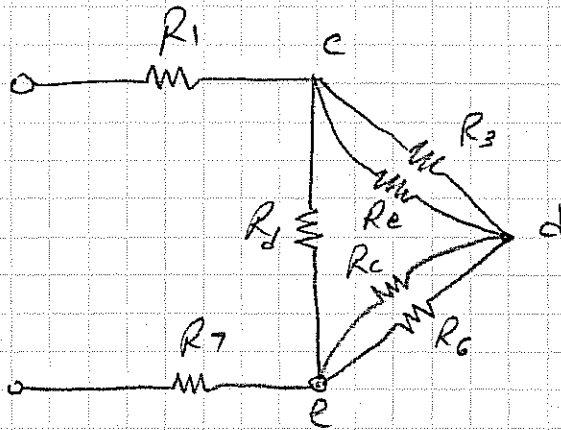Hint: Do a Y \rightarrow Δ transformation involving R_2 , R_4 and R_5 , the following equivalent circuit will emerge:



Using equations 3.47 to 3.49:

$$R_c = \frac{R_2 R_4 + R_4 R_5 + R_5 R_2}{R_2} = \frac{800}{10} = 80 \Omega$$

$$R_d = \frac{R_2 R_4 + R_4 R_5 + R_5 R_2}{R_4} = \frac{800}{40} = 20 \Omega$$

$$R_e = \frac{R_2 R_4 + R_4 R_5 + R_5 R_2}{R_5} = \frac{800}{8} = 100 \Omega$$

$$R_{ab} = R_1 + R_{ce} + R_7$$

$$\begin{aligned} \text{with } R_{ce} &= R_d \parallel \left((R_3 \parallel R_e) + (R_4 \parallel R_c) \right) \\ &= 20 \parallel \left(\frac{50 \times 100}{150} + \frac{4 \times 80}{84} \right) \\ &= 20 \parallel 3.333 + 3.8095 \\ &= \frac{20 \times 7.142857}{27.142857} = 5.2632 \Omega \end{aligned}$$

$$R_{ab} = 1 + 5.26 + 7 = 13.26 \Omega$$