

Ch. 3: Simple Resistive Circuits

Analytical Box so far contains:

- Ohm's Law
- Kirchoff's current and voltage laws.
- Tools of this chapter will allow us to tackle more complex interconnections.

- Terminology: dc current source means dc constant current source, and dc voltage source means dc constant voltage source.

Practical Perspective: A rear window defroster.

3.1 Resistors in Series


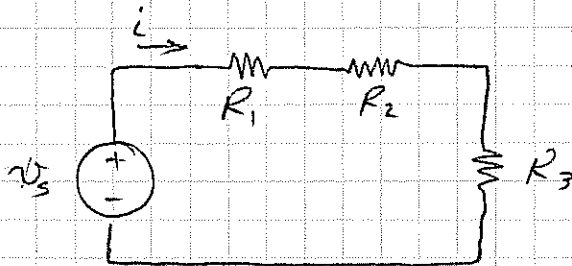


Fig. 1.


$$\begin{aligned} \text{KVL: } v_s &= iR_1 + iR_2 + iR_3 \Rightarrow \\ v_s &= i(R_1 + R_2 + R_3) = iR_{eq} \end{aligned}$$

$$\text{where } R_{eq} = R_1 + R_2 + R_3$$

So an equivalent circuit would be =

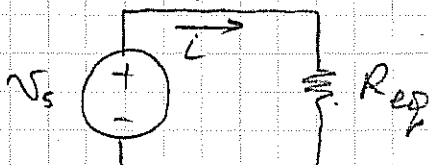

3.2 Resistors in Parallel

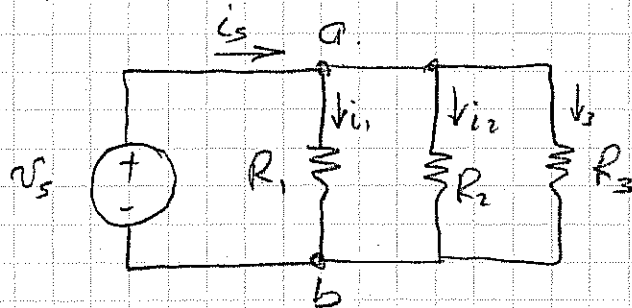

KCL at node a:

$$i_s = i_1 + i_2 + i_3 \quad (1)$$

Resistances share the same voltage:

$$v_s = R_1 i_1 = R_2 i_2 = R_3 i_3$$


$$\text{so } i_1 = \frac{v_s}{R_1}, \quad i_2 = \frac{v_s}{R_2}, \quad i_3 = \frac{v_s}{R_3}$$

replace in KCL above:

$$i_s = v_s \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \Rightarrow$$

$$i_s = v_s \frac{1}{R_{eq}} \Rightarrow R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$$

Assessment Problem 3.1

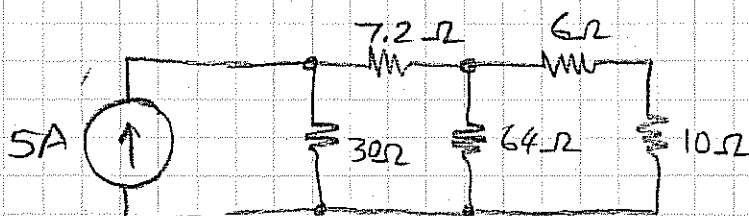

- Find v
- Power delivered by the 5A source
- Power dissipated in 10 ohm resistor.

Solution:

a) i) Combine the 6Ω and 10Ω in series:

$$R_1 = 6 + 10 = 16\Omega$$

ii) Combine $R_1 = 16\Omega$ in parallel with the 64Ω

$$R_2 = \frac{16 \times 64}{80} = 12.8\Omega$$


iii) Now $R_2 = 12.8\Omega$ is in series with the 7.2Ω resistor:

$$R_3 = 12.8 + 7.2 = 20\Omega$$

iv) Finally $R_3 = 20\Omega$ is in parallel with the 30Ω resistor:

$$R_4 = \frac{20 \times 30}{20 + 30} = 12\Omega$$

So the final equivalent circuit is:

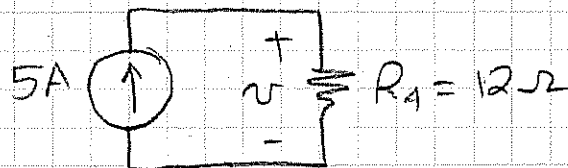


$$\text{So } V = 5 \times 12 = 60V$$

b) Power delivered by the $5A$ source:

$$P_{5A} = 60 \times 5 = 300W$$

c) Power dissipated in the 10Ω resistor:

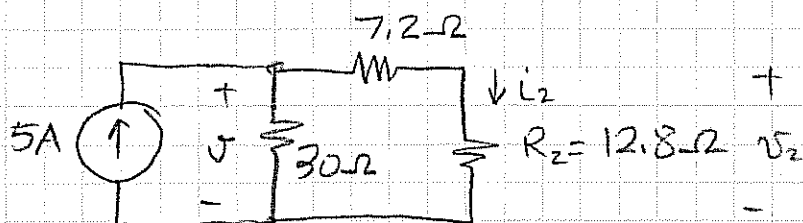
i) Find the current in R_2 which is the same at that of the current in the 7.2Ω :



$$i_2 = \frac{v}{7.2 + 12.8} = \frac{60}{20} = 3 \text{ A}$$

The voltage $v_2 = R_2 i_2 = 12.8 \times 3 = 38.4 \text{ V}$

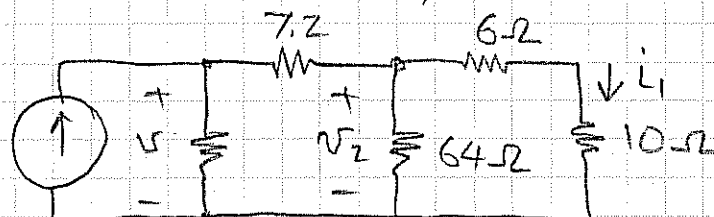Now the current in R_1 , or in the 10Ω resistance can be found:




$$i_1 = 38.4 / (16) = 2.4 \text{ A}$$

Power dissipated in 10Ω resistance:

$$P_{10\Omega} = (2.4)^2 \times 10 = 57.6 \text{ W}$$

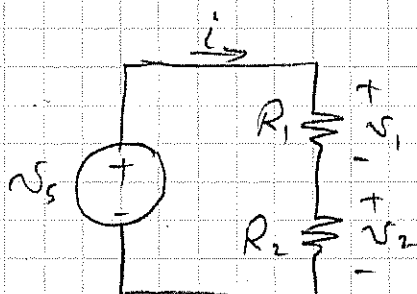3.3 The Voltage-Divider and Current-Divider Circuits.



KVL in loop:

$$v_s = v_1 + v_2$$

$$= iR_1 + iR_2$$

$$\text{So } i = \frac{v_s}{R_1 + R_2}$$

Using Ohm's law on R_1 and R_2 :

$$v_1 = iR_1 = v_s \frac{R_1}{R_1 + R_2}$$


V_{max} occurs when R_2 is 10% high and R_1 is 10% low:

$$V_{\text{max}} = 100 \frac{110}{110 + 22.5} = 83.02 \text{ V}$$

V_{min} occurs when R_1 is 10% low and R_2 is 10% high:

$$V_{\text{min}} = 100 \frac{90}{90 + 27.5} = 76.60 \text{ V}$$

The Current Divider Circuit:

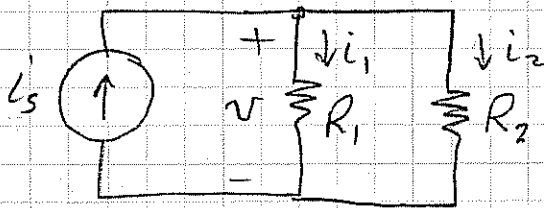

The resistances share the same voltage:


$$V = R_1 i_1 = R_2 i_2 = R_{\text{eq}} I_s = \frac{R_1 R_2}{R_1 + R_2} I_s$$

From equation above:

$$R_1 i_1 = \frac{R_1 R_2}{R_1 + R_2} I_s \Rightarrow i_1 = \frac{R_2}{R_1 + R_2} I_s$$


$$R_2 i_2 = \frac{R_1 R_2}{R_1 + R_2} I_s \Rightarrow i_2 = \frac{R_1}{R_1 + R_2} I_s$$

Example 3.3

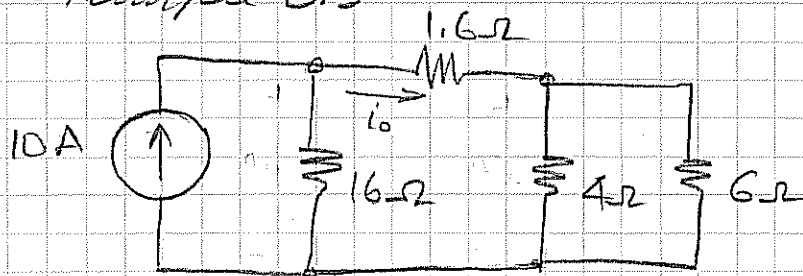

Find power dissipated in the 6Ω resistor.

The above circuit simplifies to:

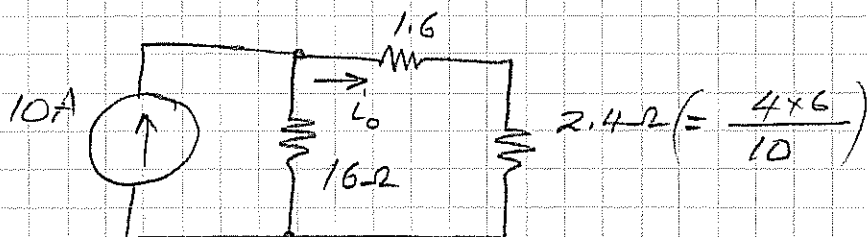

$$i_0 = 10 \frac{16}{16 + 4} = 8A$$

Now the current i_0 divides between the 4Ω and 6Ω resistors. The current in the 6Ω resistor is:


$$i_{6\Omega} = 8 \times \frac{4}{10} = 3.2A.$$

$$P_{6\Omega} = 6 \times (3.2)^2 = 61.4W.$$

3.4 Voltage and Current Division

This is a generalization of the rules developed in the previous section:

Voltage Division:

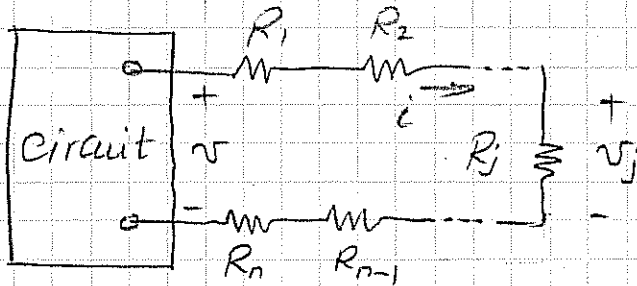


All resistances - have the same current

$$i = \frac{v}{R_{eq}} \quad R_{eq} = \sum_{j=1}^n R_j$$

The voltage v_j is given by:

$$v_j = i R_j = v \frac{R_j}{R_{eq}}$$

Current Division:

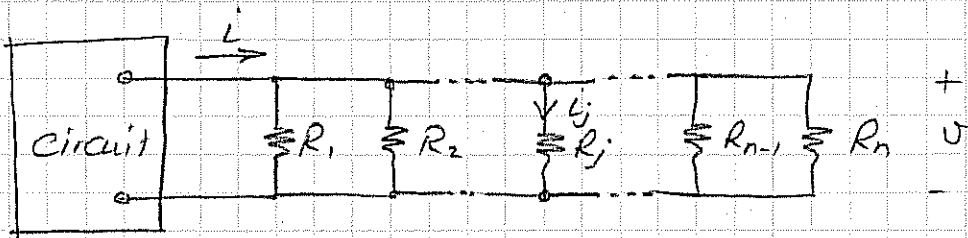


All resistances have the same voltage v :

$$v = i R_{eq} \quad R_{eq} = \left(\sum_{j=1}^n \frac{1}{R_j} \right)^{-1}$$

The current in resistance R_j is given by:

$$I_j = \frac{V}{R_j} = \frac{R_{eq}}{R_j} i$$

Example 3.4

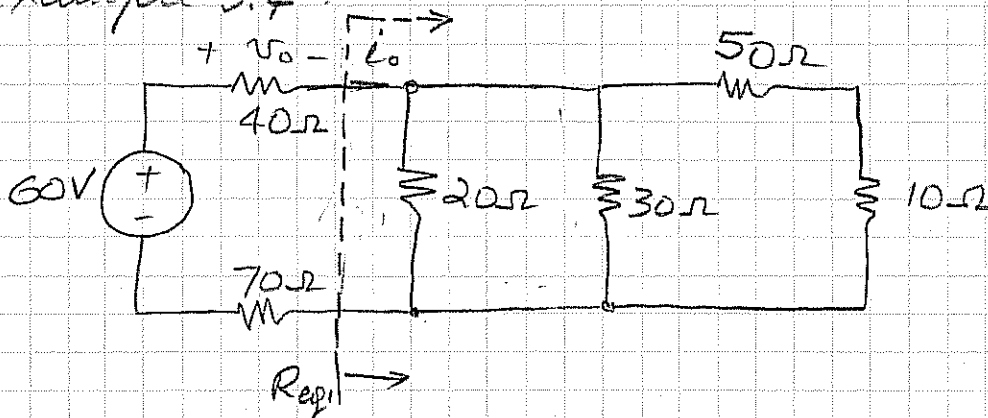


- Use voltage division to determine v_0
- Find i_0 and use current division to determine current in the 30Ω resistor
- Find power dissipated in the 50Ω resistor.

Solution:

a) Find R_{eq1} :


$$\begin{aligned} R_{eq1} &= 20 \parallel 30 \parallel (50 + 10) \\ &= \left(\frac{1}{20} + \frac{1}{30} + \frac{1}{60} \right)^{-1} = 10\Omega \end{aligned}$$

The equivalent circuit is now:

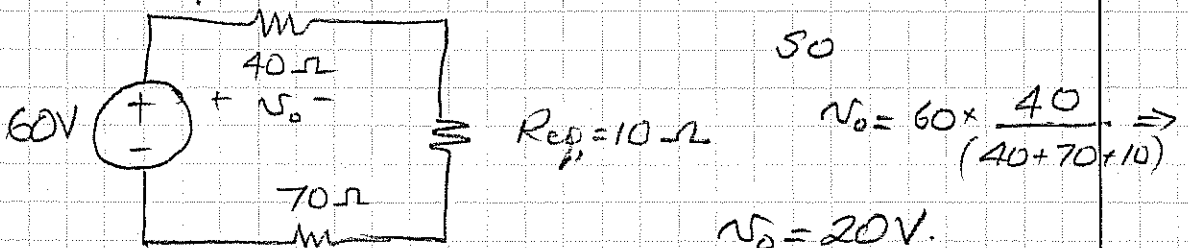

$$v_2 = i R_2 = v_s \frac{R_2}{R_1 + R_2}$$

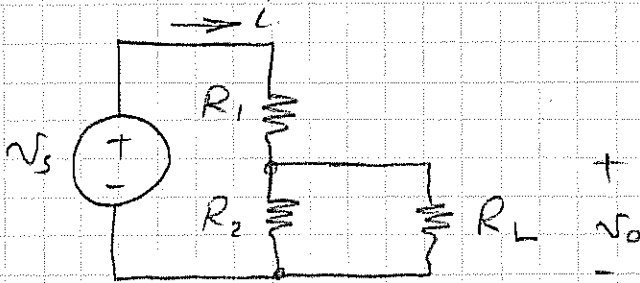A voltage divider connected to a load resistor R_L :



In the circuit above find v_o :

i) Find the equivalent resistance of $R_2 \parallel R_L$:


$$R_{eq} = R_2 \parallel R_L = \frac{R_2 R_L}{R_2 + R_L}$$

ii) The voltage v_o is found using the current divider rule:

$$v_o = v_s \frac{R_{eq}}{R_1 + R_{eq}}$$

$$\text{As } R_L \rightarrow \infty \Rightarrow R_{eq} \rightarrow R_2$$

Example 3.2:

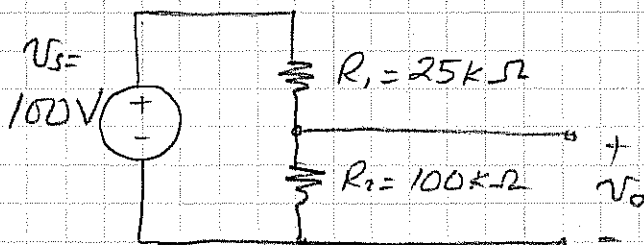

The tolerance on the values of R_1 and R_2 is $\pm 10\%$.

Find the maximum and minimum value of v_o .

$$b) \quad i_0 = \frac{V_0}{40} = \frac{20}{40} = 0.5 \text{ A.}$$

The current in the 30Ω resistor is given by:

$$i_{30} = \frac{R_{eq1}}{30} i_0 = \frac{10}{30} \times 0.5 = 0.1667 \text{ A} \\ = 166.7 \text{ mA}$$

$$c) \quad P_{50 \Omega} = ?$$

The current in the 50Ω resistor is given by:

$$i_{50} = \frac{R_{eq1}}{(50+10)} i_0 = \frac{10}{60} \times 0.5 = 0.08333 \text{ A} \\ = 83.33 \text{ mA.}$$

$$P_{50 \Omega} = 50 i_{50}^2 = 50 \times 0.0833^2 \\ = 0.3472 \text{ W} = 347.2 \text{ mW.}$$


3.5 Measuring Voltage and Current:

Two methods of measuring:

- digital (used in modern equipment).
- Analog (historical; uses the d'Arsonval movement) used up until the early 1970's.

The digital meter measures the voltage across a resistance and converts the signal to a digital signal using an

analog to digital converter (ADC):

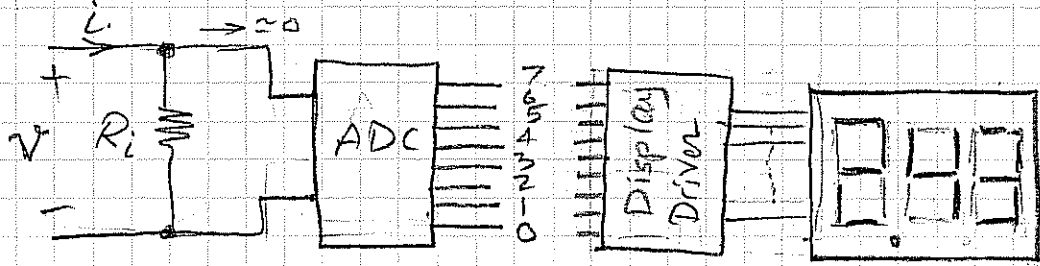

Range of v : 10V

Range of i : 0.1mA

7 6 5 4 3 2 1 0 5V

0 0 0 0 0 0 0 0 0V

0 0 0 0 0 0 0 1

0 0 0 0 0 0 1 0

0 0 0 0 0 0 1 1

0 0 0 0 0 1 0 0

1 1 1 1 1 1 0 0

1 1 1 1 1 1 0 1

1 1 1 1 1 1 1 0

1 1 1 1 1 1 1 1 9.99

} 2^8 values n

$2^8 - 1$ intervals = 255

each interval has voltage increment of:

$$\Delta V = \frac{9.99}{2^8 - 1} = \frac{9.99}{255} = 0.039218 \text{ V}$$


So if the output of ADC is:

$$\begin{array}{cccccccc} 7 & 6 & 5 & 4 & 3 & 2 & 1 & 0 \\ 0 & 0 & 1 & 1 & 1 & 1 & 1 & 0 \end{array} \rightarrow (2^5 + 2^4 + 2^3 + 2^2 + 2^1) \times 0.039218$$

$$= 62 \times 0.039218 = 2.43 \text{ V}$$

So the display is 2.43V ...

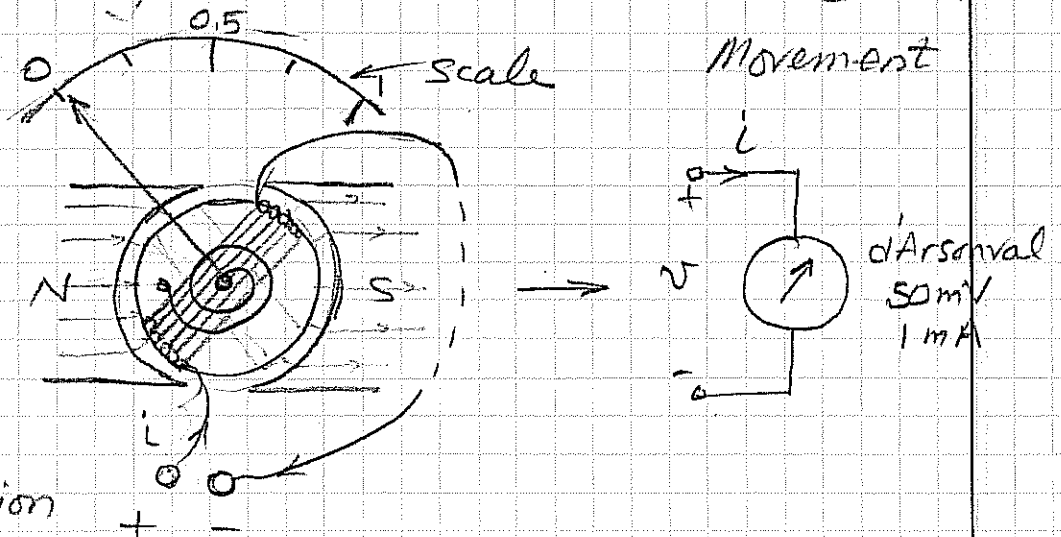
The analog meter is based on the d'Arsonval Movement




Operation

- * Current flows in coil creates a torque proportional to current
- * The torque causes the coil to rotate
- * The spring deforms and creates a balancing torque
- * For a given movement a current of 1 mA causes the pointer to move 1 full scale. If the voltage applied is 50 mV , it means that the internal resistance is $50\ \Omega$
- * So when the current entering is 0.5 mA , the pointer is at mid scale and the applied voltage is $0.5 \times 50 = 25\text{ mV}$.

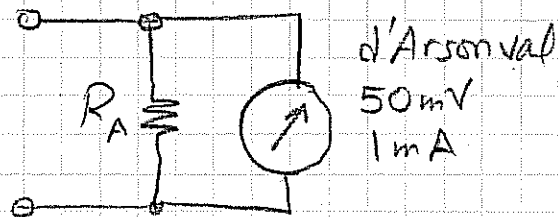We can construct an ammeter using the d'Arsonval movement by adding a resistor across it as shown



A voltmeter is constructed by adding a resistance R_V in series with the d'Arsonval movement as shown:

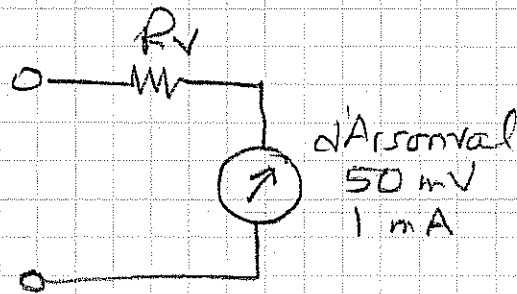

Example 3.5: d'Arsonval Ammeter

a) what should R_A be for a fullscale reading of 10mA.

The current in R_A is $10 - 1 = 9\text{mA}$.

Since the voltage is 50mV, then

$$R_A = \frac{50}{9} = 5.55\text{-}\Omega$$

b) What should R_A be for a full scale reading of 1 A

$$R_A = \frac{50}{1000-1} = 50.05 \text{ m}\Omega$$

c) How much resistance is added to the circuit when the 10 mA ammeter is added to the circuit.

$$R_m = \frac{50 \text{ mV}}{10 \text{ mA}} = 5 \Omega$$

Example 3.6: d'Arsonval Voltmeter

a) What should R_V for a full-scale reading of 150 V?

Full scale requires 50 mV across the movement with a current of 1 mA.

$$(R_V + 50) \times 1 \times 10^{-3} = 150 \Rightarrow$$

$$R_V = \frac{150}{10^{-3}} - 50 = 149950 \Omega$$

b) for a full scale reading of 5 V:

$$(R_V + 50) \times 10^{-3} = 5 \Rightarrow$$

$$R_V = \frac{5}{10^{-3}} - 50 = 4950 \Omega$$