

Ch. 1: Circuit Variables

1.1 Electrical Engineering Overview.

- It is an integral part of engineering system: building, airplane
- Major classifications of electrical systems:
 - Communication systems to transmit and receive signals
 - Computer systems to process information
 - control systems to regulate processes
 - power systems to generate and distribute electricity
 - Signal processing systems: To process signals and information into suitable form (
- Circuit Theory is a special case of electromagnetic field theory to study static and moving charges from a macro-view point.
- Problem Solving.

1.2 International System of Units

defined quantities	length	(m)	electric current (A)
	mass	(kg)	Thermodynamic Temp. (K)
	time	(s)	Amount of substance (mol)
			luminous intensity (cd)

Derived Quantities:

Frequency	hertz (Hz)	s^{-1}
Force	newton (N)	$kg \cdot m / s^2$
Energy or Work	joule (J)	N.m
Power	watt (W)	J/s
Electric Charge	coulomb (C)	A.s
Electric Potential	volt (V)	J/C
Electric Resistance	ohms (Ω)	V/A
Electric Conductance	siemens (S)	A/V
Electric Capacitance	farad (F)	C/V
Magnetic flux	weber (Wb)	V.s
Inductance	henry (H)	Wb/A

1.3 Circuit Analysis

- Circuit Model
- Ideal circuit components
- Describe behavior using physics and equations
- Solve equations to deduce required variable
- Build Prototype

1.4 Voltage and Current

- Important characteristics of electric charge:

- charge is bipolar meaning that electrical effects are described in terms of positive or negative charges.
- electric charges are discrete multiples of the electronic charge $1.6022 \times 10^{-19} \text{ C}$.
- electrical effects are due to charges in motion and separation of charges.

Definition of Voltage:

$$- v = \frac{dw}{dq} \quad \text{energy per unit charge}$$

v voltage in V

w energy in J

q charge in C

$$- i = \frac{dq}{dt} \quad \text{rate of charge flow}$$


i current in A

t time in s .

1.5 The Ideal Basic Circuit Element:

It has three attributes:

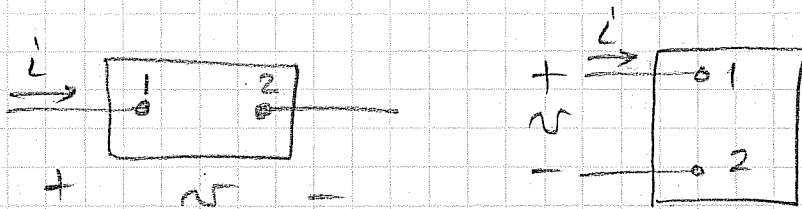- i) Two terminals to connect to other components.
- ii) Described mathematically in terms of current and voltage.
- iii) Cannot be subdivided further



Graphical representation of an ideal circuit element.

Passive sign convention: Current entering positive pole (1)

Example 1.3: 5 V source, 1 A , the current is defined by the arrow i

$$i = 0 \quad t < 0$$

$$i = 20e^{-5000t} \text{ A} \quad t \geq 0$$

calculate total charge in coulombs (C) entering the element.


$$i = \frac{dq}{dt} \Rightarrow q(t) = \int_0^t 20e^{-5000t} dt + q(0)$$

if $v = 5V$ and $i = 2A$, then

$$P = 5 \times 2 = 10 \text{ W}$$


The device is said to consume 10W!

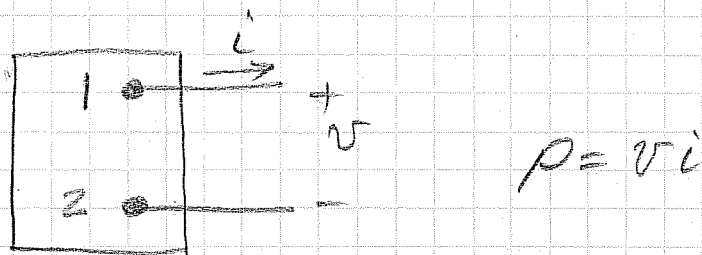Active Sign Convention: used for generators:



Then p is the power delivered by device

Example 1.7: dc transmission line.

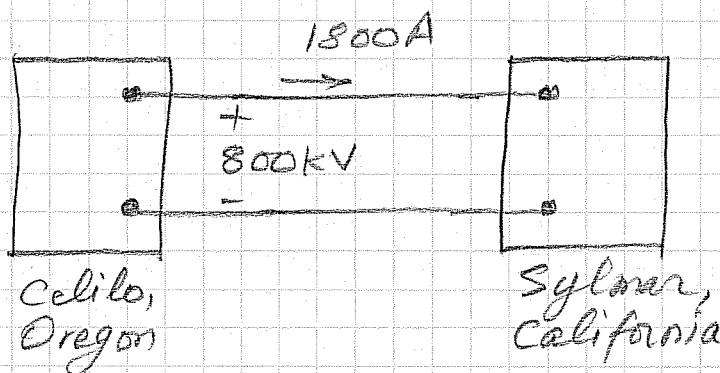

Celilo acts as a generator it delivers

$$P_1 = 800 \times 1.8 = 1440 \text{ MW}$$

Sylmar acts as a load, it receives or consumes 1440 MW.

charge entering =

$$\Delta Q = q(\infty) - q(0) = \frac{20}{5000} = 4000 \times 10^{-6} \text{ C}$$

Example 1.4: Maximum current is when

$$\frac{di}{dt} = 0!$$

1.6 Power and Energy

$$p = \frac{dw}{dt} \quad \text{power (p) is energy per unit time.}$$


p power in W

w energy in J.

$$\text{But } p = \frac{dw}{dt} = \frac{dw}{dq} \frac{dq}{dt} \Rightarrow i$$

$$p = vi$$

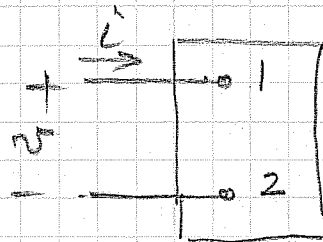
Given the ideal circuit element using a passive sign convention.



Then power consumed by device is:

$$p = vi$$

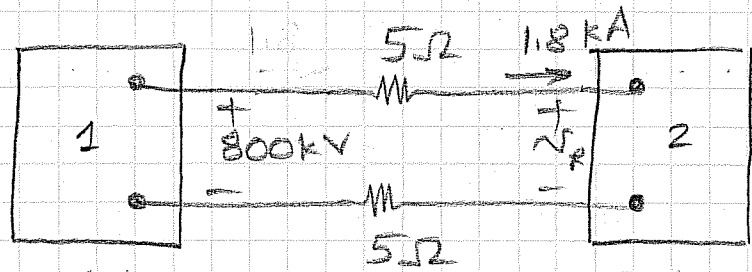Suppose we have a resistance $R = 2 \times 5 \Omega$



Clilo
Oregon

Sylmar
California.

$$800 = 1.8 \times 5 + V_R + 1.8 \times 5 \Rightarrow \text{(KVL)}$$

$$V_R = 782 \text{ kV.}$$

Power Supplied from Clilo:

$$P_1 = 800 \times 1.8 = 1440 \text{ MW.}$$

Power received at Sylmar:

$$P_2 = 782 \times 1.8 = 1408 \text{ MW.}$$

Power consumed in TL (Power loss):

$$P_{TL} = 1440 - 1408 = 32 \text{ MW}$$

$$\eta_{TL} = \frac{P_2}{P_1} = \frac{1408}{1440} = 97.8 \%$$

Recommended Problems: 1.18, 1.19, 1.20, 1.21, 1.24,

Conservation of energy: $\sum v_k i_k = 0!$