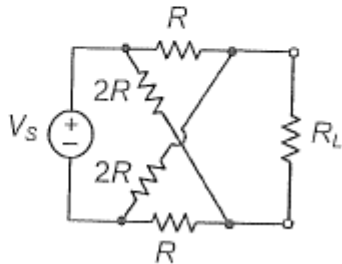



2. Determine R_L for maximum power transfer, and calculate the value of this power, assuming $V_S = 12\text{ V}$ and $R = 3\ \Omega$.

- A. $4\ \Omega$; 1 W
- B. $8\ \Omega$; 0.5 W
- C. $4\ \Omega$; 4 W
- D. $8\ \Omega$; 2 W
- E. None of the above




12 - Determine the maximum power transfer to the load R_L in the following network. (The resistance are given in Ω)

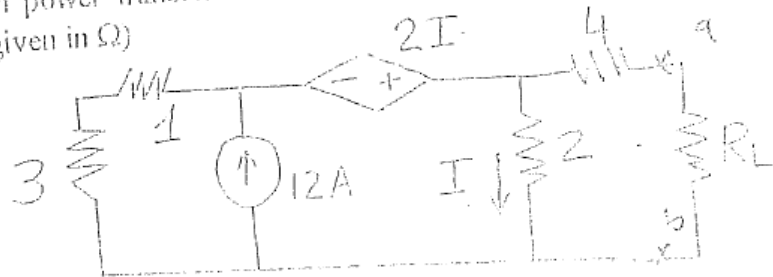- a) 24 W
 b) 36 W
 c) 6 R_L
 d) 36 R_L
 e) none of the above




8. The source current in the circuit shown is $3 \cos(5000t)$ A. What impedance should be connected across the terminals a,b for maximum average power transfer.

- a. $10 - 20j \Omega$
- b. $20 - 10j \Omega$
- c. $10 + 20j \Omega$
- d. $10 - 20j \Omega$
- e. None of the above.

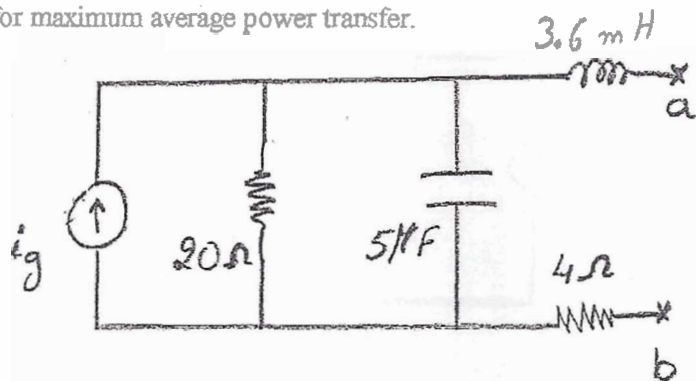

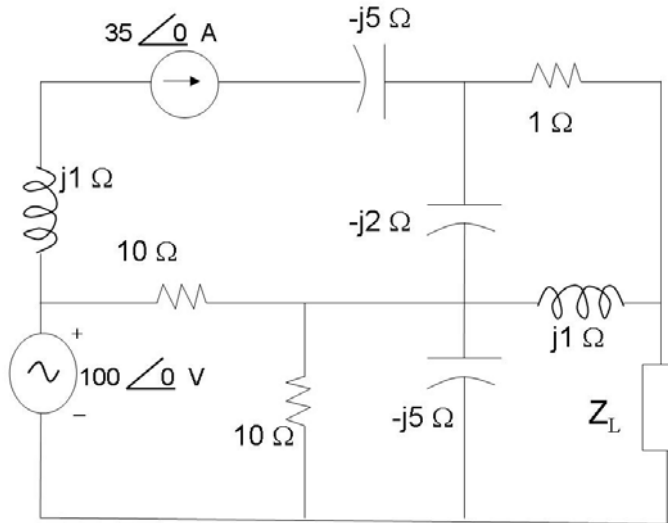
Problem 2

Find the value of the load impedance Z_L such that maximum real power is delivered to it



- A) $3.0 + j1.0 \Omega$
- B) $1.75 + j0.25 \Omega$
- C) $1.5 - j0.5 \Omega$
- D) $3.0 + j1.1 \Omega$
- E) None of the above

Problem 16

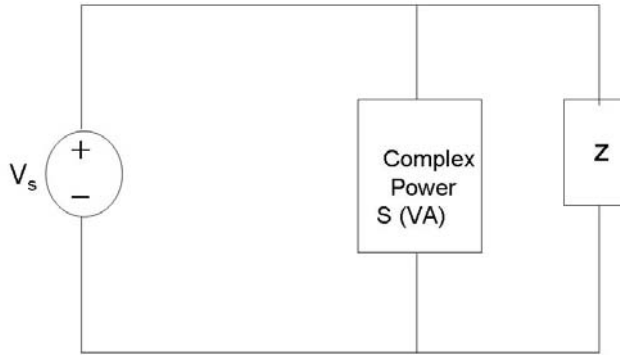


It is given that the load above has complex power $S = 20 + 15j$ KVA. It is required to connect an element Z in parallel with the load so as to correct the power factor to unity (power factor = 1). The source voltage is $V_s = 200 \angle 50^\circ$ V rms and the frequency is 60 Hz [that is $V_s = 200 \cos(377t + 50^\circ)$ V (rms)]. Determine the value and nature of this element Z .

- A) Capacitor with value $C = 994.7 \mu\text{F}$
- B) Inductor with value $L = 7.07 \text{ mH}$
- C) Capacitor with value $C = 663.13 \mu\text{F}$
- D) Inductor with value $L = 10.61 \text{ mH}$
- E) None of the above.

Problem 8 (14 pts)

Consider the circuit shown

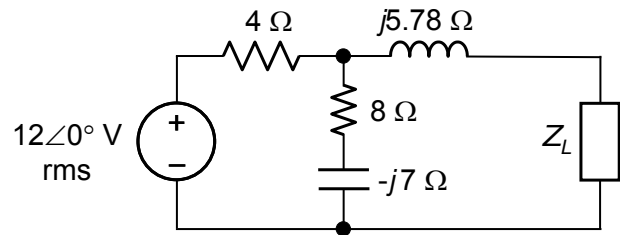- a. Determine the value of the load Z_L to maximize the average power absorbed by the load. (4 pts)



$$Z_{src} = j5.78 + \frac{4(8 - j7)}{12 - j7}$$

$$= 3 + j5.2 \Omega;$$

$$Z_{Lm} = 3 - j5.2 \Omega.$$

- b. For the value obtained in (a), determine the average power developed by the voltage source and the average power absorbed by the load. (4 pts)

$$V_{Th} = 12 \frac{8 - j7}{12 - j7} = 9 - j1.74 \text{ V};$$

$$|V_{Th}| = 9.18 \text{ V};$$

$$I_L = V_{Th}/6 = 1.5 - j0.29 \text{ A}; \quad 12\angle 0^\circ \text{ V rms}$$

$$V_1 = (3 - j0.58)I_L = 4.68 + j0 \text{ V}$$

$$I_{SRC} = \frac{12 - 4.68}{4} = 1.83 + j0 \text{ A}$$

$$P_{SRC} = V_1 I_{SRC} = 12 \times 1.83 \cong 22 \text{ W}; \quad P_L = \frac{(9.18)^2}{4 \times 3} \cong 7 \text{ W}.$$

- c. For a purely resistive load, determine its value R_{max} for maximum power transfer and find the power absorbed by the load. (3 pts)


$$R_m = \sqrt{(3)^2 + (5.2)^2} \cong 6 \Omega; \quad |I| = |V_{Th}|/|Z| = \frac{9.18}{\sqrt{(3+6)^2 + (5.2)^2}} = 0.883 \text{ A}$$

$$P = |I|^2 \times 6 = 4.68 \text{ W}.$$


- d. For a purely resistive load with $R_L = 2R_{max}$ (R_{max} of part c), determine the power absorbed by the load. (3 pts)

$$|I| = |V_{Th}|/|Z| = \frac{9.18}{\sqrt{(3+12)^2 + (5.2)^2}} = 0.578 \text{ A}; \quad P = |I|^2 \times 12 \cong 4 \text{ W}$$


17. If a capacitor with impedance Z_2 is connected in parallel to a load $Z_1 = 300 + j450 \Omega$. What should be Z_2 in ohms so that the equivalent load is purely resistive?

- a) $-928.6 j$
- b) $-1112.5 j$
-  c) $-650 j$
- d) $-750 j$
- e) None of the above

18. What is the power factor of the equivalent load of the previous question?

- a) 0.8
- b) 0.6
- c) 0
-  d) 1
- e) None of the above

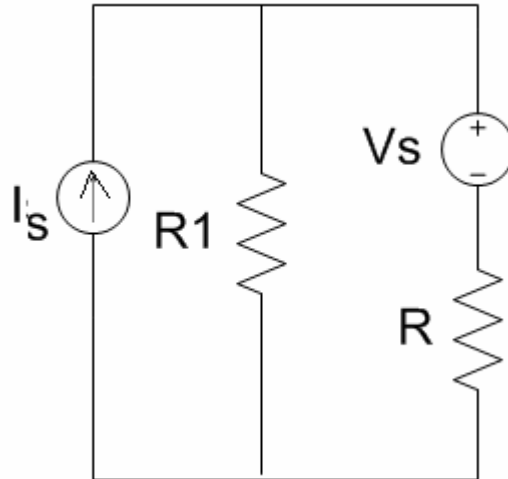23. Find the maximum power dissipated in R if: $I_s=2\text{mA}$, $R_1=100\text{k}\Omega$, $V_s=50\text{V}$.



- a) $P= 12.5 \text{ mW}$
- b) $P= 1.25 \text{ mW}$
- c) $P= 50 \text{ mW}$
- d) $P= 56.25 \text{ mW}$
- e) None of the above

-1- Two inductive loads of 0.88 KW and 1.32 KW at power factors of 0.8 and 0.6 respectively are connected in parallel across a 220-V (rms), 50Hz supply. Calculate the total current taken by this combination.

- a. 1A b. 14.86A c. 10.86A d. 15.45A e. None of the above


-2- For the previous problem, find the value of capacitance in microfarads, to be connected in parallel with the loads to bring the combined power factor to 0.9 lagging.

- a. 89 b. 35.8 c. 25.6 d. 44.5 e. None of the above

-6- Two impedances $Z=(2+j4) \Omega$ and $Z'=R \Omega$ are connected in parallel. Find R so that the power factor of the circuit is 0.9 lag.

- a. 1.3Ω b. 3.2Ω c. 2.4Ω d. 3Ω e. None of the above

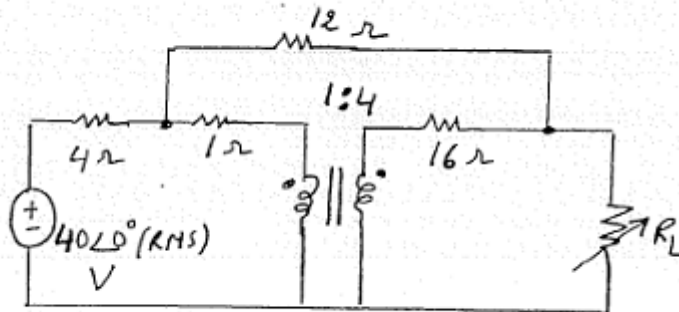
8. Find the maximum average power given that R_L is adjusted for maximum power transfer.



- A. 50 W
 B. 10 W
 C. 100 W
 → D. 25 W
 E. None of the above

8%

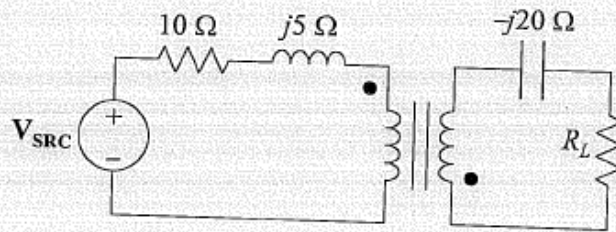4. R_L and the turns ratio of the ideal transformer can be varied over an arbitrary range. Determine R_L for maximum power transfer to it.




- A. 10 Ω B. 20 Ω C. 30 Ω **D. 40 Ω** E. None of the above

Solution: To have the reactances add to zero, the transformer turns ratio must be 2, primary-to-secondary. Hence $R_L = 4 \times 10 = 40 \Omega$.


18%

9. Given an ideal autotransformer having three windings of $N_1 = 200$ turns, $N_2 = 300$ turns, and $N_3 = 500$ turns. Determine R_{Th} .

100 ohms

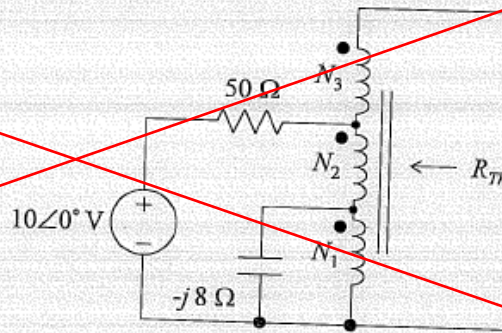

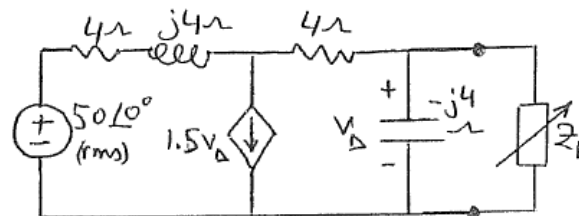- 3-** The load impedance Z_L for the circuit shown is adjusted until maximum average power is delivered to the load. Find this maximum power.




- a. 5W b. 25.34W c. 296.8W **d. 7.81W** e. None of the above

11. Determine the frequency at which maximum power is dissipated in the $10\ \Omega$ resistor, assuming $L = 1\ \text{H}$.


Solution: $\frac{1}{\omega C} = \frac{1}{\omega}\ \Omega$. Maximum power is

dissipated in the $10\ \Omega$ resistor when $X_L = -X_C$,

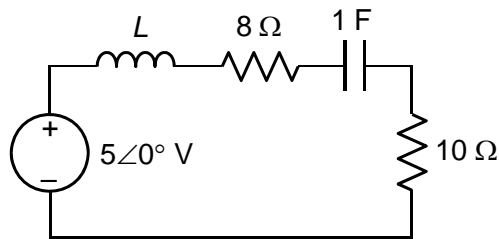which gives $\omega L = \frac{1}{\omega}$, or $\omega = \frac{1}{\sqrt{L}}$ rad/s.



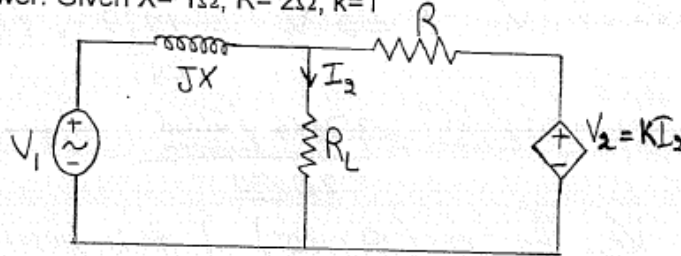
4. Consider the following circuit where V_2 is a current dependent source of voltage. R_L is a variable pure resistive load. Calculate the value of R_L that dissipates the maximum average power. Given $X = 1\Omega$, $R = 2\Omega$, $k=1$



- A. $\sqrt{5}\Omega$
- B. $1/\sqrt{5}\Omega$
- C. $2/\sqrt{5}\Omega$
- D. 2Ω
- E. None of the above


(70)

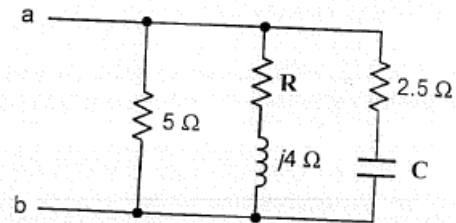7. Given that the complex power absorbed by the inductive branch is $12 + j16$ VA, find the smallest C that gives unity power factor at terminals ab , assuming $\omega = 1$ rad/s.




- A. 0.2 F
- B. 0.1 F
- C. 0.05 F
- D. 0.15 F
- E. None of the above

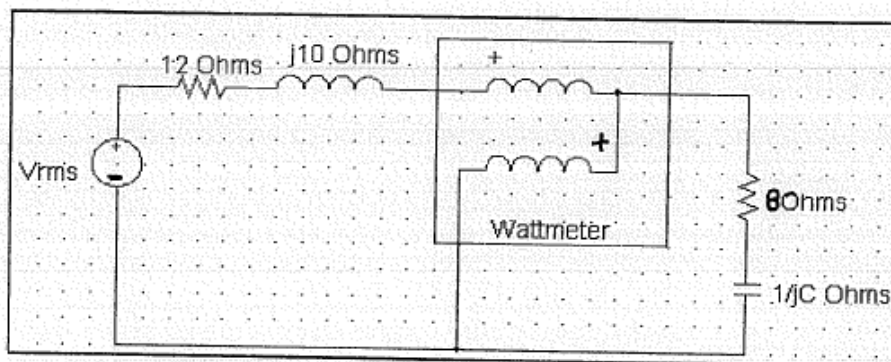18. Find the wattmeter reading of the circuit below. Where $C = 1/2$ F
 $V_{rms} = 150 \angle 0^\circ$ V



- (a) $P = 387.93$ W
- (b) $P = 412.84$ W
- (c) $P = 445.54$ W
- (d) $P = 279.4$ W
- (e) None of the above

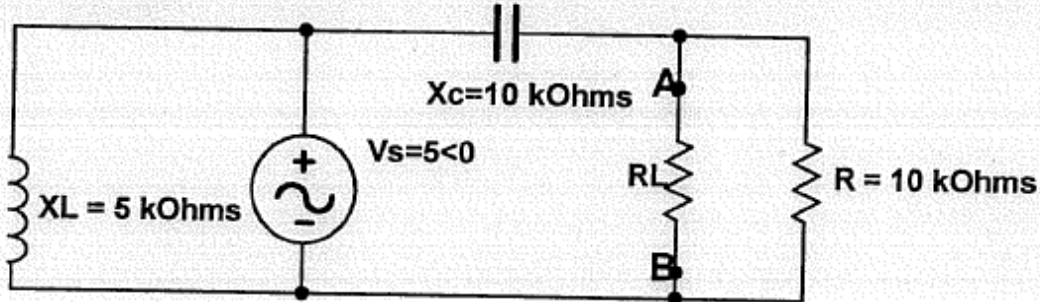
9. What should be the value of resistance R_L for maximum power to be transferred to it?



- a. $R_L = 5K\Omega$
- b. $R_L = 10K\Omega$
- c. $R_L = 7.62K\Omega$
- d. $R_L = 7.07K\Omega$
- e. None of the above

5. An electric motor draws an active power of 100 kW at 0.8 p.f lagging from a 240 V, 60 Hz source. This motor is connected in parallel to another load of $0.1 + j0.4 \Omega$. What is the size of the parallel connected capacitor needed to raise the total power factor to 0.95 lagging.

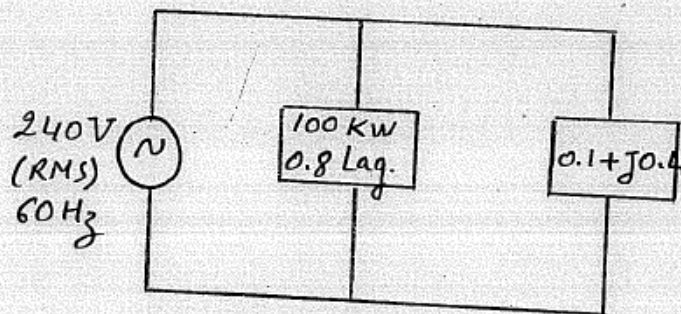- a. 6.27 mF
- b. 4.25 mF
- c. 7.68 mF
- d. 2.88 mF
- e. None of the above



2. A $1\ \Omega$ resistor is connected in parallel with a d'Arsonval movement having a full scale deflection of $1\ \text{mA}$. If a $40\ \text{mA}$ current produces a deflection that is 80% of full scale, determine the resistance of the d'Arsonval movement.

a) $58\ \Omega$

→ b) $49\ \Omega$

c) $37\ \Omega$

d) $76\ \Omega$

e) None of the above

8. A 300-V voltmeter that draws 2mA current for full-scale reading is used to measure the voltage across the 50-K Ω resistor of Figure 6. The voltmeter reading is:
- 60V
 - 120V
 - 40V
 - 90V
 - None of the above



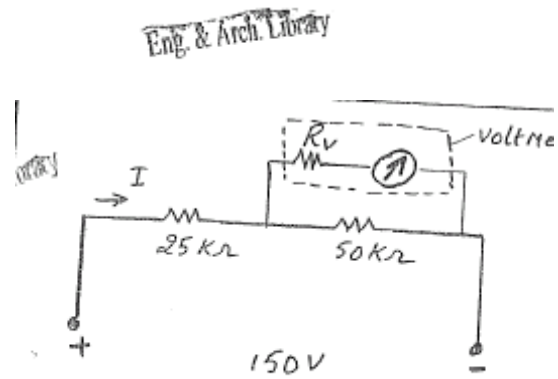


Fig. 6

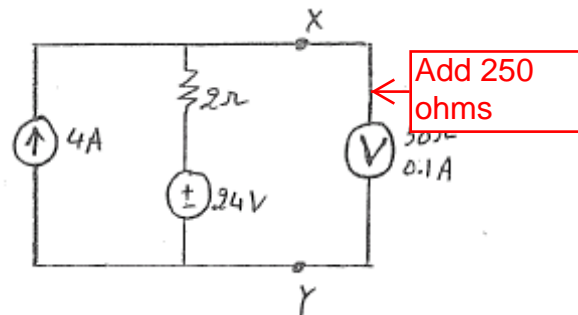15. A 50 Ω , 0.1A d'Arsonval meter movement is used in a voltmeter circuit (Figure 13). Determine the voltmeter reading across the terminals x-y on a full-scale of 30V.
- 26.49V
 - 32V
 - 31.79V
 - 36V
 - None of the above




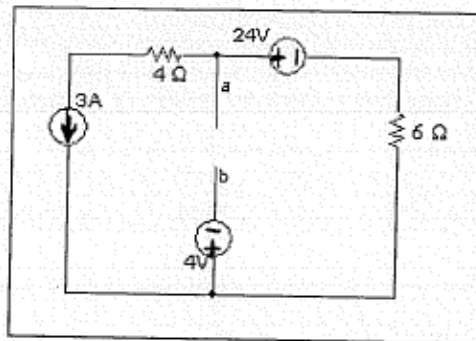10. A load resistance in the range of $[1,5] \Omega$ is to be connected across the terminals a,b in such a way that maximum power is delivered to it. Determine the power dissipated by R.



- a) 10.58 W
 → b) 4.13 W
 c) 5.95 W
 d) 8.26 W
 e) none of the above

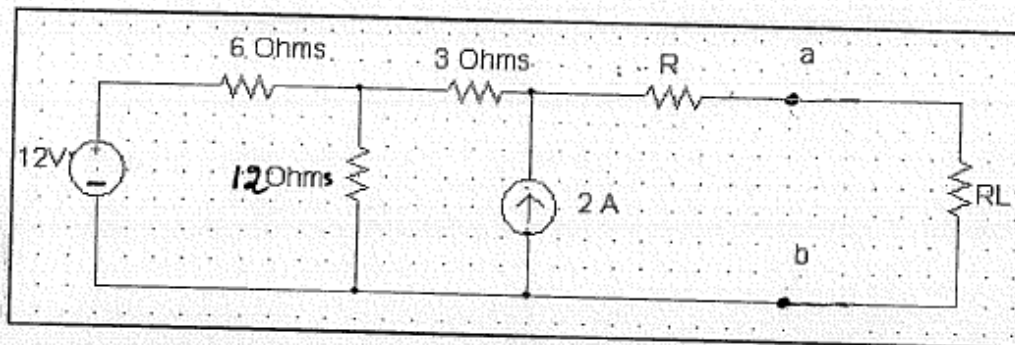13. Find the maximum power transfer in the circuit below, where $R = 2\Omega$




- a) 13.44 W
 (b) 10.08 W
 (c) 12.1 W
 (d) 8.34 W
 (e) None of the above

7%

4. For what value of R is maximum power transferred to R_L ?

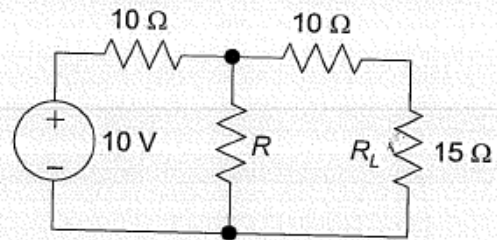
- A. $10\ \Omega$
B. $15\ \Omega$
C. $20\ \Omega$
→ D. Infinite resistance
E. None of the above



7%


5. A circuit N has an open-circuit voltage of 15 V between terminals ab, and an unknown source resistance R_S . A voltmeter across ab reads 12 V when $R_L = 10\ \text{k}\Omega$ and 10 V when $R_L = 40/9\ \text{k}\Omega$. Determine R_S and R_V , the resistance of the voltmeter.

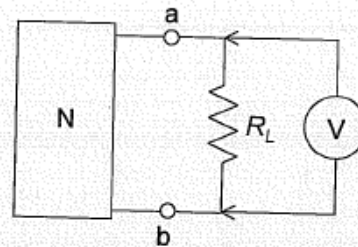- A. $R_S = 2\ \text{k}\Omega$, $R_V = 40\ \text{k}\Omega$
B. $R_S = 2\ \text{k}\Omega$, $R_V = 80\ \text{k}\Omega$
C. $R_S = 4\ \text{k}\Omega$, $R_V = 40\ \text{k}\Omega$
D. $R_S = 4\ \text{k}\Omega$, $R_V = 80\ \text{k}\Omega$
E. None of the above



17%

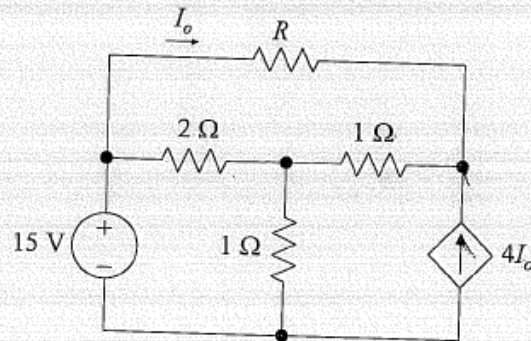7. Determine R for maximum power transfer to it and the value of this power.




Solution: When R is replaced by an open circuit, the current source is set to zero. The circuit becomes as shown. $V_{Th} = V_{ab} =$

$$15 \times \frac{20}{30} = 10 \text{ V.}$$

When a source V_T is applied, with the 15 V short circuited, and I_T as shown, the polarity of the current source is reversed. From KVL: $V_T = 5I_T$


$(1 + 2 \parallel 1)$. This gives $\frac{V_T}{I_T} = R = R_{Th} = \frac{25}{3} \Omega$. Max

power transferred is $\frac{100}{4 \times 25/3} = 3 \text{ W.}$

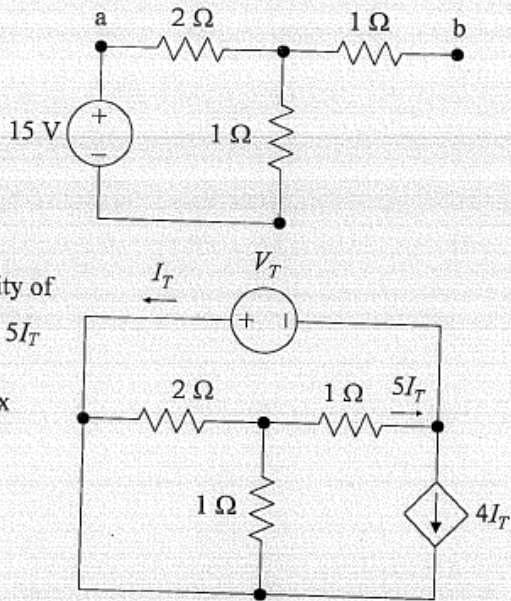

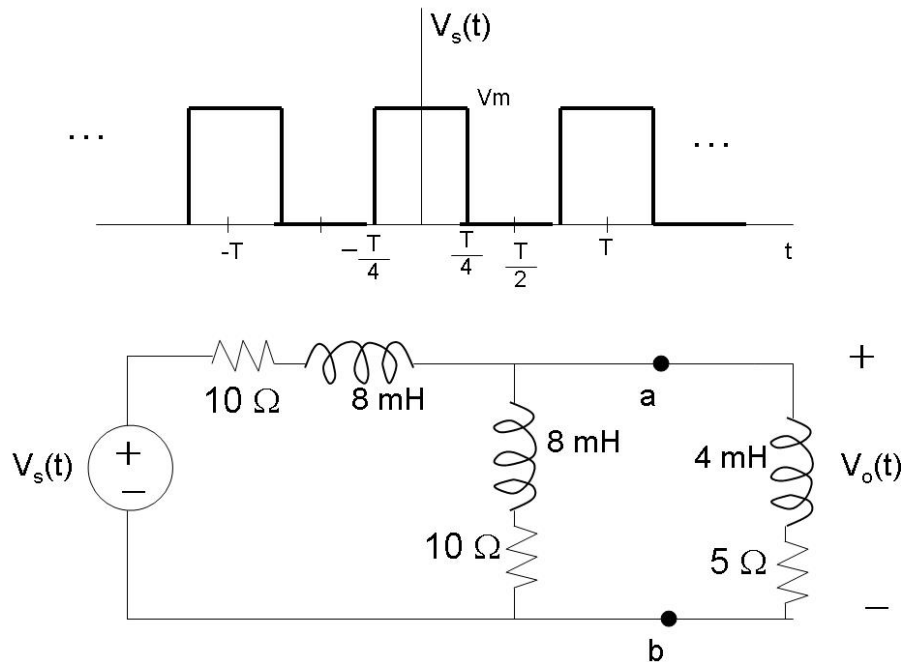Problem 3

Consider the periodic signal $V_s(t)$ shown below. Assume this signal is applied to the circuit in the figure below, find an expression for the voltage $V_o(t)$ across the terminals a,b as shown.



→ A) $V_o(t) = \frac{V_m}{8} + \frac{V_m}{2\pi} \sum_{n=1}^{\infty} \frac{\sin \frac{n\pi}{2}}{n} \cos n\omega_o t$

B) $V_o(t) = \frac{V_m}{8} + \frac{V_m}{4\pi} \sum_{n=1}^{\infty} \frac{\sin \frac{n\pi}{4}}{n} \cos n\omega_o t$

C) $V_o(t) = \frac{V_m}{4} + \frac{V_m}{2\pi} \sum_{n=1}^{\infty} \frac{\sin \frac{n\pi}{2}}{n} \cos n\omega_o t$

D) $V_o(t) = \frac{V_m}{4} + \frac{V_m}{2\pi} \sum_{n=1}^{\infty} \frac{\sin \frac{n\pi}{2}}{n} \cos n\omega_o t$

E) None of the above

-1- Consider the two signals :

$$F(t) = 2 + 3\cos(100\pi t) + 4\cos(200\pi t) + 6\cos(400\pi t)$$

$$G(t) = \frac{\cos(100\pi t) \cdot \sin(300\pi t) - \sin(100\pi t) \cdot \cos(300\pi t)}{\sin(200\pi t)}$$

Find the period of each of the signals, TF and TG. (p25)

a) $TF = 1/100$ $TG = 1/100$

b) $TF = 1/200$ $TG = 1/300$

c) $TF = 1/50$ $TG = 1/50$

d) $TF = 7/200$ $TG = 1/200$

→ e) None of the above

$TF = 1/50, G(t) = 1$

-2- The signal $F(t)$ given in (1) is an approximation of the real signal $f(t)$ with average power equal to 50Watt.

What is the %average power error in the approximation? (take $R = 1\Omega$) (p25)

- a) 31% b) 35% c) 65% d) 39% e) None of the above

-3- Consider the trigonometric Fourier series representation of $f(t)$ as given over the interval $(-2, 2)$: $f(t) = t + 1$ $-1 \leq t \leq 0$

$$-t + 1 \quad 0 \leq t \leq 1$$

$$0 \quad \text{elsewhere}$$

The Fourier series is also a representation of the periodic signal $F(t)$ obtained by repeating $f(t)$ periodically. The period of $F(t)$ is:

- a) 3 b) 2 c) 1 d) 4 e) None of the above

-4- Two periodic functions of period 6 seconds each are given by:

$$f(t) = -t \quad -3 < t \leq 0$$

$$g(t) = 1 \quad 0 < t < 3$$

$$t \quad 0 \leq t < 3$$


$$-1 \quad 3 < t < 6$$

Find the ratio of the amplitude of the 3rd harmonic present in $f(t)$ to that present in $g(t)$. (p25)

- a) $1/\pi$ b) $3/\pi$ c) $\pi/3\pi$ d) π e) None of the above


-5- Calculate the rms value of the current flowing in the circuit shown. (p26)

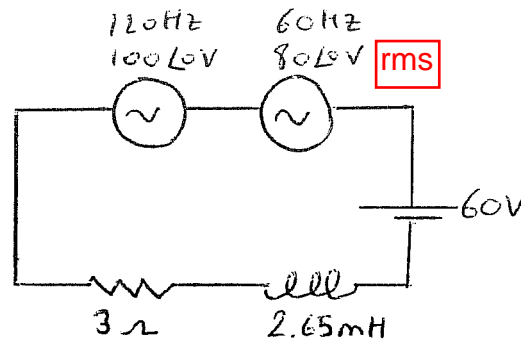- a) 8.5A b) 54.85A **c) 42.58A**
 d) 25A e) None of the above



-6- For the wave shown, calculate A_0 , A_5 and B_5 . (p26)

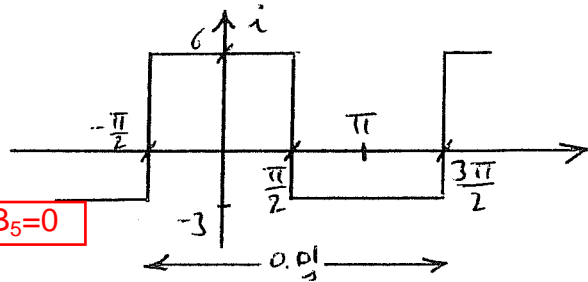- a) $A_0=1.5$, $A_5=1.5$ **b) $A_5=1.15$**
 c) $B_5=1.5$ d) $A_5=1.5$, $B_5=1.15$
 e) None of the above **$A_0=1.5$, $A_5=1.15$, $B_5=0$**





-7- Find the average power in a resistance $R=2\Omega$, if the voltage is $v = 32\sin(3t)\cos^2(t/2)$ (p26)

- a) 256W b) 512W c) 192W **d) 96W** e) None of the above

-8- In a circuit : $v(t) = 5\sin(t) + 10\sin(3t)$,
 $I(t) = 7\sin(2t) + 50\sin(8t)$
 What is the average power ? (p26)

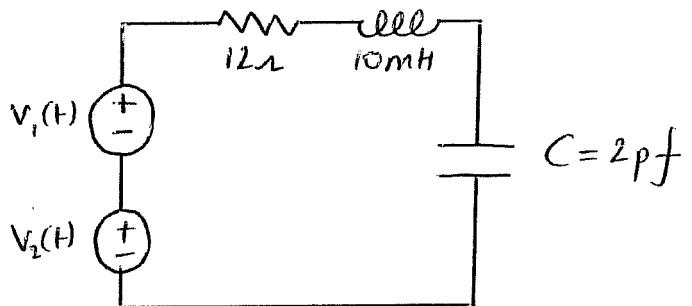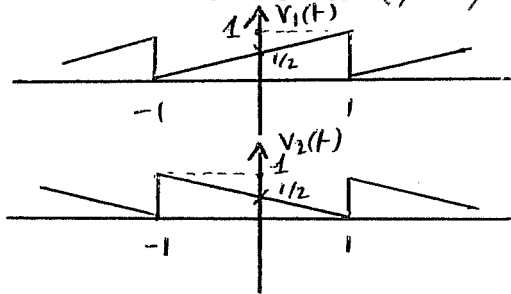- a) 267.5 W **b) 0 W** c) 250 W d) 35 W e) None of the above

-9- Two periodic voltages $V_1(t)$ and $V_2(t)$ of the same period ($T=2s$) are applied to the circuit. Find the current in this circuit due to the first harmonic. (p26)




- a) **12 Cos(pi t)** b) 12 Sin(pi t) c) 12Cos(pi t)+12Sin(pi t)
 d) 0 e) None of the above

-10- The function e^x ($0 < x < 1$) is to be represented by a cosine series, find a_2 . (p26)

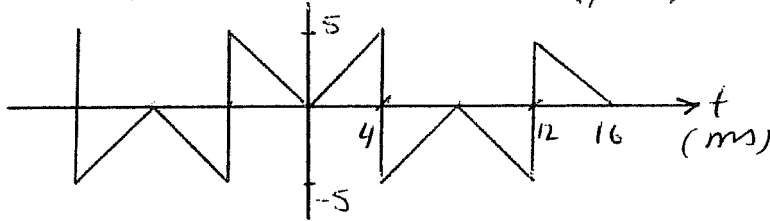- a) -0.684 b) -0.0827 **c) 0.0848** d) 0.0424 e) None of the above

- 11-** Consider the wave form $f(t)$. Find the amplitude and phase of the 3rd harmonic components of this waveform. (p27)



- a) $C_3 = 5.1$ $\theta_3 = \pm 90^\circ$ b) $C_3 = 2.57$ $\theta_3 = \pm 90^\circ$
 c) $C_3 = 4.8$ $\theta_3 = \pm 180^\circ$ d) $C_3 = 5.1$ $\theta_3 = \pm 180^\circ$ e) None of the above

- 12-** A rectifier system with input $f(t)$ and output $g(t)$ is described by: $g(t) = |f(t)|$. For an input of $f(t) = (\pi/4)\sin(\omega_0 t)$, the coefficient of the exponential Fourier series of $g(t)$ with n even is: (p27)

- a) $1/2(1-n^2)$ b) $1/(1-n^2)$ c) $2/(1-n^2)$ d) $1/(\pi-\pi n^2)$ e) None of the above

- 13-** Let the signal $f(t)$ be a signal defined between $-\pi$ and π . $F(t)$ is zero outside the following exponential Fourier series: (p27)

$$\sum_{n=-\infty}^{\infty} C_n \cdot e^{j \frac{nt}{2}}$$

The series represents the periodic extension of $f(t)$ with period T . Find T .

- a) 8π b) 2π c) 6π d) 4π e) None of the above

- 14-** Consider the following signal :

$$F(t) = 2\cos(100\pi t) + 3\cos(300\pi t) + 6\cos(500\pi t) + 9\sin(300\pi t)$$

Find the coefficients of the exponential Fourier series of $F(t)$. (p27)

- a) $C_1 = C_{-1} = 1$; $C_3 = 1.5 - 4.5j$ $C_{-3} = 1.5 + 4.5j$; $C_5 = C_{-5} = 3$
 b) $C_1 = C_{-1} = -1$; $C_3 = 4.5 - 1.5j$ $C_{-3} = 4.5 + 1.5j$; $C_5 = C_{-5} = -3$
 c) $C_1 = C_{-1} = 2$; $C_3 = 2.5 - 4.5j$ $C_{-3} = 2.5 + 4.5j$; $C_5 = C_{-5} = 3$;
 d) $C_1 = C_{-1} = 2$; $C_3 = 2.5 - 4.5j$ $C_{-3} = 2.5 + 4.5j$; $C_5 = C_{-5} = 3$;
 e) None of the above

1. Find the rms value of $v(t)$ in Fig. 1 over the time interval $(0, 5)$. (p70)

A. $v_{\text{rms}} = 0.54$

B. $v_{\text{rms}} = 0.98$

C. $v_{\text{rms}} = 0.86$

D. $v_{\text{rms}} = 0.68$

E. None of the above

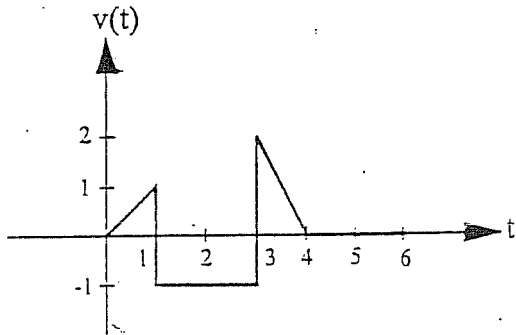


Figure 1.

10. Find the expression for the Fourier coefficients C_n for the periodic function shown in Fig. 9. ($p72$)

- A. $1/2\pi n, n \neq 0; \quad 1/2, n = 0$
- B. $j/\pi n, n \neq 0; \quad 0, n = 0$
- C. $j/2\pi n, n \neq 0; \quad 1/2, n = 0$
- D. $j/3\pi n, n \neq 0; \quad 1, n = 0$
- E. None of the above

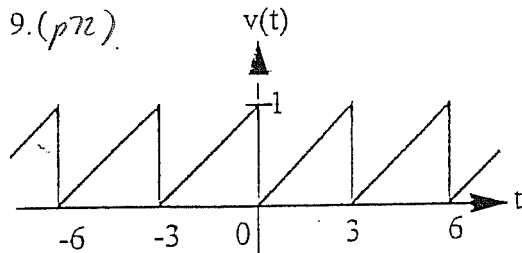


Figure 9.

11. A periodic function is represented by:

$$v(t) = \sum_{n=-\infty}^{+\infty} V_n e^{j200\pi nt}$$

Fig. 10 shows the plot of the magnitude of the coefficients V_n . Find the average and the fundamental frequency of $v(t)$. ($p72$)

- A. 2; 1 Hz
- B. 5; 10 Hz
- C. 0; 10 Hz
- D. 5; 100 Hz
- E. None of the above

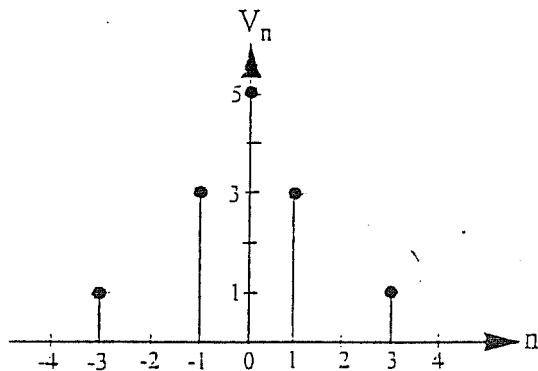


Figure 10.

14. Calculate the power dissipated in the resistor in Fig. 12 if $v_1(t) = 10\cos t$ and $v_2(t) = 10\cos 3t$. (p 73)

- A. 12.7 W
B. 50.7 W
C. 60.8 W
D. 70.5 W
E. None of the above

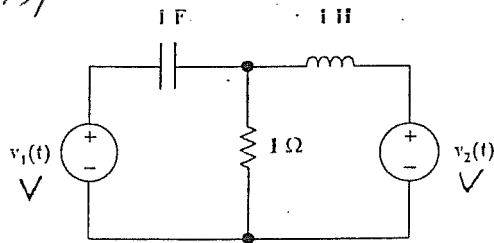


Figure 12

4. A series RL circuit in which $R = 5\Omega$ and $L = 20 \text{ mH}$ has an applied voltage $v = 100 + 50\sin \omega t + 25\sin 3\omega t \text{ V}$, with $\omega = 500 \text{ rads/s}$. Find the instantaneous current. (p104)


- a. $i = 20 + 4.47\sin(\omega t + 63.4) + 0.822 \sin(3\omega t + 80.54)$, A
- ✓ b. $i = 20 + 4.47\sin(\omega t - 63.4) + 0.822 \sin(3\omega t - 80.54)$, A
- c. $i = 8.96 + 4.47\sin(\omega t - 63.4) + 0.822 \sin(3\omega t - 80.54)$, A
- d. $i = \sin(\omega t - 63.4) + 0.822 \sin(3\omega t - 80.54)$, A
- e. None of the above

5. Determine the power dissipated in the resistor of problem 4. p(104)

- a. $\sim 50.1 \text{ W}$
- b. $\sim 51.79 \text{ W}$
- c. $\sim 2000 \text{ W}$
- ✓ d. $\sim 2053 \text{ W}$
- e. None of the above


11. The figure below shows the triangular waveform of a voltage source operating at frequency $f = 1\text{kHz}$. Find the amplitudes of the fundamental (I_1) and the second order harmonic (I_2) current that flows through an inductor of value $L = 1\text{mH}$ when it is supplied by this source.. (Answers are rounded to 2 digits after the decimal point) (p106)

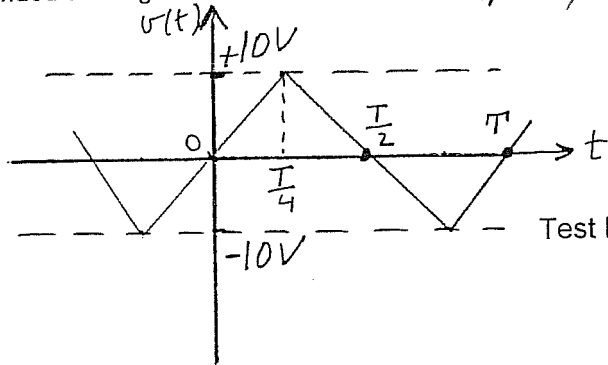- a) $I_1 = 2.31\text{ A}, I_2 = 1.10\text{ A}$
- b) $I_1 = 1.34\text{ A}, I_2 = 0\text{ A}$
- c) $I_1 = 0\text{ A}, I_2 = 1.10\text{ A}$
- d) $I_1 = 1.29\text{ A}, I_2 = 0\text{ A}$
- e) None of the above



Test ID 1000 4/7

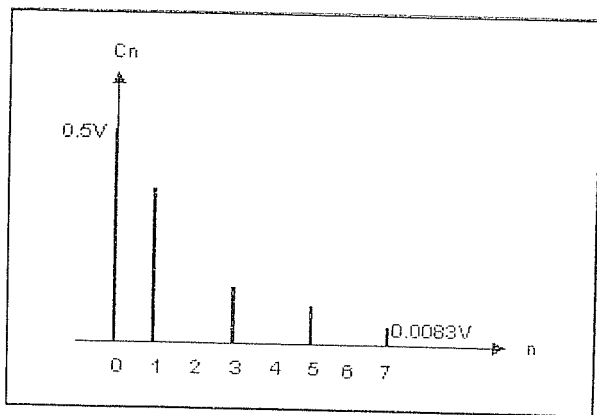8. The following spectrum is the frequency representation of which Fourier function: (p124)



- a. $f(t) = \frac{4V}{\pi} \sin \omega t + \frac{4V}{3\pi} \sin 3\omega t + \frac{4V}{5\pi} \sin 5\omega t + \dots$
- b. $f(t) = \frac{V}{2} + \frac{4V}{\pi} \sin \omega t + \frac{4V}{3\pi} \sin 3\omega t + \frac{4V}{5\pi} \sin 5\omega t + \dots$
- c. $f(t) = \frac{V}{2} + \frac{4V}{\pi^2} \cos \omega t + \frac{4V}{(3\pi)^2} \cos 3\omega t + \frac{4V}{(5\pi)^2} \cos 5\omega t + \dots$
- d. $f(t) = \frac{V}{8} + \frac{4V}{\pi^2} \sin \omega t + \frac{4V}{(3\pi)^2} \sin 3\omega t + \frac{4V}{(5\pi)^2} \sin 5\omega t + \dots$
- e. None of the above

4. A complex waveform of RMS value of 240 V has 20% 3-rd harmonic content, 5% 5-th harmonic content and 2% 7-th harmonic content. Find the RMS value of the 3-rd and 7-th harmonics respectively. (p139)

A. 11.5V, 4.6V

B. 7.6V, 1.3V

→ C. 47 V, 4.7V

D. 30V, 3.2V

E. None of the above

11. A voltage $v(t)$ is applied to a 5Ω resistor. $v(t)$ can be written as:

$$v(t) = 1 - \sum_{n=1}^{\infty} (1/n^2) \cos(500nt)$$

Estimate the Power dissipated in the resistor using the first four non-zero terms of $v(t)$. (p 141)

a. 2.36 W



~~b. 0.31W~~

c. 1.25W

d. 0.95W

e. None of the above

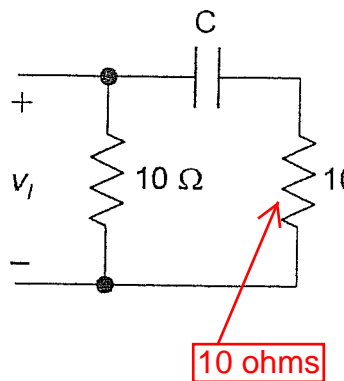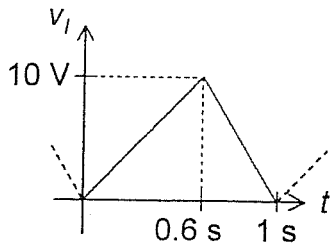18. The periodic voltage v_i is applied to the circuit shown, the reactance of C at the frequency of the fundamental being much smaller than $10\ \Omega$. Determine the power dissipated in the circuit. (p 144)



- A. $13.33\ \text{W}$
- B. $8.33\ \text{W}$
- C. $6.67\ \text{W}$
- D. $4.17\ \text{W}$
- E. None of the above

20. The current through a $1\ \mu\text{F}$ capacitor is $2\cos^2 100\pi t$ mA, where t is in s. Determine the period of the voltage across the capacitor.

A. 25 ms


B. 50 ms

C. 100 ms

D. 200 ms


~~E.~~ E. None of the above

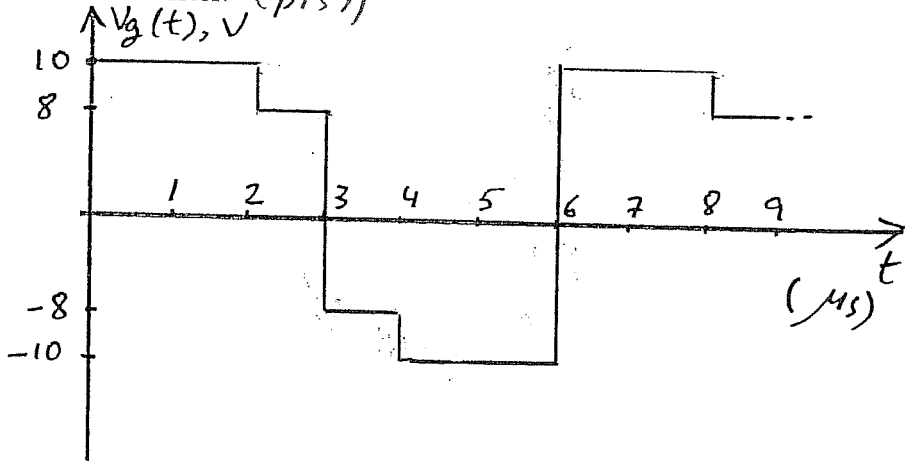4. The periodic voltage waveform shown below is applied across a $10\ \Omega$ resistor. Determine the average power dissipated in the resistor. (p157)



- a. 8.8 W
- b. 88W
- c. 77.4W
- d. 4.4W
- e. None of the above

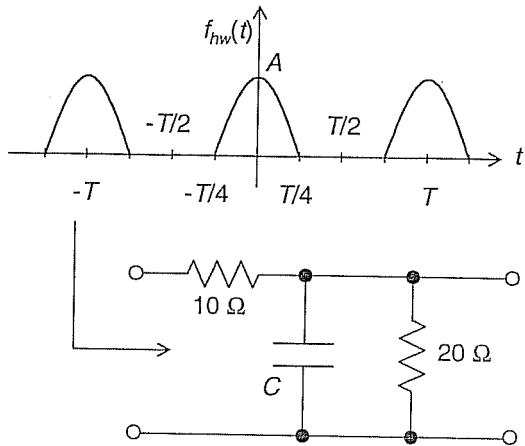9. A half-wave rectified waveform $f_{hw}(t)$ of frequency 50 Hz and having $A = 10$ V is applied to the circuit shown, where the reactance of C is negligible at 50 Hz. Determine the total power dissipated in the circuit. (P158)



- A. 0.83 W
- B. 1.49 W
- C. 1.82 W
- D. 2.5 W
- E. None of the above

8%

4. A voltage having the waveform of the figure of Problem 9 below, with $A = 8 \text{ V}$ and $T = 1 \text{ s}$ is applied to a coil having a resistance of 4Ω and an extremely large inductance. Determine the average power dissipated in the coil. *(p170)*

A. 1.56 W

B. 1 W

C. 3.28 W

D. 4 W

E. None of the above

Problem 9

Derive the trigonometric form of the FSE of the waveform shown


Solution: The function is even, and $a_0 = C_0 =$

$$\frac{1}{T} \times A \times \frac{T}{4} = \frac{A}{4}; \quad a_n = \frac{4A}{T} \int_0^{T/4} \left(-\frac{4}{T}t + 1 \right) \cos n\omega_0 t dt$$

$$= \frac{4A}{T} \left[-\frac{4}{T} \frac{1}{n^2 \omega_0^2} \cos n\omega_0 t - \frac{4}{T} \frac{t}{n\omega_0} \sin n\omega_0 t - \frac{1}{n\omega_0} \sin n\omega_0 t \right]_0^{T/4}$$

$$= \frac{16A}{T^2 n^2 \omega_0^2} \left[1 - \cos \frac{n\pi}{2} \right] = \frac{4A}{\pi^2 n^2} \left(1 - \cos \frac{n\pi}{2} \right). \text{ Hence,}$$
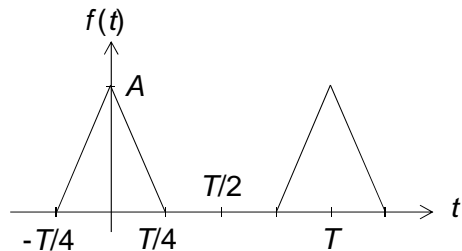
$$f(t) = \frac{A}{4} + \frac{4A}{\pi^2} \left(\cos \omega_0 t + \frac{1}{2} \cos 2\omega_0 t + \frac{1}{9} \cos 3\omega_0 t + \frac{1}{25} \cos 5\omega_0 t + \dots \right).$$



6. Consider a periodic function $f(t)$, described by the following sequence during one period of time:

$$f(t) = 0 \quad \text{for} \quad -4 \leq t < -3$$

$$f(t) = -V_m \quad \text{for} \quad -3 \leq t < -1$$

$$f(t) = 0 \quad \text{for} \quad -1 \leq t < +1$$

$$f(t) = +V_m \quad \text{for} \quad +1 \leq t < +3$$

$$f(t) = 0 \quad \text{for} \quad +3 \leq t \leq +4$$

where $V_m = 20$. Find the amplitude "A" of the third order harmonic in the Fourier series, expressed by $A \cos(3\omega t - \Theta)$. (p176)

A. $A=3$

B. $A=4$

C. $A=5$

D. $A=6$


E. None of the above

Solution: The function is as shown. It is odd and quarter-wave symmetric. Hence, $a_0 = 0$

$$\text{and } b_3 = \frac{8}{T} \int_1^2 V_m \sin 3\omega_0 t dt,$$

$$\text{where } T = 8 \text{ and } \omega_0 = \frac{2\pi}{8}$$
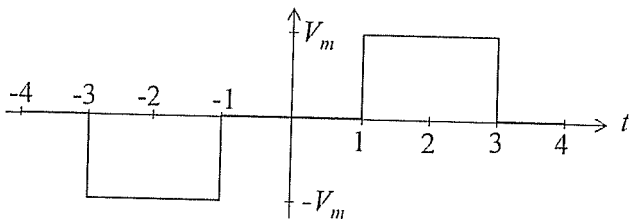
$$\frac{\pi}{4}. \text{ Hence, } b_3 = \frac{8V_m}{3\omega_0 T} [-\cos 3\omega_0 t]_1^2 = \frac{160}{6\pi} \left[-\cos \frac{3\pi}{4} + \cos \frac{\pi}{2} \right] = \frac{80}{3\pi\sqrt{2}} = 6.0$$



11. A voltage $5\sin\omega_0 t$ V applied to a given resistor dissipates 5 W. What is the power dissipated by a voltage $5|\sin\omega_0 t|$ V applied to the same resistor? (P179)

A. 5 W

B. $5\sqrt{2}$ W

C. $5/\sqrt{2}$ W

D. 10 W

E. None on the above

Solution: The two waveforms have the same rms value and would therefore dissipate the same power in a given resistor.

75.6 W

A. 8.2 W

B. 7.56 W


C. 37.8 W

D. None of the above


Solution: Mean square is

$$\frac{64 \times 2 + 100 \times 3 + 64 \times 3 + 100 \times 2}{10} = 82.$$

$$P = \frac{82}{10} = 8.2 \text{ W}$$

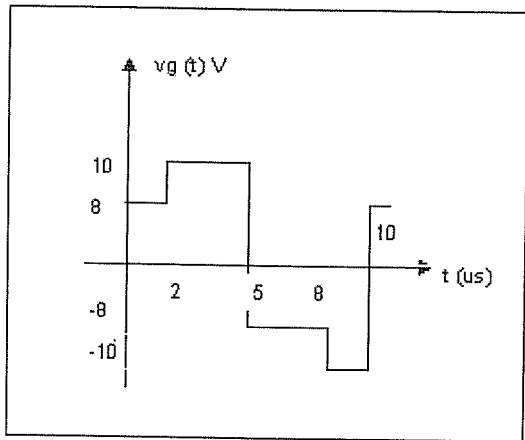

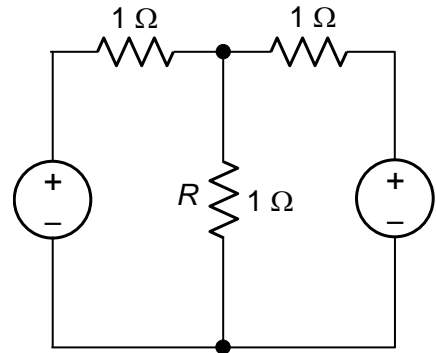1. In the circuit shown, each source is $15\cos 10t$ V. The power dissipated in R is 50 W. If the frequency of one of the sources is doubled, the power dissipated in R is:
- A. 100 W
 - B. 50W
 - C. 25 W
 - D. 12.5 W
 - E. None of the above.




Solution: The current due to each source is $\frac{1}{2} \left(\frac{15}{1.5} \right) \cos 10t = 5 \cos 10t$ A. The power is

$$\left(\frac{5}{\sqrt{2}} \right)^2 = 12.5 \text{ W. the power dissipated due to both}$$

sources is 25 W.

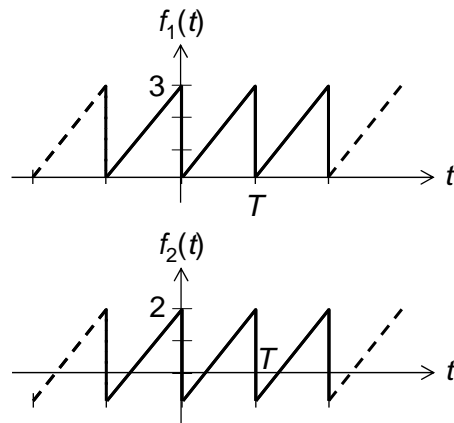2. $f_2(t)$ is the function $f_1(t)$ lowered by 1 unit, as shown. If $F_{1\text{rms}}$ and $F_{2\text{rms}}$ are the rms values of $f_1(t)$ and $f_2(t)$, respectively, then:




- A. $F_{1\text{rms}} = F_{2\text{rms}}$
- B. $F_{1\text{rms}} > F_{2\text{rms}}$
- C. $F_{1\text{rms}} < F_{2\text{rms}}$

Solution: The AC components of $f_1(t)$ and $f_2(t)$ are the same. The DC component of $f_1(t)$ is larger than that of $f_2(t)$. Hence, $F_{1\text{rms}} > F_{2\text{rms}}$.

5. The Fourier coefficients a_k and b_k for the periodic function shown are:

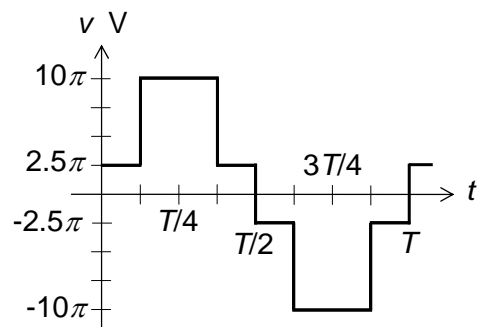- A. $a_k = 0$ for all k ; $b_k = 0$ for k odd and is non-zero for k even
- B. $b_k = 0$ for all k ; $a_k = 0$ for k even and is non-zero for k odd
- C. $b_k = 0$ for all k ; $a_k = 0$ for $k = 0$, $a_k = 0$ for k odd and is non-zero for k even




- D. $a_k = 0$ for all k ; $b_k = 0$ for k even and is non-zero for k odd
- E. None of the above.

Solution: The function is odd, half-wave symmetric. Its average is zero; it contains no cosine terms, only odd sine terms.

11. The current through an inductor of 1 H is given by the periodic triangular wave. The amplitude of the fundamental component of the voltage across the inductor is:

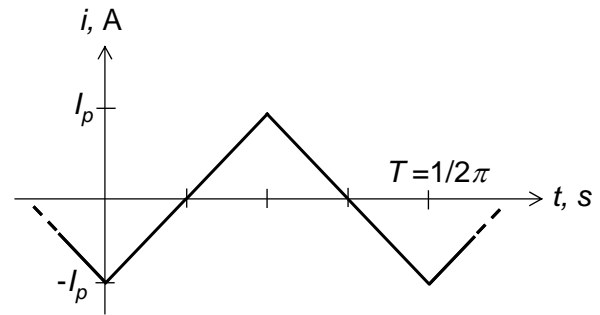- A. $4I_p$
- B. $8I_p$
- C. $16I_p$
- D. $32I_p$
- E. None of the above.




Solution: $v = L \frac{di}{dt} = 1 \times \frac{2I_p}{1/4\pi} = 8\pi I_p$, which is the amplitude of the square waveform

representing v . the amplitude of the fundamental is $\frac{4 \times 8\pi I_p}{\pi} = 32I_p$.

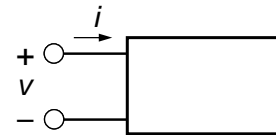15. The voltage and current at the terminals of a circuit are:

$$v = 15 + 400 \cos 500 t + 100 \sin 1500 t \text{ V}$$

$$i = 2 + 5 \sin(500t + 60^\circ) + 3 \cos(1500t - 15^\circ) \text{ A}$$



3% a) Calculate the average power delivered to the circuit.

$$P = V_{dc} I_{dc} + \sum_{n=1}^3 \frac{V_m I_m}{2} \cos(\theta_{v_n} - \theta_{i_n}) = 15 \times 2 + \frac{1}{2} \times 400 \times 5 \cos(30^\circ) + \frac{1}{2} \times 100 \times 3 \times \cos(-75^\circ)$$

$$= 934.85 \text{ W}$$

3% b) Calculate the rms value of v .


$$V_{rms} = \sqrt{(15)^2 + \frac{(400)^2}{2} + \frac{(100)^2}{2}} = 291.93 \text{ V}$$

2% c) Calculate the rms value of i .

$$I_{rms} = \sqrt{(2)^2 + \frac{(5)^2}{2} + \frac{(3)^2}{2}} = 4.58 \text{ A}$$

12. For $n = 1, 2, 3, \dots$, the function shown has:

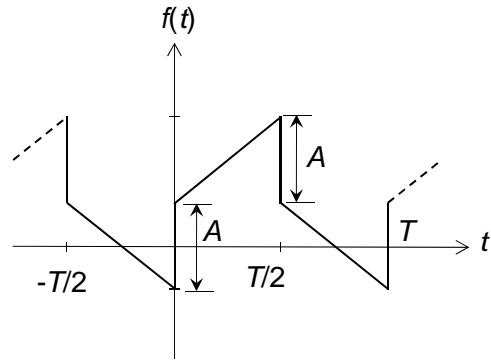- A. a_n and b_n nonzero for all n
- B. a_n and b_n are zero for even n
- C. a_n and b_n are zero for odd n
- D. $a_n = 0$ for all n
- E. $b_n = 0$ for all n



Solution: When the dc value is removed, the ac

component has half-wave symmetry but is neither even nor odd. Hence, a_n and b_n are zero for even n .


13. Determine the total power dissipated if v_l is a full-wave rectified waveform given by: $v_l = 6|\sin(500t)|$ V.

Solution: $\frac{1}{\omega C} = \frac{1}{500 \times 100} = 2 \times 10^{-5} \ll 5 \text{ ohms}; V_{dc} = \frac{2V_m}{\pi};$

$$P_{dc} = \frac{4V_m^2}{10\pi^2} = 0.04053V_m^2;$$

$$\frac{V_m^2}{2} = \frac{4V_m^2}{\pi^2} + V_{ac}^2; V_{ac}^2 = V_m^2 \left(\frac{1}{2} - \frac{4}{\pi^2} \right) = 0.09472V_m^2; P_{ac} = \frac{0.09472V_m^2}{5} = 0.01894V_m^2;$$

$$P = 0.05947V_m^2.$$

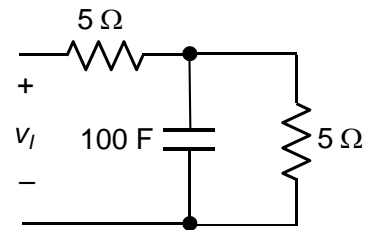


14. A period of a periodic function $f(t)$ is given by: $K(4 + 2\sin t)$, $0 < t < 2\pi$. Determine the rms value of $f(t)$, if $K = 0.5$.

Solution: The square of $f(t)$ is $K^2(16 + 16\sin t + 4\sin^2 t) =$


$K^2(16 + 2 + 16\sin t - 2\cos 2t)$. The area under the square is

$$\int_0^{2\pi} K^2(16 + 2 + 16\sin t - 2\cos 2t) dt = 36\pi K^2; \text{ the mean square is } \frac{36\pi K^2}{2\pi} = 18K^2 \text{ and the rms}$$

value is $3\sqrt{2}K$.

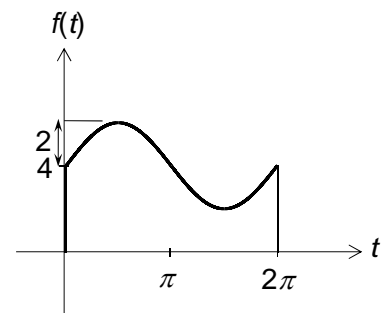

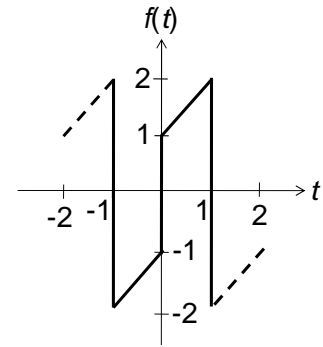16. Derive the trigonometric Fourier expansion of the given periodic function $f(t)$.



Solution: Since $f(t)$ is odd, $a_0 = 0 = a_n$; $T = 2$, $\omega_0 = 2\pi/T = \pi$, $f(t) = t + 1$;


$$b_n = \frac{4}{T} \int_0^{T/2} f(t) \sin(n\omega_0 t) dt = 2 \operatorname{Im} \left[\int_0^{T/2} f(t) e^{jn\omega_0 t} dt \right] = 2 \operatorname{Im} \left[\frac{te^{jn\omega_0 t}}{jn\omega_0} - \frac{e^{jn\omega_0 t}}{(jn\omega_0)^2} + \frac{e^{jn\omega_0 t}}{jn\omega_0} \right]_0^1 =$$

$$2 \operatorname{Im} \left[\frac{e^{jn\pi}}{jn\pi} + \frac{e^{jn\pi}}{(n\pi)^2} + \frac{e^{jn\pi}}{jn\pi} - 0 + \frac{1}{n^2\pi^2} - \frac{1}{jn\pi} \right] = 2 \left[-\frac{2 \cos n\pi}{n\pi} + \frac{1}{n\pi} \right] = \frac{2}{\pi} \left[\frac{1}{n} (1 - 2 \cos n\pi) \right] =$$

$$\frac{2}{\pi} \left[\frac{1}{n} (1 + 2(-1)^{n+1}) \right] \quad f(t) = \frac{2}{\pi} \left[3 \sin \pi t - \frac{\sin 2\pi t}{2} + \sin 3\pi t - \frac{\sin 4\pi t}{4} + \dots \right].$$

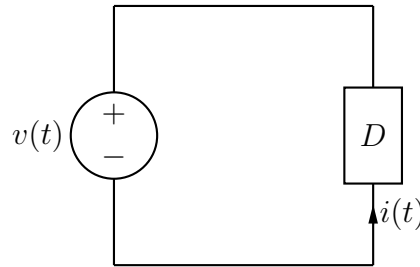Problem 18


The device D in the following circuit is powered by a voltage $v(t) = 2 + 2 \cos(1000t) + \cos(2000t)$ (V). The current across is given by $i(t) = 1 + \sin(1000t) + 0.5 \sin(2000t)$ (A) find the average power associated with D.



- A) 2W
- B) -2W
- C) 4W
- D) -4W
- E) None of the above

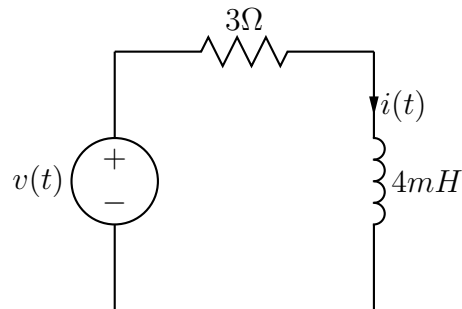Problem 19

The following circuit is powered by a periodic voltage source that has the following Fourier expansion: $v(t) = 21 + 20 \cos(1000t) + 10 \cos(2000t)$. Find the RMS value of the current $i(t)$.




- A) 6.68A
- B) 8.14A
- C) 7.3A
- D) 7.6A
- E) None of the above

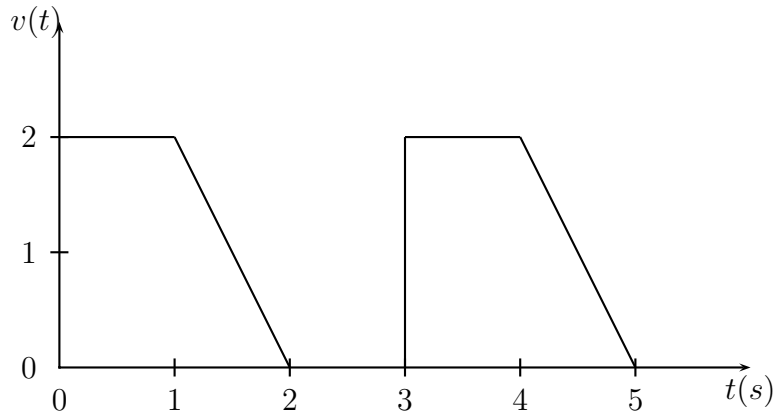Problem 20


For the function $v(t)$ given below, find the value of a_5 . You may use the following:

$$\int t \cos(\alpha t) = \frac{\cos(\alpha t)}{\alpha^2} + \frac{t \sin(\alpha t)}{\alpha}$$



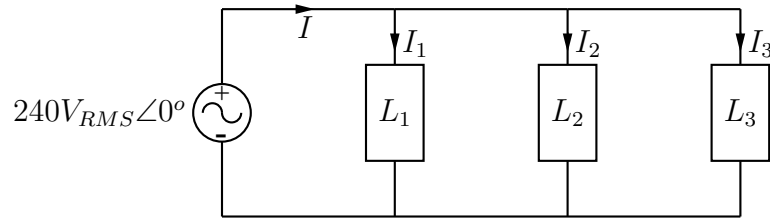- A) 0
B) -0.0162
C) 1.27
D) -16.7
E) None of the above

The following given is used in the next 5 problems. 3 electrical elements are powered by a $240V_{RMS}$, 60Hz source:



The following is given for the three elements:

L1: 240W, PF=0.6 Lag

L2: 200VARs, PF=0.5 Lag

L3: 100VA, PF=0 Lead

Problem 11

Find the total apparent power.

- A) 725.67VA
- B) 626.33VA
- C) 550.2VA
- D) 888.8VA
- E) None of the above

Problem 12

Find the total power factor.

- A) 0.567 Lag
- B) 0.646 Lag
- C) 0.808 Lag
- D) 0.747 Lag
- E) None of the above

Problem 13

Find the magnitude of the total current I.

- A) 5.21A
- B) 3.02A
- C) 2.292A
- D) 7.40A
- E) None of the above

Problem 14

Find the capacitor that needs to be placed in parallel with the loads to adjust the power factor to 0.9 Lag.

- A) $62.7\mu\text{F}$
- B) $147\mu\text{F}$
- C) $49\mu\text{F}$
- D) $11.4\mu\text{F}$
- E) None of the above $C=2.74\text{ mF}$


Problem 15

Find the magnitude of I again after the power factor is adjusted as in the previous problem.

- A) 1.64A
- B) 3.29A
- C) 0.91A
- D) 2.13A
- E) None of the above

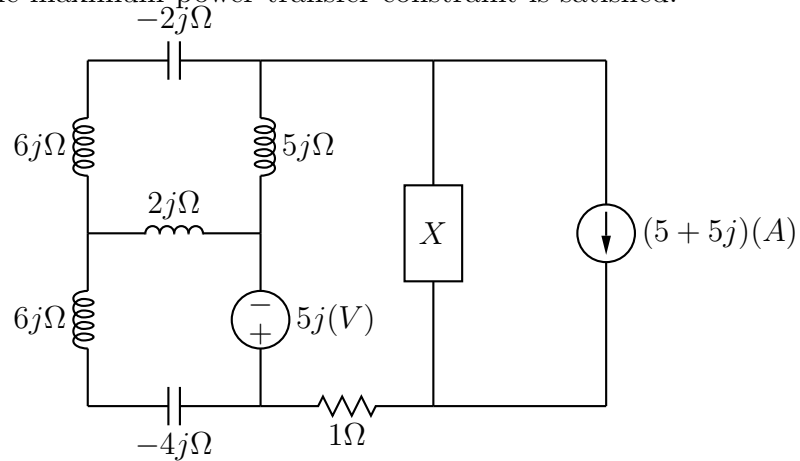Problem 10


Find X such that the maximum power transfer constraint is satisfied.



- A) $1 - 2.5j\Omega$
- B) $1 + 2.5j\Omega$
- C) $2 - 2.5j\Omega$
- D) $2 + 2.5j\Omega$
- E) None of the above

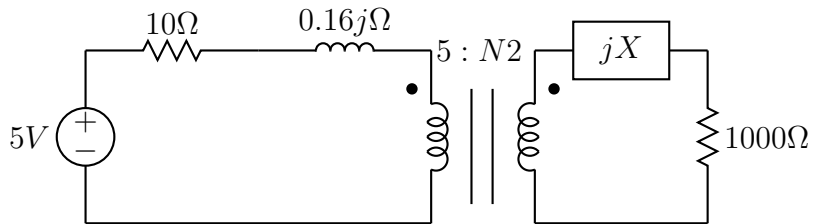Problem 8


Find N_2 and X such that maximum power is delivered to the 1000Ω resistor.



- A) $N_2 = 50, X = -16$
B) $N_2 = 10, X = -16$
C) $N_2 = 10, X = -0.64$
D) $N_2 = 2, X = -0.64$
E) None of the above

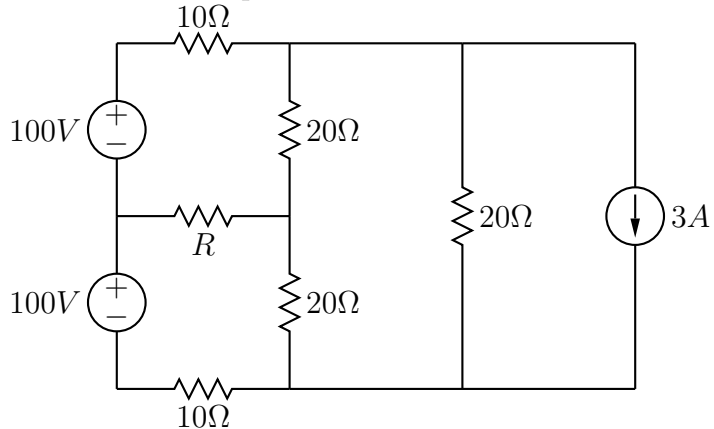Problem 3

Find R that satisfies the maximum power transfer constraint.




- A) 14Ω
- B) 15Ω
- C) 16.33Ω
- D) 17.46Ω
- E) None of the above

Problem 2


Find the average power **delivered** with the 6A current source between A and B.

assume rms values

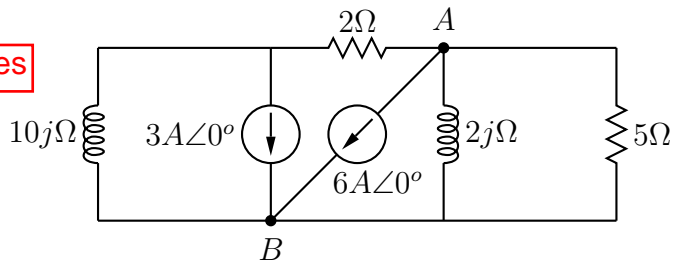


- A) -23.86W
- B) 23.86W
- C) 28.71W
- D) -28.71W
- E) None of the above

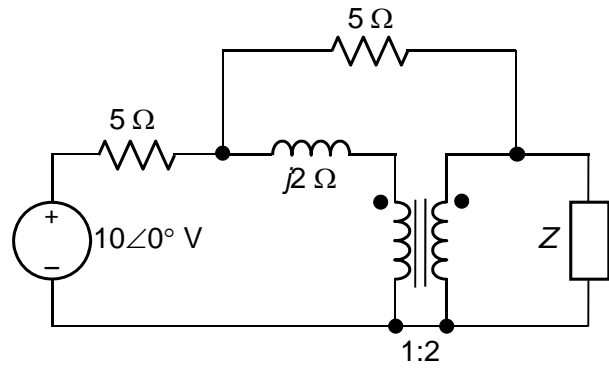18. Determine Z so that maximum power is transferred to it and calculate this power given that the source voltage is 10 V peak value.




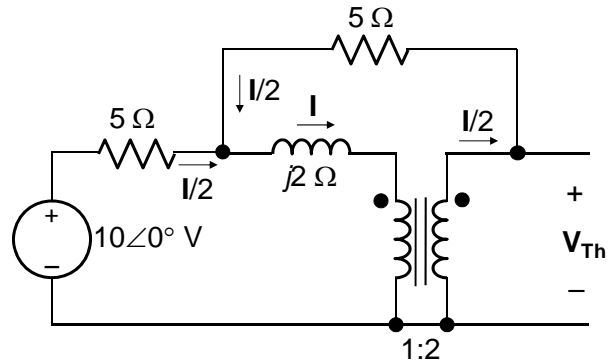Solution: We will determine TEC as seen by Z . On open circuit, the currents are as shown. From KVL: $10\angle 0^\circ - 5I/2 + 5I/2 = \mathbf{V_{Th}}$. In This particular problem, the voltages across the 5 Ω resistors cancel out. Hence, $\mathbf{V_{Th}} = 10\angle 0^\circ$ V peak value



When Z is replaced by a short circuit, the currents are as shown. From

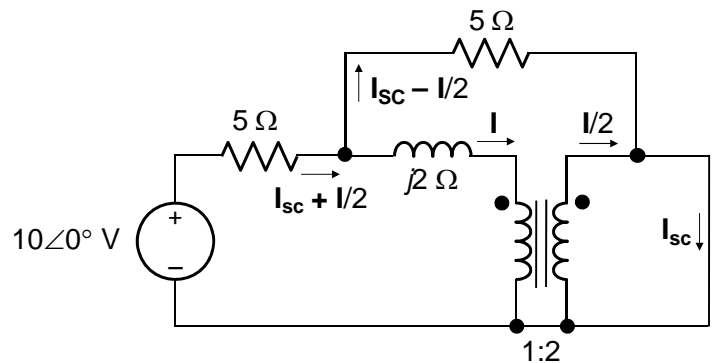KVL: $10\angle 0^\circ - 5(I_{sc} + I/2) - 5(I_{sc} - I/2) = \mathbf{0}$. Again, the terms involving I cancel out. Hence, $\mathbf{I_{sc}} = 1\angle 0^\circ$ A, and $\mathbf{Z_{Th}} =$




$\frac{10\angle 0^\circ}{1\angle 0^\circ} = 10 \Omega$. It follows that for maximum power transfer, $\mathbf{Z} = 10 \Omega$. The power dissipated in the

load is $\left(\frac{V_{Th}}{\sqrt{2}}\right)^2 \frac{1}{4 \times 10} = 1.25$ W.

~~$\frac{20}{R} R_x = 10$, or $R_x = \frac{R}{2}$.~~

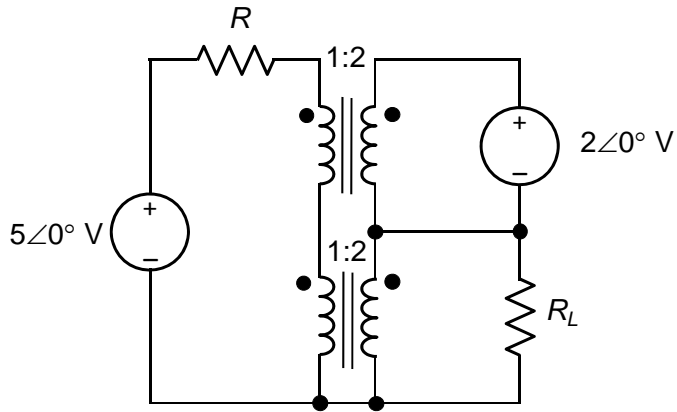7. Determine the maximum power that can be delivered to R_L , assuming $R = 0.5 \Omega$.

Solution: The primary voltage of the upper transformer is always 1 V. On



open circuit, the source current is zero, the primary voltage is $5 - 1 = 4$ V, and $V_{Th} = 8$ V. On short circuit, the primary voltage of the lower transformer is zero, the source current is $(5 - 1)/R$ and the short circuit current is $2/R$. This gives, $R_{Th} = 4R$. The maximum power delivered is $(8)^2/(4 \times 4R) = 4/R$.


8. Given that the load L consumes 1200 W at 0.8 p.f. lagging and the magnitude of the voltage across L is 300 V rms. Determine the power dissipated in the resistance R_{line} , if $R_{line} = 0.5 \Omega$.

Solution: The reactive power absorbed by the load

is $\frac{1200}{0.8} \times 0.6 = 900$ VAR. The reactive power absorbed by the capacitor is $\frac{V^2}{-30} = -3000$

VAR. The total complex power is $1200 + j(900 - 3000) = 1200 - j2100$ VA. The magnitude of

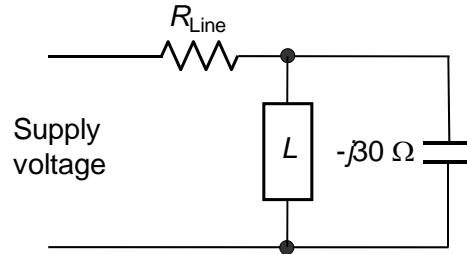the line current $\frac{\sqrt{(1200)^2 + (2100)^2}}{300} = \sqrt{65}$ A. The power dissipated in R_{line} is $65R_{line}$.



4. Determine the reactive power absorbed in the circuit, given that $\mathbf{I} = 1 \angle 0^\circ$ A rms.


Solution: The equivalent series impedance is

$$\frac{j5(5 - j5)}{j5 + 5 - j5} = 5 + j5. \text{ The reactive power is } 5|\mathbf{I}|^2 \text{ VAR. As a}$$


check, the current in the capacitive branch is $\frac{j5}{j5 + 5 - j5} \mathbf{I} = \mathbf{I}$; the reactive power absorbed

by the capacitor is $-5|\mathbf{I}|^2 = -5|\mathbf{I}|^2$ VAR. The current in the inductive branch is $\frac{5 - j5}{j5 + 5 - j5} \mathbf{I} = (1$

$-j)\mathbf{I} = \sqrt{2} \angle -45^\circ \mathbf{I}$; the reactive power absorbed by the inductor is $5|\sqrt{2} \mathbf{I}|^2 = 10|\mathbf{I}|^2$ VAR. The total reactive power absorbed is $10|\mathbf{I}|^2 - 5|\mathbf{I}|^2 = 5|\mathbf{I}|^2$ VAR.

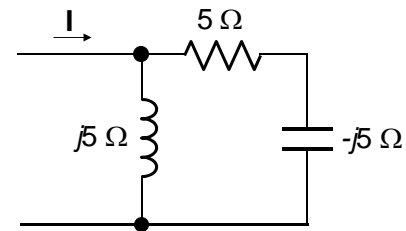

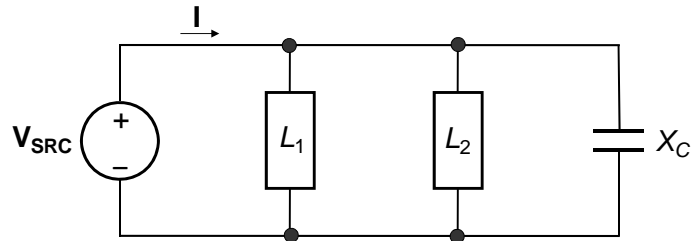
5. In the circuit shown, L_1 consumes 160 W at 0.8 p.f. lagging and L_2 consumes 320 VAR at 0.6 p.f. lagging. Determine \mathbf{I} when X_C is chosen for unity power factor, assuming $\mathbf{V}_{\text{SRC}} = 200 \angle 0^\circ$ V rms.



Solution: At unity p.f. the total reactance seen by the source is zero and the source applies only real power. The real power consumed by L_2 is $\frac{320}{0.8} \times 0.6 = 240$ W. The total real power supplied by the load is $160 + 240 = 400$ W. The current is $\frac{400}{V_{SRC} \angle 0^\circ} = \frac{400}{V_{SRC}} \angle 0^\circ$ A rms.

8%

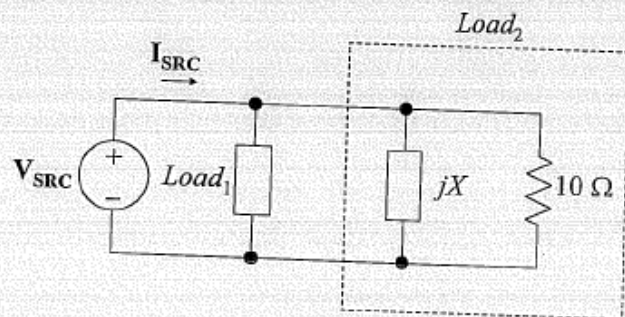
5. The complex powers absorbed by L_1 and L_2 are $1 + j0.2$ kVA and $1 - j0.2$ kVA. Determine \mathbf{I}_{SRC} , assuming that the phase angle of \mathbf{V}_{SRC} is zero. Note that X need not be given.



- A. $20 \angle 90^\circ$ A B. $10 \angle 90^\circ$ A
C. $10 \angle 0^\circ$ A \rightarrow D. $20 \angle 0^\circ$ A
E. None of the above

Solution: The complex power delivered by the source is 2 kVA. The real power absorbed by L_2 is in the 10Ω resistor. If $\mathbf{V}_{\text{SRC}} = V_m \angle 0$ V, then $\frac{|V_m|^2}{10} = 1000$, or $V_m = 100$ V. It follows that $I_m = \frac{2000}{100} = 20$ A, and $\mathbf{I}_{\text{SRC}} = 20 \angle 0$ A.

Problem 14

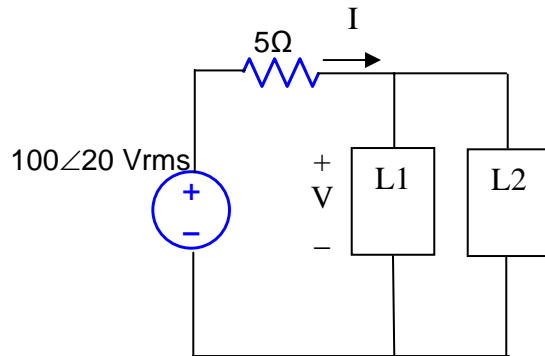

It is given that the complex power of $L1$ is $5+j10 \text{ VA}$. It is also given that $L2$ absorbs 20W at lagging power factor of 0.8 . What is the phase difference between I and V as shown in figure?

- A) 45.00°
- B) 39.81°
- C) 63.33°
- D) 60.00°
- E) None of the above.


Problem 15

What is the impedance of a load if it absorbs 20KVAR at lagging power factor of 0.6 when a current of magnitude 50 A rms flows through it?

- A) $6 + 8j \text{ ohms}$
- B) $3 + 4j \text{ ohms}$
- C) $4 + j3 \text{ ohms}$
- D) $8 + j6 \text{ ohms}$
- E) None of the above.


4. How much complex power is delivered by the $5\angle 30^\circ$ A (rms) current source to the circuit shown in figure.

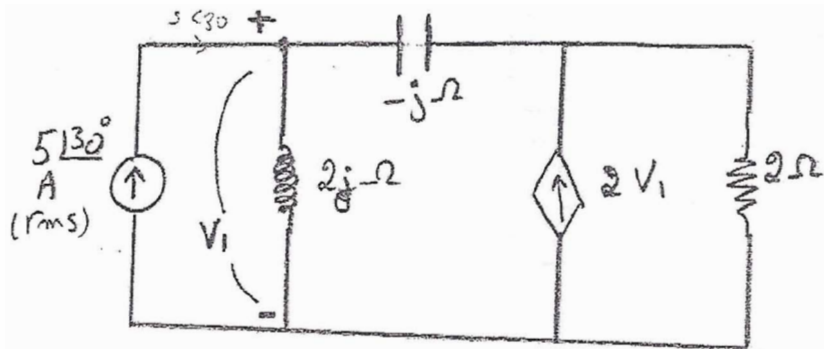- a. $7.5\angle 137.48^\circ$ VA.
- b. 0 VA.
- c. 100 VA.
- d. $15.35\angle 137.48^\circ$ VA.
- e. None of the above.




1. The values of R_1 , R_2 , C and L are unknown. Load 1 absorbs a complex power of $50\angle -45^\circ$ VA and load 2 absorbs a complex power of $100\angle 45^\circ$ VA. Determine R_2 if $V_s = 250\angle 0^\circ$ V **rms.**

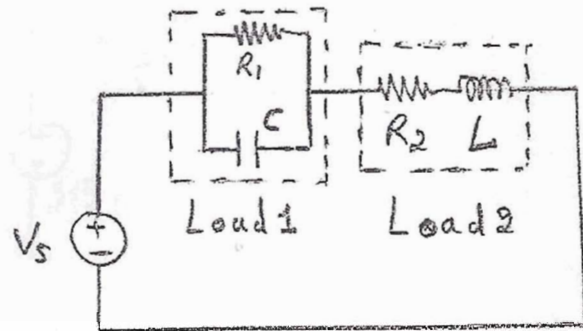- a. $250\sqrt{2} \Omega$
b. $125\sqrt{2} \Omega$
c. 125Ω
d. $125/\sqrt{2} \Omega$
e. None of the above.



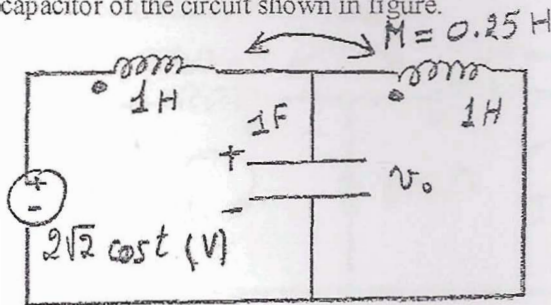5. Find the voltage $v_o(t)$ across the capacitor of the circuit shown in figure.



- a. $1.60 \cos(2t) V.$
- b. $1.60 \sin(t) V.$
- c. $3.2 \cos(t) V.$
- d. $2.26 \cos(t) V.$
- e. None of the above.

6. Two impedances $Z_1 = 9.8 \angle -78^\circ \Omega$ and $Z_2 = 18.5 \angle 21.8^\circ \Omega$ are connected in parallel and the combination in series with an impedance $Z_3 = 5 \angle 53^\circ \Omega$. If this circuit is connected across a 100-V source (rms), how much average power will be supplied by the source.

- a. 980.8 W.
- b. 490 W.
- c. 1960 W.
- d. 1391.6 W.
- e. None of the above.

1. An impedance $Z_1 = (4 + j4) \Omega$ is connected in parallel with an impedance $Z_2 = (12 + j6) \Omega$. If the input reactive power is 1000 VAR (lagging), what is the total active (average) power ?

- A. 1210 W
- B. 3025 W
- C. 826.39 W
- D. 1150 W
- E. None of the above

3. The conjugate of the complex power delivered by a current source is $200 - j200$ VA. If the source current is $\frac{10}{\sqrt{2}} \angle 45^\circ$ A peak, determine the rms voltage across the source.

A. 40 V rms


B. $j40$ V rms

C. 80 V rms

D. $-j40$ V rms

→ E. None of the above $j40\sqrt{2}$ rms

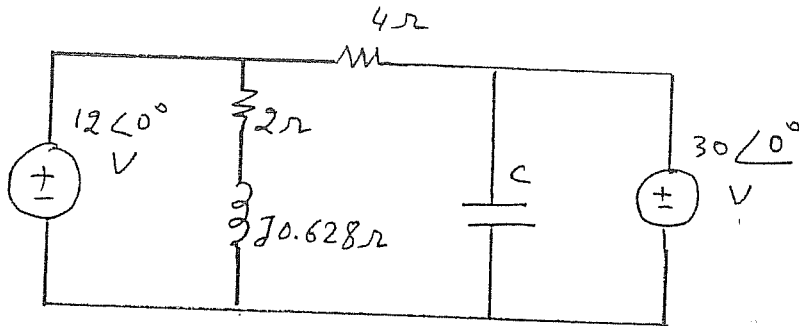
11. Determine the value of C in the circuit shown if C takes 5 VAR. The operating frequency is 50 Hz.



- A. $12.63 \mu\text{F}$
- B. $14.74 \mu\text{F}$
- C. $17.68 \mu\text{F}$
- D. $3 \mu\text{F}$
- E. None of the above

2. In the circuit shown, the capacitance absorbs -200 VAR. Determine the average power dissipated in R if $R = 5 \Omega$.

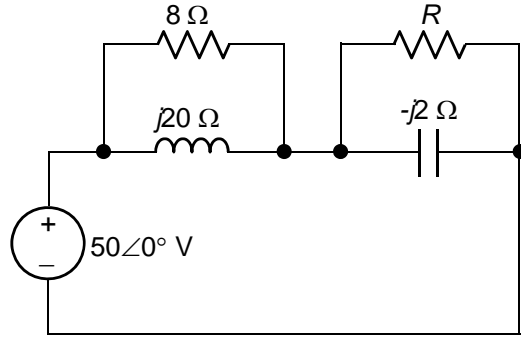- A. 57.1 W
B. 80 W
 C. 44.4 W
 D. 66.7 W
 E. 50 W




Solution: $Q = -BV_{\text{rms}}^2$, where V_{rms} is the rms voltage across R and C , and $B = -1/X = 1/2$ S.

Substituting, $-200 = -\frac{1}{2}V_{\text{rms}}^2$, and $V_{\text{rms}} = 20$ V. It follows that $P_R = \frac{V_{\text{rms}}^2}{R} = \frac{400}{5} = 80$ W.

3. Determine I_x assuming $I_{\text{SRC}} = j$ A.

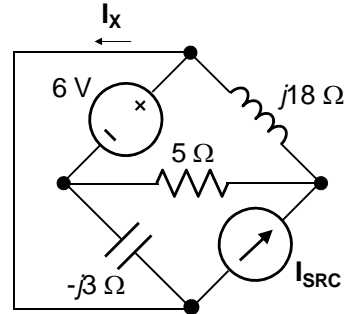- A. $j6$ A
 B. $-j3$ A
C. $j3$ A
 D. $-j6$ A
 E. $j4$ A



Solution: The voltage across the $-j3 \Omega$ capacitor is 6 V and the current through this capacitor, directed upwards is $j2$ A. It follows that $I_x = I_{\text{SRC}} + j2 = j3$ A.

5. Two coils are tightly coupled to a high-permeability core, so that the leakage flux is negligibly small. If coil 1 has 100 turns and an inductance of 10 mH, and the mutual inductance is 12.5 mH, determine the number of turns of coil 2.

- A. 125**
 B. 250
 C. 150
 D. 175
 E. 200

Solution: From the definitions of self and mutual inductance, with negligible leakage flux,

$$L_1 = \frac{N_1 \phi_{21}}{i_1} \text{ and } M = \frac{N_2 \phi_{21}}{i_1}. \text{ It follows that } N_2 = \frac{M}{L_1} N_1 = 10M = 125.$$

6. Determine the inductance of coil 2 of the preceding problem.

- A. 22.5 mH
- B. 30.63 mH
- C. 15.63 mH
- D. 40 mH
- E. 50.63 mH

Solution: Since the coils are tightly coupled to the core, $k = 1$, so that $M^2 = L_1 L_2$, or

$L_2 = \frac{M^2}{L_1} = 0.1M^2$ mH. It also follows from the solution of the preceding problem that

$$N_1 = \frac{M}{L_2} N_2. \text{ Dividing, } L_2 = L_1 \left(\frac{N_2}{N_1} \right)^2 = 0.1M^2 = 0.1 \times (12.5)^2 = 15.625 \text{ mH.}$$

7. A D'Arsonval movement has a resistance of $R \Omega$ and a full-scale deflection of $100 \mu\text{A}$. Determine the shunt resistance that will result in a full-scale deflection of $150 \mu\text{A}$, assuming $R = 50 \Omega$.

- A. 150Ω
- B. 200Ω
- C. 300Ω
- D. 100Ω
- E. 250Ω

Solution: At full-scale deflection, the voltage drop across the movement and shunt is $(R \Omega) \times (100 \mu\text{A}) = 100R \mu\text{V}$. The shunt has to pass $50 \mu\text{A}$, so its resistance is $R_{\text{shunt}} = 100R/50 = 2R = 100 \Omega$.


8. When a 9950Ω resistance is connected in series with a D'Arsonval movement of unknown resistance and full-scale deflection current, a voltage of 1 V across the series combination gives a certain full-scale deflection. If an additional $10,000 \Omega$ is connected in series with the combination, 2 V are required for full-scale deflection. Determine the resistance of the D'Arsonval movement.

- A. 150Ω
- B. 100Ω
- C. 75Ω
- D. 125Ω
- E. 50Ω

Solution: Let the resistance of the movement be R_m , its FSD current be I_{FSD} , and the FSD voltage with series resistance be V_{FSD} . Then $I_{FSD}(R + R_m) = V_{FSD}$, and $I_{FSD}(10,000 + R + R_m) = 2V_{FSD}$. It follows that $R + R_m = 10,000$, or $R_m = 10,000 - R = 50 \Omega$.

9. Determine L_{eq} if $L = 1 \text{ H}$.

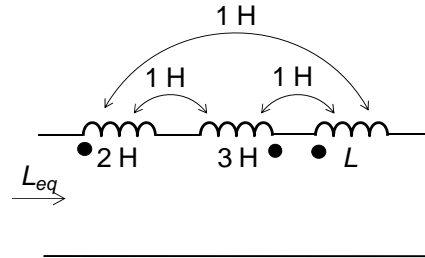
- A. 6 H
- B. 4 H**
- C. 8 H
- D. 7 H
- E. 5 H




Solution: Consider that a voltage V is applied, causing a current I to flow. $V = j\omega I[(2 - 1 + 1) + (3 - 1 - 1) + (L + 1 - 1)]$; $L_{eq} = 3 + L = 4 \text{ H}$.

10. Determine V_{Th} , assuming $V_{SRC} = 1 \angle 0^\circ \text{ V}$

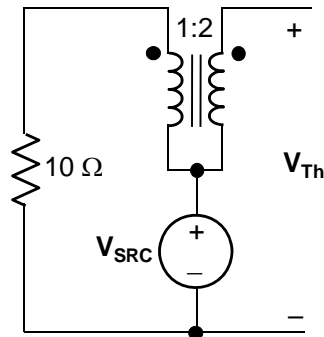- A. $-1 \angle 0^\circ \text{ V}$**
- B. $1 \angle 0^\circ \text{ V}$
- C. $-2 \angle 0^\circ \text{ V}$
- D. $2 \angle 0^\circ \text{ V}$
- E. $4 \angle 0^\circ \text{ V}$



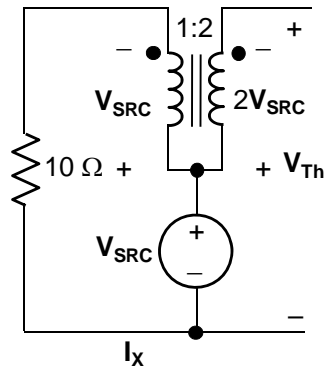Solution: On open circuit, no current flows. The primary voltage is V_{SRC} as shown, and $V_{Th} = -V_{SRC} = -1 \angle 0^\circ \text{ V}$




11. Determine Z_L for maximum average power

delivered to it if $R = 5 \Omega$ and $I_x = k \angle -45^\circ$

where $k = \sqrt{2} \text{ A rms}$.

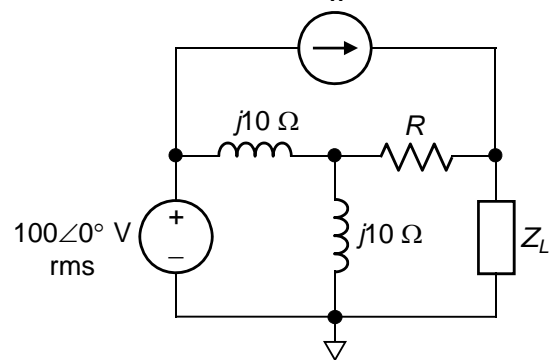- A. $10 + j10 \Omega$
- B. $5 + j5 \Omega$
- C. $5 - j5 \Omega$**
- D. $10 - j10 \Omega$
- E. $15 - j15 \Omega$



Solution: Z_{Th} is $(R + j5) \Omega$. Hence, Z_L for maximum power transfer is $(R - j5) = (5 - j5) \Omega$.


12. Determine the maximum average power delivered to Z_L in Problem 11, assuming that $R = 5 \Omega$ and \mathbf{I}_x is as in Problem 11.
- A. 90 W
 - B. 200 W
 - C. 320 W
 - D. 180 W**
 - E. 245 W

Solution: \mathbf{V}_{Th} as seen by Z_L is determined from superposition as $\frac{j10}{j10 + j10} \times 100 \angle 0^\circ +$

$$(5 + j10 \parallel j10)\mathbf{I}_x = 50 \angle 0^\circ + 5(1 + j)\mathbf{I}_x = 50 \angle 0^\circ + (5\sqrt{2} \angle 45^\circ) \times k \angle -45^\circ = 50 + 5\sqrt{2}k;$$

$$P_{L_{max}} = \frac{(50 + 5\sqrt{2}k)^2}{4R_{Th}} = \frac{(50 + 5\sqrt{2}k)^2}{20} = \frac{(50 + 5\sqrt{2} \times \sqrt{2})^2}{20} = \frac{(60)^2}{20} = 180 \text{ W.}$$

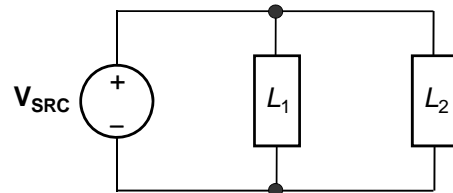13. Load L_1 absorbs 15 kVA at 0.6 p.f. lagging, whereas Load L_2 absorbs 4.8 kW at 0.8 p.f. leading. If $\mathbf{V}_{SRC} = 200 \angle 0^\circ$ V rms at $f = 50$ Hz, determine the capacitor that must be connected in parallel with L_1 and L_2 to have maximum magnitude of current through the source.



- A. 0.67 mF**
- B. 0.55 mF
- C. 0.34 mF
- D. 0.46 mF
- E. 1.24 mF

Solution: The reactive power absorbed by L_1 is 15×0.8 kVAR = 12 kVAR, whereas the

reactive power absorbed by L_2 is $-\frac{4.8}{0.8} \times 0.6 = -3.6$ kVAR. For maximum magnitude of

source current, the p.f. should be unity. The capacitor must add a reactive power of $-(12 -$

$3.6) = -8400$ VAR. hence, $-8400 = -\omega C \times |\mathbf{V}_{SRC}|^2$, or $C = \frac{8400}{100\pi |\mathbf{V}_{SRC}|^2} = \frac{84}{\pi |\mathbf{V}_{SRC}|^2} =$

$$\frac{84}{\pi(200)^2} \cong 0.67 \text{ mF.}$$

14. A periodic current is shown, where over a period,

$$i = 6 + A \sin 2t \quad 0 \leq t \leq \pi$$

$$i = -4 + A \sin 2(t - \pi) \quad \pi \leq t \leq 2\pi$$

Determine the rms value of i if $A = 1$ A.


A. 5.83 A

B. 5.15 A

C. 6.20 A

D. 5.29 A

E. 5.52 A

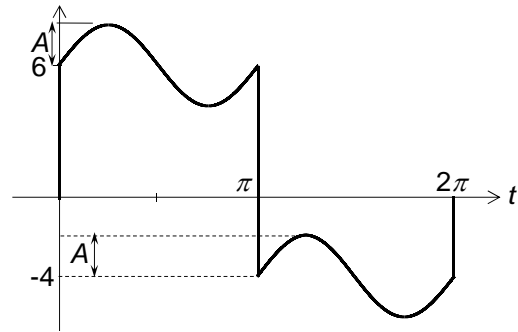

Solution: The waveform consists of three components: i) a dc component of 1 A, ii) a square wave of 5 V amplitude, and iii) a sinusoidal wave of amplitude A . It follows that the

rms value is $I = \sqrt{1^2 + 5^2 + A^2 / 2} = \sqrt{26 + A^2 / 2} = \sqrt{26.5} = 5.15$ A.

15. The current waveform of the preceding problem is applied to a 2Ω resistor in parallel with a very large capacitor. Determine the voltage across the parallel combination.

A. 2.5 V

B. 2 V

C. 3 V

D. 4 V

E. 3.5 V

Solution: The ac voltage will be negligibly small. The dc voltage is the dc component of current multiplied by R , or $V = 1 \times R = 2$ V.


16. The period of a periodic function $f(t)$ is defined as:

$$f(t) = \cos(t + \pi) - 2, \quad -\pi < t < -\pi/2$$

$$f(t) = -\cos(t) + k, \quad -\pi/2 < t < \pi/2$$

$$f(t) = \cos(t - \pi) - 2, \quad \pi/2 < t < \pi$$

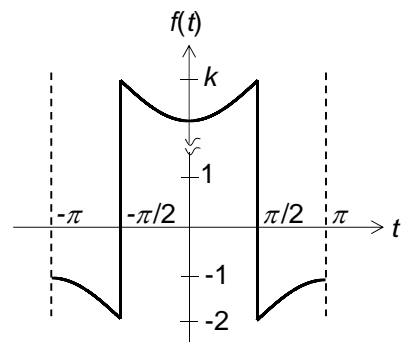Derive the trigonometric Fourier series expansion of $f(t)$, assuming $k = 3$.



$$\text{Solution: } a_0 = \frac{1}{\pi} \left[\int_0^{\pi/2} (-\cos t + k) dt + \int_{\pi/2}^{\pi} (\cos(t - \pi) - 2) dt \right] =$$

$$\frac{1}{\pi} \left[k \int_0^{\pi/2} dt - 2 \int_{\pi/2}^{\pi} dt - \int_0^{\pi/2} \cos t dt - \int_{\pi/2}^{\pi} \cos t dt \right] = \frac{1}{\pi} \left[k \int_0^{\pi/2} dt - 2 \int_{\pi/2}^{\pi} dt \right] = \frac{1}{\pi} \left[\frac{k\pi}{2} - \pi \right] = \frac{k}{2} - 1.$$

$$a_n = \frac{2}{\pi} \left[\int_0^{\pi/2} (-\cos t + k) \cos ntdt + \int_{\pi/2}^{\pi} (\cos(t - \pi) - 2) \cos ntdt \right] =$$

$$\frac{2}{\pi} \left[- \int_0^{\pi} \cos t \cos ntdt + \int_0^{\pi/2} k \cos ntdt - \int_{\pi/2}^{\pi} 2 \cos ntdt \right] =$$

$$\frac{2}{\pi} \left[- \frac{1}{2} \int_0^{\pi} \cos(n-1)t dt - \frac{1}{2} \int_0^{\pi} \cos(n+1)t dt + k \int_0^{\pi/2} \cos ntdt - 2 \int_{\pi/2}^{\pi} \cos ntdt \right] =$$

$$- \frac{1}{\pi} \left[\frac{\sin(n-1)t}{n-1} + \frac{\sin(n+1)t}{n+1} \right]_0^{\pi} + \frac{2k}{n\pi} [\sin nt]_0^{\pi/2} - \frac{4}{n\pi} [\sin nt]_{\pi/2}^{\pi} =$$


$$0 - 0 + \frac{2k}{n\pi} \sin \frac{n\pi}{2} - 0 - 0 + \frac{4}{n\pi} \sin \frac{n\pi}{2} = \frac{2(k+2)}{n\pi} \sin \frac{n\pi}{2} . a_n \text{ is zero for even values, and the}$$

odd harmonics alternate in sign. Thus,


$$f(t) = \left(\frac{k}{2} - 1 \right) \frac{1}{2} + \frac{2(k+2)}{\pi} \left(\cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t - \frac{1}{7} \cos 7t + \dots \right)$$

$$= \frac{1}{2} + \frac{10}{\pi} \left(\cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t - \frac{1}{7} \cos 7t + \dots \right) .$$

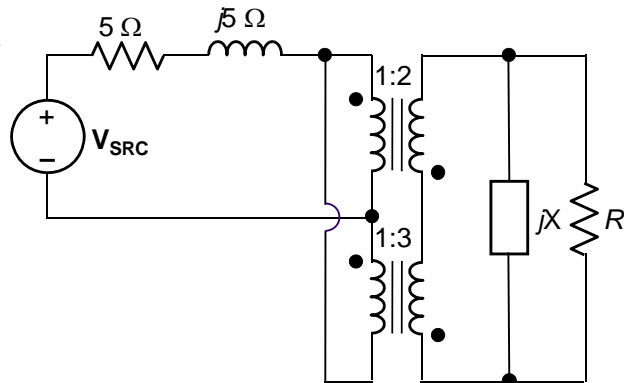19. Determine X and R for maximum power transfer to R and calculate this power. Assume $\mathbf{V}_{\text{SRC}} = 4\angle 0^\circ \text{ V rms}$.



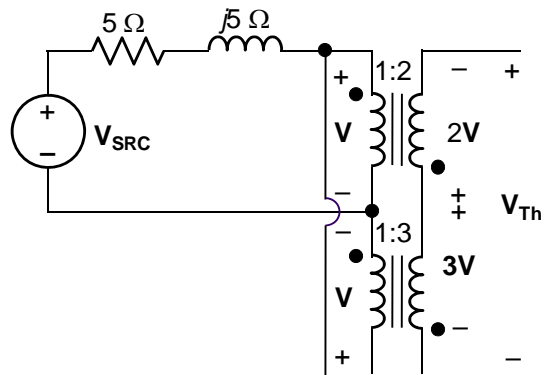
Solution: On open circuit, $\mathbf{V}_{\text{TH}} = \mathbf{V} = \mathbf{V}_{\text{SRC}}$. On short circuit, $\mathbf{V} = 0$ and $\mathbf{I}_N = \mathbf{I} = \frac{\mathbf{V}_{\text{SRC}}}{5(1+j)}$. $Y_N = \frac{1}{5(1+j)} = 0.1(1-j) \text{ S}$. For maximum power transfer, $G_L = 0.1 \text{ S}$, or $R = 10 \Omega$, and $B_L = 0.1 \text{ S}$, or $X = -10 \Omega$.



Under conditions of maximum power transfer, the current in R is $0.5|I_N| = \frac{0.5|V_{SRC}|}{10}$

and the power transferred is $\frac{0.25|V_{SRC}|^2}{10} =$

$$\frac{|V_{SRC}|^2}{40} = \frac{16}{40} = 0.4 \text{ W.}$$

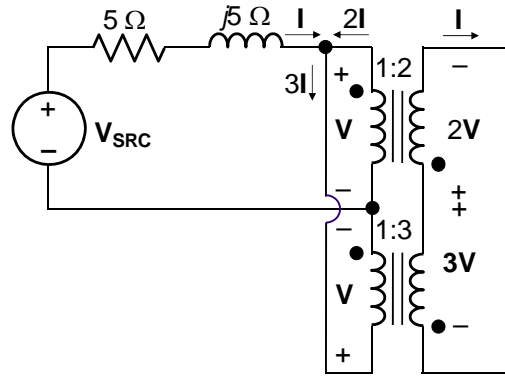

20. Determine the complex power delivered by each source given that $V_{SRC} = 5\cos\omega t$, $I_{SRC} = -2\sin\omega t$, and assuming $Z_L = k(1 - j)$ where $k = 1$.

Solution: The currents and voltages are as shown. Equating mmfs: $100 \times 2 \angle 90^\circ + 200I_L = 0$, or $j2 = -2I_L$, and $I_L = -j$ A, $I_1 = I_L - j2 = -j3$ A.

$V_L = Z_L I_L = -jk(1 - j) = -k(1 + j)$ V. $V_2 = V_L - 5 = -(k + 5) - jk$. $V_1 = V_2/2 = -(k + 5)/2 - jk/2$ V. $V_1 = 5 - V_1 = (15 + k)/2 + jk/2$ V.

Power delivered by voltage source = $S_V =$

$$\frac{V_{src}}{\sqrt{2}} \frac{I_1^*}{\sqrt{2}} = \frac{1}{2} (5)(j3) = \frac{j15}{2} = j7.5 \text{ VA}$$

Power delivered by current source $S_I =$



$$\frac{V_1}{\sqrt{2}} \frac{I_{SRC}^*}{\sqrt{2}} = \frac{1}{2} \left(\frac{15 + k}{2} + \frac{jk}{2} \right) (-j2) = \frac{1}{2} (k - j(15 + k)) = 0.5 - j8 \text{ VA}$$

Total power delivered by sources =

$$\frac{1}{2} (j15 + k - j15 - jk) = \frac{k}{2} (1 - j)$$


As a check, $S_L =$
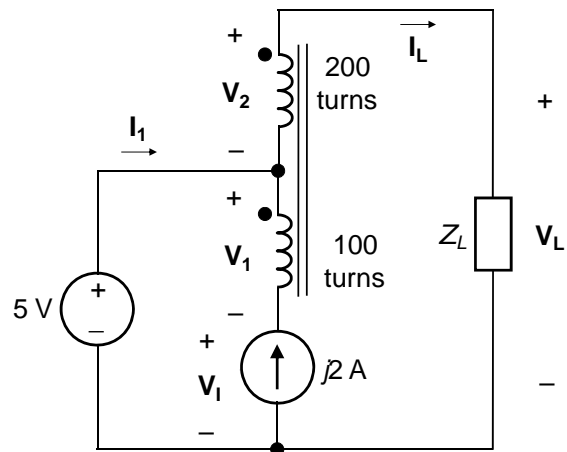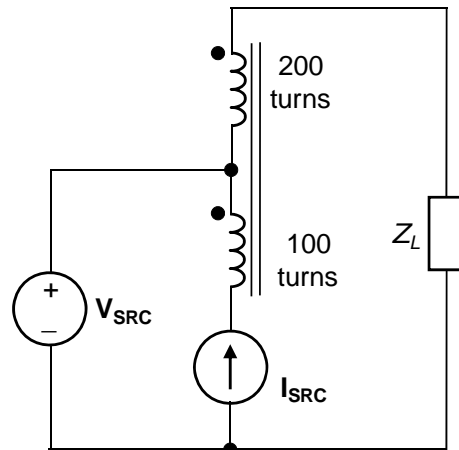
$$\frac{V_{Lm}}{\sqrt{2}} \frac{I_{Lm}^*}{\sqrt{2}} = \frac{1}{2} (-jk(1 - j))(j) = \frac{k}{2} (1 - j) \text{ VA.}$$



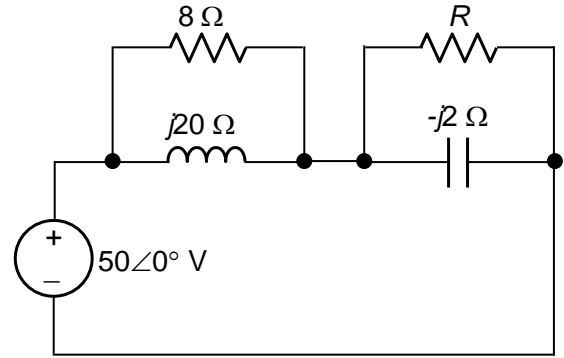2. In the circuit shown, the capacitance absorbs -200 VAR. Determine the average power dissipated in R if $R = 5 \Omega$.

Solution: $Q = -BV_{\text{rms}}^2$, where V_{rms} is the rms voltage across R and C , and $B = -1/X = 1/2 \text{ S}$.
 Substituting, $-200 = -\frac{1}{2}V_{\text{rms}}^2$, and $V_{\text{rms}} = 20 \text{ V}$. It follows that $P_R = \frac{V_{\text{rms}}^2}{R} = \frac{400}{5} = 80 \text{ W}$.




8. When a 9950Ω resistance is connected in series with a D'Arsonval movement of unknown resistance and full-scale deflection current, a voltage of 1 V across the series combination gives a certain full-scale deflection. If an additional $10,000 \Omega$ is connected in series with the combination, 2 V are required for full-scale deflection. Determine the resistance of the D'Arsonval movement.

Solution: Let the resistance of the movement be R_m , its FSD current be I_{FSD} , and the FSD voltage with series resistance be V_{FSD} . Then $I_{\text{FSD}}(R + R_m) = V_{\text{FSD}}$, and $I_{\text{FSD}}(10,000 + R + R_m) = 2V_{\text{FSD}}$. It follows that $R + R_m = 10,000$, or $R_m = 10,000 - R = 50 \Omega$.

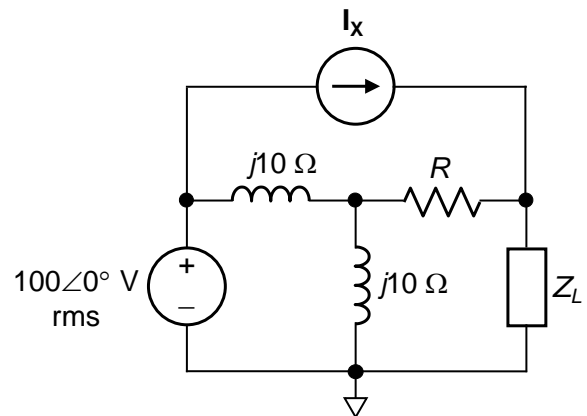11. Determine Z_L for maximum average power delivered to it if $R = 5 \Omega$ and $\mathbf{I}_x = k\angle -45^\circ$ where $k = \sqrt{2} \text{ A rms}$.

Solution: Z_{Th} is $(R + j5) \Omega$. Hence, Z_L for maximum power transfer is $(R - j5) = (5 - j5) \Omega$.




12. Determine the maximum average power delivered to Z_L in Problem 11, assuming that $R = 5 \Omega$ and \mathbf{I}_x is as in Problem 11.

Solution: \mathbf{V}_{Th} as seen by Z_L is determined from superposition as $\frac{j10}{j10 + j10} \times 100\angle 0^\circ +$

$$(5 + j10 \parallel j10)\mathbf{I}_x = 50\angle 0^\circ + 5(1 + j)\mathbf{I}_x = 50\angle 0^\circ + (5\sqrt{2}\angle 45^\circ) \times k\angle -45^\circ = 50 + 5\sqrt{2}k;$$

$$P_{L_{\text{max}}} = \frac{(50 + 5\sqrt{2}k)^2}{4R_{\text{Th}}} = \frac{(50 + 5\sqrt{2}k)^2}{20} = \frac{(50 + 5\sqrt{2} \times \sqrt{2})^2}{20} = \frac{(60)^2}{20} = 180 \text{ W}.$$

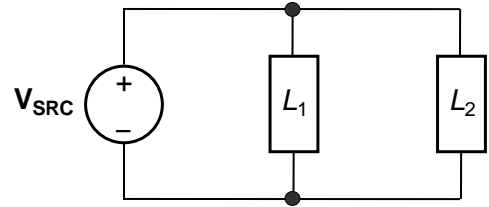13. Load L_1 absorbs 15 kVA at 0.6 p.f. lagging, whereas Load L_2 absorbs 4.8 kW at 0.8 p.f. leading. If $\mathbf{V}_{\text{SRC}} = 200\angle 0^\circ$ V rms at $f = 50$ Hz, determine the capacitor that must be connected in parallel with L_1 and L_2 to have maximum magnitude of current through the source.



Solution: The reactive power absorbed by L_1 is 15×0.8 kVAR = 12 kVAR, whereas the reactive power absorbed by L_2 is $-\frac{4.8}{0.8} \times 0.6 = -3.6$ kVAR. For maximum magnitude of source current, the p.f. should be unity. The capacitor must add a reactive power of $-(12 - 3.6) = -8400$ VAR. hence, $-8400 = -\omega C \times |\mathbf{V}_{\text{SRC}}|^2$, or $C = \frac{8400}{100\pi |\mathbf{V}_{\text{SRC}}|^2} = \frac{84}{\pi |\mathbf{V}_{\text{SRC}}|^2} = 84/(\pi 200^2) \approx 0.67$ mF.

20. Determine the complex power delivered by each source given that $\mathbf{V}_{\text{SRC}} = 5\cos\omega t$, $\mathbf{I}_{\text{SRC}} = -2\sin\omega t$, and assuming $Z_L = k(1 - j)$ where $k = 1$.

Solution: The currents and voltages are as shown. Equating mmfs: $100 \times 2 \angle 90^\circ + 200 \mathbf{I}_L = 0$, or $j2 = -2\mathbf{I}_L$, and $\mathbf{I}_L = -j$ A, $\mathbf{I}_1 = \mathbf{I}_L - j2 = -j3$ A.

$\mathbf{V}_L = Z_L \mathbf{I}_L = -jk(1 - j) = -k(1 + j)$ V. $\mathbf{V}_2 = \mathbf{V}_L - 5 = -(k + 5) - jk$. $\mathbf{V}_1 = \mathbf{V}_2/2 = -(k + 5)/2 - jk/2$ V. $\mathbf{V}_1 = 5 - \mathbf{V}_1 = (15 + k)/2 + jk/2$ V.

Power delivered by voltage source = $S_v =$

$$\frac{V_{\text{src}}}{\sqrt{2}} \frac{I_1^*}{\sqrt{2}} = \frac{1}{2} (5)(j3) = \frac{j15}{2} = j7.5 \text{ VA}$$

Power delivered by current source $S_i =$



$$\frac{V_1}{\sqrt{2}} \frac{I_{\text{SRC}}^*}{\sqrt{2}} = \frac{1}{2} \left(\frac{15 + k}{2} + \frac{jk}{2} \right) (-j2) = \frac{1}{2} (k - j(15 + k)) = 0.5 - j8 \text{ VA}$$

Total power delivered by sources =

$$\frac{1}{2} (j15 + k - j15 - jk) = \frac{k}{2} (1 - j)$$

As a check, $S_L =$
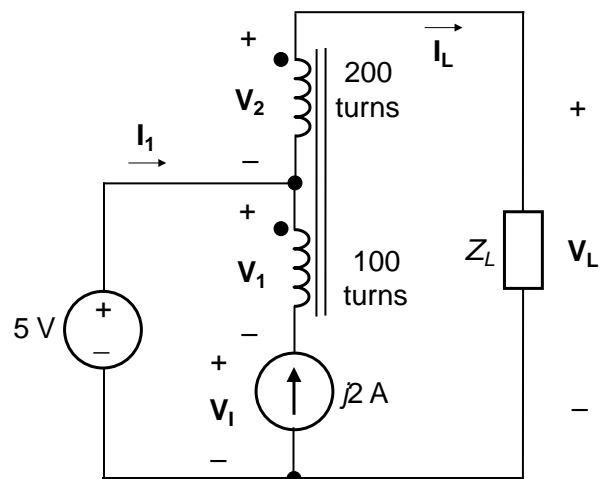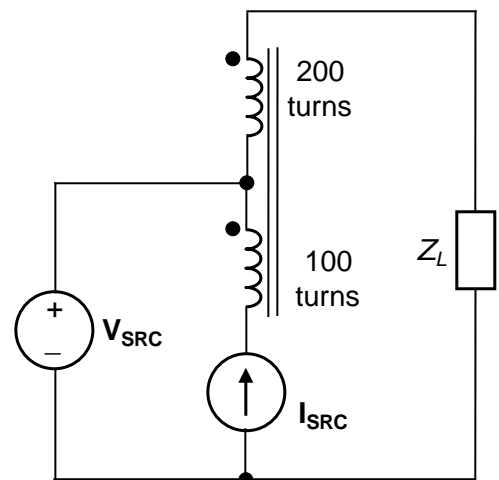
$$\frac{V_{Lm}}{\sqrt{2}} \frac{I_{Lm}^*}{\sqrt{2}} = \frac{1}{2} (-jk(1 - j))(j) = \frac{k}{2} (1 - j) \text{ VA.}$$



15. The current waveform of the preceding problem is applied to a 2Ω resistor in parallel with a very large capacitor. Determine the voltage across the parallel combination.

Solution: The ac voltage will be negligibly small. The dc voltage is the dc component of current multiplied by R , or $V = 1 \times R = 2 \text{ V}$.


16. The period of a periodic function $f(t)$ is defined as:

$$f(t) = \cos(t + \pi) - 2, \quad -\pi < t < -\pi/2$$

$$f(t) = -\cos(t) + k, \quad -\pi/2 < t < +\pi/2$$

$$f(t) = \cos(t - \pi) - 2, \quad \pi/2 < t < \pi$$

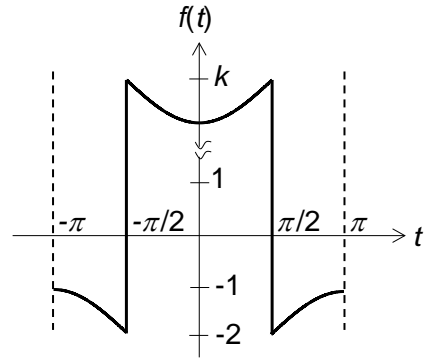Derive the trigonometric Fourier series expansion of $f(t)$, assuming $k = 3$.



Solution: $a_0 = \frac{1}{\pi} \left[\int_0^{\pi/2} (-\cos t + k) dt + \int_{\pi/2}^{\pi} (\cos(t - \pi) - 2) dt \right] =$

$$\frac{1}{\pi} \left[k \int_0^{\pi/2} dt - 2 \int_{\pi/2}^{\pi} dt - \int_0^{\pi/2} \cos t dt - \int_{\pi/2}^{\pi} \cos t dt \right] = \frac{1}{\pi} \left[k \int_0^{\pi/2} dt - 2 \int_{\pi/2}^{\pi} dt \right] = \frac{1}{\pi} \left[\frac{k\pi}{2} - \pi \right] = \frac{k}{2} - 1.$$

$$a_n = \frac{2}{\pi} \left[\int_0^{\pi/2} (-\cos t + k) \cos nt dt + \int_{\pi/2}^{\pi} (\cos(t - \pi) - 2) \cos nt dt \right] =$$

$$\frac{2}{\pi} \left[- \int_0^{\pi/2} \cos t \cos nt dt + \int_0^{\pi/2} k \cos nt dt - \int_{\pi/2}^{\pi} 2 \cos nt dt \right] =$$

$$\frac{2}{\pi} \left[- \frac{1}{2} \int_0^{\pi} \cos(n-1)t dt - \frac{1}{2} \int_0^{\pi} \cos(n+1)t dt + k \int_0^{\pi/2} \cos nt dt - 2 \int_{\pi/2}^{\pi} \cos nt dt \right] =$$

$$- \frac{1}{\pi} \left[\frac{\sin(n-1)t}{n-1} + \frac{\sin(n+1)t}{n+1} \right]_0^{\pi} + \frac{2k}{n\pi} [\sin nt]_0^{\pi/2} - \frac{4}{n\pi} [\sin nt]_{\pi/2}^{\pi} =$$

$$0 - 0 + \frac{2k}{n\pi} \sin \frac{n\pi}{2} - 0 - 0 + \frac{4}{n\pi} \sin \frac{n\pi}{2} = \frac{2(k+2)}{n\pi} \sin \frac{n\pi}{2}. \quad a_n \text{ is zero for even values, and the}$$

odd harmonics alternate in sign. Thus,

$$f(t) = \left(\frac{k}{2} - 1 \right) \frac{1}{2} + \frac{2(k+2)}{\pi} \left(\cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t - \frac{1}{7} \cos 7t + \dots \right)$$

$$= \frac{1}{2} + \frac{10}{\pi} \left(\cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t - \frac{1}{7} \cos 7t + \dots \right).$$


7. A D'Arsonval movement has a resistance of $R \Omega$ and a full-scale deflection of $100 \mu\text{A}$.

Determine the shunt resistance that will result in a full-scale deflection of $150 \mu\text{A}$,


assuming $R = 50 \Omega$.

Solution: At full-scale deflection, the voltage drop across the movement and shunt is $(R \Omega) \times (100 \mu\text{A}) = 100R \mu\text{V}$. The shunt has to pass $50 \mu\text{A}$, so its resistance is $R_{\text{shunt}} = 100R/50 = 2R = 100 \Omega$.

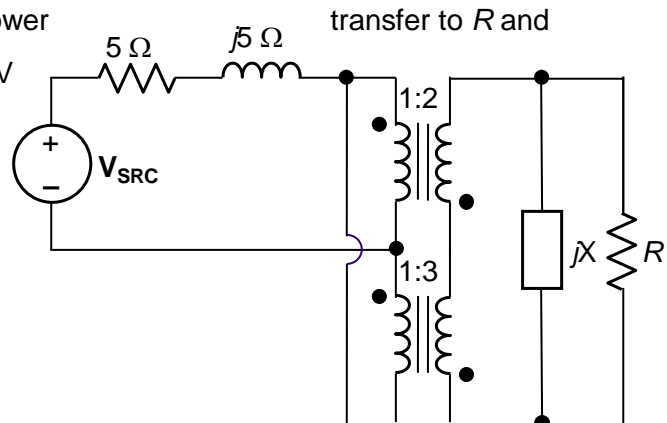19. Determine X and R for maximum power transfer to R and calculate this power. Assume $\mathbf{V}_{\text{SRC}} = 4\angle 0^\circ \text{ V}$ rms.




Solution: On open circuit, $\mathbf{V}_{\text{TH}} = \mathbf{V} = \mathbf{V}_{\text{SRC}}$. On short circuit, $\mathbf{V} = 0$ and $\mathbf{I}_{\text{N}} = \mathbf{I} = \frac{\mathbf{V}_{\text{SRC}}}{5(1+j)}$. $Y_{\text{N}} = \frac{1}{5(1+j)} = 0.1(1-j) \text{ S}$. For maximum power transfer, $G_{\text{L}} = 0.1 \text{ S}$, or $R = 10 \Omega$, and $B_{\text{L}} = 0.1 \text{ S}$, or $X = -10 \Omega$.

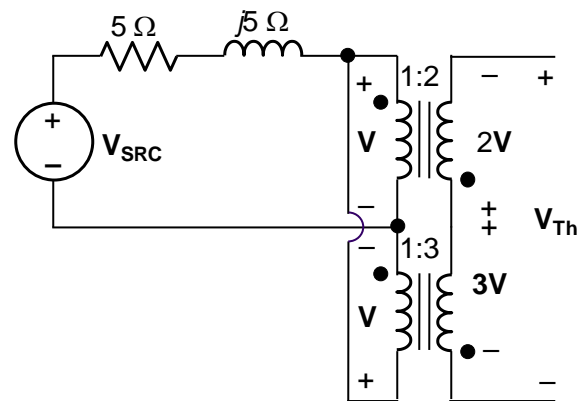

Under conditions of maximum power transfer, the current in R is $0.5|\mathbf{I}_{\text{N}}| = \frac{0.5|\mathbf{V}_{\text{SRC}}|}{10}$

and the power transferred is $\frac{0.25|\mathbf{V}_{\text{SRC}}|^2}{10} =$

$$\frac{|\mathbf{V}_{\text{SRC}}|^2}{40} = \frac{16}{40} = 0.4 \text{ W}.$$

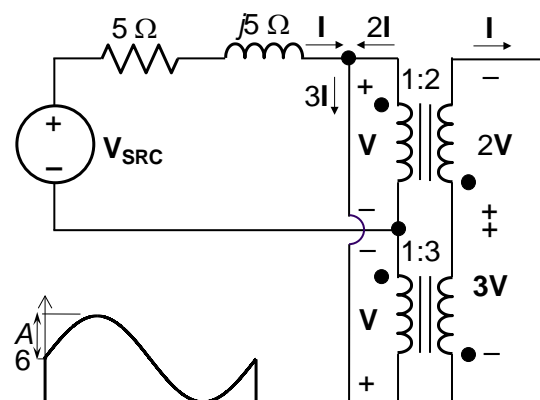

14. A periodic current is shown, where over a period,

$$i = 6 + A \sin 2t \quad 0 \leq t \leq \pi$$

$$i = -4 + A \sin 2(t - \pi) \quad \pi \leq t \leq 2\pi$$

Determine the rms value of i if $A = 1 \text{ A}$.

Solution: The waveform consists of three components: i) a dc component of 1 A , ii) a square wave of 5 V amplitude, and iii) a sinusoidal wave of amplitude A . It follows that the

rms value is $I = \sqrt{1^2 + 5^2 + A^2/2} = \sqrt{26 + A^2/2} = \sqrt{26.5} = 5.15 \text{ A}$.

