

**Quiz 3 – December 18, 2010**

4%

1. A current  $i = I_m \cos(\omega t + 30^\circ)$  flows through an impedance  $(5 - j5) \Omega$ . Determine the rms phasor voltage across the impedance if  $I_m = 2.5$  A.

**Solution:** The phasor current is  $I_m \angle 30^\circ$  A. The impedance is  $5\sqrt{2} \angle -45^\circ \Omega$ . The phasor voltage is  $5I_m \sqrt{2} \angle -15^\circ$  V peak value or  $5I_m \angle -15^\circ$  V rms.

**Version 1:**  $I_m = 2.5$  A,  $V = 12.5 \angle -15^\circ$  V rms

**Version 2:**  $I_m = 5$  A,  $V = 25 \angle -15^\circ$  V rms


**Version 3:**  $I_m = 7.5$  A,  $V = 37.5 \angle -15^\circ$  V rms

**Version 4:**  $I_m = 10$  A,  $V = 50 \angle -15^\circ$  V rms

**Version 4:**  $I_m = 12.5$  A,  $V = 62.5 \angle -15^\circ$  V rms.

4%

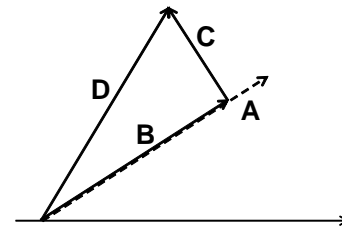2. In the phasor diagram shown, phasor **A** is a current, the other phasors **B**, **C**, and **D** are voltages. To which of the following combinations of circuit elements does this phasor diagram apply?



- A.  $R$  in series with  $L$
- B.  $R$  in series with  $C$
- C.  $R$  in parallel with  $C$
- D.  $L$  in series with  $C$
- E.  $L$  in parallel with  $C$ .


**Solution:** The phasor diagram represents a series  $RL$  circuit, Phasor **B** is the voltage across  $R$ . Phasor **C** is the voltage across  $L$ , leading the current by  $90^\circ$ , and phasor **D** is the voltage across the series combination.

4%

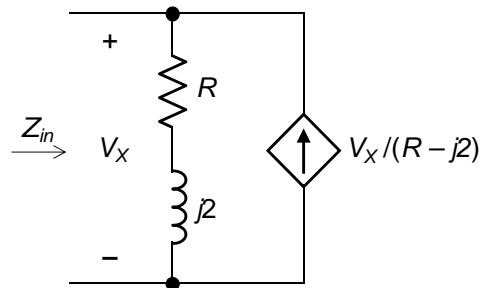3. Determine the input impedance  $Z_{in}$  assuming  $R = 2 \Omega$ .

**Solution:** If a test voltage source  $V_T$  is applied,  $I_T$

$$= \left( \frac{1}{R + j2} - \frac{1}{R - j2} \right) V_T, \text{ or } Z_{in} =$$



$$\frac{1}{\left(\frac{1}{R+j2} - \frac{1}{R-j2}\right)} = \frac{(R+j2)(R-j2)}{R-j2-R-j2} = \frac{R^2+4}{-j4} = j\left(1 + \frac{R^2}{4}\right) \Omega. \text{ Alternatively, the dependent}$$

source is equivalent to an impedance  $-(R-j2)$  and  $Z_{in} = (R+j2) \parallel [-(R-j2)] \Omega$ .

**Version 1:**  $R = 2 \Omega$ ;  $Z_{in} = j2 \Omega$

**Version 2:**  $R = 3 \Omega$ ;  $Z_{in} = j3.25 \Omega$

**Version 3:**  $R = 4 \Omega$ ;  $Z_{in} = j5 \Omega$

**Version 4:**  $R = 5 \Omega$ ;  $Z_{in} = j7.25 \Omega$

**Version 5:**  $R = 6 \Omega$ ;  $Z_{in} = j10 \Omega$ .

4%

4. Determine  $Z_Y$  so that  $V_L$  is in phase with  $V_{SRC}$ , assuming  $X = -5 \Omega$  with  $R_L$  and  $V_{SRC}$  unknown.

**Solution:** TEC as seen from terminals a and b will have  $Z_{Th} = jX/2$ . For  $V_L$  to be in phase with

$V_{SRC}$ ,  $Z_Y = -jX/2$ .



**Version 1:**  $X = -5 \Omega$ ;  $Z_Y = j2.5 \Omega$

**Version 2:**  $X = 5 \Omega$ ;  $Z_Y = -j2.5 \Omega$

**Version 3:**  $X = -10 \Omega$ ;  $Z_Y = j5 \Omega$

**Version 4:**  $X = 10 \Omega$ ;  $Z_Y = -j5 \Omega$

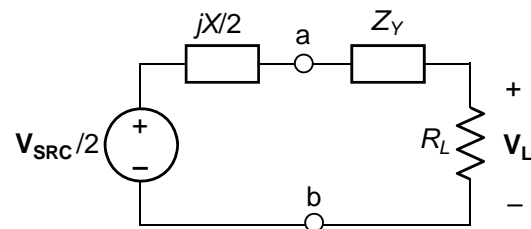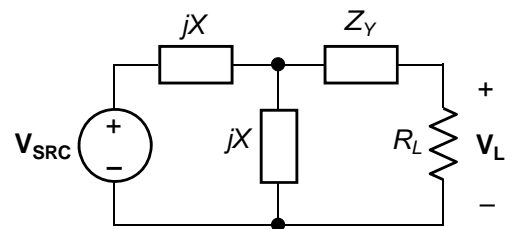**Version 5:**  $X = -15 \Omega$ ;  $Z_Y = j7.5 \Omega$ .



4%

5. Determine  $V_O$  if  $\omega = 1 \text{ krad/s}$  and  $V_{SRC} = 3 \text{ V}$ .

**Solution:**  $\omega CR = 1$ ;

$$\frac{V_O}{V_{SRC}} = \frac{R/(1+j\omega CR)}{R/(1+j\omega CR) + R - j/\omega C} =$$

$$\frac{R/(1+j)}{R/(1+j) + R - j/\omega C} = \frac{1/(1+j)}{1/(1+j) + 1 - j} = \frac{1}{1 + (1+j)(1-j)} = \frac{1}{1+1-j^2} = \frac{1}{3}$$


**Version 1:**  $V_{SRC} = 3 \text{ V}$ ;  $V_O = V_{SRC}/3 = 1 \text{ V}$

**Version 2:**  $V_{SRC} = 4.5 \text{ V}$ ;  $V_O = V_{SRC}/3 = 1.5 \text{ V}$

**Version 3:**  $V_{SRC} = 6 \text{ V}$ ;  $V_O = V_{SRC}/3 = 2 \text{ V}$

**Version 4:**  $V_{SRC} = 7.5 \text{ V}$ ;  $V_O = V_{SRC}/3 = 2.5 \text{ V}$

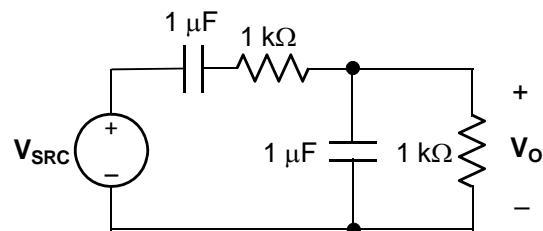**Version 5:**  $V_{SRC} = 9 \text{ V}$ ;  $V_O = V_{SRC}/3 = 3 \text{ V}$ .



4%

6. Two coils are wound on a core of high permeability. Coil 1 has 100 turns and coil 2 has 400 turns. A current of 1 A in coil 1, with coil 2 open circuited, produces a core flux of 0.5 mWb. Determine the magnitude of the core flux produced by a current of 0.8 A in coil 2, with coil 1 open circuited.

**Solution:** From the definition of mutual inductance,  $\frac{N_2\phi_{21}}{i_1} = \frac{N_1\phi_{12}}{i_2}$ , so that  $\phi_{12} = \frac{i_2}{i_1} \frac{N_2}{N_1} \phi_{21} =$

$$\frac{0.8}{1} \frac{400}{100} \phi_{21} = 3.2\phi_{21}.$$

**Version 1:**  $\phi_{21} = 0.5$  mWb;  $\phi_{12} = 3.2 \times 0.5 = 1.6$  mWb

**Version 2:**  $\phi_{21} = 0.6$  mWb;  $\phi_{12} = 3.2 \times 0.6 = 1.92$  mWb

**Version 3:**  $\phi_{21} = 0.7$  mWb;  $\phi_{12} = 3.2 \times 0.7 = 2.24$  mWb

**Version 4:**  $\phi_{21} = 0.8$  mWb;  $\phi_{12} = 3.2 \times 0.8 = 2.56$  mWb

**Version 5:**  $\phi_{21} = 0.9$  mWb;  $\phi_{12} = 3.2 \times 0.9 = 2.88$  mWb.


4%

7. Determine the stored **magnetic energy** under dc conditions, assuming  $V_{SRC} = 1$  V.

**Solution:** The branch containing the capacitor carries no current under dc conditions. The current in the other two branches is  $V_{SRC}/0.5$  A and the stored magnetic energy is  $W =$

$$\frac{1}{2} (L_1 I^2 + L_2 I^2 + 2MI^2) =$$

$$\frac{1}{2} \left( \frac{V_{SRC}}{0.5} \right)^2 (2 + 3 + 2 \times 1) = 14 V_{SRC}^2.$$

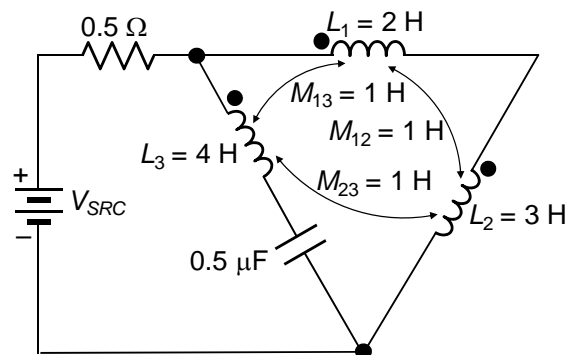

**Version 1:**  $V_{SRC} = 1$  V;  $W = 6 \times 1 = 14$  J

**Version 2:**  $V_{SRC} = 1.5$  V;  $W = 6 \times 2.25 = 13.5$  J

**Version 3:**  $V_{SRC} = 2$  V;  $W = 6 \times 4 = 24$  J

**Version 4:**  $V_{SRC} = 2.5$  V;  $W = 6 \times 6.25 = 37.5$  J

**Version 5:**  $V_{SRC} = 3$  V;  $W = 6 \times 9 = 54$  J.

4%

8. Given  $v_{SRC} = 6\cos\omega t$ , where  $\omega$  is unknown and  $k = 0.97$ . Determine  $X$  so that no power is dissipated in the circuit.

**Solution:** Considering mesh currents  $I_1$  and  $I_2$ , then for no power dissipation,  $I_2 = 0$ . The mesh-current equation for mesh 2 is:

$$-(j\omega M + jX)I_1 + (j40 + jX + 10)I_2 = 0$$

For  $I_2$  to be zero,  $\omega M + X = 0$ , or  $X = -\omega M = -\omega k\sqrt{L_1 L_2} = -k\sqrt{(\omega L_1)(\omega L_2)} = -k\sqrt{400} = -20k$ .

Alternatively, it follows from the T-equivalent circuit that if  $X = -\omega M$  the shunt branch will have zero impedance so  $I_2 = 0$ .

**Version 1:**  $k = 0.97$ ;  $X = -0.97 \times 20 = -19.4 \Omega$

**Version 2:**  $k = 0.96$ ;  $X = -0.96 \times 20 = -19.2 \Omega$

**Version 3:**  $k = 0.95$ ;  $X = -0.95 \times 20 = -19 \Omega$

**Version 4:**  $k = 0.94$ ;  $X = -0.94 \times 20 = -18.8 \Omega$

**Version 5:**  $k = 0.93$ ;  $X = -0.93 \times 20 = -18.6 \Omega$ .

4%

9. Determine  $Z_{in}$ , assuming  $R = 10 \Omega$ , and  $\omega = 1$  Mrad/s.

**Solution:**  $M = k\sqrt{L \times L} = 2 \mu\text{H}$ . It follows that the series branches of the T-equivalent circuit are zero and the

shunt branch is  $j\omega M = j2 \Omega$ ;  $-\frac{j}{\omega C} = -j$ . The parallel

impedance of  $j2$  and  $-j$  is  $\frac{2}{j2 - j} = -j2 \Omega$ .  $Z_{in} = R - j2$

$\Omega$ .





**Version 1:**  $R = 10 \Omega$ ;  $Z_{in} = 10 - j2 \Omega$

**Version 2:**  $R = 12 \Omega$ ;  $Z_{in} = 12 - j2 \Omega$

**Version 3:**  $R = 15 \Omega$ ;  $Z_{in} = 15 - j2 \Omega$

**Version 4:**  $R = 20 \Omega$ ;  $Z_{in} = 20 - j2 \Omega$

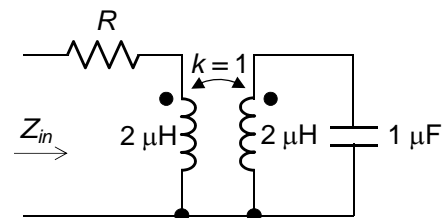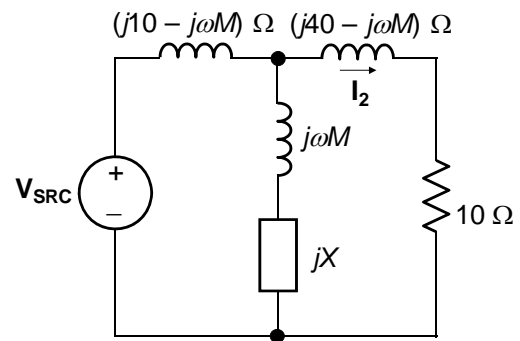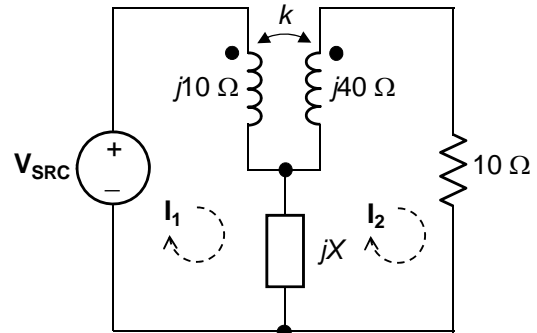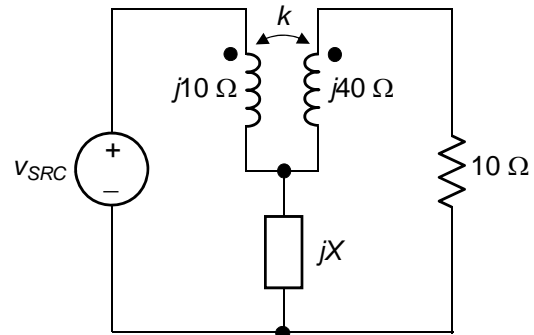**Version 5:**  $R = 22 \Omega$ ;  $Z_{in} = 22 - j2 \Omega$ .



4%


10. Determine the input admittance  $Y_{in}$  assuming  $Z_L = 10\angle 45^\circ \Omega$ .

**Solution:** It follows from the circuit shown that  $V_L = -2V_1$ , so that

$\frac{V_L}{V_1} = -2$ . Since the ideal autotransformer does not dissipate

power, and  $V_L = -2V_1$ ,  $V_L \times I_L = V_1 \times I_1$ ,  $\frac{I_L}{I_1} = -\frac{1}{2}$ . It follows that

$$Y_{in} = \frac{I_1}{V_1} = \frac{4}{Z_L} \text{ S.}$$

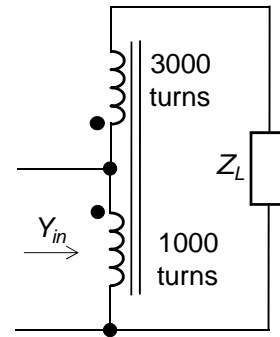


**Version 1:**  $Z_L = 10\angle 45^\circ \Omega$ ;  $Y_{in} \equiv \frac{4}{10\angle 45^\circ} = 0.4\angle -45^\circ \text{ S}$

**Version 2:**  $Z_L = 10\angle -45^\circ \Omega$ ;  $Y_{in} \equiv \frac{4}{10\angle -45^\circ} = 0.4\angle 45^\circ \text{ S}$

**Version 3:**  $Z_L = 20\angle 45^\circ \Omega$ ;  $Y_{in} \equiv \frac{4}{20\angle 45^\circ} = 0.2\angle -45^\circ \text{ S}$

**Version 4:**  $Z_L = 20\angle -45^\circ \Omega$ ;  $Y_{in} \equiv \frac{4}{20\angle -45^\circ} = 0.2\angle 45^\circ \text{ S}$

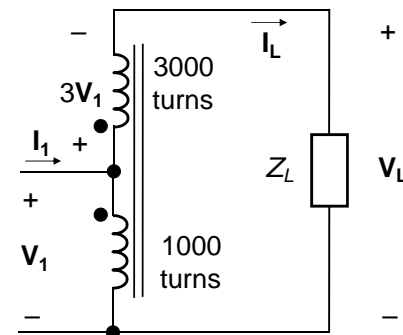**Version 5:**  $Z_L = 40\angle 45^\circ \Omega$ ;  $Y_{in} \equiv \frac{4}{40\angle 45^\circ} = 0.1\angle -45^\circ \text{ S.}$




20%

11. Determine  $Z_{Th}$  looking into terminals a and b.


**Solution-Method 1:** Apply a test voltage  $V_T$ , with the independent sources replaced by circuits. The secondary voltage is  $V_T$  and the

primary voltage is  $2V_T$ . The current through each capacitor is  $N_T/10$  as shown, so that the current in the short-circuit replacing the 2 V source is zero. For the ideal transformer,  $I_T = j2V_T/10$ . It follows that

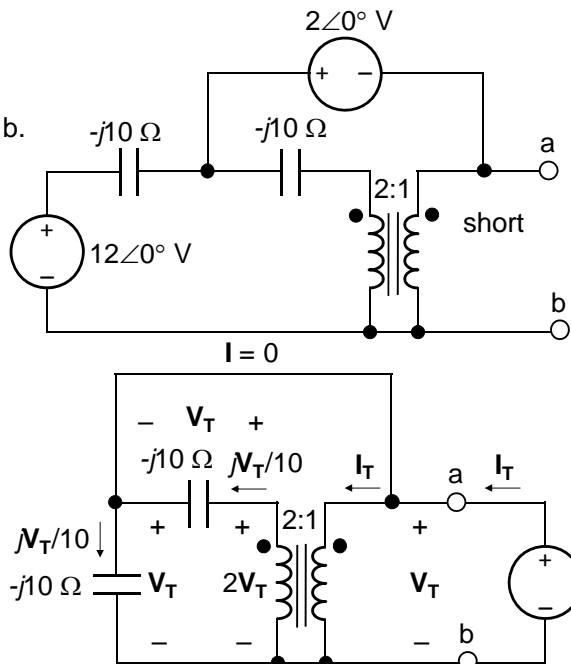
$$\frac{V_T}{I_T} = \frac{5}{j} = -j5 \Omega.$$



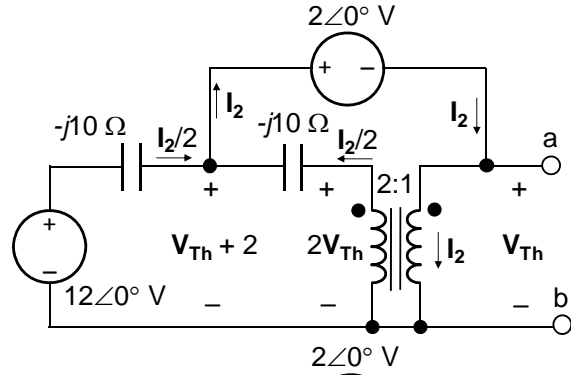*Method 2:* Under open circuit conditions, the currents and voltages will be as shown. The voltages across the two capacitors are of equal magnitude but opposite polarity. It follows that  $2V_{Th} = 12\text{ V}$ , and  $V_{Th} = 6\text{ V}$ .



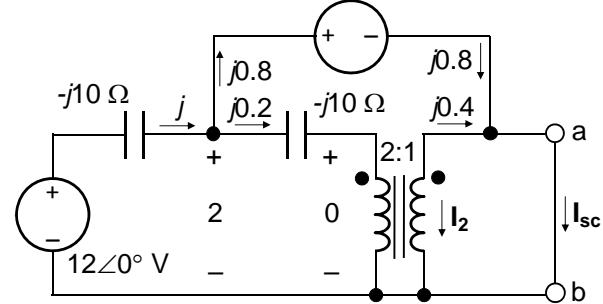Under open circuit conditions, the currents and voltages will be as shown. It follows that  $I_{SC} = j1.2\text{ A}$ . Hence,  $Z_{Th} = 6/j1.2 = -j5\ \Omega$ .




20%

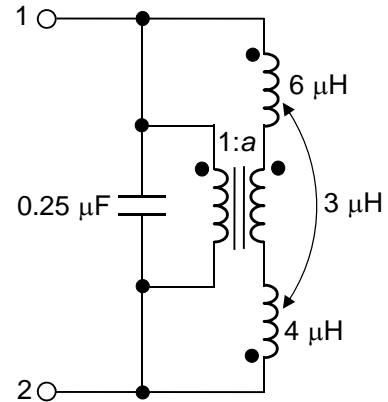12. Determine the turns ratio  $a$  so that Norton's admittance looking into terminals 1 and 2 is zero, assuming  $\omega = 1\text{ Mrad/s}$ .

**Solution-Method 1:** The impedances are:  $j\omega 6 = j6\ \Omega$ ,  $j\omega 4 = j4\ \Omega$ ,  $j\omega 3 = j3\ \Omega$ , and  $1/j\omega C = 1/(j10^6 \times 0.25 \times 10^{-6}) = -j4\ \Omega$ .

When a test source  $V_T$  is applied, the test current  $I_T$  should be zero. The voltages and currents in the circuit will be as shown.



From KVL in the branch containing the coupled coils,

$$V_T = j(6 - 3)I + aV_T + j(4 - 3)I = aV_T + j4I\text{ V,}$$

$$\text{or } (1 - a)V_T = j4I \quad (1)$$


From KCL at node 1,  $aI = I + \frac{V_T}{-j4}$ , or

$$\frac{V_T}{j4} = (1 - a)I \quad (2)$$


Dividing Equation 1 by Equation 2:

$$j4(1 - a) = \frac{j4}{(1 - a)}, (a - 1)^2 = 1; a = 1 \pm 1,$$


which gives  $a = 2$ .

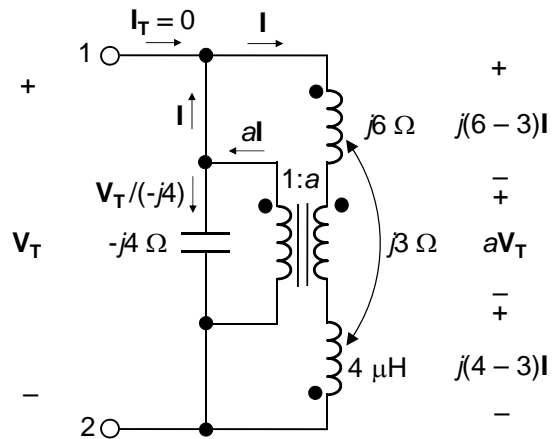

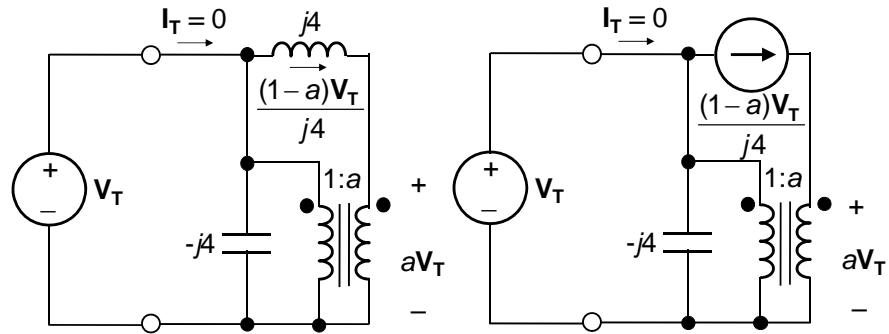Method 2: The circuit can be redrawn as shown, where the two coupled coils in series have been replaced by the equivalent



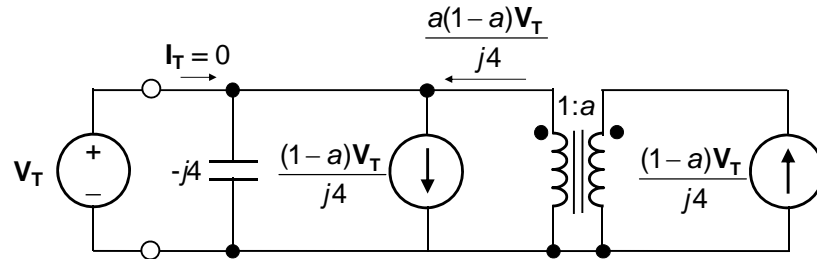inductance  $(j6 + j4 - j6) = j4 \Omega$ . This inductance carries a current  $\frac{(1-a)}{j4} V_T$  and can be replaced



by a current source of this value in accordance with the substitution theorem. This source can then be rearranged as two sources, as shown. From KCL,

$$\frac{a(1-a)}{j4} V_T = \frac{(1-a)}{j4} V_T + \frac{V_T}{-j4}, \quad a - a^2 = 1 - a - 1, \quad \text{which gives } a = 0 \text{ or } 2, \text{ so } a \text{ must equal } 2.$$

20%


13. Determine  $V_L$ .

**Solution-Method 1:** Derive TEC

at the primary terminals.  $V_x =$

$0.1V_x(5 + j5)$ , which gives  $V_x = 0$

and  $V_{TH} = 3 \text{ V}$ .

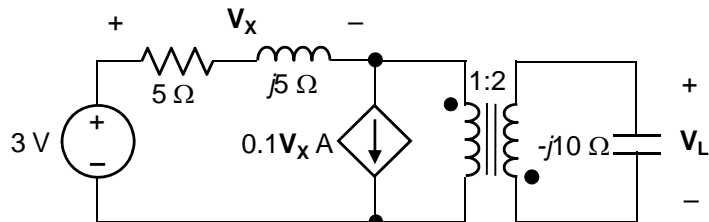


On short

circuit,  $V_x =$

$3 \text{ V}$  and  $3 \text{ V}$

$0.1 V_x = 0.3 \text{ A}$

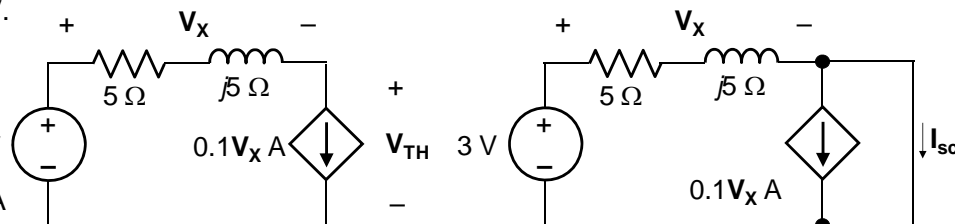


From KCL,

$$\frac{3}{5 + j5} = 0.3 + I_{SRC}$$

which gives,  $I_{SRC} = -$

$j0.3 \text{ A}$  and  $Z_{TH} =$
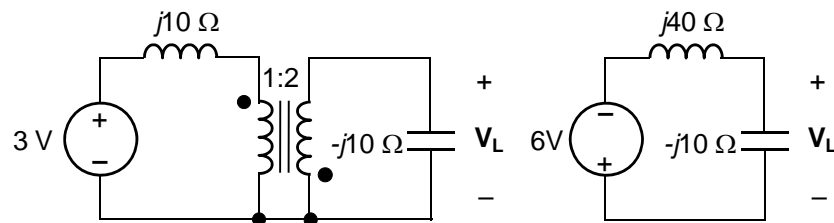
$$\frac{3}{-j0.3} = j10 \Omega. \text{ TEC}$$




becomes as shown. Reflecting this to the secondary, it follows from voltage division that

$$\mathbf{V}_L = -\frac{-j10}{j30} \times 6 = 2 \text{ V.}$$


*Method 2:* No reflections.

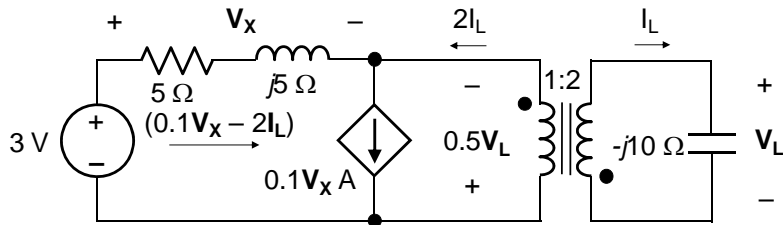The primary voltage and current will be as shown in the figure. From KCL, the current in the  $(5 + j5) \Omega$  impedance is  $(0.1\mathbf{V}_x - 2\mathbf{I}_L)$ ,




so that  $\mathbf{V}_x = (0.1\mathbf{V}_x - 2\mathbf{I}_L)(5 + j5)$  and  $\mathbf{I}_L = \mathbf{V}_L/(-j10) = j0.1\mathbf{V}_L$ . Substituting for  $\mathbf{I}_L$ ,  $\mathbf{V}_x = (0.1\mathbf{V}_x - j0.2\mathbf{V}_L)(5 + j5) = 0.5\mathbf{V}_x + j0.5\mathbf{V}_x - j(1 + j)\mathbf{V}_L$ , or,  $0.5(1 - j)\mathbf{V}_x = (1 - j)\mathbf{V}_L$ , which gives,  $\mathbf{V}_x = 2\mathbf{V}_L$ . From KVL on the primary side,  $0.5\mathbf{V}_L + 3 - \mathbf{V}_x = 0$ ; substituting for  $\mathbf{V}_x$ ,  $1.5\mathbf{V}_L = 3$  and  $\mathbf{V}_L = 2 \text{ V.}$

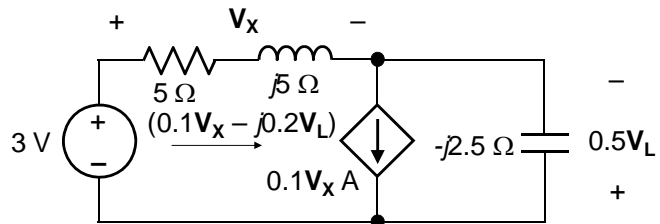*Method 3:* The capacitive branch is reflected to the primary side together with  $\mathbf{V}_L$ . From KCL, the current through the  $(5 + j5) \Omega$  impedance is  $0.1\mathbf{V}_x - 0.5\mathbf{V}_L/(-j2.5) = 0.1\mathbf{V}_x - j0.2\mathbf{V}_L$ ,



so that  $\mathbf{V}_x = (0.1\mathbf{V}_x - j0.2\mathbf{V}_L)(5 + j5) = (0.5\mathbf{V}_x - j\mathbf{V}_L)(1 + j) = 0.5\mathbf{V}_x + j0.5\mathbf{V}_x - j\mathbf{V}_L(1 + j)$ , or  $0.5(1 - j)\mathbf{V}_x = (1 - j)\mathbf{V}_L$ , which gives  $\mathbf{V}_x = 2\mathbf{V}_L$ . From KVL on the primary side,  $0.5\mathbf{V}_L + 3 - \mathbf{V}_x = 0$ ; substituting for  $\mathbf{V}_x$ ,  $1.5\mathbf{V}_L = 3$  and  $\mathbf{V}_L = 2 \text{ V.}$

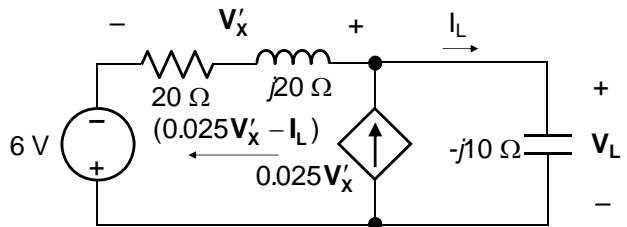*Method 4:* The primary circuit is reflected to the secondary side. The  $(5 + j5) \Omega$  is multiplied by 4. The source voltage and  $\mathbf{V}'_x$  are multiplied by 2 and reversed in



sign. To maintain the same dependency relation, with the dependent source still on the primary side,  $k$  is divided by 2 and reversed in sign. When reflected to the secondary side, this current source must be divided by 2. The overall effect is to divide  $k$  by 4 and reverse the sign of the current source as shown. It follows that  $\mathbf{V}'_x = (0.025\mathbf{V}'_x - \mathbf{I}_L)(20 + j20) = (0.5\mathbf{V}'_x - j2\mathbf{V}_L)(1 + j) = 0.5\mathbf{V}'_x + j0.5\mathbf{V}'_x + 2\mathbf{V}_L(1 - j)$ , or,  $0.5\mathbf{V}'_x(1 - j) = 2\mathbf{V}_L(1 - j)$ , which gives  $\mathbf{V}'_x = 4\mathbf{V}_L$ . From KVL,  $\mathbf{V}_L - \mathbf{V}'_x + 6 = 0$ . Substituting for  $\mathbf{V}'_x$ ,  $\mathbf{V}_L = 2 \text{ V.}$