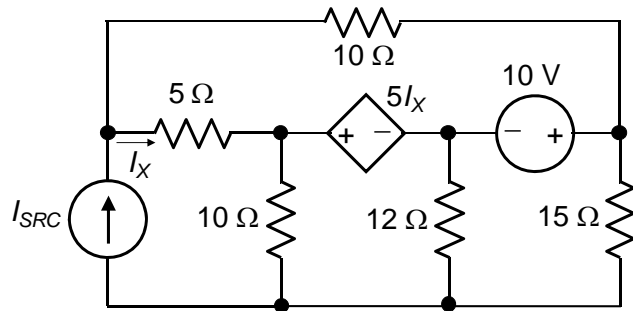


Final Exam – 2010-2011

3%

1. Determine I_X , assuming $I_{SRC} = 1$ A
(Hint: write one KVL equation and one KCL equation).

- A. 4 A
- B. 2 A
- C. 3 A
- D. 1 A
- E. 5 A



Solution: Let the current through the 10Ω resistor be I_Y . From KVL around the mesh abcda: $5I_X + 5I_X - 10 - 10I_Y = 0$, which gives, $I_Y = I_X - 1$. From KCL at node a, $I_{SRC} = I_Y + I_X$, or $I_{SRC} = 2I_X - 1$. It follows that $I_X = (I_{SRC} + 1)/2$.

Version 1: $I_{SRC} = 1$ A, $I_X = (1 + 1)/2 = 1$ A

Version 2: $I_{SRC} = 1.5$ A, $I_X = (1.5 + 1)/2 = 1.25$ A

Version 3: $I_{SRC} = 2$ A, $I_X = (2 + 1)/2 = 1.5$ A


Version 4: $I_{SRC} = 2.5$ A, $I_X = (2.5 + 1)/2 = 1.75$ A

Version 5: $I_{SRC} = 3$ A, $I_X = (3 + 1)/2 = 2$ A

3%

2. In the circuit shown, the capacitance absorbs -200 VAR. Determine the average power dissipated in R if $R = 5 \Omega$.

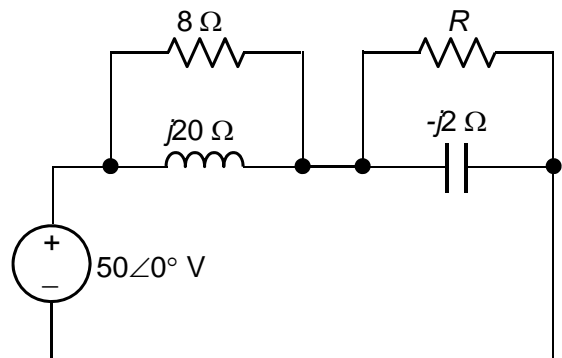- A. 57.1 W
- B. 80 W
- C. 44.4 W
- D. 66.7 W
- E. 50 W



Solution: $Q = -BV_{rms}^2$, where V_{rms} is the rms voltage across R and C , and $B = -1/X = 1/2$ S.

Substituting, $-200 = -\frac{1}{2}V_{rms}^2$, and $V_{rms} = 20$ V. It follows that $P_R = \frac{V_{rms}^2}{R}$.

Version 1: $R = 5 \Omega$, $P_R = \frac{400}{5} = 80$ W

Version 2: $R = 6 \Omega$, $P_R = \frac{400}{6} = 66.7$ W

Version 3: $R = 7 \Omega$, $P_R = \frac{400}{7} = 57.1 \text{ W}$


Version 4: $R = 8 \Omega$, $P_R = \frac{400}{8} = 50 \text{ W}$

Version 5: $R = 9 \Omega$, $P_R = \frac{400}{9} = 44.4 \text{ W}$

3%

3. Determine I_x assuming $I_{SRC} = j \text{ A}$.

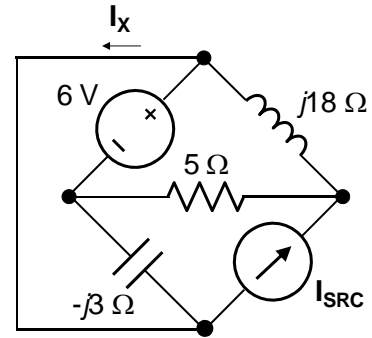- A. $j6 \text{ A}$
- B. $-j3 \text{ A}$
- C. $j3 \text{ A}$
- D. $-j6 \text{ A}$
- E. $j4 \text{ A}$



Solution: The voltage across the $-j3 \Omega$ capacitor is 6 V and

the current through this capacitor, directed upwards is $j2 \text{ A}$. It follows that $I_x = I_{SRC} + j2 \text{ A}$.

Version 1: $I_{SRC} = j \text{ A}$, $I_x = j + j2 = j3 \text{ A}$

Version 2: $I_{SRC} = j2 \text{ A}$, $I_x = j2 + j2 = j4 \text{ A}$

Version 3: $I_{SRC} = j3 \text{ A}$, $I_x = j3 + j2 = j5 \text{ A}$


Version 4: $I_{SRC} = j4 \text{ A}$, $I_x = j4 + j2 = j6 \text{ A}$

Version 5: $I_{SRC} = j5 \text{ A}$, $I_x = j5 + j2 = j7 \text{ A}$

3%

4. Determine the resistance between nodes a and b assuming that all resistances are 1Ω .

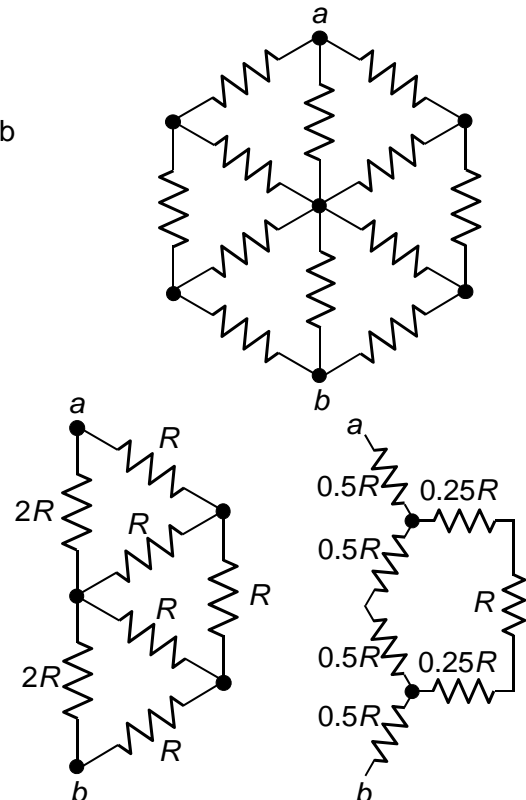- A. 4Ω
- B. 2.4Ω
- C. 3.2Ω
- D. 1.6Ω
- E. 0.8Ω



Solution: The resistances can be split into two halves in parallel, where the resistances in the middle become $2R$. Applying Δ -Y transformation,

the resistances become as shown. It follows that $2R_{ab} = 0.5R + R \parallel 1.5R + 0.5R = R + 0.6R = 1.6R$, so that $R_{ab} = 0.8R$.

Version 1: $R = 1 \Omega$, $R_{ab} = 0.8 \times 1 = 0.8 \Omega$

Version 2: $R = 2 \Omega$, $R_{ab} = 0.8 \times 2 = 1.6 \Omega$

Version 3: $R = 3 \Omega$, $R_{ab} = 0.8 \times 3 = 2.4 \Omega$

Version 4: $R = 4 \Omega$, $R_{ab} = 0.8 \times 4 = 3.2 \Omega$

Version 5: $R = 5 \Omega$, $R_{ab} = 0.8 \times 5 = 4 \Omega$

3%

5. Two coils are tightly coupled to a high-permeability core, so that the leakage flux is negligibly small. If coil 1 has 100 turns and an inductance of 10 mH, and the mutual inductance is 12.5 mH, determine the number of turns of coil 2.

- A. 125
- B. 250
- C. 150
- D. 175
- E. 200

Solution: From the definitions of self and mutual inductance, with negligible leakage flux,

$$L_1 = \frac{N_1 \phi_{21}}{i_1} \text{ and } M = \frac{N_2 \phi_{21}}{i_1}. \text{ It follows that } N_2 = \frac{M}{L_1} N_1 = 10M.$$

Version 1: $M = 12.5 \text{ mH}$, $N_2 = 10 \times 12.5 = 125 \text{ turns}$

Version 2: $M = 15 \text{ mH}$, $N_2 = 10 \times 15 = 150 \text{ turns}$

Version 3: $M = 17.5 \text{ mH}$, $N_2 = 10 \times 17.5 = 175 \text{ turns}$

Version 4: $M = 20 \text{ mH}$, $N_2 = 10 \times 20 = 200 \text{ turns}$

Version 5: $M = 22.5 \text{ mH}$, $N_2 = 10 \times 22.5 = 225 \text{ turns}$

3%

6. Determine the inductance of coil 2 of the preceding problem.

- A. 22.5 mH
- B. 30.63 mH
- C. 15.63 mH
- D. 40 mH
- E. 50.63 mH

Solution: Since the coils are tightly coupled to the core, $k = 1$, so that $M^2 = L_1 L_2$, or

$L_2 = \frac{M^2}{L_1} = 0.1M^2$ mH. It also follows from the solution of the preceding problem that

$$N_1 = \frac{M}{L_2} N_2. \text{ Dividing, } L_2 = L_1 \left(\frac{N_2}{N_1} \right)^2 = 0.1M^2$$

Version 1: $M = 12.5$ mH, $L_2 = 0.1 \times (12.5)^2 = 15.625$ mH

Version 2: $M = 15$ mH, $L_2 = 0.1 \times (15)^2 = 22.5$ mH

Version 3: $M = 17.5$ mH, $L_2 = 0.1 \times (17.5)^2 = 30.625$ mH

Version 4: $M = 20$ mH, $L_2 = 0.1 \times (20)^2 = 40$ mH

Version 5: $M = 22.5$ mH, $L_2 = 0.1 \times (22.5)^2 = 50.625$ mH

3%

7. A D'Arsonval movement has a resistance of $R \Omega$ and a full-scale deflection of $100 \mu\text{A}$.

Determine the shunt resistance that will result in a full-scale deflection of $150 \mu\text{A}$, assuming $R = 50 \Omega$.

- A. 150Ω
- B. 200Ω
- C. 300Ω
- D. 100Ω
- E. 250Ω

Solution: At full-scale deflection, the voltage drop across the movement and shunt is $(R \Omega) \times (100 \mu\text{A}) = 100R \mu\text{V}$. The shunt has to pass $50 \mu\text{A}$, so its resistance is $R_{\text{shunt}} = 100R/50 = 2R \Omega$.

Version 1: $R = 50 \Omega$, $R_{\text{shunt}} = 2 \times 50 = 100 \Omega$

Version 2: $R = 75 \Omega$, $R_{\text{shunt}} = 2 \times 75 = 150 \Omega$

Version 3: $R = 100 \Omega$, $R_{\text{shunt}} = 2 \times 100 = 200 \Omega$

Version 4: $R = 125 \Omega$, $R_{\text{shunt}} = 2 \times 125 = 250 \Omega$

Version 5: $R = 150 \Omega$, $R_{\text{shunt}} = 2 \times 150 = 300 \Omega$

3%

8. When a 9950Ω resistance is connected in series with a D'Arsonval movement of unknown resistance and full-scale deflection current, a voltage of 1 V across the series combination gives a certain full-scale deflection. If an additional $10,000 \Omega$ is connected in series with the combination, 2 V are required for full-scale deflection. Determine the resistance of the D'Arsonval movement.

- A. 150 Ω
- B. 100 Ω
- C. 75 Ω
- D. 125 Ω
- E. 50 Ω

Solution: Let the resistance of the movement be R_m , its FSD current be I_{FSD} , and the FSD voltage with series resistance be V_{FSD} . Then $I_{FSD}(R + R_m) = V_{FSD}$, and $I_{FSD}(10,000 + R + R_m) = 2V_{FSD}$. It follows that $R + R_m = 10,000$, or $R_m = 10,000 - R$.

Version 1: $R = 9950 \Omega$, $R_m = 10,000 - 9950 = 50 \Omega$

Version 2: $R = 9925 \Omega$, $R_m = 10,000 - 9925 = 75 \Omega$

Version 3: $R = 9900 \Omega$, $R_m = 10,000 - 9900 = 100 \Omega$


Version 4: $R = 9875 \Omega$, $R_m = 10,000 - 9875 = 125 \Omega$

Version 5: $R = 9850 \Omega$, $R_m = 10,000 - 9850 = 150 \Omega$

3%

9. Determine L_{eq} if $L = 1$ H.

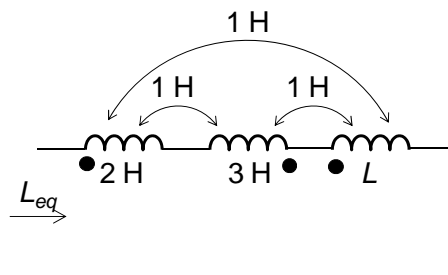- A. 6 H
- B. 4 H
- C. 8 H
- D. 7 H
- E. 5 H



Solution: Consider that a voltage V is applied, causing a current I to flow. $V = j\omega I[(2 - 1 + 1) + (3 - 1 - 1) + (L + 1 - 1)]$; $L_{eq} = 3 + L$.

Version 1: $L = 1$ H, $L_{eq} = 4$ H

Version 2: $L = 2$ H, $L_{eq} = 5$ H

Version 3: $L = 3$ H, $L_{eq} = 6$ H


Version 4: $L = 4$ H, $L_{eq} = 7$ H

Version 5: $L = 5$ H, $L_{eq} = 8$ H.

3%

10. Determine V_{Th} , assuming $V_{SRC} = 1\angle 0^\circ$ V

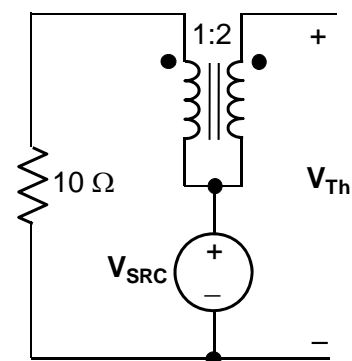- A. $-1\angle 0^\circ$ V
- B. $1\angle 0^\circ$ V
- C. $-2\angle 0^\circ$ V
- D. $2\angle 0^\circ$ V
- E. $4\angle 0^\circ$ V



Solution: On open circuit, no current flows. The primary voltage is V_{SRC} as shown, and $V_{\text{Th}} = -V_{\text{SRC}}$.


Version 1: $V_{\text{SRC}} = 1\angle 0^\circ \text{ V}$, $V_{\text{Th}} = -1\angle 0^\circ \text{ V}$

Version 2: $V_{\text{SRC}} = 2\angle 0^\circ \text{ V}$, $V_{\text{Th}} = -2\angle 0^\circ \text{ V}$

Version 3: $V_{\text{SRC}} = 3\angle 0^\circ \text{ V}$, $V_{\text{Th}} = -3\angle 0^\circ \text{ V}$

Version 4: $V_{\text{SRC}} = 4\angle 0^\circ \text{ V}$, $V_{\text{Th}} = -4\angle 0^\circ \text{ V}$

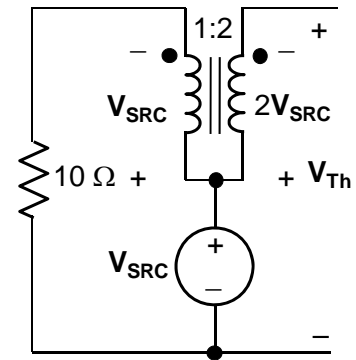Version 5: $V_{\text{SRC}} = 5\angle 0^\circ \text{ V}$, $V_{\text{Th}} = -5\angle 0^\circ \text{ V}$




3%

11. Determine Z_L for maximum average power delivered to it if $R = 5 \Omega$ and $I_x = k\angle -45^\circ$

where $k = \sqrt{2} \text{ A rms}$.

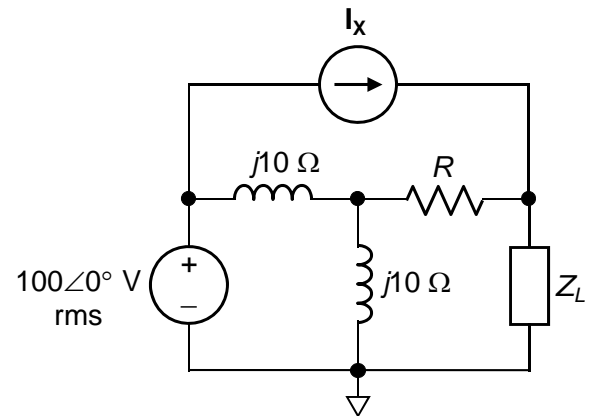- A. $10 + j10 \Omega$
- B. $5 + j5 \Omega$
- C. $5 - j5 \Omega$
- D. $10 - j10 \Omega$
- E. $15 - j15 \Omega$



Solution: Z_{Th} is $(R + j5) \Omega$. Hence, Z_L for maximum power transfer is $(R - j5) \Omega$.

Version 1: $R = 5 \Omega$, $Z_{L_{\text{max}}} = (5 - j5) \Omega$

Version 2: $R = 6 \Omega$, $Z_{L_{\text{max}}} = (6 - j5) \Omega$

Version 3: $R = 7 \Omega$, $Z_{L_{\text{max}}} = (7 - j5) \Omega$

Version 4: $R = 8 \Omega$, $Z_{L_{\text{max}}} = (8 - j5) \Omega$

Version 5: $R = 9 \Omega$, $Z_{L_{\text{max}}} = (9 - j5) \Omega$

3%

12. Determine the maximum average power delivered to Z_L in Problem 11, assuming that $R = 5 \Omega$ and I_x is as in Problem 11.

- A. 90 W
- B. 200 W
- C. 320 W
- D. 180 W
- E. 245 W

Solution: V_{Th} as seen by Z_L is determined from superposition as $\frac{j10}{j10 + j10} \times 100\angle 0^\circ +$

$$(5 + j10 \parallel j10)I_x = 50\angle 0^\circ + 5(1 + j)I_x = 50\angle 0^\circ + (5\sqrt{2}\angle 45^\circ) \times k\angle -45^\circ = 50 + 5\sqrt{2}k;$$

$$P_{L_{max}} = \frac{(50 + 5\sqrt{2}k)^2}{4R_{Th}} = \frac{(50 + 5\sqrt{2}k)^2}{20}$$

Version 1: $k = \sqrt{2}$ A, $P_{L_{max}} = \frac{(50 + 5\sqrt{2} \times \sqrt{2})^2}{20} = \frac{(60)^2}{20} = 180$ W

Version 2: $k = 2\sqrt{2}$ A, $P_{L_{max}} = \frac{(50 + 5\sqrt{2} \times 2\sqrt{2})^2}{20} = \frac{(70)^2}{20} = 245$ W


Version 3: $k = 3\sqrt{2}$ A, $P_{L_{max}} = \frac{(50 + 5\sqrt{2} \times 3\sqrt{2})^2}{20} = \frac{(80)^2}{20} = 320$ W

Version 4: $k = 4\sqrt{2}$ A, $P_{L_{max}} = \frac{(50 + 5\sqrt{2} \times 4\sqrt{2})^2}{20} = \frac{(90)^2}{20} = 405$ W

Version 5: $k = 5\sqrt{2}$ A, $P_{L_{max}} = \frac{(50 + 5\sqrt{2} \times 5\sqrt{2})^2}{20} = \frac{(100)^2}{20} = 500$ W

3%

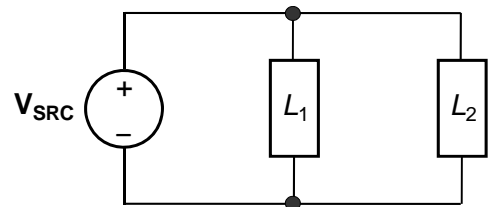13. Load L_1 absorbs 15 kVA at 0.6 p.f. lagging, whereas Load L_2 absorbs 4.8 kW at 0.8 p.f. leading. If $V_{SRC} = 200\angle 0^\circ$ V rms at $f = 50$ Hz, determine the capacitor that must be connected in parallel with L_1 and L_2 to have maximum magnitude of current through the source.



- A. 0.67 mF
- B. 0.55 mF
- C. 0.34 mF
- D. 0.46 mF
- E. 1.24 mF

Solution: The reactive power absorbed by L_1 is 15×0.8 kVAR = 12 kVAR, whereas the reactive power absorbed by L_2 is $-\frac{4.8}{0.8} \times 0.6 = -3.6$ kVAR. For maximum magnitude of source current, the p.f. should be unity. The capacitor must add a reactive power of $-(12 - 3.6) = -8400$ VAR. hence, $-8400 = -\omega C \times |V_{SRC}|^2$, or $C = \frac{8400}{100\pi |V_{SRC}|^2} = \frac{84}{\pi |V_{SRC}|^2}$.

Version 1: $|V_{\text{SRC}}| = 200 \text{ V}$, $C = \frac{84}{\pi(200)^2} \equiv 0.67 \text{ mF}$

Version 2: $|V_{\text{SRC}}| = 220 \text{ V}$, $C = \frac{84}{\pi(220)^2} \equiv 0.55 \text{ mF}$

Version 3: $|V_{\text{SRC}}| = 240 \text{ V}$, $C = \frac{84}{\pi(240)^2} \equiv 0.46 \text{ mF}$

Version 4: $|V_{\text{SRC}}| = 260 \text{ V}$, $C = \frac{84}{\pi(260)^2} \equiv 0.40 \text{ mF}$

Version 5: $|V_{\text{SRC}}| = 280 \text{ V}$, $C = \frac{84}{\pi(280)^2} \equiv 0.34 \text{ mF}$

3%


14. A periodic current is shown, where over a period,

$$i = 6 + A \sin 2t \quad 0 \leq t \leq \pi$$

$$i = -4 + A \sin 2(t - \pi) \quad \pi \leq t \leq 2\pi$$

Determine the rms value of i if $A = 1 \text{ A}$.

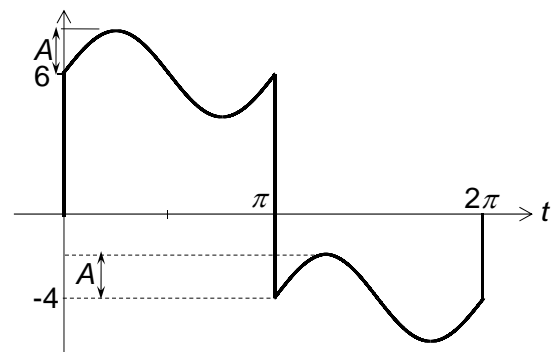- A. 5.83 A
- B. 5.15 A
- C. 6.20 A
- D. 5.29 A
- E. 5.52 A



Solution: The waveform consists of three components: i) a dc component of 1 A, ii) a square wave of 5 V amplitude, and iii) a sinusoidal wave of amplitude A . It follows that the

rms value is $I = \sqrt{1^2 + 5^2 + A^2 / 2} = \sqrt{26 + A^2 / 2} \text{ A}$

Version 1: $A = 1$; $I = \sqrt{26 + A^2 / 2} = \sqrt{26.5} = 5.15 \text{ A}$

Version 2: $A = 2$; $I = \sqrt{26 + A^2 / 2} = \sqrt{28} = 5.29 \text{ A}$

Version 3: $A = 3$; $I = \sqrt{26 + A^2 / 2} = \sqrt{30.5} = 5.52 \text{ A}$

Version 4: $A = 4$; $I = \sqrt{26 + A^2 / 2} = \sqrt{34} = 5.83 \text{ A}$

Version 5: $A = 5$; $I = \sqrt{26 + A^2 / 2} = \sqrt{38.5} = 6.20 \text{ A}$.

3%

15. The current waveform of the preceding problem is applied to a 2Ω resistor in parallel with a very large capacitor. Determine the voltage across the parallel combination.

- A. 2.5 V
- B. 2 V
- C. 3 V
- D. 4 V
- E. 3.5 V

Solution: The ac voltage will be negligibly small. The dc voltage is the dc component of current multiplied by R , or $V = 1 \times R$.

Version 1: $R = 2 \Omega$; $V = R = 2 \text{ V}$

Version 2: $R = 2.5 \Omega$; $V = R = 2.5 \text{ V}$

Version 3: $R = 3 \Omega$; $V = R = 3 \text{ V}$

Version 4: $R = 3.5 \Omega$; $V = R = 3.5 \text{ V}$


Version 5: $R = 4 \Omega$; $V = R = 4 \text{ V}$

11%

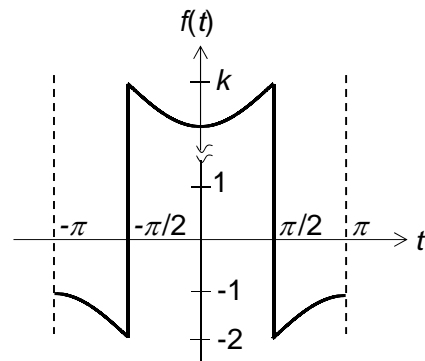16. The period of a periodic function $f(t)$ is defined as:

$$\begin{aligned} f(t) &= \cos(t + \pi) - 2, & -\pi < t < -\pi/2 \\ f(t) &= -\cos(t) + k, & -\pi/2 < t < +\pi/2 \\ f(t) &= \cos(t - \pi) - 2, & \pi/2 < t < \pi \end{aligned}$$

Derive the trigonometric Fourier series expansion of $f(t)$, assuming $k = 3$.



Solution:

$$a_0 = \frac{1}{\pi} \left[\int_{-\pi}^{-\pi/2} (-\cos t + k) dt + \int_{-\pi/2}^{\pi/2} (\cos(t - \pi) - 2) dt \right] =$$

$$\frac{1}{\pi} \left[k \int_{-\pi/2}^{\pi/2} dt - 2 \int_{-\pi/2}^{\pi/2} dt - \int_{-\pi}^{-\pi/2} \cos t dt - \int_{\pi/2}^{\pi} \cos t dt \right] = \frac{1}{\pi} \left[k \int_{-\pi/2}^{\pi/2} dt - 2 \int_{-\pi/2}^{\pi/2} dt \right] = \frac{1}{\pi} \left[\frac{k\pi}{2} - \pi \right] = \frac{k}{2} - 1.$$

$$a_n = \frac{2}{\pi} \left[\int_{-\pi}^{-\pi/2} (-\cos t + k) \cos ntdt + \int_{-\pi/2}^{\pi/2} (\cos(t - \pi) - 2) \cos ntdt \right] =$$

$$\frac{2}{\pi} \left[- \int_{-\pi}^{-\pi/2} \cos t \cos ntdt + \int_{-\pi/2}^{\pi/2} k \cos ntdt - \int_{\pi/2}^{\pi} 2 \cos ntdt \right] =$$

$$\frac{2}{\pi} \left[- \frac{1}{2} \int_{-\pi}^{\pi} \cos(n-1)t dt - \frac{1}{2} \int_{-\pi}^{\pi} \cos(n+1)t dt + k \int_{-\pi/2}^{\pi/2} \cos ntdt - 2 \int_{\pi/2}^{\pi} \cos ntdt \right] =$$

$$- \frac{1}{\pi} \left[\frac{\sin(n-1)t}{n-1} + \frac{\sin(n+1)t}{n+1} \right]_{-\pi}^{\pi} + \frac{2k}{n\pi} [\sin nt]_{-\pi/2}^{\pi/2} - \frac{4}{n\pi} [\sin nt]_{\pi/2}^{\pi} =$$

$$0 - 0 + \frac{2k}{n\pi} \sin \frac{n\pi}{2} - 0 - 0 + \frac{4}{n\pi} \sin \frac{n\pi}{2} = \frac{2(k+2)}{n\pi} \sin \frac{n\pi}{2}. a_n \text{ is zero for even values, and the}$$

odd harmonics alternate in sign. Thus,

$$f(t) = \left(\frac{k}{2} - 1\right) \frac{1}{2} + \frac{2(k+2)}{\pi} \left(\cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t - \frac{1}{7} \cos 7t + \dots \right)$$

Version 1: $k = 3$, $f(t) = \frac{1}{2} + \frac{10}{\pi} \left(\cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t - \frac{1}{7} \cos 7t + \dots \right)$

Version 2: $k = 4$, $f(t) = 1 + \frac{12}{\pi} \left(\cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t - \frac{1}{7} \cos 7t + \dots \right)$

Version 3: $k = 5$, $f(t) = \frac{3}{2} + \frac{14}{\pi} \left(\cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t - \frac{1}{7} \cos 7t + \dots \right)$

Version 4: $k = 6$, $f(t) = 2 + \frac{16}{\pi} \left(\cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t - \frac{1}{7} \cos 7t + \dots \right)$


Version 5: $k = 7$, $f(t) = \frac{5}{2} + \frac{18}{\pi} \left(\cos t - \frac{1}{3} \cos 3t + \frac{1}{5} \cos 5t - \frac{1}{7} \cos 7t + \dots \right)$

11%

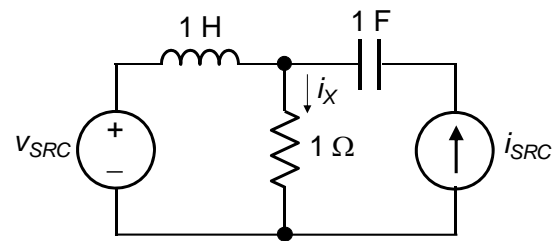17. Given $v_{SRC} = \cos t$ V and $i_{SRC} = \sin 2t$ A.

6% (a) Derive the expression for i_X in the time domain.

5% (b) Determine the power dissipated in the resistor.



Solution: (a) Let the amplitude of v_{SRC} and i_{SRC} be K . With the current source replaced by an

open circuit, $\mathbf{I}_{x1} = \frac{K \angle 0^\circ}{1} \frac{1}{1+j} = \frac{K}{2} (1-j)$; $i_{x1} = \frac{K}{\sqrt{2}} \cos(t - 45^\circ)$ A. With the current source

replaced by a short circuit, $\mathbf{I}_{x2} = K \angle 0^\circ \frac{j2}{1+j2} = \frac{2K}{\sqrt{5}} \angle (90^\circ - \tan^{-1} 2)$; $i_{x2} = \frac{2K}{\sqrt{5}} \sin(2t + 26.57^\circ)$

A. Hence, $i_X = \frac{K}{\sqrt{2}} \cos(t - 45^\circ) + \frac{2K}{\sqrt{5}} \sin(2t + 26.57^\circ)$ A.

(b) Power dissipated is $P = \frac{1}{2} \left(\frac{K^2}{2} + \frac{4K^2}{5} \right) = 0.65K^2$ W.

Version 1: $K = 1$, $0.71 \cos(t - 45^\circ) + 0.89 \sin(2t + 26.57^\circ)$ A, $P = 0.65$ W

Version 2: $K = 2$, $1.14 \cos(t - 45^\circ) + 1.79 \sin(2t + 26.57^\circ)$ A, $P = 2.60$ W

Version 3: $K = 3$, $2.12 \cos(t - 45^\circ) + 2.68 \sin(2t + 26.57^\circ)$ A, $P = 5.85$ W

Version 4: $K = 4$, $2.83 \cos(t - 45^\circ) + 3.58 \sin(2t + 26.57^\circ)$ A, $P = 10.4$ W

Version 5: $K = 5$, $3.54 \cos(t - 45^\circ) + 4.47 \sin(2t + 26.57^\circ)$ A, $P = 16.25$ W

11%


18. Given the circuit shown, with $a = 1$.

3% (a) Determine the current in the capacitor

2% (b) Replace the capacitor by a current source, in accordance with the substitution theorem


3% (c) Rearrange the current source as two current sources across the transformer windings

3% (d) Determine I_{SRC} .

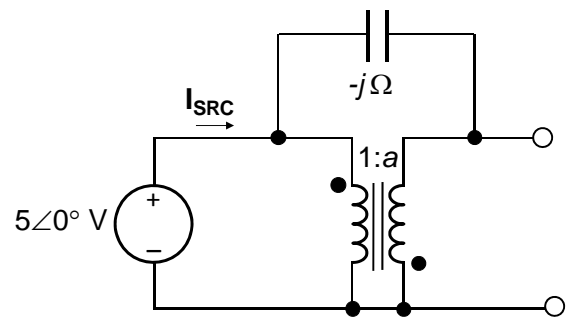


Solution: (a) The voltage across the capacitor is $5(1 + a)$ V. The current through the capacitor is $j\sqrt{5}(1 + a)$ A directed from primary to secondary.

(b)

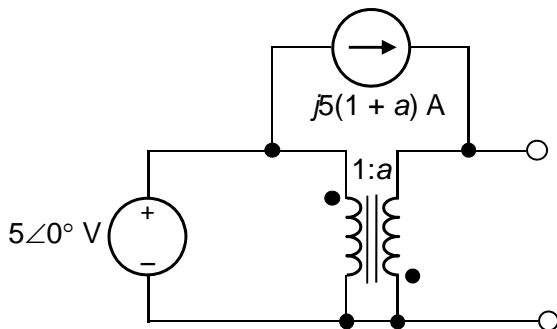

(c)

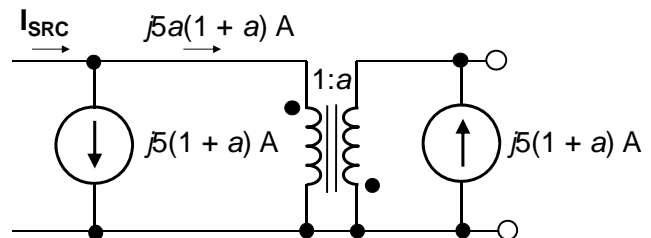

(d) It follows that $I_{\text{SRC}} = j\sqrt{5}(a + 1)^2$ A.

Version 1: $a = 2$, $I_{\text{SRC}} = j\sqrt{5}(2 + 1)^2 = j45$ A

Version 2: $a = 3$, $I_{\text{SRC}} = j\sqrt{5}(3 + 1)^2 = j80$ A

Version 3: $a = 4$, $I_{\text{SRC}} = j\sqrt{5}(4 + 1)^2 = j125$ A


Version 4: $a = 5$, $I_{\text{SRC}} = j\sqrt{5}(5 + 1)^2 = j180$ A

Version 5: $a = 6$, $I_{\text{SRC}} = j\sqrt{5}(6 + 1)^2 = j245$ A

11%

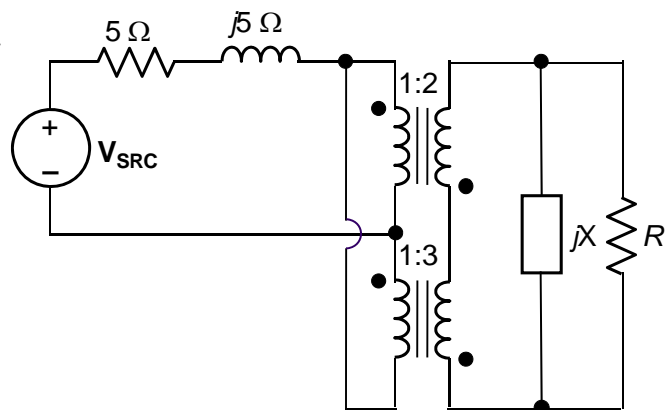19. Determine X and R for maximum power transfer to R and calculate this power.

Assume $V_{\text{SRC}} = 4\angle 0^\circ$ V rms.



Solution: On open circuit, $V_{TH} = V = V_{SRC}$. On

short circuit, $V = 0$ and $I_N = I = \frac{V_{SRC}}{5(1+j)}$. $Y_N =$

$\frac{1}{5(1+j)} = 0.1(1-j)$ S. For maximum power

transfer, $G_L = 0.1$ S, or $R = 10 \Omega$, and $B = 0.1$ S, or $X = -10 \Omega$.

Under conditions of maximum power

transfer, the current in R is $0.5|I_N| = \frac{0.5|V_{SRC}|}{10}$

and the power transferred is $\frac{0.25|V_{SRC}|^2}{10} =$

$\frac{|V_{SRC}|^2}{40}$ W.



Version 1: $V_{SRC} = 4\angle 0^\circ$ rms, $P = \frac{16}{40} = 0.4$ W

Version 2: $V_{SRC} = 5\angle 0^\circ$ rms, $P = \frac{25}{40} = 0.625$ W

Version 3: $V_{SRC} = 6\angle 0^\circ$ rms, $P = \frac{36}{40} = 0.9$ W

Version 4: $V_{SRC} = 7\angle 0^\circ$ rms, $P = \frac{49}{40} = 1.225$ W

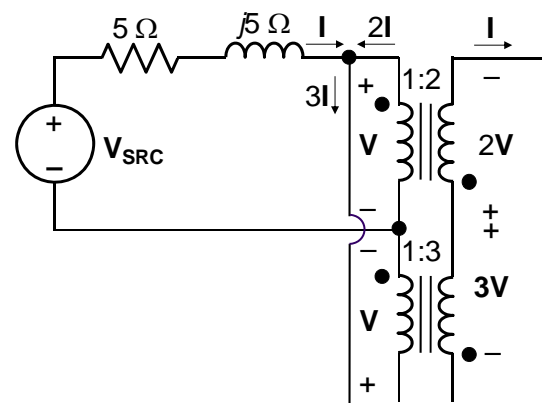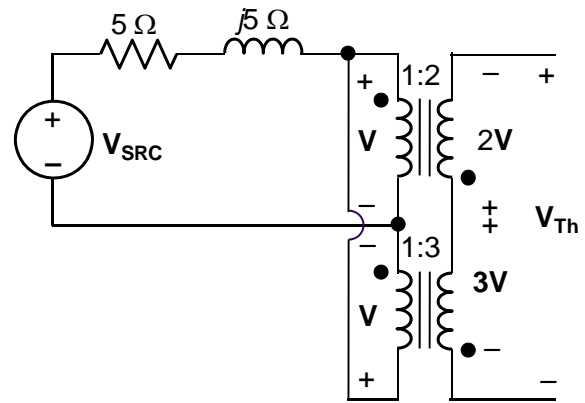Version 5: $V_{SRC} = 8\angle 0^\circ$ rms, $P = \frac{64}{40} = 1.6$ W.



11%

20. Determine the complex power delivered by each


source given that $V_{SRC} = 5\cos\omega t$, $I_{SRC} = -2\sin\omega t$,

and assuming $Z_L = k(1-j)$ where $k = 1$.

Solution: The currents and voltages are as shown.

Equating mmfs: $100 \times 2\angle 90^\circ + 200I_L = 0$, or $j2 = -2I_L$, and $I_L = -j$ A, $I_1 = I_L - j2 = -j3$ A.

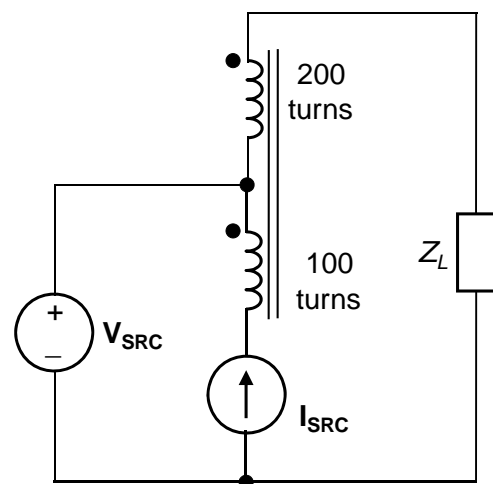$V_L = Z_L I_L = -jk(1-j) = -k(1+j)$ V. $V_2 = V_L - 5 = -(k+5) - jk$. $V_1 = V_2/2 = -(k+5)/2 - jk/2$ V. $V_1 = 5 - V_1 = (15+k)/2 + jk/2$ V.



Power delivered by voltage source = $S_v = \frac{V_{SRC}}{\sqrt{2}} \frac{I_1^*}{\sqrt{2}} = \frac{1}{2}(5)(j3) = \frac{j15}{2}$ VA

Power delivered by current source $S_I =$

$$\frac{V_1}{\sqrt{2}} \frac{I_{SRC}^*}{\sqrt{2}} = \frac{1}{2} \left(\frac{15+k}{2} + \frac{jk}{2} \right) (-j2) = \frac{1}{2} (k - j(15+k)) \text{ VA}$$

Total power delivered by sources =

$$\frac{1}{2} (j15 + k - j15 - jk) = \frac{k}{2} (1 - j)$$

As a check, $S_L =$

$$\frac{V_{Lm}}{\sqrt{2}} \frac{I_{Lm}^*}{\sqrt{2}} = \frac{1}{2} (-jk(1-j))(j) = \frac{k}{2} (1-j) \text{ VA.}$$

Version 1: $k = 1$, $S_v = j7.5 \text{ VA}$; $S_I = 0.5 - j8 \text{ VA}$

Version 2: $k = 2$, $S_v = j7.5 \text{ VA}$; $S_I = 1 - j8.5 \text{ VA}$

Version 3: $k = 3$, $S_v = j7.5 \text{ VA}$; $S_I = 1.5 - j9 \text{ VA}$

Version 4: $k = 4$, $S_v = j7.5 \text{ VA}$; $S_I = 2 - j9.5 \text{ VA}$

Version 5: $k = 5$, $S_v = j7.5 \text{ VA}$; $S_I = 2.5 - j10 \text{ VA}$

