

Homework 9

P7.1.4 An impedance $4 + j4 \, \Omega$ is connected in parallel with an impedance $12 + j16 \, \Omega$. If the total reactive power absorbed is 2500 VAR, what is the total real power absorbed? Verify your answer by working in terms of the overall impedance and admittance.

Solution P7.1.4

$$Z = (4 + j4)(12 + j16)/(16 + j20) = 3.024 + j3.22 \, \Omega.$$

$$Q = |I|^2 X, \text{ and } P = |I|^2 R, \text{ so that } P = 2500R/X = 2348 \, \text{W}.$$

$$Y = \frac{1}{4 + j4} + \frac{1}{12 + j16} = 0.155 - j0.165 \, \text{S}; \quad Q = -|V|^2 B, \text{ and } P = |V|^2 G, \text{ so that } P = -2500G/B = 2348 \, \text{W}.$$

P7.1.5

Determine C in Figure P7.1.5 if the capacitor absorbs 5 VAR and the frequency is 50Hz. Derive the power absorbed by C from conservation of power in the circuit.

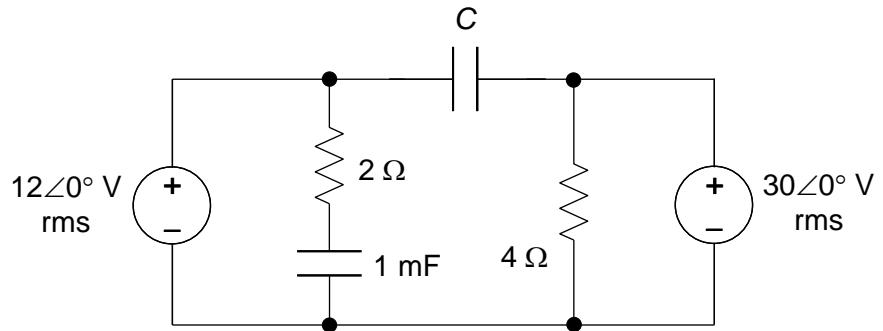


Figure P7.1.5

Solution P7.1.5

Voltage across C is 18 V.

Hence, $\omega C|V|^2 = 5$, which gives $C = 49.1 \mu\text{F}$.

$$I_C = j\omega C(12 - 30) = -j5/18 \text{ A.}$$

For the 1 mF capacitor, $X = -1/(100\pi \times 10^{-3}) =$

$$-10/\pi, I_1 = \frac{12}{2 + jX} = 1.70 + j2.70 \text{ A.}$$

Hence, $I_{\text{SRC1}} = I_1 + I_C = 1.70 + j2.43 \text{ A};$

$$I_{\text{SRC2}} = 7.5 - I_C = 7.5 + j0.28 \text{ A.}$$


Complex power delivered by 12 V source: $S_{\text{SRC1}} = 12 I_{\text{SRC1}}^* = 20.38 - j29.1 \text{ VA};$

complex power delivered by 30 V source: $S_{\text{SRC2}} = 30 I_{\text{SRC2}}^* = 225 - j8.33 \text{ VA};$

complex power absorbed by capacitive branch: $S_1 = 12 I_1^* = 20.38 - j32.43 \text{ VA};$

power absorbed by resistive branch is $900/4 = 225 \text{ W}.$

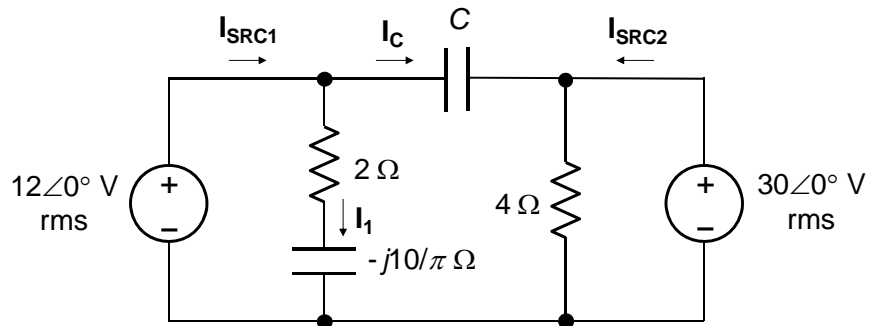Power absorbed by capacitor is $S_{\text{SRC1}} + S_{\text{SRC2}} - S_1 - 225 = -j5 \text{ VAR}.$



P7.1.6 Determine R and the rms magnitude of \mathbf{V}_{SRC} in Figure P7.1.6, given that each resistor absorbs 2 W and $\omega = 1,000$ rad/s.

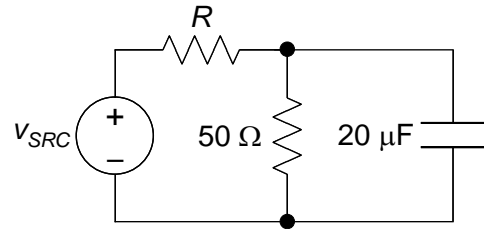


Figure P7.1.6

Solution P7.1.6

$$\frac{1}{\omega C} = \frac{1}{10^3 \times 20 \times 10^{-6}} = 50 \Omega.$$

Since the 50Ω resistor absorbs 2 W, $\frac{|V_L|^2}{50} = 2$,

$$|V_L| = 10 \text{ V rms};$$

reactive power absorbed by capacitor is

$$-\frac{|V_L|^2}{50} = -2 \text{ VAR};$$


complex power absorbed by parallel capacitive branch is $2 - j2$ VA;

current through R is $\mathbf{I}_{\text{SRC}} = (2 + j2)/10 = 0.2 + j0.2 = 0.2\sqrt{2}\angle 45^\circ$ A rms.

Since the power dissipated in R is 2 W, $R = 2/(0.04 \times 2) = 25 \Omega$.

Complex power delivered by source is $4 - j2 = \mathbf{V}_{\text{SRC}}(0.2 - j0.2)$;
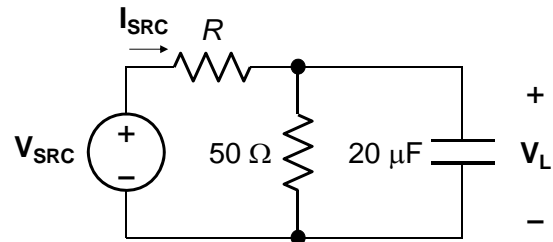
$$\text{hence, } \mathbf{V}_{\text{SRC}} = \frac{4 - j2}{0.2 - j0.2} = 15 + j5 = 5\sqrt{10}\angle 18.4^\circ \text{ V rms.}$$



P7.1.9 Determine the complex power delivered by \mathbf{V}_{SRC1} and \mathbf{V}_{SRC2} in Figure P7.1.9 given that L_1 absorbs 4 kW at a power factor of 0.6 lagging, L_2 absorbs 3 kW at a power factor of 0.6 leading, and the complex power absorbed by L_3 is $12 + j5$ kVA. Assume that $\mathbf{V}_{\text{SRC1}} = 400\angle 0^\circ$ V rms and $\mathbf{V}_{\text{SRC2}} = 400\angle 90^\circ$ V rms.

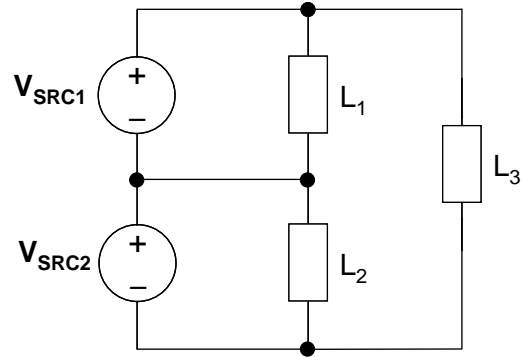


Figure P7.1.9

Solution P7.1.9

$$S_1 = 4 + j \frac{4 \times 0.8}{0.6} = 4 + j16/3 \text{ kVA};$$

$$S_2 = 3 - j \frac{3 \times 0.8}{0.6} = 3 - j4 \text{ kVA}; \quad S_3 = 12 + j5 \text{ kVA};$$

$$S_1 = 400 I_1^*, \quad S_2 = j400 I_2^*, \quad S_3 = 400(1 + j) I_3^*.$$

$$\text{It follows that } \mathbf{I}_1 = \frac{4 - j16/3}{400} \times 1000 =$$

$$10 - j40/3 \text{ A};$$

$$\mathbf{I}_2 = \frac{3 + j4}{-j400} \times 1000 = -10 + j7.5 \text{ A};$$

$$\mathbf{I}_3 = \frac{12 - j5}{400(1 - j)} \times 1000 = 21.25 + j8.75 \text{ A};$$


$$\mathbf{I}_{\text{SRC1}} = \mathbf{I}_1 + \mathbf{I}_3 = 31.25 - j4.58;$$

$$\mathbf{I}_{\text{SRC2}} = \mathbf{I}_2 + \mathbf{I}_3 = 11.25 + j16.25 \text{ A};$$

$$\text{hence, } S_{\text{SRC1}} = 400(31.25 + j4.58)/1000 = 12.5 + j1.83 \text{ kVA};$$

$$S_{\text{SRC2}} = j400(11.25 - j16.25)/1000 = 6.5 + j4.5 \text{ kVA}.$$
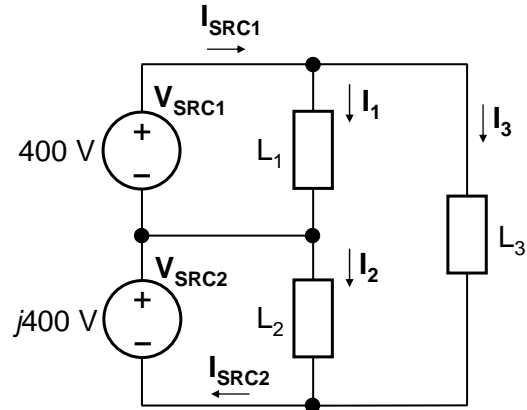
$$\text{As a check, } S_{\text{SRC1}} + S_{\text{SRC2}} = 19 + j19/3 = S_1 + S_2 + S_3.$$



P7.1.11 In Figure P7.1.11, find the instantaneous power, the real power, and reactive power delivered by the source, given that

$$v_{SRC} = 10 \cos 10^6 t.$$

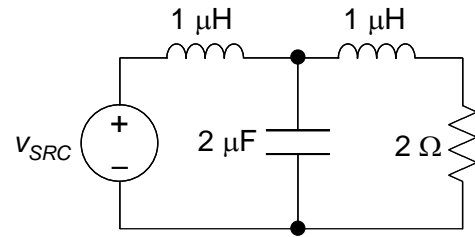


Figure P7.1.11

Solution P7.1.11


$$\omega L = 1 \, \Omega; \quad 1/\omega C = 0.5 \, \Omega;$$

$$\mathbf{I} = \frac{10}{j + (-j \cdot 0.5) \parallel (j + 2)} = 5 - j20 = 20.62 \angle -76^\circ \equiv$$

$$20.62 \cos(10^6 t - 76^\circ) \text{ A.}$$

The instantaneous power is $206.2(\cos 10^6 t) \cos(10^6 t - 76^\circ) = 103.1[\cos(76^\circ) + \cos(2 \times 10^6 t - 76^\circ)] \text{ VA}$.

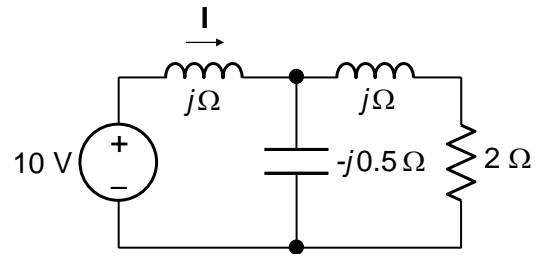The complex power is $10(5 + j20)/2 = 103.1 \angle 76^\circ \text{ VA}$ in terms of rms values, so that the real power is $103.1 \cos(76^\circ) = 25 \text{ W}$ and the reactive power is $103.1 \sin(76^\circ) = 100 \text{ VAR}$.



P7.2.9 Determine Z_L in Figure P7.2.9 that makes it absorb maximum power and calculate this power.


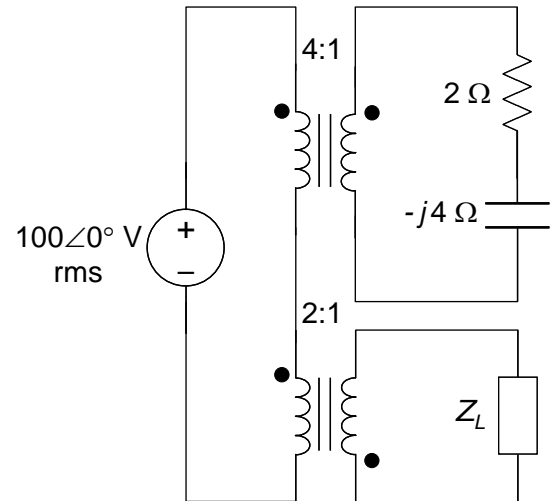


Figure P7.2.9

Solution P7.2.9

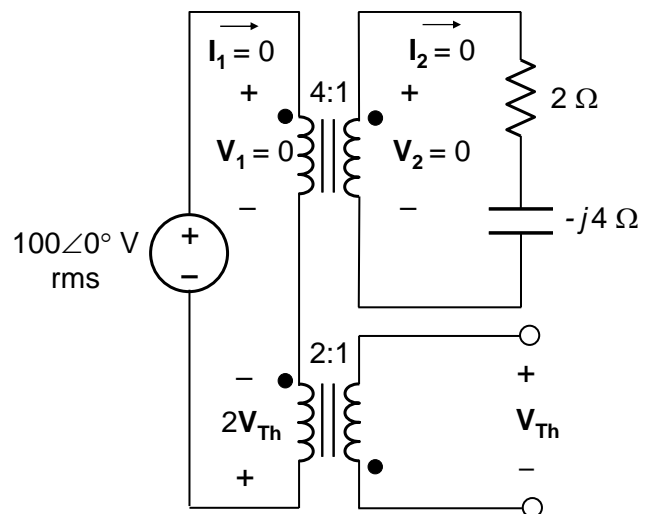On open circuit, $I_1 = 0$, so that $I_2 = 0$, $V_2 = 0$, and $V_1 = 0$. It follows that $2V_{Th} = -100$ V, and $V_{Th} = -50$ V.




On short circuit, $V_3 = 0$; hence, $4V_2 = 100$, and

$$V_2 = 25 \text{ V}; 4I_1 = \frac{25}{2 - j4}, \text{ and } I_{sc} = -2I_1 =$$

$$\frac{-25}{4(1 - j2)}. \text{ Hence } Z_{Th} = 8(1 - j2) \Omega.$$

It follows that for maximum power transfer, $Z_{Lm} = 8(1 + j2) \Omega$. $|I_{Lm}| = 50/16$ A, and $R_{Lm}|I_{Lm}|^2 = 8(50/16)^2 = 78.125$ W.

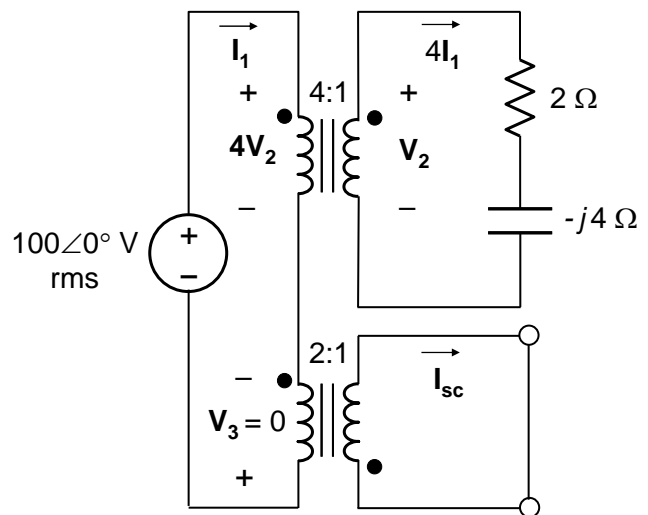

P7.2.13 Determine Z_L in Figure P7.2.13 that will absorb maximum power and calculate this power.

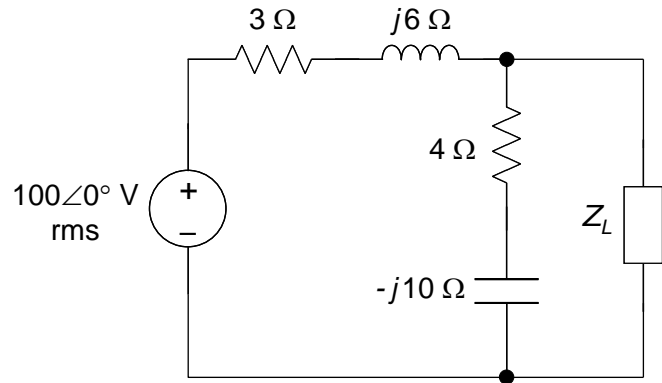


Figure P7.2.13

Solution P7.2.13

If Z_L is removed, the open-circuit voltage is: $\mathbf{V}_{Th} = \frac{4 - j10}{7 - j4} \times 100 = \frac{68 - j54}{65} \times 100 = 104.6 - j83.08 = 133.6 \angle -38.5^\circ \text{ V}.$

If the voltage source is set to zero, $\mathbf{Z}_{Th} = \frac{(3 + j6)(4 - j10)}{7 - j4} = 8.123 + j3.785 \Omega.$

Hence for maximum power transfer, $\mathbf{Z}_{Lm} = 8.123 - j3.785 \Omega.$

The maximum power transferred is $(V_{Th})^2 / 4R_{Lm} = (133.6)^2 / (4 \times 8.123) = 549.2 \text{ W}.$