

Homework 10

P7.2.16 R_L in Figure P7.2.16 is restricted to the range 1 to 8 Ω . Determine the value of R_L that results in maximum power transfer to it and calculate the value of this power.

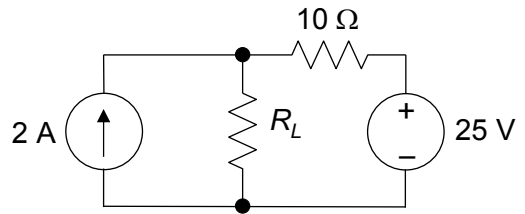


Figure P7.2.16

Solution P7.2.16

If R_L is removed, and superposition applied, it follows that $V_{Th} = 25 + 2 \times 10 = 45$ V.

When both sources are set to zero, $R_{Th} = 10$ Ω .

Maximum power is transferred to R_L if R_L is closest to this value, i.e., $R_L = 8$ Ω .

Under these $I_L = 45/18 = 2.5$ A, and the power dissipated in R_L is $(2.5)^2 \times 8 = 50$ W.

P7.2.20 (a) Assuming $B = 30 \text{ S}$, determine the turns ratio a in Figure P7.2.20 so that

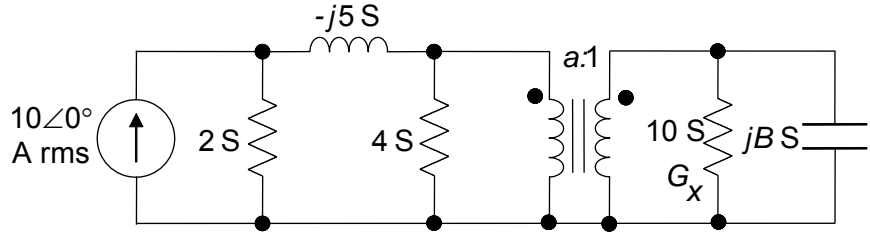


Figure 7.2.20

maximum power is absorbed in the 10 S resistor and calculate this power. (b) Assuming $a = 2$ and $G_x = 10 \text{ S}$, determine B that results in maximum power absorption in G_x and calculate this power. (c) Assuming $a = 2$ and $B = 15 \text{ S}$, determine G_x that results in maximum power absorption in this resistor and calculate this power. (d) Assuming $a = 2$ and G_x and B are variable, determine G_x and B that will result in maximum power absorption in G_x and calculate this power.

Solution P7.2.20

We first derive NEC of the circuit connected to the primary side.

$$I_N = \frac{-j5}{2-j5} \times 10 = \frac{50}{29}(5-j2) = 9.285\angle-21.8^\circ \text{ A};$$

$$Y_N = 4 - \frac{j10}{2-j5} = \frac{166}{29} - j\frac{20}{29} = 5.766\angle-6.87^\circ \Omega.$$

(a) Reflected to the secondary, Y_N is multiplied by a^2 ; $|Y_x| = |10 + j30| \Omega$. Hence $a = \sqrt{\frac{10\sqrt{10}}{5.766}} = 2.34$.

$$\text{Assuming this value of } a, |V_L| = \frac{|aI_N|}{2|Y_x|} = \frac{2.34 \times 50 / \sqrt{29}}{2 \times 10\sqrt{10}} = 0.344 \text{ V};$$

$$\text{power dissipated in } Y_x = (0.344)^2 \times 10 = 1.18 \text{ W}.$$

(b) When $a = 2$, NEC reflected to the secondary becomes $\frac{100}{29}(5-j2) \text{ A}$ in parallel with $Y_N =$

$$\frac{664}{29} - j\frac{80}{29} \text{ S};$$

$$\text{maximum power is transferred when } B = \frac{80}{29} \text{ S. } |V_L| = \frac{100}{\sqrt{29}} \times \frac{1}{(10 + 664/29)} = 0.565 \text{ V};$$

$$\text{power dissipated in } Y_x = (0.565)^2 \times 10 = 3.19 \text{ W}.$$

$$(c) \quad G_x = \sqrt{(664/29)^2 + (15 - 80/29)^2} = 25.96 \text{ S};$$

$$|V_L| = \frac{100}{\sqrt{29}} \times \frac{1}{\sqrt{(G_x + 664/29)^2 + (15 - 80/29)^2}} = 0.369 \text{ V};$$

$$\text{power dissipated} = (0.369)^2 \times 25.96 = 3.53 \text{ W}.$$

$$(d) \text{ In this case } G_x = \frac{664}{29} \text{ S and } B = \frac{80}{29} = 2.76 \text{ S}.$$

$$|V_L| = \frac{100}{\sqrt{29 \times 2 \times (664/29)}} = 0.406 \text{ V}; \text{ power dissipated} = (0.406)^2 \times 22.9 = 3.77 \text{ W}.$$

P7.3.3 In Figure 7.3.3, the voltmeter has a full-scale reading of 800 V and a 1mA/100 mV D'Arsonval movement. Determine the % error in the reading of the voltmeter.

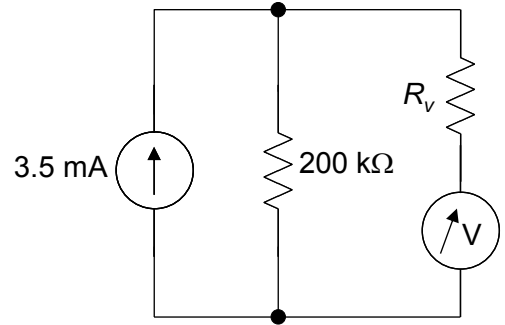


Figure P7.3.3

Solution P7.3.3

The total resistance of the voltmeter is

$\frac{800 \text{ V}}{1 \text{ mA}} = 800 \text{ k}\Omega$. The current through the voltmeter is

$3.5 \times \frac{200}{1000} = 0.7 \text{ mA}$. The meter reading is $800 \times \frac{0.7}{1} = 560 \text{ V}$. The true reading is $3.5 \times 200 = 700$

V. The percentage error is $\left(\frac{560 - 700}{700} \right) \times 100 = -20\%$.

P7.3.5 A series resistance is used with a 100 μA /100 Ω D'Arsonval movement to make it read 1000 V full scale. The meter, including the series resistance, is to be converted to a voltmeter that reads 400 V full scale. Determine the resistance required.

Solution P7.3.5

To read 1000 V the total resistance is $(1000 \text{ V})/(0.1 \text{ mA}) = 10 \text{ M}\Omega$. The series resistance is $R_{s1} = 10 \text{ M}\Omega - 100 \Omega$. To read 400 V, the total resistance in series with the meter should be $(400 \text{ V})/(0.1 \text{ mA}) = 4 \text{ M}\Omega$. The series resistance should be $R_{s2} = 4 \text{ M}\Omega - 100 \Omega$. The resistance that must be connected in parallel with R_{s1} is $\frac{1}{1/R_{s2} - 1/R_{s1}} = 6,666,433 \Omega$.

P7.3.6 A shunt is used with a 100 μA /100 Ω D'Arsonval movement to make it read 1 mA full scale. The meter, including the shunt, is to be converted to a voltmeter that reads 500 V full scale. Determine the series resistance required.

Solution P7.3.6

The meter with the shunt becomes a 1 mA meter, the combined resistance being $(10 \text{ mV})/(1 \text{ mA}) = 10 \Omega$.

To read 500 V, the total resistance must be $(500 \text{ V})/(1 \text{ mA}) = 500 \text{ k}\Omega$.

The resistance that must be added is $500 \text{ k}\Omega - 10 \text{ }\Omega = 499,990 \text{ }\Omega$.

P7.3.7 A $50 \text{ }\mu\text{A}/100 \text{ }\Omega$ meter is converted to a voltmeter that reads 20 V full scale by adding a series resistance R_v . (a) Determine R_v . This same resistance is added in series with a $100 \text{ }\mu\text{A}/100 \text{ }\Omega$ meter. (b) Determine the full-scale reading of the resulting voltmeter. (c) The two voltmeters are connected in series across a voltage supply as shown in Figure P7.3.7. What should be the values of R_1 and R_2 if each voltmeter is to read full scale, with the current from the supply being $200 \text{ }\mu\text{A}$?

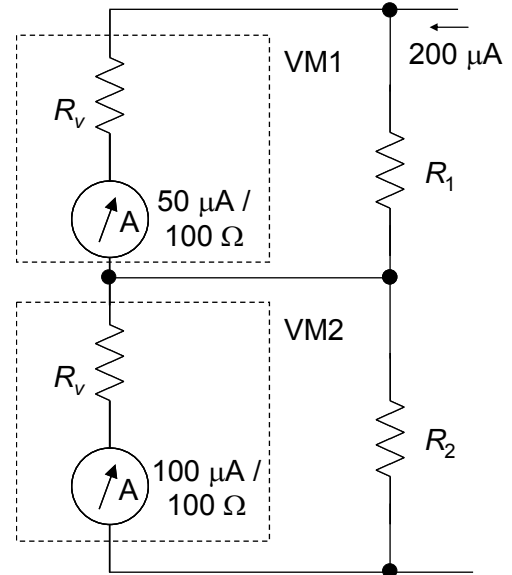


Figure P7.3.7

Solution P7.3.7

(a) $R_v = \frac{20 \text{ V}}{50 \text{ }\mu\text{A}} - 100 = 399,900 \text{ }\Omega$.

(b) When this resistance is added in series with a $100 \text{ }\mu\text{A}/100 \text{ }\Omega$ meter, the total resistance is $400 \text{ k}\Omega$. The FSD is therefore $100 \text{ }\mu\text{A} \times 400 \text{ k}\Omega = 40 \text{ V}$.

(c) When the voltmeters connected as required, $R_1 = \frac{20 \text{ V}}{150 \text{ }\mu\text{A}} = \frac{400}{3} \text{ k}\Omega$ and $R_2 = \frac{40 \text{ V}}{100 \text{ }\mu\text{A}} = 0.4$

$\text{M}\Omega$.