

## Homework 2

**P1.3.6** The triangular voltage waveform of Figure P1.3.6 is applied to a  $100\ \Omega$  resistor. Determine: (a) the resistor current, (b) instantaneous power

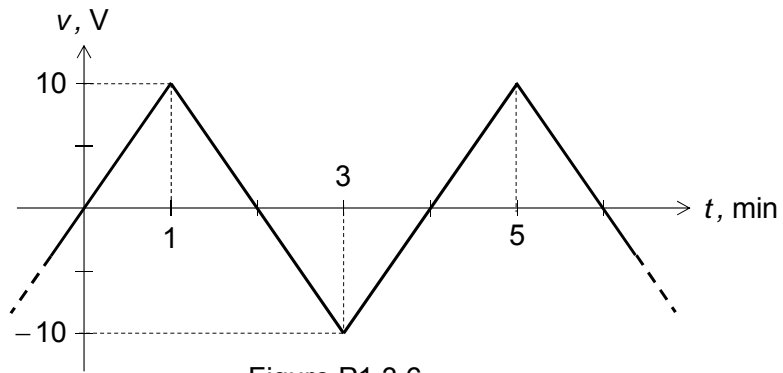


Figure P1.3.6

dissipation in the resistor, and (c) the average power dissipation. Is the statement 'the average power in a resistor is the product of the average voltage across the resistor and the average current through the resistor' valid? Justify your answer.

### Solution P1.3.6

$$v = 10t\text{ V}, 0 \leq t \leq 1\text{ min};$$

$$v = -10t + 20\text{ V}, 1 \leq t \leq 3\text{ min};$$

$$v = 10t - 40\text{ V}, 3 \leq t \leq 4\text{ min}.$$

$$(a) \ i = \frac{v}{100} = 0.1t\text{ A}, 0 \leq t \leq 1\text{ min};$$

$$i = -0.1t + 0.2\text{ A}, 1 \leq t \leq 3\text{ min};$$

$$i = 0.1t - 0.4\text{ A}, 3 \leq t \leq 4\text{ min}.$$

$$(b) \ p = \frac{v^2}{R} = t^2\text{ W}, 0 \leq t \leq 1\text{ min};$$

$$p = \frac{(-10t + 20)^2}{100} = (t - 2)^2\text{ W}, 1 \leq t \leq 3\text{ min};$$

$$p = \frac{(10t - 40)^2}{100} = (t - 4)^2\text{ W}, 3 \leq t \leq 4\text{ min}.$$

$$(c) \ P = \frac{1}{T} \int_0^T p dt = \frac{1}{4} \left[ \int_0^1 t^2 dt + \int_1^3 (t^2 - 4t + 4) dt + \int_3^4 (t^2 - 8t + 16) dt \right]$$

$$= \frac{1}{4} \left\{ \left[ \frac{t^3}{3} \right]_0^1 + \left[ \frac{t^3}{3} - 2t^2 + 4t \right]_1^3 + \left[ \frac{t^3}{3} - 4t^2 + 16t \right]_3^4 \right\}$$

$$= \frac{1}{4} \left\{ \frac{1}{3} + \frac{2}{3} + \frac{1}{3} \right\} = \frac{1}{3}\text{ W}.$$

The following should be noted:

1. The integral is in  $V \times I \times \text{min}$ . When divided by  $T$  in min, the result is in W.
2. The area under each quarter of a cycle is the same, which means that the average is the same. Hence the average can be determined from the first quarter cycle:

$$P = \frac{1}{1} \int_0^1 t^2 dt = \left[ \frac{t^3}{3} \right]_0^1 = \frac{1}{3} \text{ W.}$$

3. If  $t$  is converted to seconds, then  $v$  during the first quarter cycle is  $v = \frac{10t}{60} = \frac{t}{6} \text{ V}$ ,

$$i = \frac{t}{600} \text{ A}, p = \frac{t^2}{3600} \quad 0 \leq t \leq 60 \text{ s};$$

$$P = \frac{1}{60} \int_0^{60} \frac{t^2}{3600} dt = \frac{1}{60^3} \left[ \frac{t^3}{3} \right]_0^{60} = \frac{1}{3} \text{ W.}$$

- (d)  $V_{avg} = 0$ , since the waveform is symmetrical about the horizontal axis. This makes  $I_{avg} = 0$  as well. Thus,  $V_{avg} \times I_{avg} = 0$ , whereas  $P \neq 0$ . The average power in a resistor is not the product of the average voltage across the resistor and the average current through the resistor, because power, being the product of voltage and current, is a nonlinear quantity. The product of a negative voltage and a negative current is positive power, which contributes to the average power

**P1.3.9** The voltage shown in Figure P1.3.9 is applied across a  $5\ \Omega$  resistor. (a) Determine  $p$ ,  $0 \leq t \leq 1\text{ min}$ ; (b) the energy dissipated in the resistor at  $t = 3\text{ min}$ .

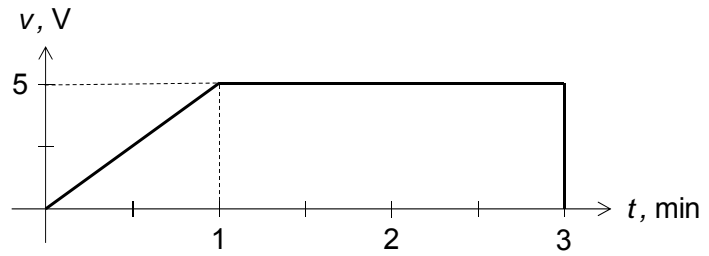


Figure P1.3.9

**Solution P1.3.9**

$$v\text{ (V)} = \begin{cases} t/12 & 0 \leq t \leq 60\text{ s} \\ 5 & 60 \leq t < 180\text{ s} \\ 0 & t > 180\text{ s} \end{cases}$$

(a)  $0 \leq t \leq 60\text{ s}$ ;  $p = \frac{v^2}{R} = \frac{1}{5} \left( \frac{t}{12} \right)^2 = \frac{t^2}{720}\text{ W}$ , where  $t$  is in s.

(b)  $w = \int_0^{180} p dt = \int_0^{60} \frac{t^2}{720} dt + \int_{60}^{180} \frac{25}{5} dt = 700\text{ J}$ .

**P1.4.12** The triangular voltage pulse of Figure P1.4.12 is applied to a  $0.1\mu\text{F}$  capacitor that is initially uncharged. Plot as function of time: (a) the charge on the capacitor; (b) the energy stored in the capacitor, as derived from Equation 1.8.4, (c) the capacitor current; (d) the instantaneous power input to the capacitor. How is the energy stored in (b) related to the instantaneous power in (d)?


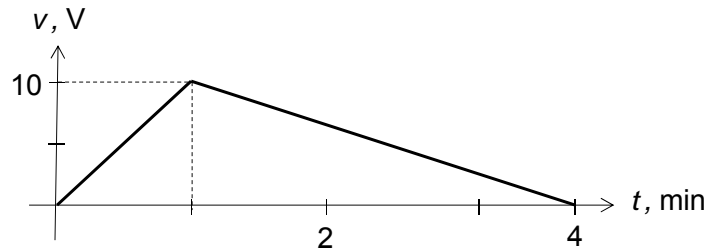


Figure P1.4.12

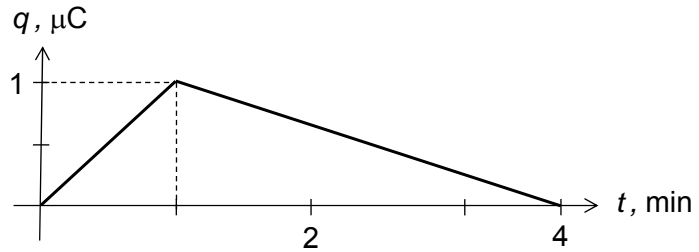
**Solution P1.4.12**

$$v = \frac{t}{6} \text{ V}, 0 \leq t \leq 60 \text{ s}; v = -\frac{t}{18} + \frac{40}{3} \text{ V}, 60 \leq t \leq 240 \text{ s}; v = 0, t \geq 240 \text{ s}.$$


$$\begin{aligned} \text{(a) } q &= Cv = \frac{t}{60} \mu\text{C}, 0 \leq t \leq 60 \text{ s}; \\ &= -\frac{t}{180} + \frac{4}{3} \mu\text{C}, 60 \leq t \leq 240 \text{ s}; \\ &= 0, t \geq 240 \text{ s}. \end{aligned}$$


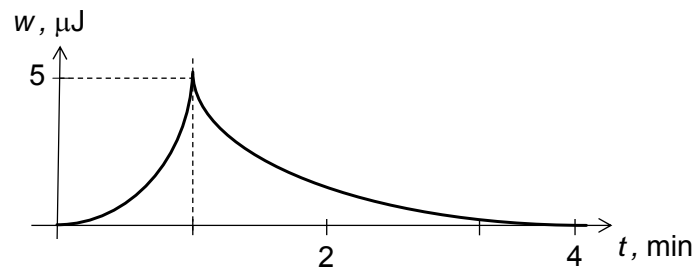
$$\begin{aligned} \text{(b) } w &= \frac{1}{2} qv = \frac{t^2}{720} \mu\text{J}, 0 \leq t \leq 60 \text{ s}; \\ &= \frac{1}{180} \left( \frac{t^2}{36} - \frac{40t}{3} + 1600 \right) \mu\text{J}, \\ &\quad 60 \leq t \leq 240 \text{ s}; \\ &= 0, t \geq 240 \text{ s}. \end{aligned}$$


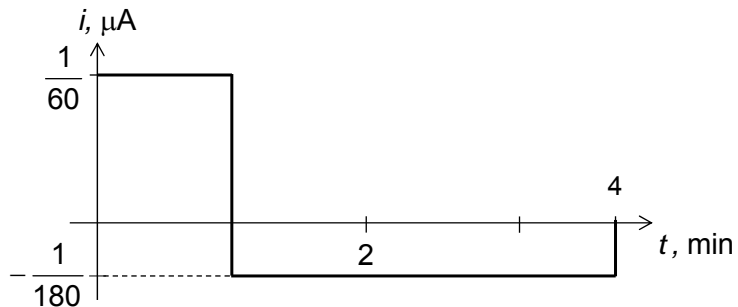
$$\begin{aligned} \text{(c) } i &= \frac{dq}{dt} = \frac{1}{60} \mu\text{A}, 0 < t < 60 \text{ s}; \\ &= -\frac{1}{180} \mu\text{A}, 60 < t < 240 \text{ s}; \\ &= 0, t > 240 \text{ s, where } \frac{1}{60} \mu\text{A} \\ &\quad \text{may also be expressed as} \\ &\quad 1 \mu\text{C/min}. \end{aligned}$$




$$(d) \quad p = vi = \frac{t}{360} \mu W, \quad 0 \leq t \leq 60 \text{ s};$$

$$= \frac{1}{180} \left( \frac{t}{18} - \frac{40}{3} \right) \mu W,$$

$$60 \leq t \leq 240 \text{ s};$$
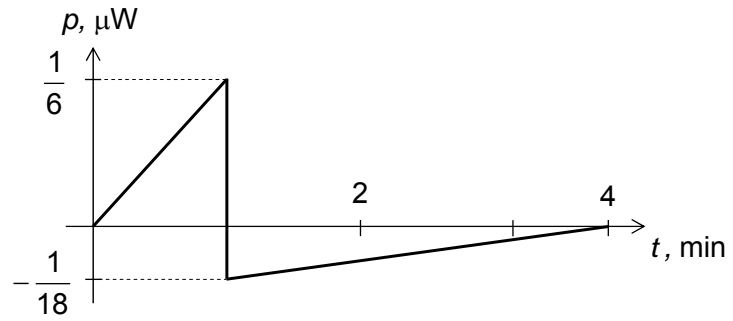
$$= 0, \quad t \geq 240 \text{ s}, \quad \text{where } \frac{1}{6} \mu W$$



may also be expressed as  $10 \mu J/\text{min}$ .

It is seen that  $w = \int p dt$ . Thus  $\int_0^t \frac{t}{360} dt = \frac{t^2}{720} \mu J, \quad 0 \leq t \leq 60 \text{ s}$ . At  $t = 60 \text{ s}$ ,  $w = 5 \mu J$ .

$$\text{For } 60 \leq t \leq 240 \text{ s} \quad w = \int_{60}^t \frac{1}{180} \left( \frac{t}{18} - \frac{40}{3} \right) dt + 5 = \frac{1}{180} \left( \frac{t^2}{36} - \frac{40t}{3} + 1600 \right) \mu J.$$

**P1.5.9** A triangular current waveform is described by Figure P1.4.12, with the current in amperes replacing the voltage in volts. The triangular current pulse is applied to a  $0.1\mu\text{H}$

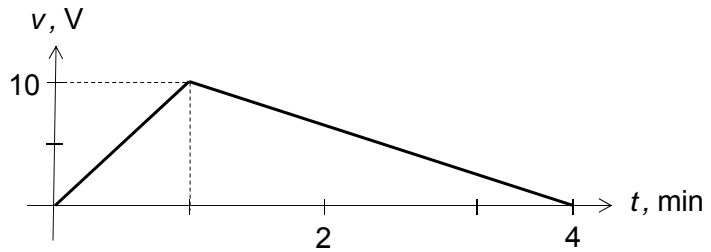


Figure P1.4.12

inductor that has no initial energy storage. Plot as function of time: (a) the flux linkage in the inductor; (b) the energy stored in the inductor, as derived from Equation 1.9.10; (c) the voltage across the inductor; (d) the instantaneous power input to the inductor. How is the energy stored in (b) related to the instantaneous power in (d)?

**Solution P1.5.9**

$$i = \frac{t}{6} \text{ A}, \quad 0 \leq t \leq 60 \text{ s};$$

$$i = -\frac{t}{18} + \frac{40}{3} \text{ A}, \quad 60 \leq t \leq 240 \text{ s};$$


$$i = 0, \quad t \geq 240 \text{ s}.$$

$$(a) \lambda = Li = \frac{t}{60} \mu\text{Wb-turns},$$

$$0 \leq t \leq 60 \text{ s};$$

$$= -\frac{t}{180} + \frac{4}{3} \mu\text{Wb-turns},$$
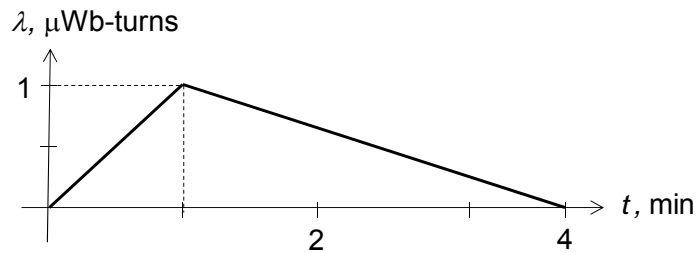
$$60 \leq t \leq 240 \text{ s} = 0, \quad t \geq 240 \text{ s}.$$




$$(b) w = \frac{1}{2} \lambda i = \frac{t^2}{720} \mu\text{J}, \quad 0 \leq t \leq 60 \text{ s};$$

$$= \frac{1}{180} \left( \frac{t^2}{36} - \frac{40t}{3} + 1600 \right) \mu\text{J},$$

$$60 \leq t \leq 240 \text{ s};$$

$$= 0, \quad t \geq 240 \text{ s}.$$

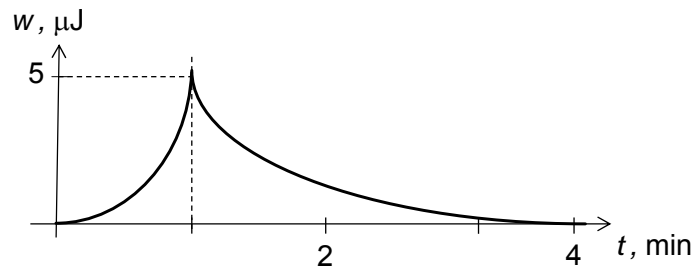


$$(c) \ v = \frac{d\lambda}{dt} = \frac{1}{60} \mu\text{V}, \ 0 < t < 60 \text{ s};$$

$$= -\frac{1}{180} \mu\text{V}, \ 60 < t < 240 \text{ s};$$

$$= 0, \ t > 240 \text{ s, where } \frac{1}{60} \mu\text{V}$$

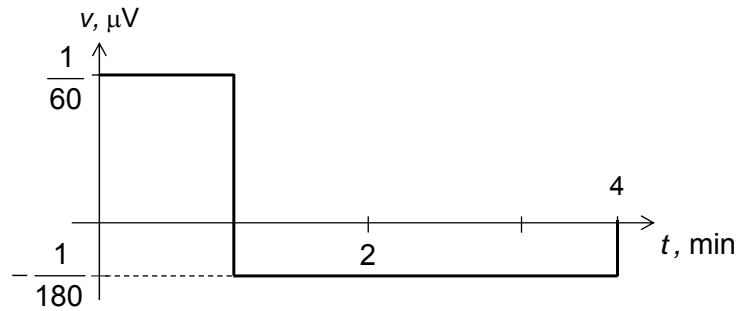may also be expressed as  
1  $\mu\text{Wb-turns/min}$ .




$$(d) \ p = vi = \frac{t}{360} \mu\text{W}, \ 0 \leq t \leq 60 \text{ s};$$

$$= \frac{1}{180} \left( \frac{t}{18} - \frac{40}{3} \right) \mu\text{W},$$

$$60 \leq t \leq 240 \text{ s};$$

$$= 0, \ t \geq 240 \text{ s, where } \frac{1}{6} \mu\text{W}$$

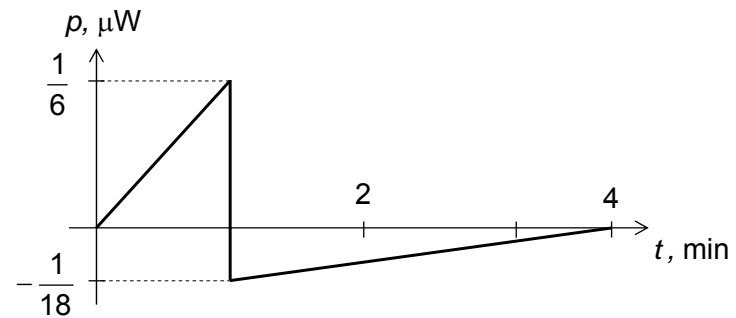may also be expressed as 10  
 $\mu\text{J/min}$ .



It is seen that  $w = \int p dt$ . Thus  $\int_0^t \frac{t}{360} dt = \frac{t^2}{720} \mu\text{J}, \ 0 \leq t \leq 60 \text{ s}$ . At  $t = 60 \text{ s}$ ,  $w = 5 \mu\text{J}$ .

$$\text{For } 60 \leq t \leq 240 \text{ s } w = \int_{60}^t \frac{1}{180} \left( \frac{t}{18} - \frac{40}{3} \right) dt + 5 = \frac{1}{180} \left( \frac{t^2}{36} - \frac{40t}{3} + 1600 \right) \mu\text{J}.$$

Note that the numerical values in this problem are identical to those of P1.4.12, if  $v$  and  $i$ , and  $q$  and  $\lambda$ , are interchanged.

**P2.1.4** Determine the voltage across each current source and the current through each voltage source in Figure P2.1.4.

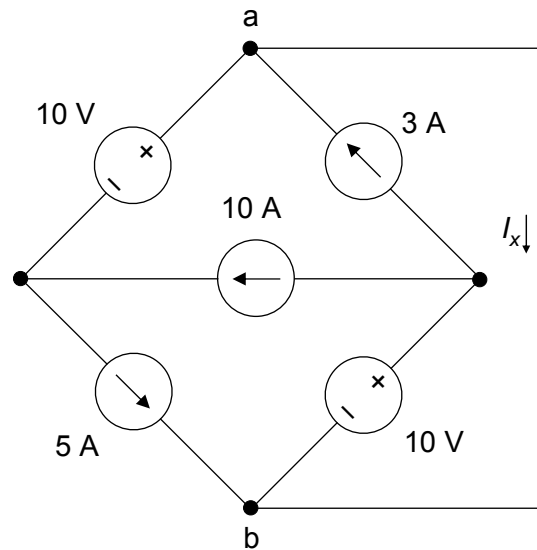


Figure P2.1.4

**Solution P2.1.4**

From KCL at node c:  $10 = 5 + I_A$ , so  $I_A = 5$  A.

From KCL at node d:  $I_\phi = 10 + 3 = 13$  A.

From KCL at node a:  $I_x = 3 + I_A = 8$  A.


As a check, KCL at node b:  $I_x + 5 = I_\phi$ , or  $8 + 5 = 13$ .

From KVL around the outer loop, starting from node a:  $-V_3 + 10 = 0$ , or  $V_3 = 10$  V.

From KVL around the mesh on the RHS, starting from node a:  $+10 - V_1 = 0$ , or  $V_1 = 10$  V.

From KVL around the mesh cdb, starting from node c:  $V_2 - 10 - V_3 = 0$ . This gives:  $V_2 = 20$  V.

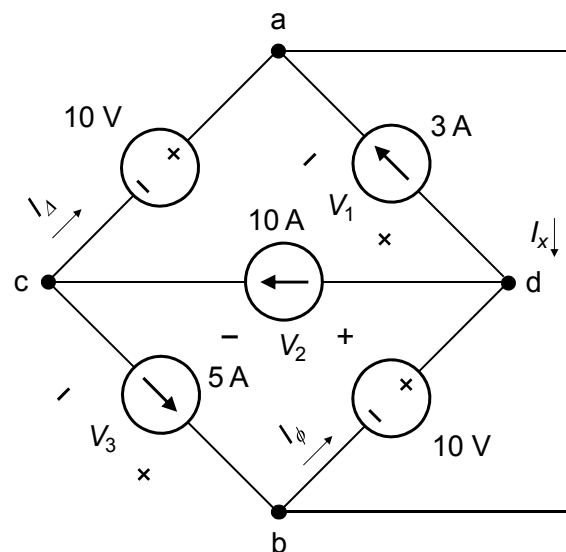As a check, KVL around the mesh adc, starting from node a:  $V_1 - V_2 + 10 = 0$ , or  $10 - 20 + 10 = 0$ .





**P2.2.5** Determine  $G_{eq}$  between terminals ab in Figure P2.2.5.

**Solution P2.2.5**

$G$  in series with  $\frac{3}{2}G$  is  $\frac{1 \times 1.5}{2.5} = 0.6G$ .

The two  $0.6G$  resistors are in parallel, giving a total conductance of  $1.2G$ . This conductance is in series with  $1.5G$ , which gives

$$\frac{1.5 \times 1.2}{1.5 + 1.2}G = \frac{2}{3}G; \text{ hence, } G_{ab} = \frac{G}{2} + \frac{2G}{3} = \frac{7}{6}G.$$


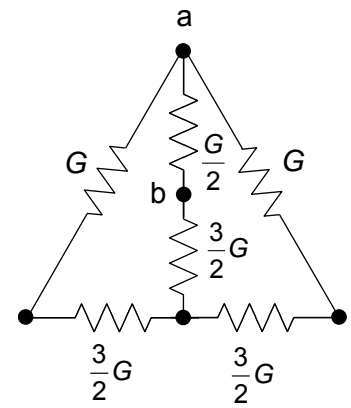


Figure P2.2.5

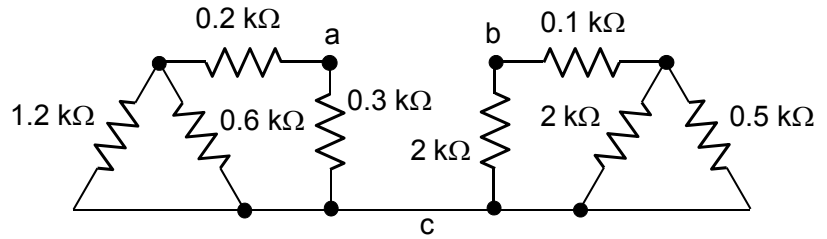**P2.2.6** Determine  $R_{eq}$   
between terminals ab  
in Figure P2.2.6.



**Solution P2.2.6**

Starting with the RHS,  $(2 \text{ k}\Omega) \parallel (0.5 \text{ k}\Omega) = \frac{2 \times 0.5}{2.5} = 0.4 \text{ k}\Omega$ ,  $0.1 + 0.4 = 0.5 \text{ k}\Omega$ ,

$$R_{bc} = (2 \text{ k}\Omega) \parallel (0.5 \text{ k}\Omega) = 0.4 \text{ k}\Omega;$$

on the LHS,  $(1.2 \text{ k}\Omega) \parallel (0.6 \text{ k}\Omega) = \frac{1.2 \times 0.6}{1.8} = 0.4 \text{ k}\Omega$ ,  $0.2 + 0.4 = 0.6 \text{ k}\Omega$ ,

$$R_{ac} = (0.3 \text{ k}\Omega) \parallel (0.6 \text{ k}\Omega) = \frac{0.3 \times 0.6}{0.9} = 0.2 \text{ k}\Omega;$$

$$R_{ab} = 0.4 + 0.2 = 0.6 \text{ k}\Omega.$$