

Homework 8

P6.3.3 Determine i_o in Figure P6.3.3, given that $v_{SRC} = 200\sin(1,000t)$ V. Simulate with PSpice.

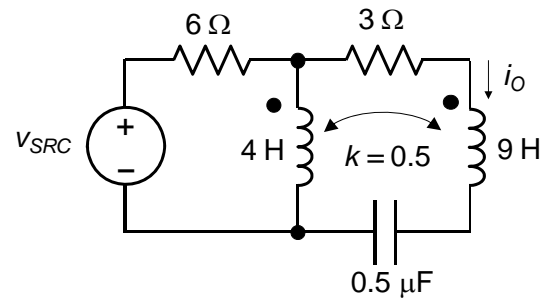


Figure P6.3.3

Solution P6.3.3

$$1/j\omega C = 1/(j1000 \times 0.5 \times 10^{-6}) = -j2000 \Omega;$$

$$j\omega L_1 = j1000 \times 4 = j4000 \Omega;$$

$$j\omega L_2 = j1000 \times 9 = j9000 \Omega;$$


$$j\omega M = j1000 \times 0.5 \sqrt{4 \times 9} = j3000 \Omega;$$

Considering I_1 to be a mesh current and I_o to be the current in the outer loop, KVL gives:

$$(6 + j4000)I_1 + (j3000 + 6)I_o = -j200,$$

$$\text{and, } (j3000 + 6)I_1 + (9 + j7000)I_o = -j200$$

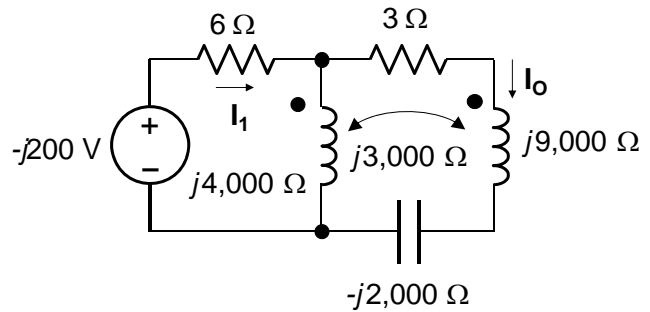Solving, gives $I_o = -0.0105 \equiv -0.0105\cos(1,000t)$ A.



P6.3.4 Determine Z_x in Figure P6.3.4 so that $V_o = 0$.

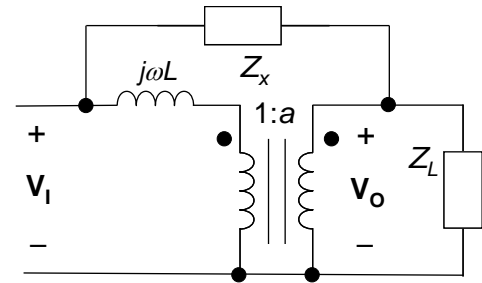



Figure P6.3.4

Solution P6.3.4

If $V_o = 0$, then $V_1 = 0$, $I_1 = \frac{1}{j\omega L} V_1$, and $I_x = \frac{1}{Z_x} V_1$.

But $I_1 + aI_x = 0$;

hence, $Z_x = -j\omega La$.

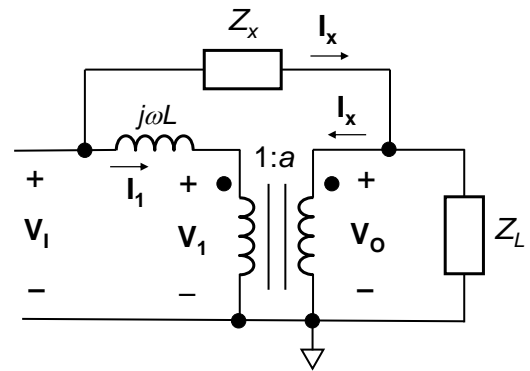

P6.3.7 Determine V_x and V_y in

Figure P6.3.47,
assuming $f = 50$ Hz.

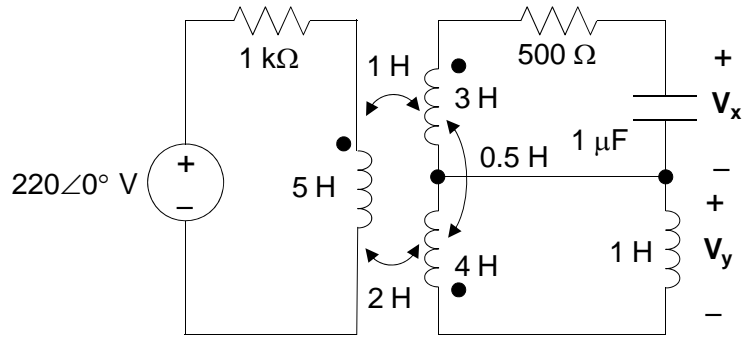


Figure P6.3.7

Solution P6.3.7

The mesh current equations are:

$$(10^3 + j\omega 5)\mathbf{I}_1 - j\omega 1\mathbf{I}_2 + j\omega 2\mathbf{I}_3 = 220$$

$$-j\omega 1\mathbf{I}_1 + (500 + j\omega 3 - j/(\omega \times 10^{-6}))\mathbf{I}_2 - j\omega 0.5\mathbf{I}_3 = 0$$

$$; +j\omega 2\mathbf{I}_1 - j\omega 0.5\mathbf{I}_2 + j\omega 5\mathbf{I}_3 = 0$$


Substituting $\omega = 100\pi$ and solving gives:

$$\mathbf{I}_2 = -0.0059 + j0.013 \text{ A, and } \mathbf{I}_3 = -0.0319 + j0.0432 \text{ A.}$$

$$\text{Hence, } \mathbf{V}_x = [-j/(\omega \times 10^{-6})]\mathbf{I}_2 = 41.3 + j18.6 =$$

$$45.3\angle 25.3^\circ \equiv 45.3\cos(100\pi t + 25.3^\circ) \text{ V,}$$
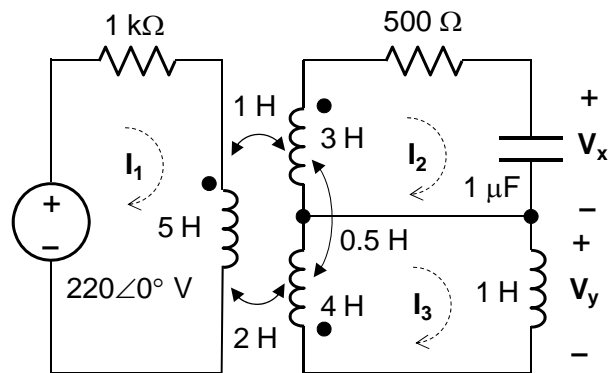
$$\mathbf{V}_y = j\omega \mathbf{I}_3 = -13.6 - j10.03 = 16.89\angle -143.6^\circ \equiv 16.89\cos(100\pi t - 143.6^\circ) \text{ V.}$$



P6.3.10 Determine

i_o in

Figure

P6.3.10,

given that

$V_{SRC} =$

$100\sin(100\pi t)$ V.


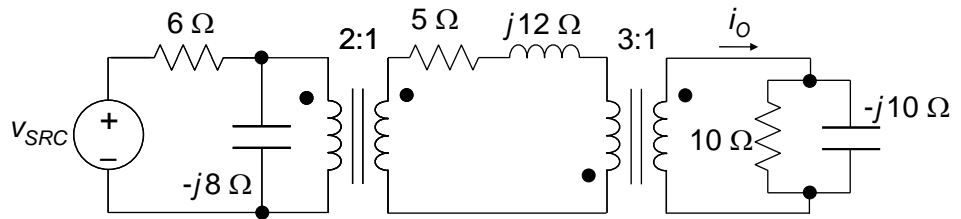


Figure P6.3.10

Solution P6.3.10

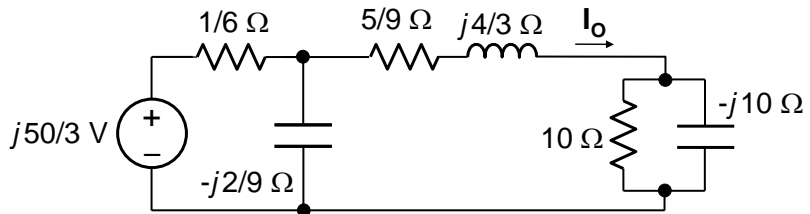The $-j100$ V source is reflected through the two transformers by dividing it by 2 and then by -3, becoming $j50/3$ V, as shown.




The 6Ω and $-j8 \Omega$ are stepped

down by $(2)^2 \times (3)^2 = 36$, becoming $1/6 \Omega$ and $-j2/9 \Omega$, as shown.

The 5Ω and $j12 \Omega$ are stepped down by 9, becoming $5/9 \Omega$

and $j4/3 \Omega$, as shown.

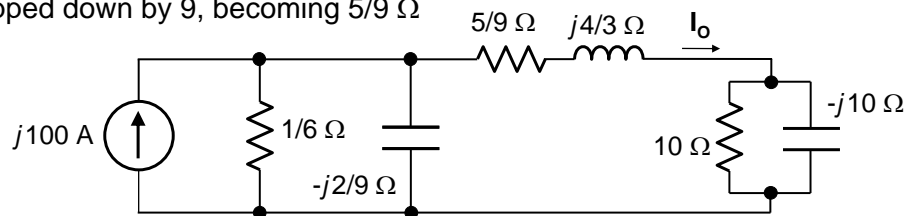The voltage source is transformed to a current source as shown.



Let $Z = \frac{5}{9} + j\frac{4}{3} + \frac{1}{0.1 + j0.1}$; then $Y = \frac{1}{Z} = 0.125 + j0.0828$ S.

Hence, $I_o = \frac{Y}{Y + 6 + j4.5} (j100) = 0.116 + j1.96$ A $= 1.96 \angle 86.6^\circ = 1.96 \cos(100\pi t + 86.6^\circ)$ A.

P6.3.12 Determine \mathbf{V}_O in Figure P6.3.12, given that $\mathbf{V}_{\text{SRC}} = 50\angle 45^\circ \text{ V}$.

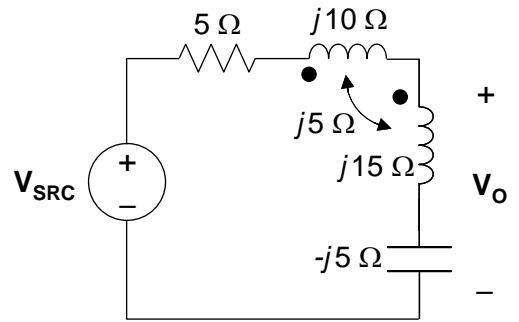


Figure P6.3.12


Solution P6.3.12

$$\mathbf{I}_{\text{SRC}} [5 + j10 + j15 + 2 \times j5 - j5] = 50(\cos 45^\circ + j \sin 45^\circ);$$

$$\mathbf{I}_{\text{SRC}} = \frac{50(\cos 45^\circ + j \sin 45^\circ)}{5 + j30},$$

$$\mathbf{V}_O = (j15 + j5 - j5)\mathbf{I}_{\text{SRC}} = \frac{j750(\cos 45^\circ + j \sin 45^\circ)}{5 + j30} =$$

$$14.33 + j20.07 \text{ V}.$$

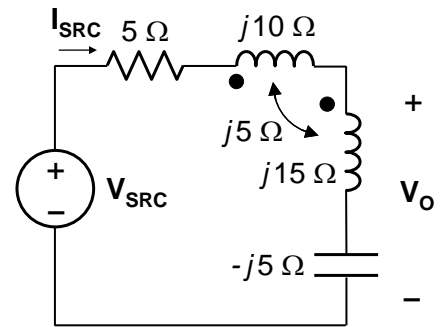

P6.3.15 Derive TEC between terminals ab in Figure P6.3.15.

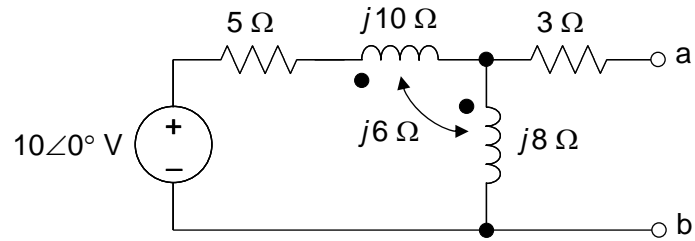



Figure P6.3.15

Solution P6.3.15

The linear transformer is replaced by its T-equivalent circuit. It follows that $\mathbf{V}_{Th} =$

$$\frac{j14}{5 + j30} \times 10 = \frac{28}{37}(6 + j) = 4.6 \angle 9.46^\circ \text{ V.}$$

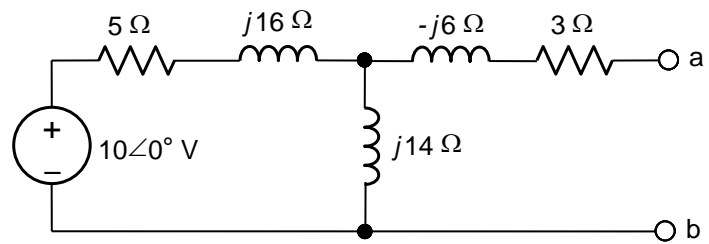When the voltage source is set to zero, the impedance looking into terminal ab is



$$\mathbf{Z}_{Th} = 3 - j6 + \frac{j14(5 + j16)}{5 + j30} = \frac{751 + j304}{185} = 4.060 + j1.643 = 4.38 \angle 22.04^\circ \Omega.$$

P6.3.21 Determine Z_{in} in Figure P6.3.21.

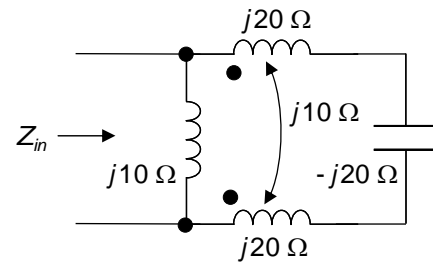


Figure P6.3.21

Solution P6.3.21

The impedance encountered by the current \mathbf{I} is
 $j\omega L_1 + j\omega L_2 - j2\omega M - j/\omega C = j20 + j20 - j20 - j20$
 $= 0.$

Hence, $Z_{in} = j10 \parallel 0 = 0.$

