

Homework 6

P5.1.6 Given the sinusoidal time function v of Figure P5.1.6. Express v as a function of time and as a phasor.

Solution P5.1.6

$$v = 10\cos(\omega t + \varphi) \text{ V.}$$

$$\omega = 2\pi/T = 2\pi/(10 \cdot 10^{-3}) = 200\pi.$$

At $t = 0$, $v = 3$, so that $\cos(\varphi) = 0.3$, or, $\varphi = 72.54^\circ$.

As a time function, $v = 10\cos(200\pi t + 72.54^\circ) \text{ V}$.

As a phasor, $\mathbf{V} = 10\angle 72.54^\circ \text{ V}$.

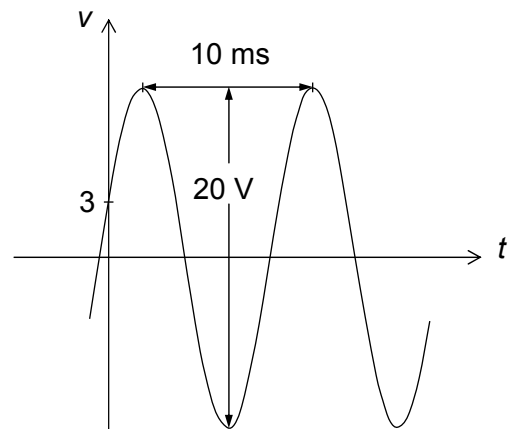


Figure P5.1.6

- P5.2.1** Given $i = 8\sqrt{2} \cos(2,500\pi t - 45^\circ)$ A and $i_1 = 2\cos 2,500\pi t$ A in Figure P5.2.1. Determine:
 (a) v and i_2 in the time and frequency domains; (b) Z , if composed of i) two series elements, or ii) two parallel elements.

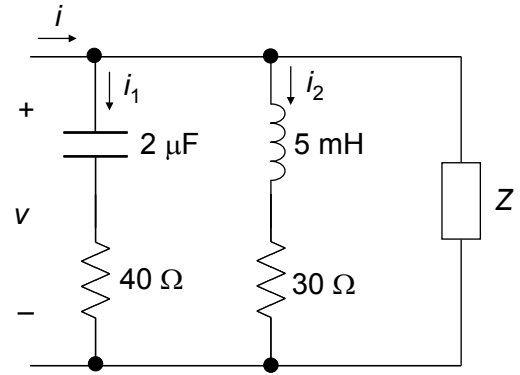


Figure P5.2.1

Solution P5.2.1

At $\omega = 2,500\pi$ rad/s

$$R - j/\omega C = 40 - j/(2500\pi \times 2 \times 10^{-6}) = 40 - j63.7 = 75.21 \angle -57.87^\circ \Omega.$$

$$(a) \mathbf{V} = \mathbf{I}_1(75.21 \angle -57.87^\circ) = (2 \angle 0^\circ) \times 75.21 \angle -57.87^\circ \text{ V} = 150.43 \angle -57.87^\circ \text{ V}.$$

$$v = 150.43 \cos(2500\pi t - 57.87^\circ) \text{ V}.$$

$$\mathbf{I}_2 = \mathbf{V}/(30 + j\omega L) = (150.43 \angle -57.87^\circ)/(30 + j2500\pi \times 5 \times 10^{-3}) \text{ A} = (150.43 \angle -57.87^\circ)/(49.718 \angle 52.62^\circ) = 3.04 \angle -110.49^\circ = -1.065 - j2.85.$$

$$i_2 = 3.04 \cos(2500\pi t - 110.49^\circ) \text{ A}.$$

$$(b) \mathbf{Z} = \mathbf{V}/(\mathbf{I} - \mathbf{I}_1 - \mathbf{I}_2) = (150.43 \angle -57.87^\circ)/(8 - j8 - 2 + 1.065 + j2.85) \Omega = (150.43 \angle -57.87^\circ)/(7.065 - j5.15) \Omega = (150.43 \angle -57.87^\circ)/(8.74 \angle -36.1^\circ) \Omega = 17.21 \angle -21.78^\circ = 15.98 - j6.39 \Omega.$$

$$(i) \text{ If } Z \text{ is composed of two series elements } R \text{ and } C, R = 15.98 \Omega \text{ and } C = 1/(2500\pi \times 6.39) = 19.93 \mu\text{F}.$$

$$(ii) \text{ If } Z \text{ is composed of two parallel elements, } Y = \frac{1}{17.21 \angle -21.78^\circ} = 0.053 + j0.021 \text{ S} = G + j\omega C, \text{ where } G = 0.053 \text{ S and } C = 0.021/2500\pi = 2.67 \mu\text{F}.$$

P5.2.5 Determine the input impedance Z_i in Figure P5.2.5.

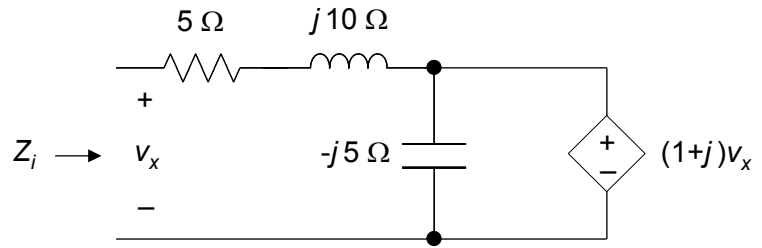


Figure P5.2.5

Solution P5.2.5

If a source v_x is applied, the source current being i_x , then: $v_x = 5i_x + j10i_x + (1+j)v_x$.

$$\frac{v_x}{i_x} = \frac{5 + j10}{-j} = -10 + j5 \Omega.$$

Alternatively, the capacitor may be removed because it is in parallel with a voltage source. The

current i_x is $\frac{v_x - (1+j)v_x}{5 + j10} = \frac{-jv_x}{5 + j10}$. This gives $\frac{v_x}{i_x} = \frac{5 + j10}{-j} = -10 + j5 \Omega$, as before.

P5.3.32 Determine I_1 , I_2 , and V_{ab} in Figure P5.3.32, given that $V_{SRC} = 50\angle 60^\circ$ V. Draw a phasor diagram showing these quantities.

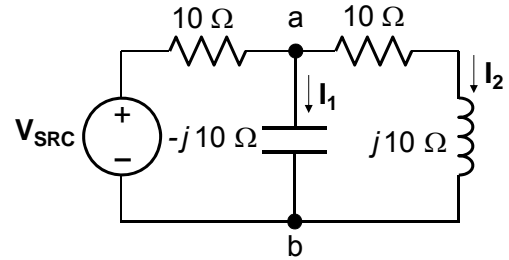


Figure P5.3.32

Solution P5.3.32


Taking node b as a reference, KCL at node a gives:

$$\frac{1}{-j10} V_a + \frac{1}{10 + j10} V_a + \frac{1}{10} V_a = 5\angle 60^\circ.$$

This gives $V_a = V_{ab} = 31.63\angle 41.6^\circ$ V.

$$I_1 = \frac{1}{-j10} V_a = 3.16\angle 131.6^\circ \text{ A},$$
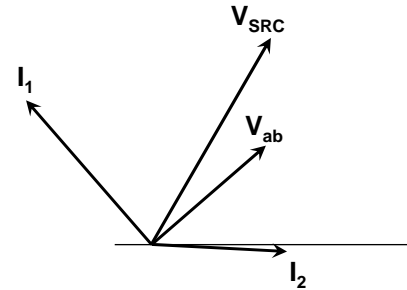
$$\text{and } I_2 = \frac{1}{10 + j10} V_a = 2.24\angle -3.43^\circ \text{ A}.$$



The phasor diagram is shown, where the voltage and current scales are different.

P5.3.35 Figure P5.3.35 shows a **Maxwell**

bridge that may be used for measuring the inductance and resistance of a coil in terms of known capacitance and resistance values. Show that at bridge balance: $R_2 = \frac{R_1 R_3}{R_4}$ and

$$L_2 = C_4 R_1 R_3.$$

Note that the first condition is a DC balance condition, the same as in the Wheatstone bridge.

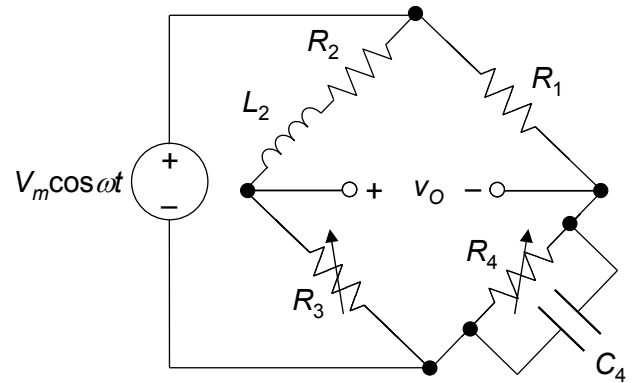


Figure P5.3.35

Solution P5.3.35

The impedance of arm 4 is: $\frac{R_4}{1 + j\omega C_4 R_4}$. At bridge balance: $\frac{R_2 + j\omega L_2}{R_3} = \frac{R_1(1 + j\omega R_4 C_4)}{R_4}$.

Equating real parts: $\frac{R_2}{R_3} = \frac{R_1}{R_4}$.

Equating imaginary parts: $\frac{L_2}{R_3} = C_4 R_1$.