

Homework 12

P9.2.1 The triangular pulse train of Figure 9.3.2 is applied as the input v_I to the circuit of Fig. P9.2.1. Determine v_O . Show that if $\omega CR \ll 1$, $v_O \rightarrow \frac{dv_I}{dt}$, and v_O becomes the square pulse train of Figure 9.2.8 with appropriate amplitude.

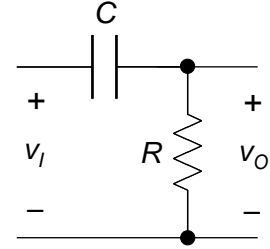


Figure P9.2.1

Solution P9.2.1

From Equation 9.3.13: $v_I = \frac{-8A_m}{\pi^2} \left[\cos \omega_0 t + \frac{1}{9} \cos 3\omega_0 t + \frac{1}{25} \cos 5\omega_0 t + \dots \right]$.

In terms of phasors: $\frac{V_O}{V_I} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega CR}{1 + j\omega CR}$, where $\omega = n\omega_0$.

If $v_I = A \cos \omega t$, then $v_O = \frac{-\omega CR}{\sqrt{1 + \omega^2 C^2 R^2}} A \sin(\omega t - \alpha)$, where $\tan \alpha = \omega CR$.

It follows that: $v_O = \frac{8A_m}{\pi^2} \left[\frac{\omega_0 CR}{\sqrt{1 + \omega_0^2 C^2 R^2}} \sin(\omega_0 t - \alpha) + \frac{\omega_0 CR}{3\sqrt{1 + 9\omega_0^2 C^2 R^2}} \sin(3\omega_0 t - \alpha) + \frac{\omega_0 CR}{5\sqrt{1 + 25\omega_0^2 C^2 R^2}} \sin(5\omega_0 t - \alpha) + \dots \right]$

If $\omega CR \ll 1$, then $\frac{V_O}{V_I} \cong j\omega CR$, and $v_O(t) = CR \frac{dv_I(t)}{dt}$. The circuit acts as a differentiating circuit.

P9.2.3 In Figure P9.2.3 v_{SRC} is the full-wave rectified waveform of Figure 9.4.1b having $T = 1/50$ s and an amplitude of 50 V.

Between v_{SRC} and the 4 k Ω load is the LC filter shown whose purpose is to attenuate the AC components, leaving a near DC voltage across the load.

Determine the first four nonzero terms in the FSE of v_O and compare with those

of v_{SRC} . What is the rms value of the AC component in the first four nonzero terms in the FSE of v_O ?

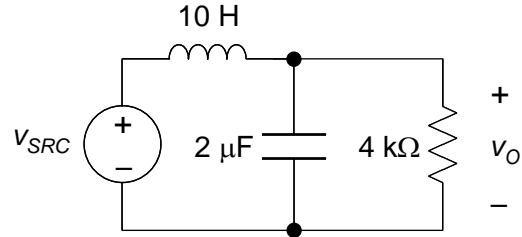


Figure P9.2.3

Solution P9.2.3

$$\omega_0 = \frac{2\pi}{T} = 100\pi.$$

$$\text{From Equation 9.4.2 } v_{SRC} = \frac{100}{\pi} + \frac{200}{\pi} \left(\frac{1}{3} \cos 200\pi t - \frac{1}{15} \cos 400\pi t + \frac{1}{35} \cos 600\pi t \right) \text{ V,}$$

retaining the first four terms.

$$\text{In terms of phasors: } \frac{V_O}{V_{SRC}} = \frac{R}{1 + j\omega CR} \times \frac{1}{j\omega L + \frac{R}{1 + j\omega CR}} = \frac{R}{R - \omega^2 LCR + j\omega L}.$$

The DC term remains unchanged.

$$\text{At } \omega = 200\pi, \text{ the first AC term is } \frac{200}{3\pi} \times \frac{4000}{4000 - (200\pi)^2 \times 10 \times 2 \times 10^{-6} \times 4000 + j2000\pi}. \text{ Its}$$

$$\text{magnitude is } \frac{200}{3\pi} \times \frac{4}{\sqrt{(4 - 3.2\pi^2)^2 + (2\pi)^2}} = 3 \text{ V and its phase angle is } -\tan^{-1} \frac{2\pi}{4 - 3.2\pi^2} = 13.1^\circ.$$

$$\text{At } \omega = 400\pi, \text{ the amplitude of the second AC term is } \frac{200}{15\pi} \times \frac{4}{\sqrt{(4 - 12.8\pi^2)^2 + (4\pi)^2}} = 0.138 \text{ V}$$

$$\text{and its phase angle is } \tan^{-1} \frac{4\pi}{4 - 12.8\pi^2} = -5.89^\circ.$$

$$\text{At } \omega = 600\pi, \text{ the amplitude of the third AC term is } \frac{200}{35\pi} \times \frac{4}{\sqrt{(4 - 28.8\pi^2)^2 - (6\pi)^2}} = 0.026 \text{ V and}$$

$$\text{its phase angle is } -\tan^{-1} \frac{6\pi}{4 - 28.8\pi^2} = 3.85^\circ.$$

The first four terms of the FSE are: $v_o(t) = 31.83 + 3.00\cos(200\pi t + 13.1^\circ) + 0.138\cos(400\pi t - 5.89^\circ) + 0.026\cos(600\pi t + 3.85^\circ)$ V.

Relative rates of attenuation are 1 for the DC term $\frac{3.00}{21.22} = 0.14$ for the fundamental, $\frac{0.138}{4.24} = 0.033$ for the second harmonic, and $\frac{0.026}{1.82} = 0.014$ for the third harmonic.

The rms of AC components of output is $\sqrt{\left(\frac{3}{\sqrt{2}}\right)^2 + \left(\frac{0.138}{\sqrt{2}}\right)^2 + \left(\frac{0.026}{\sqrt{2}}\right)^2} = 2.12$ V.

P9.3.2 Determine the rms value of i in Figure P9.3.2.

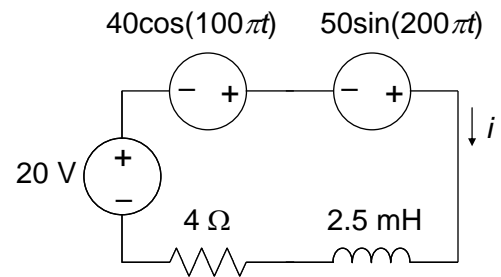


Figure P9.3.2

Solution P9.3.2

Applying superposition, $i_{DC} = \frac{20}{4} = 5 \text{ A}$;

at $\omega = 100\pi$, $\omega L = 100\pi \times 2.5 \times 10^{-3} = 0.785 \Omega$, and $i_1 = \frac{40}{\sqrt{2}} \times \frac{1}{\sqrt{(4)^2 + (0.785)^2}} = 6.94 \text{ A rms}$;

at $\omega = 200\pi$, $\omega L = 1.57 \Omega$, and $i_3 = \frac{50}{\sqrt{2}} \times \frac{1}{\sqrt{(4)^2 + (1.57)^2}} = 8.23 \text{ A rms}$;

rms value of $i = \sqrt{(5)^2 + (6.94)^2 + (8.23)^2} = 11.87 \text{ A}$.

P9.3.6 Determine the rms value of the voltage waveform shown in Figure P9.3.6.

Solution P9.3.6

The equation of the initial part is t .

The area under the square of this

function is $\int_0^{10} t^2 dt = \left[\frac{t^3}{3} \right]_0^{10} = \frac{1000}{3}$.

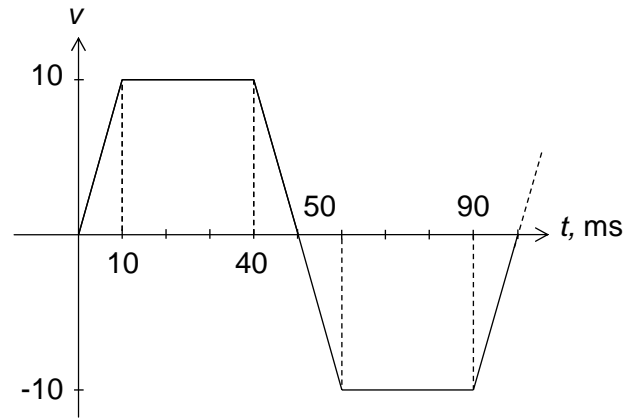


Figure P9.3.6

The area under the square of the function from $t = 10$ s to $t = 25$ s is $100 \times 15 = 1500$; the total area under the quarter period is $5,500/3$.

The mean square is $5,500/(25 \times 3) = 220/3$.

The rms value is $2\sqrt{55/3}$ V.

- P9.3.8** A periodic signal consists of a fundamental of amplitude 20, frequency 1k rad/s and 3rd, 5th, and 7th harmonics of relative amplitudes, with respect to the fundamental of 0.2, 0.05, and 0.01, respectively. The phase angle of the fundamental and 5th harmonics is $+90^\circ$, whereas the phase angle of the 3rd and 7th harmonics is -90° .
- (a) Determine the rms value of the signal. (b) Express the signal as a FSE. (c) Specify whether or not the signal is even or odd and whether or not it has half-wave symmetry. Repeat the above for the same signal but with the phase angles of the components negated.

Solution P9.3.8

- (a) The amplitudes of the 3rd, 5th, and 7th harmonics are: $0.2 \times 20 = 4$, $0.05 \times 20 = 1$, and $0.01 \times 20 =$

0.2, respectively. The rms value is $\frac{20}{\sqrt{2}} \sqrt{1 + (0.2)^2 + (0.05)^2 + (0.01)^2} = 14.44$.

- (b) $f(t) = 20\cos(10^3t + 90^\circ) + 4\cos(3 \times 10^3t - 90^\circ) + \cos(5 \times 10^3t + 90^\circ) + 0.2\cos(7 \times 10^3t - 90^\circ) =$
 $-20\sin 10^3t + 4\sin 3 \times 10^3t - \sin 5 \times 10^3t + 0.2\sin 7 \times 10^3t$.

- (c) Since it is a sinusoidal, the function is odd. If we substitute $(t + T/2)$ for t , the function becomes: $-20\sin(10^3t + \pi) + 4\sin(3 \times 10^3t + 3\pi) - \sin(5 \times 10^3t + 5\pi) + 0.2(\sin 7 \times 10^3t + 7\pi) =$
 $20\sin 10^3t - 4\sin 3 \times 10^3t + \sin 5 \times 10^3t - 0.2\sin 7 \times 10^3t$. Since the function becomes negated, it is half-wave symmetric.

If the phase angles are negated, $f_1(t) = 20\cos(10^3t - 90^\circ) + 4\cos(3 \times 10^3t + 90^\circ) + \cos(5 \times 10^3t - 90^\circ) + 0.2\cos(7 \times 10^3t + 90^\circ) = 20\sin 10^3t - 4\sin 3 \times 10^3t + \sin 5 \times 10^3t - 0.2\sin 7 \times 10^3t$.

Since it is sinusoidal, the function is odd.

If we substitute $(t + T/2)$ for t , the function becomes: $20\sin(10^3t + \pi) - 4\sin(3 \times 10^3t + 3\pi) + \sin(5 \times 10^3t + 5\pi) - 0.2(\sin 7 \times 10^3t + 7\pi) = -20\sin 10^3t + 4\sin 3 \times 10^3t - \sin 5 \times 10^3t + 0.2\sin 7 \times 10^3t$.

Since the function becomes negated, it is half-wave symmetric.

P9.3.9 The voltage at two given terminals of a circuit is: $v = 4\sin t + 5\cos 2t + 10\sin 4t$ V. The current input at these terminals, in the direction of the voltage drop, is: $i = 6\sin t + 8\cos 5t + 12\sin 8t$ A. Determine: (a) the rms value of v ; (b) the rms value of i ; (c) the average power delivered to the network at the given terminals.

Solution P9.3.9

(a) The rms value of the voltage is $\sqrt{\left(\frac{4}{\sqrt{2}}\right)^2 + \left(\frac{5}{\sqrt{2}}\right)^2 + \left(\frac{10}{\sqrt{2}}\right)^2} = 8.40$ V.

(b) The rms value of the current is $\sqrt{\left(\frac{6}{\sqrt{2}}\right)^2 + \left(\frac{8}{\sqrt{2}}\right)^2 + \left(\frac{12}{\sqrt{2}}\right)^2} = 11.04$ A.

(c) The power dissipated is due to the fundamental only and equals $(4 \times 6)/2 = 12$ W.