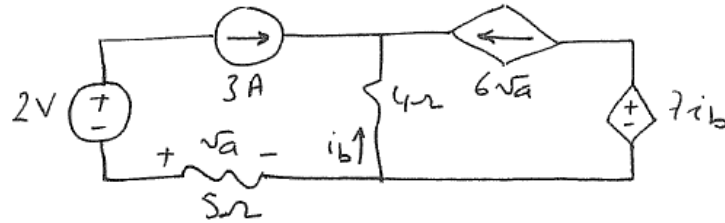


PR.2 Given the circuit, determine whether the dependent voltage source is supplying or absorbing power; then find that power.



(a) $P_{\text{absorbed}} = 58.6\text{W}$

(b) $P_{\text{absorbed}} = 40\text{W}$

(c) $P_{\text{delivered}} = 58.6\text{W}$

(d) $P_{\text{delivered}} = 450\text{W}$

→ (e) none of the above **54.81 kW**

PR.3 A resistor draws a current $I = 8\sin\omega t$ at a voltage $V = 200\sin\omega t$. Calculate the average power dissipated in the resistor.

(a) 400W

→ (b) 800W

(c) 1600W

(d) 0W

(e) none of the above

PR.4 Find V_S and I_S in the following circuit:


(a) $I_S = 10\text{A}$

(b) $I_S = 30\text{A}$


(c) $V_S = 60\text{V}$

(d) $I_S = 20\text{A}$

→ (e) none of the above **120 V, 20 A**

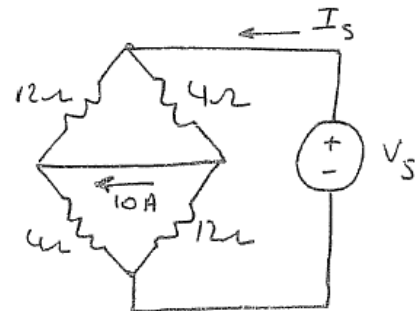

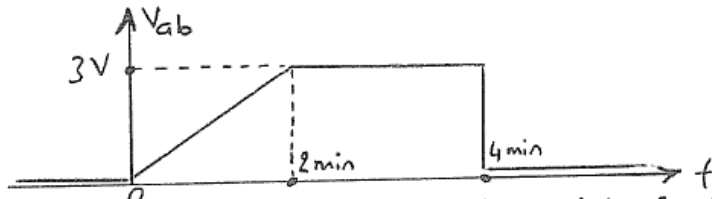PR.5 Given a 2Ω resistor connected between terminals a and b and given that the voltage is shown in the graph below:



Find the power delivered by the resistor for $0 < t < 2 \text{ min}$.

- (a) $9t^2/8$ (b) $-9t^2/8$ (c) $-3t^2/960$
 (d) $3t^2/960$ \rightarrow (e) none of the above $t/3200 \text{ W, } t \text{ is in s}$

PR.6 For the same given of problem 5, find the energy in joules converted into heat by the resistor for $2 < t < 4 \text{ min}$.

- \rightarrow (a) 540 (b) 180 (c) 1080
 (d) 90 (e) none of the above

PR.7 A 110 light bulb takes 0.9A and operates 12h/day. At the rate of 7cents/Kwh, find the cost to operate the bulb for 30 days.

- (a) 5\$ \rightarrow (b) 2.5\$ approx (c) 2\$
 (d) 252¢ (e) none of the above

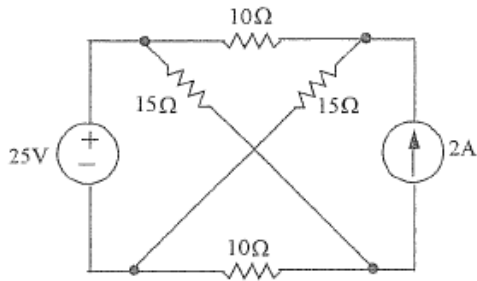


Figure 1

1. In the circuit shown in figure 1, calculate the total power delivered by the two sources.

- a) 88 W
- b) 72 W
- c) 98 W
- d) 110 W
- e) None of the above

Hint: redraw as a bridge circuit

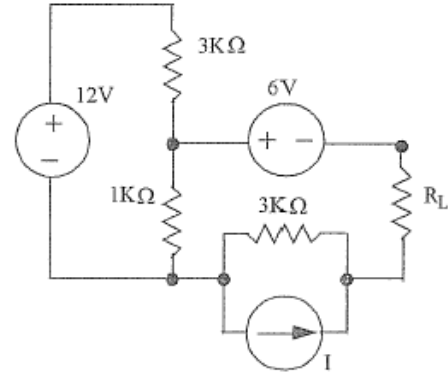


Figure 2

4. In the circuit shown in figure 2, determine I so that no current flows in R_L .

- a) 3mA
- b) 0mA
- c) 2mA
- d) -1mA
- e) None of the above

~~2. A 1Ω resistor is connected in parallel with a d'Arsonval movement having a full scale deflection of 1 mA. If a 40 mA current produces a deflection that is 80% of full scale, determine the resistance of the d'Arsonval movement.~~

- a) 58Ω
- b) 49Ω
- c) 37Ω
- d) 76Ω
- e) None of the above

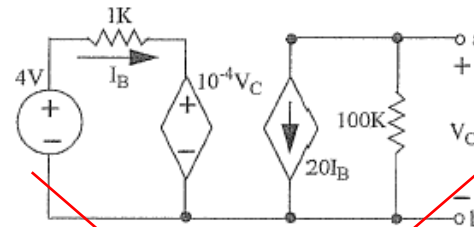


Figure 3

~~5. In the circuit shown in figure 3, determine the resistance R_L that should be connected between terminals ab for maximum transfer.~~

- a) 100kΩ
- b) 125kΩ
- c) 1kΩ
- d) 360Ω
- e) None of the above

3. A 1 cm cube of material has a resistance of $2.5K\Omega$ measured between opposite faces. Calculate the resistance of a rectangular block of this material that is 50 cm long and of 10 cm^2 cross-sectional area.

- a) 10.8kΩ
- b) 12.5kΩ
- c) 22.0kΩ
- d) 760Ω
- e) None of the above

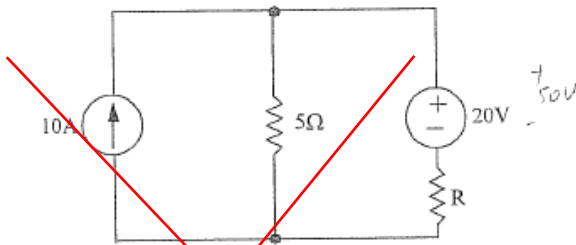


Figure 4

6. In the circuit shown in figure 4, determine the maximum power dissipation in the 5Ω resistor.

- a) 300 W
- b) 150 W
- c) 45 W
- d) 500 W
- e) None of the above

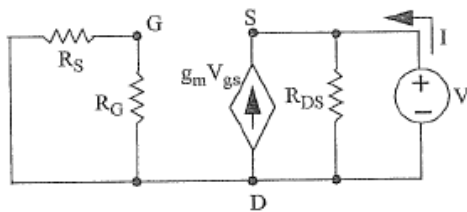


Figure 5

7. In the circuit shown in figure 5, determine $R_o = V/I$, if $V_{gd} = 0$.

- a) $R_o = R_{DS} \parallel R_G$
- b) $R_o = R_{DS}$
- c) $R_o = R_{DS} \parallel (1/g_m)$
- d) $R_o = R_S \parallel R_G \parallel R_{DS}$
- e) None of the above

8. In the circuit shown in Figure 6, find v_1 and the voltage v across both sources if i_s is given as 12 A.

- a) $v_1 = 30V$ and $v = 22.5V$
- b) $v_1 = 0.6V$ and $v = 2.25V$
- c) $v_1 = 30V$ and $v = 225V$
- d) $v_1 = 6V$ and $v = 225V$

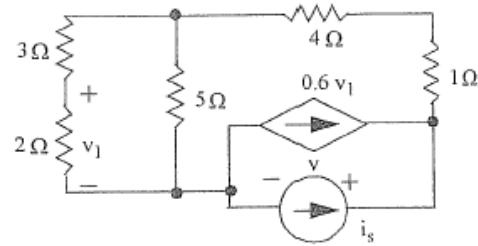


Figure 6

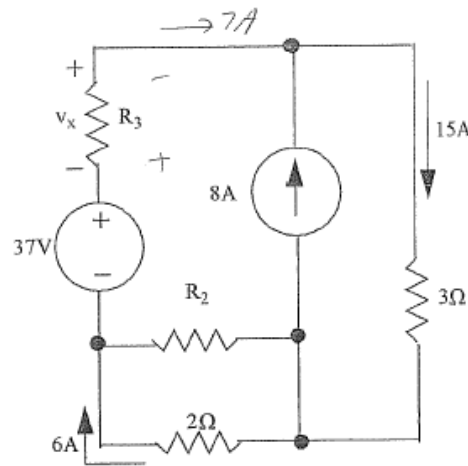


Figure 7

9. Determine v_x in the circuit of figure 7.

- a) $v_x = 20V$
- b) $v_x = -30V$
- c) $v_x = -20V$
- d) $v_x = 15V$
- e) None of the above

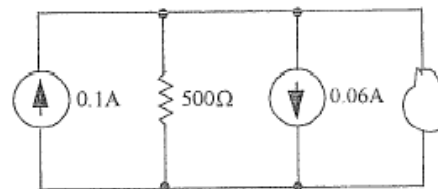


Figure 8

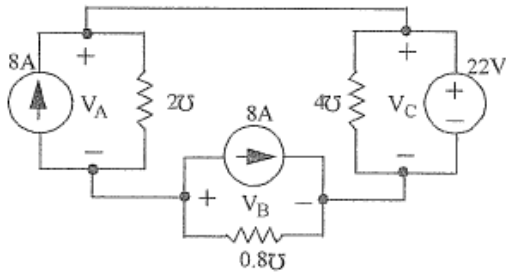


Figure 9

Hint: transform current sources to voltage sources

11. In the circuit of figure 9 find V_A , V_B and V_C . Note that the resistors are labeled with their respective conductances.

$$V_A = 12 \text{ V}, V_B = 10 \text{ V}, V_C = 22 \text{ V}$$

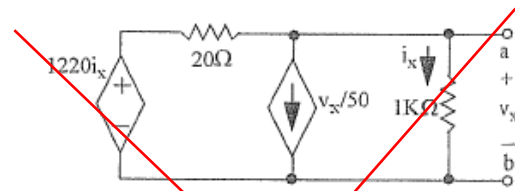


Figure 10

12. Find the Thevenin equivalent of the circuit shown in figure 10.

- a) $V_{th} = 10\text{V}$ and $R_{th} = 1\text{K}$
- b) $V_{th} = 0\text{V}$ and $R_{th} = 0.1\text{K}$
- c) $V_{th} = 10\text{V}$ and $R_{th} = 2\text{K}$
- d) $V_{th} = 1\text{V}$ and $R_{th} = 1\text{K}$
- e) None of the above

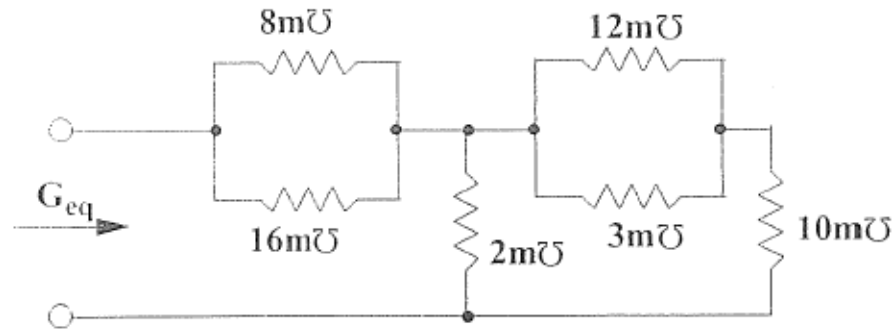


Figure 1

2. Find G_{eq} for the network of figure 1. (round off your answer to 2 decimals).

- a) 5 mhos
- b) 7 mhos
- c) 6 mhos
- d) 4 mhos
- e) None of the above


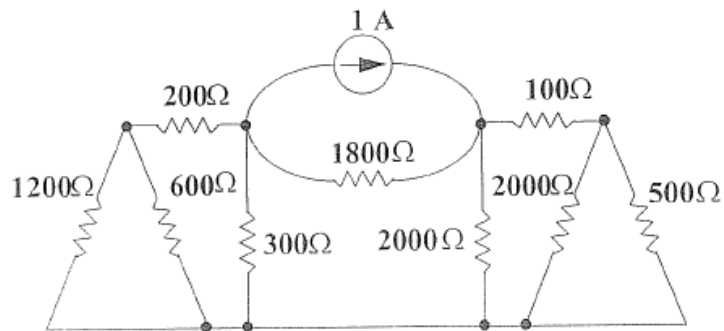


Figure 3

4. Given the circuit of figure 3. Find the power (p_{source}) supplied by the source and also the power (p_{1800}) absorbed by the 1800Ω resistor.

- a) $p_{\text{source}} = 450 \text{ W}$; $p_{1800} = 112.5 \text{ W}$
- b) $p_{\text{source}} = 4.5 \text{ W}$; $p_{1800} = 1.125 \text{ W}$
- c) $p_{\text{source}} = 112.5 \text{ W}$; $p_{1800} = 28.125 \text{ W}$
- d) $p_{\text{source}} = 18 \text{ W}$; $p_{1800} = 4.5 \text{ W}$
- e) None of the above


7. Consider the following circuit:

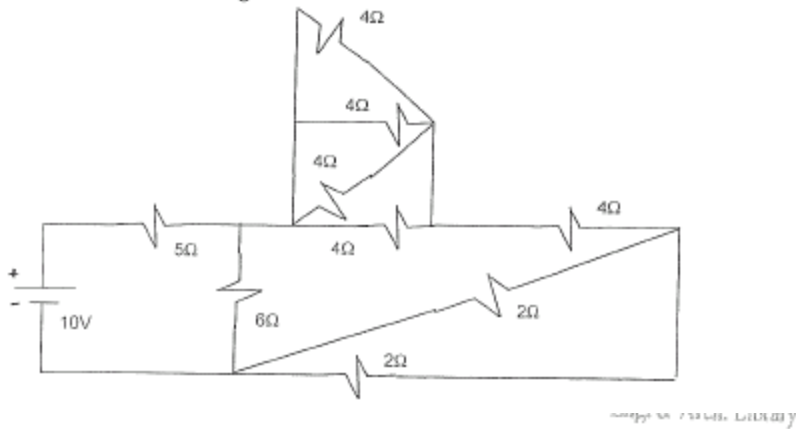

The equivalent resistance of the above circuit is:

- A. 11Ω
- B. 8Ω
- C. 6.2Ω
- D. 4Ω
- E. None of the above

8. Consider the following circuit:

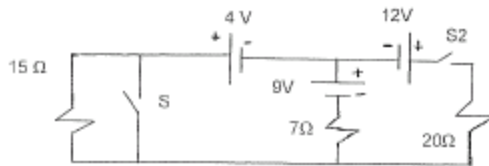


Assume switches S1 and S2 are both open, the current in the 15Ω resistor is:

- A. $0.34A$
- B. $1.86A$
- C. $0.59A$
- D. $0A$
- E. None of the above

9. In problem 8, assume switches S1 and S2 are both closed, the power generated by the $12V$ battery is:

- A. $4.8W$
- B. $-8.76W$
- C. $17.52W$
- D. $8.76W$
- E. None of the above.

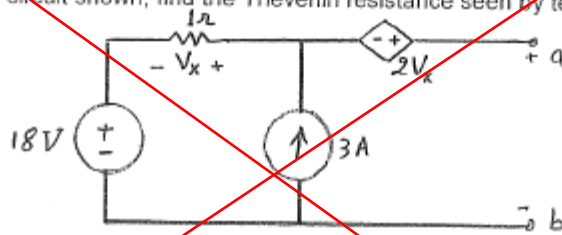10. For the circuit shown, find the Thevenin resistance seen by terminals ab




- A. 4Ω
- B. 5Ω
- C. 3Ω
- D. 6Ω
- E. None of the above.

Test ID 1000- 4/5


Eng. & Arch. Library

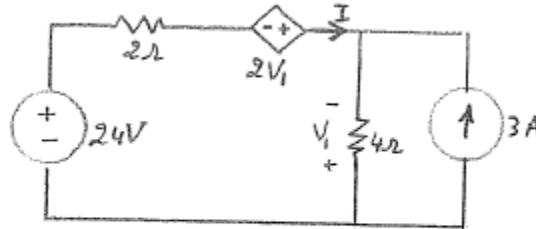11. Find the current I in the circuit shown below:



- A. $24/14$ A
- B. -0.857 A
- C. -3 A
- D. 4 A
- E. None of the above.

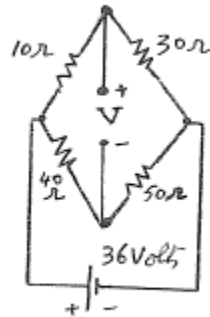13. Find the Voltage V in the circuit shown below.



- A. 25 V
- B. 7 V
- C. 16 V
- D. 9 V
- E. None of the above

2. In the circuit of Figure 1, the Thevenin resistance as seen from terminals ab is:

- a. $100/3\Omega$
- b. $100/9\Omega$
- c. $50/9\Omega$
- d. 10Ω
- e. None of the above

Arch. Library

3. In the circuit of Figure 2, the equivalent resistance seen across the terminals ab is:

- a. 7Ω
- b. 7.5Ω
- c. 6Ω
- d. 6.5Ω
- e. None of the above

Refer to figures
below

4. The current I_2 across the 6V source in Figure 3 is:

- a. 1.5A
- b. 4.5A
- c. 3A
- d. 3.5A
- e. None of the above

5. Find k in the circuit shown in Figure 4 such that the power dissipated in the 2- Ω resistor is 50W.

- a. 5
- b. 2
- c. 10
- d. 4
- e. None of the above

9. Find the resistance R in the circuit of Figure 7 such that the power supplied by the 100-V source to the network is the same as the power supplied by the 5-A source.

- a. 20Ω
- b. 30Ω
- c. 10Ω
- d. 40Ω
- e. None of the above

~~10. In the circuit of Figure 8, the Thevenin equivalent resistance, across terminals a-b, is:~~

- ~~a. 20Ω~~
- ~~b. 5Ω~~
- ~~c. -20Ω~~
- ~~d. 10Ω~~
- ~~e. None of the above~~

11. The current entering a circuit is shown in Figure 9. Determine the amount of charge that enters the circuit as a result of the current pulse.

- a. 20mC
- b. 40mC
- c. 80mC
- d. 60mC
- e. None of the above

12. Four 60-W, 110-V light bulbs are to be operated from a 230-V source (see Figure 10). Determine the value of the resistance, R , connected in series with the line so that the voltage across the bulbs does not exceed 110-V.

- a. 2 Ω
- b. 55 Ω
- c. 120 Ω
- d. 60 Ω
- e. None of the above

Eng. & Arch. Library

13. The power absorbed by the 4- Ω resistance of Figure 11 is:

- a. 100W
- b. 50W
- c. 75W
- d. 90W
- e. None of the above.

14. In the circuit of Figure 12, the power delivered by the 10-V source is:

- a. 20W
- b. -40W
- c. 40W
- d. 60W
- e. None of the above.

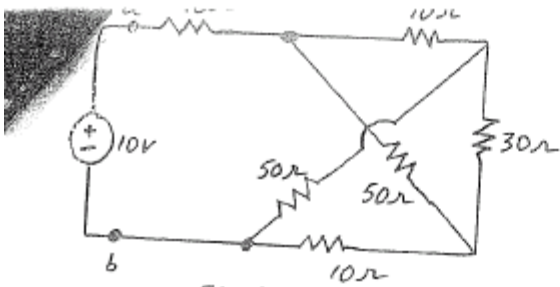


Fig. 1

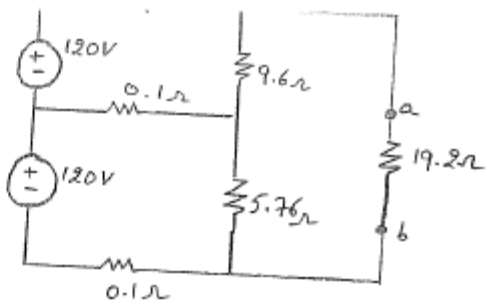


Fig. 5

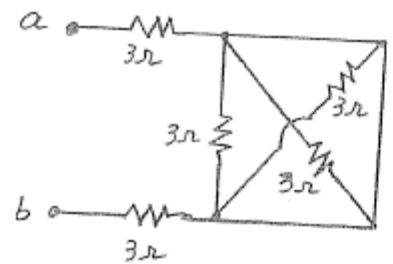


Fig. 2

Eng. & Arch. Library

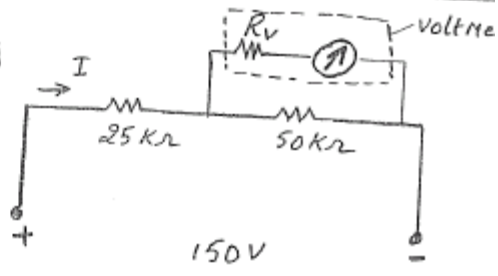


Fig. 6

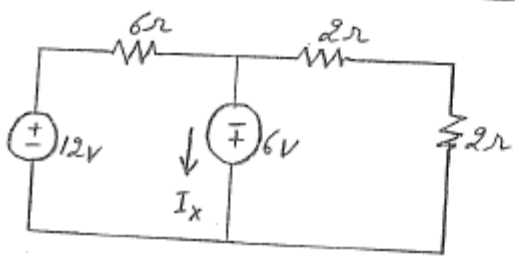


Fig. 3

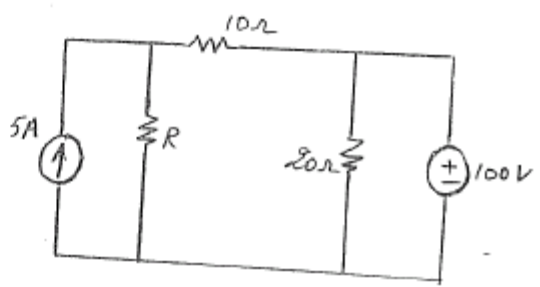


Fig. 7

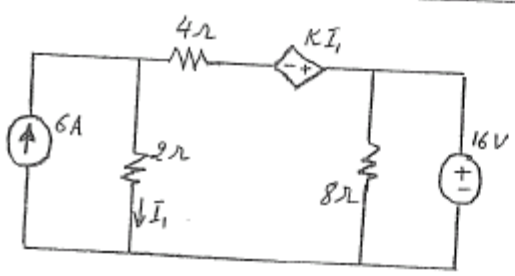


Fig. 4

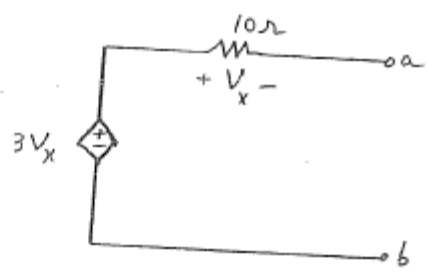


Fig. 8

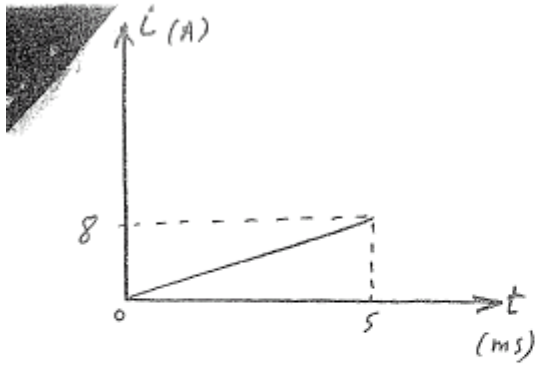


Fig. 9

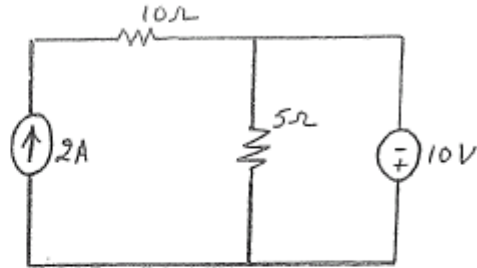


Fig. 12


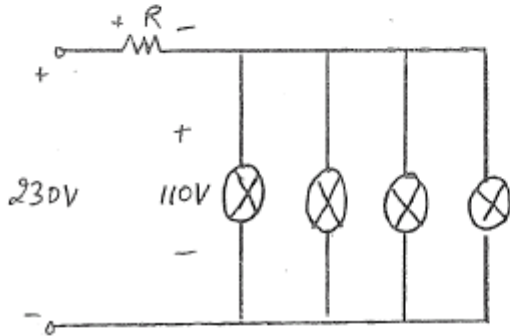


Fig. 10

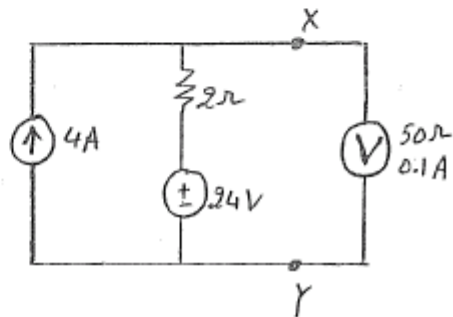

Eng. & Arch. Library

Fig. 13


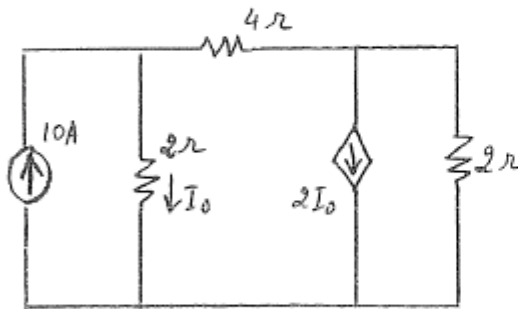


Fig. 11


2 - In the circuit shown below, determine the equivalent resistance R_{ac} .

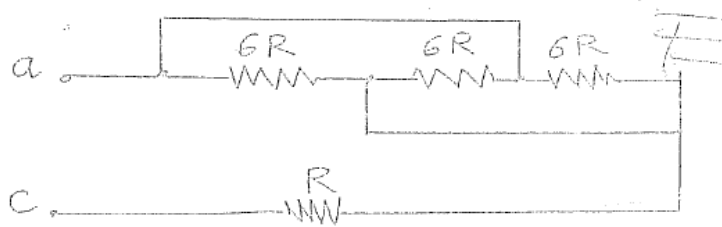- a) $10R$
- b) $18R$
- c) $2R$
- d) $3R$
- e) none of the above




3 - If the interconnection of different sources in the following circuit is valid, find the total absorbed and delivered power in this circuit.

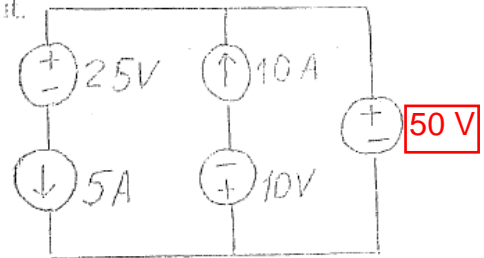- a) The interconnection is not valid
- b) $P(\text{absorbed})$ is 2400 W, $P(\text{delivered})$ is 2400 W
- c) $P(\text{absorbed})$ is 450 W, $P(\text{delivered})$ is 450 W
- d) $P(\text{absorbed})$ is 600 W, $P(\text{delivered})$ is 600 W
- e) none of the above



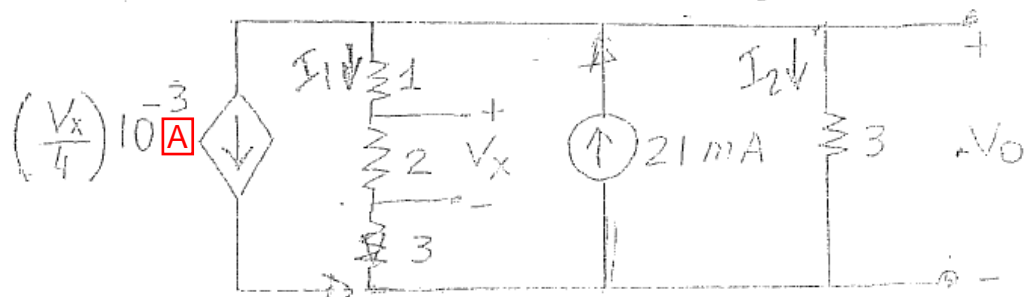
5 - Given the network below, find V_o . (The resistance are given in $k\Omega$)



- a) $36 \cdot 10^{-3}$ V, b) 41 V, c) 36 V, d) 63 V
- e) none of the above


7- Find V_o in the following circuit. (The resistance are given in Ohm)

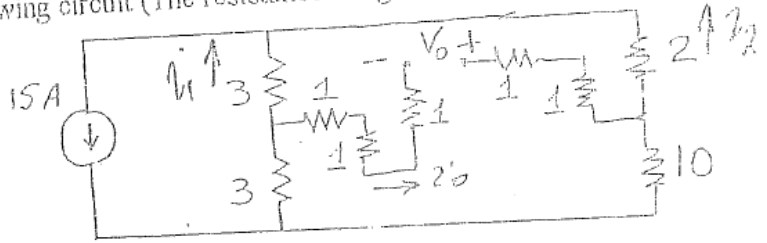- a) $V_o = 5 \text{ V}$
- b) $V_o = -200 \text{ V}$
- c) $V_o = -20 \text{ V}$
- d) $V_o = -25 \text{ V}$
- e) none of the above




1. Determine R_{in} in the figure, given that $R = 1 \text{ k}\Omega$, $m = 2$, and $k = 2$.

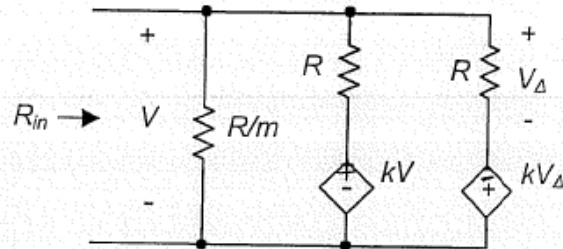- A. Infinite
 B. Zero Ω
 C. $1 \text{ k}\Omega$
 D. $2 \text{ k}\Omega$
 E. None of the above



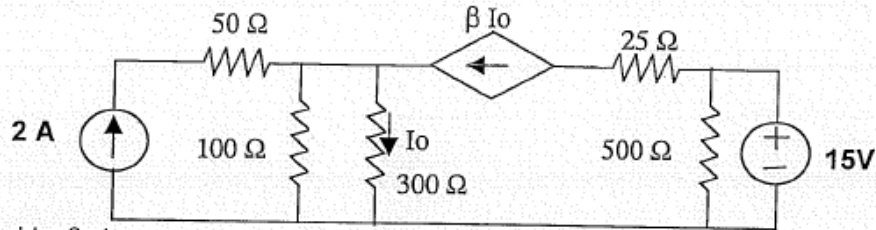
2. Considering the circuit below, find the current I_o flowing through the resistor 300Ω .



Consider $\beta=1$


- a) 0.667 A
 b) 1.000 A
 c) 1.333 A
 d) 2.000 A
 e) None of the above

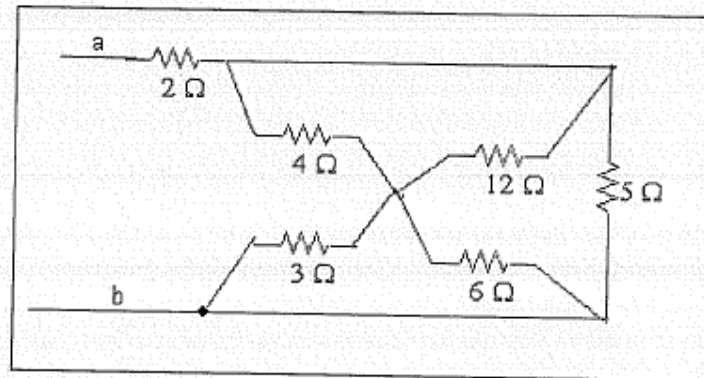11. Find the equivalent resistance between the terminals (a,b).




- a) $4.50\ \Omega$
- b) $2.25\ \Omega$
- c) $12.5\ \Omega$
- d) $8.0\ \Omega$
- e) none of the above

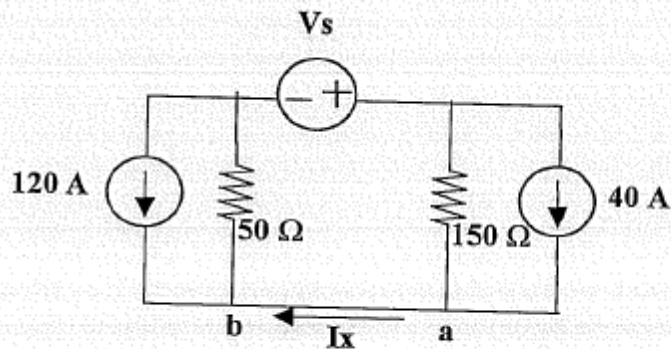2. In the circuit below, find the value of the current I_x flowing between node a and node b. ($V_s = 10V$)



- a) $+50\text{mA}$
- b) $+100\text{mA}$
- c) -30 A
- d) $+30\text{A}$
- e) None of the above

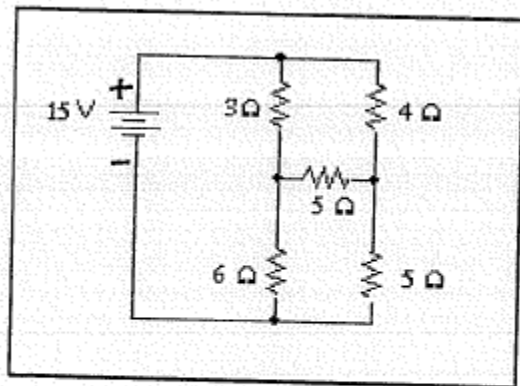10. For the circuit shown below determine the power supplied by the source.




- a. 63.1 W
- b. 36.3 W
- c. 21.6 W
- d. 50.3 W
- e. None of the above

7%

3. Determine V_{ab} , given that all current sources are 1 A and all resistances are $5\ \Omega$.

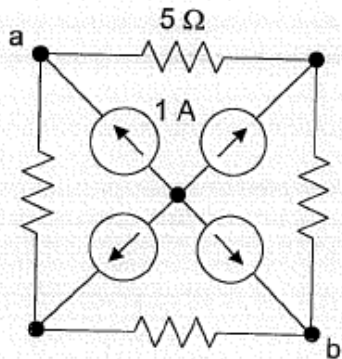- A. 5 V
- B. 10 V
- C. 15 V
- D. 20 V
- E. Not a valid connection



8%

1. Determine R_{eq} .


A. 5Ω

B. 10Ω

C. 0

D. Infinite

E. None of the above

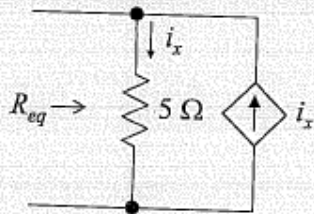

Solution: If a source v_T is applied, the source current is $i_T = i_x - i_x = 0$. The resistance seen by the source R_{eq} is therefore infinite.

8%

2. Determine I_x in the circuit shown.

A. 2 A



B. 4 A

C. -2 A

D. -4 A

E. None of the above


Solution: KCL at the upper node gives a current of $4I_x$ in the $2\ \Omega$ resistor; $2I_s = 10I_x$; from KVL around the right mesh: $10I_x = 8I_x + 4$, so that $I_x = 2\text{ A}$.

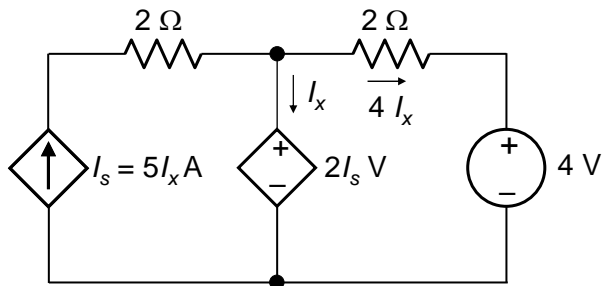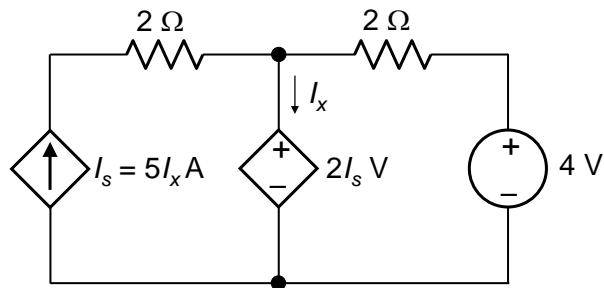

Problem 1

Find R_{ab} .


- A) 12 ohms
- B) 7.5 ohms**
- C) 10 ohms
- D) 15 ohms
- E) None of the above

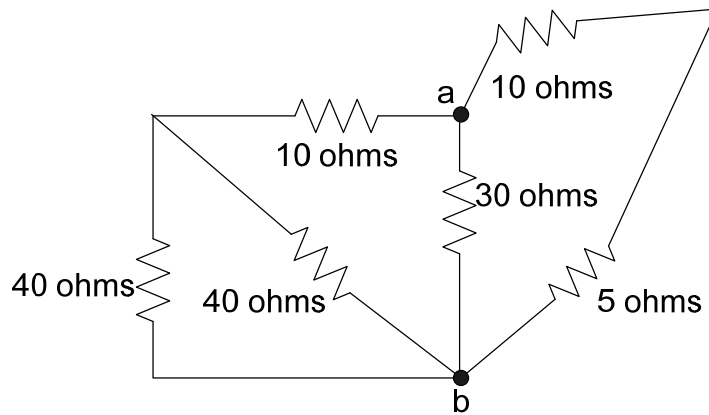

Problem 2

Find the power consumed by the 50 ohm resistor in the circuit shown below


- A) $P = 0.246 \text{ W}$
- B) $P = 0.692 \text{ W}$**
- C) $P = 2.358 \text{ W}$
- D) $P = 5.100 \text{ W}$
- E) None of the above

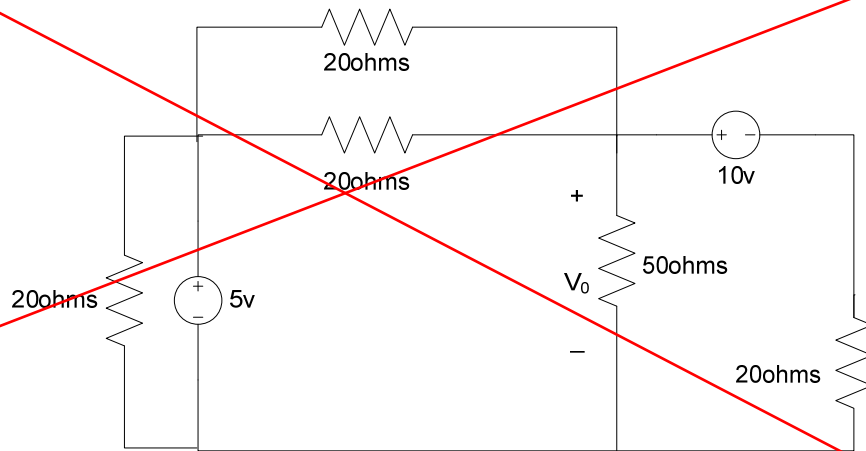


Problem 3

Find V_0 in the 30 Ohm resistor in the circuit shown below

- A) $V_0 = 6 \text{ V}$
- B) $V_0 = 66 \text{ V}$**
- C) $V_0 = 72 \text{ V}$
- D) $V_0 = 78 \text{ V}$
- E) None of the above

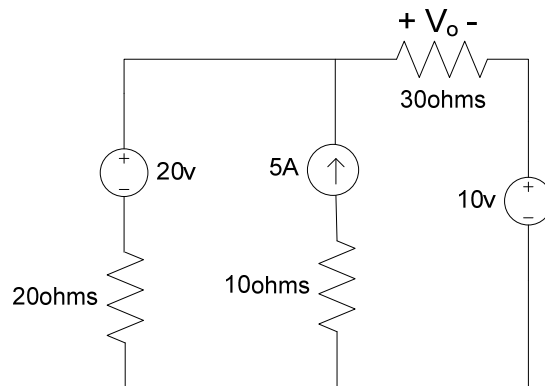


Problem 4

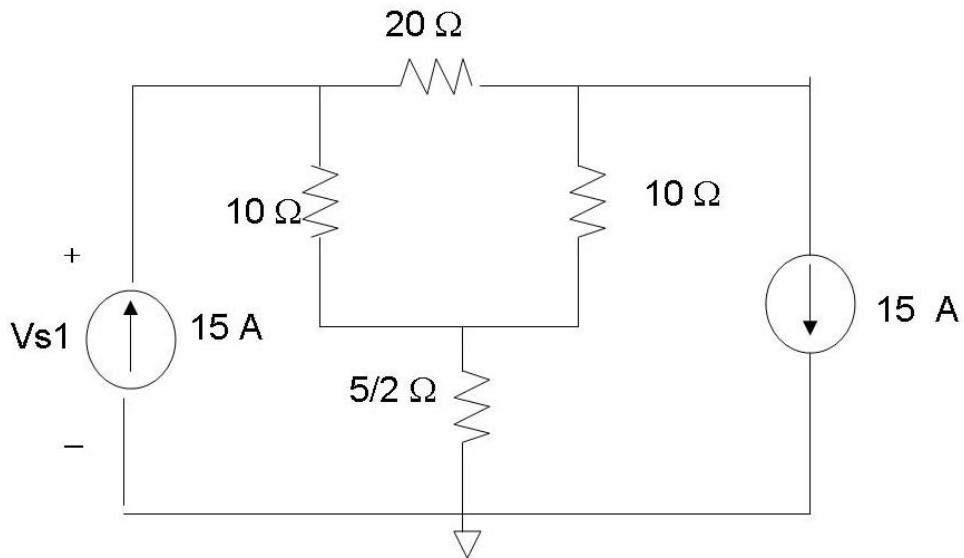

In the circuit shown, find the voltage denoted by V_{s1}

- A) $300\ \text{V}$
- B) $150\ \text{V}$
- C) $-150\ \text{V}$
- D) $75\ \text{V}$
- E) None of the above


Problem 5

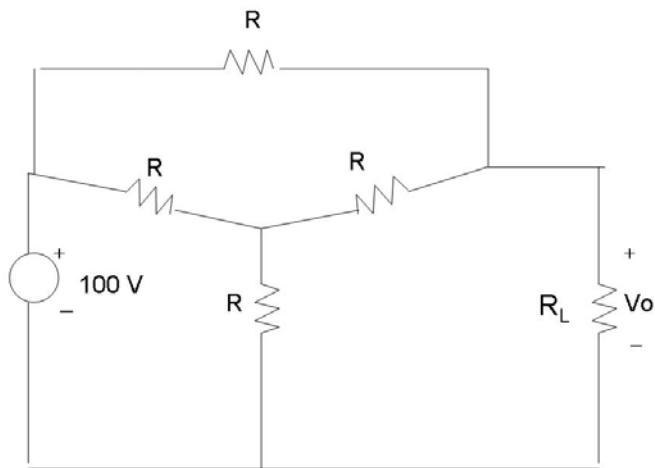

In the circuit shown above, find the value of the load resistance R_L in terms of R such that V_o is $50\ \text{V}$.

- A) $R/3$
- B) $3R$
- C) R
- D) $2R$
- E) None of the above

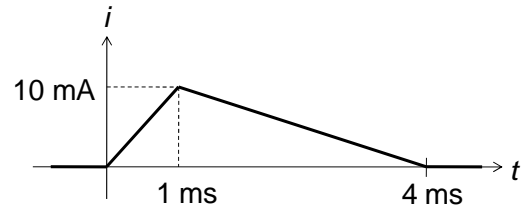1. The current in a $1 \mu\text{F}$ capacitor is shown in the figure as a function of time. The total energy stored in μJ is:




- A. 40
- B. 100
- C. 200
- D. 50
- E. 25

Solution: q at 4 ms is $\frac{10 \times 4}{2} = 20 \mu\text{C}$. The energy in μJ is $W = \frac{(20)^2}{2C} = \frac{200}{C}$, where C is in μF .

2. If $V_{\text{SRC}} = 10 \text{ V}$, determine R_x so that $I_x = 0$.

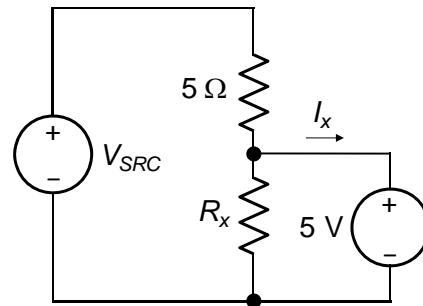- A. 5Ω
- B. 1.25Ω
- C. 2.5Ω
- D. 1Ω
- E. 1.67Ω




Solution: When $I_x = 0$, $\frac{R_x}{R_x + 5} V_{\text{SRC}} = 5$, or

$$R_x = \frac{25}{V_{\text{SRC}} - 5} \Omega.$$

3. If $R = 10 \Omega$, determine the ratio ρ/α so that $I_1 = I_2$.


- A. 4Ω
- B. 10Ω
- C. 6Ω
- D. 5Ω
- E. 8Ω

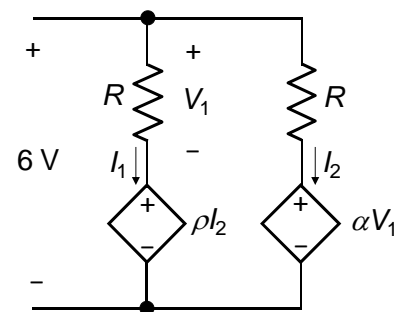

Solution: $I_1 = \frac{6 - \rho I_2}{R}$, $I_2 = \frac{6 - \alpha R I_1}{R}$, or

$$\frac{6 - \rho I_1}{R} = \frac{6 - \alpha R I_1}{R}, \text{ which gives } \rho/\alpha = R.$$

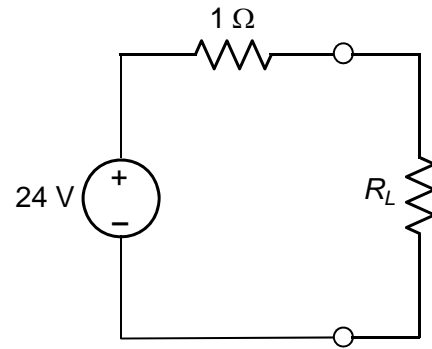4. In the figure shown, the 24 V source having a source resistance of 1Ω is replaced by the equivalent current source, the load resistance R_L being the same. If $R_L = 5 \Omega$, the ratio of the power delivered by the **ideal** current source to the power delivered by the **ideal** 24 V source is:




- A. 5
- B. 11
- C. 7
- D. 14
- E. 9

Solution: The power delivered by the ideal voltage source is $24 \times \frac{24}{R_L + 1}$. The equivalent current source is an ideal current source of 24 A in parallel with 1Ω . The power delivered by the current source is $24 \times 24 \frac{R_L \times 1}{R_L + 1}$. The ratio of the powers is numerically equal to R_L .

5. Determine V_O in the circuit shown if $R = 1 \Omega$

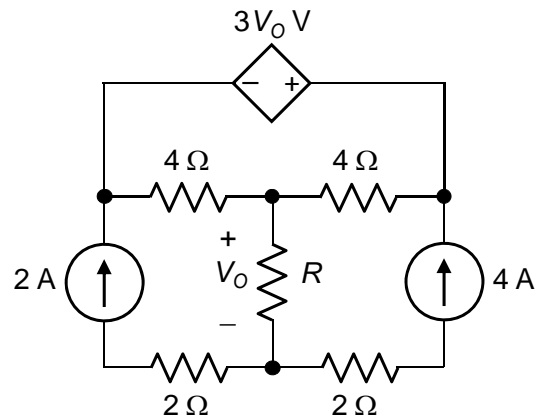
- A. 18 V
- B. 12 V
- C. 30 V
- D. 6 V
- E. 24 V



Solution: The current through R is 6 A, so that $V_O = 6R$.

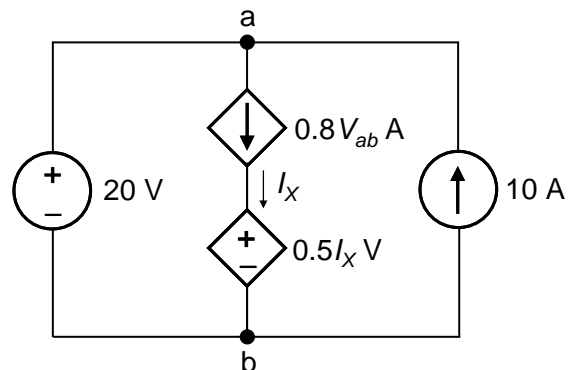6. Given the source connections shown. Determine the actual power delivered or absorbed by each source.

Solution: $I_x = 0.8 \times 20 = 16$ A. Current in 20 V source is 6 A in the direction of a voltage rise. Voltage across dependent voltage source is $0.5 \times 16 = 8$ V. Voltage across



dependent current source is $20 - 8 = 12$ V. It follows that:


Power delivered by 20 V source is $20 \times 6 = 120$ W

Power delivered by 10 A source is $20 \times 10 = 200$ W

Power absorbed by dependent current source is $12 \times 16 = 192$ W

Power absorbed by dependent voltage source is $8 \times 16 = 128$ W

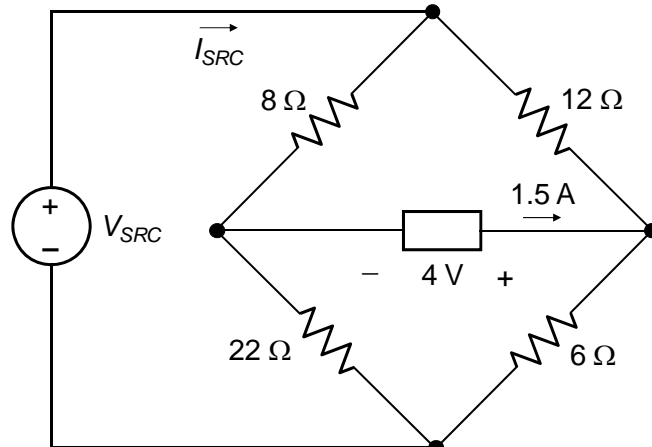7. Determine V_{SRC} , I_{SRC} , and the voltages across the four resistors in the circuit shown. (Four grade points for each answer plus 1 bonus grade).



Solution: Going CCW around the

upper mesh:

$$4 + 12I_1 - 8I_2 = 0$$

Going CW around the

lower mesh:

$$4 - 6(I_1 + 1.5) + 22(I_2 - 1.5) = 0$$

The two equations

reduce to:

$$3I_1 - 2I_2 = -1$$

$$-3I_1 + 11I_2 = 19$$

This gives: $I_1 = 1$ A; $I_2 = 2$ A. Hence,

Voltage across 12 Ω resistor: 12 V


Voltage across 6 Ω resistor: 15 V

Voltage across 8 Ω resistor: 16 V

Voltage across 22 Ω resistor: 11 V



$$V_{SRC} = 27$$

$$I_{SRC} = 3$$

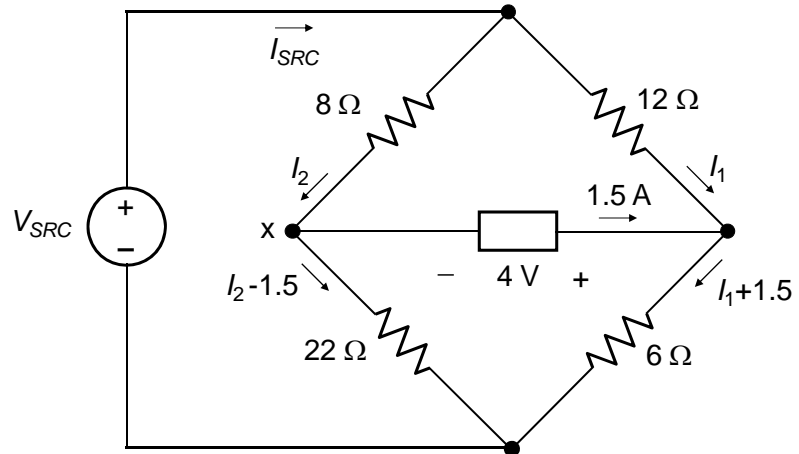

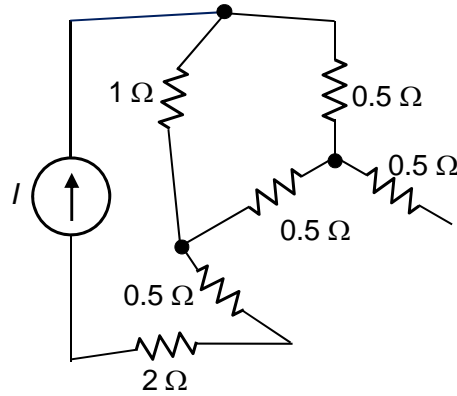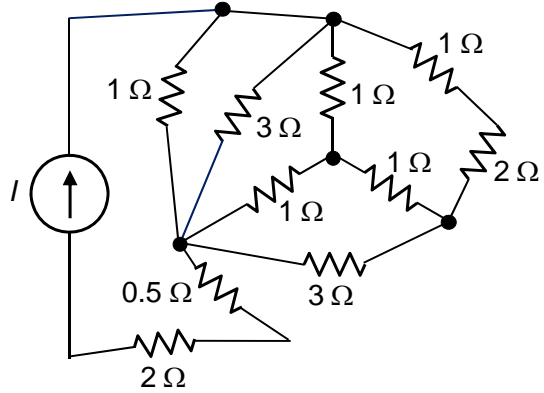1. Determine the power dissipated in the circuit, assuming $I = 1$ A.


Solution: The $1\ \Omega$ Y is paralleled with a $3\ \Omega$ Δ , so that it effectively becomes a $0.5\ \Omega$ Y, and the circuit reduces to that shown. The resistance seen by the current source is $1 \parallel 1 + 2.5 = 3\ \Omega$, so that the power dissipated in the circuit is $P = 3I^2$ W.



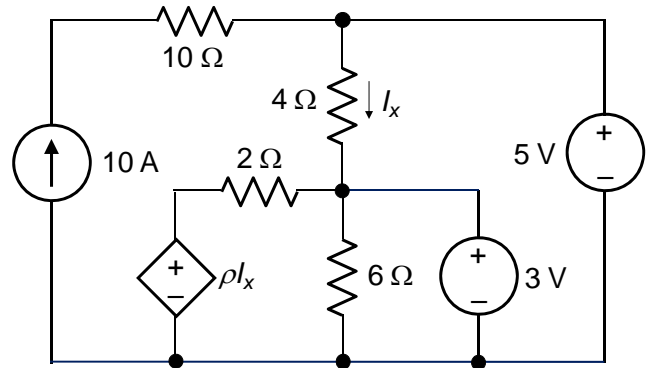2. Determine the power delivered by the 3 V source, assuming $\rho = 2$ V/A.


Solution: The upper node is at 5 V with respect to the lowest node, the middle node is at 3 V. hence, $I_x = 0.5$ A and the current in the $6\ \Omega$ resistor is also 0.5 A.

The current supplied by the 3 V source is $(3 - 0.5\rho)/2$ and the power delivered by the source is $P = 1.5(3 - 0.5\rho) = 4.5 - 0.75\rho$ W.



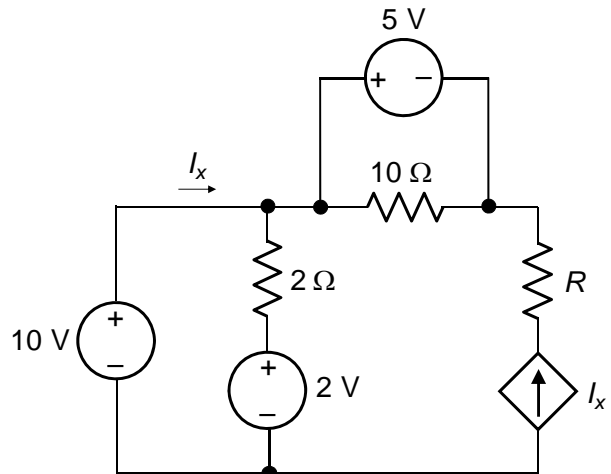6. Determine the power absorbed or delivered by the dependent source assuming $R = 1\ \Omega$.


Solution: The current in the $2\ \Omega$ resistor is $2I_x$ flowing downwards. From KVL in the mesh on the left, $10 = 4I_x + 2$, or $I_x = 2$ A. The voltage rise V_x across the dependent source is given by: $V_x - RI_x = 5$, or $V_x = 2R$



+ 5; The power P delivered by the source is $P = 2(2 \times R + 5)$.


16. Determine V_O .

Solution: The $2V_x$ source is replaced by a 10 A source. The current in the 2Ω resistor is I_x . The current in the dependent source is $5 - 2I_x$, so that the current in the 1Ω resistor is $15 - I_x$. From KVL around the mesh abcd, $2I_x + 15 - I_x = 4I_x$, which gives $I_x = 5$ A. It follows that $V_O = 15 - I_x = 10$ V.

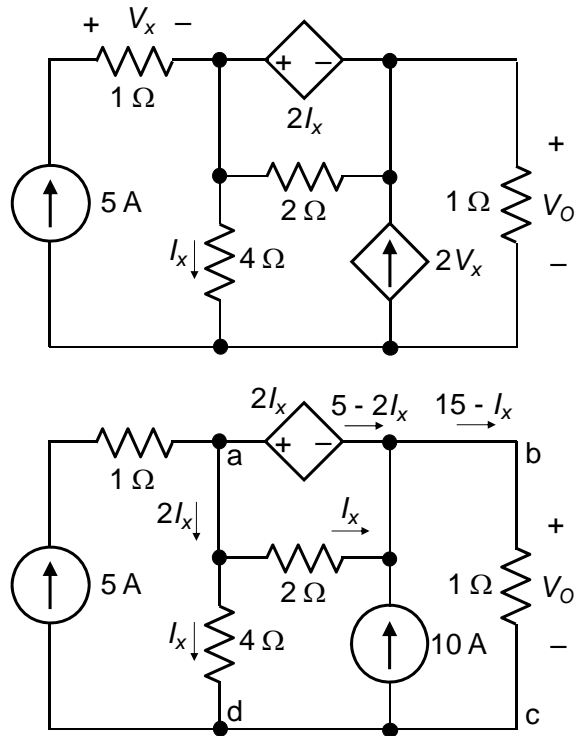

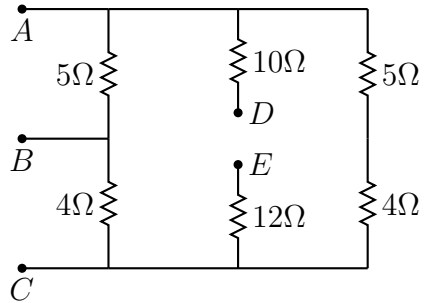Problem 1


Find the equivalent resistance between B and E.



- A) 15.11Ω
- B) 16Ω
- C) 8.33Ω
- D) 13.61Ω
- E) None of the above

Problem 2

Find V_0 .

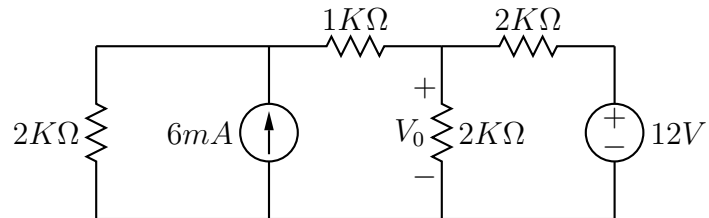

- A) $12V$
- B) $7.5V$
- C) $-12V$
- D) $-7.5V$
- E) None of the above