

American University of Beirut
Department of Electrical and Computer Engineering

EECE 210 – Electric Circuits
Quiz 2 – May 7, 2010
Closed Book – No Programmable Calculators
90 minutes

Name: _____ ID number: _____

Circle your instructor's name:

Ernst Huijer

Rabih Jabr

Danielle Nasrallah

Penalty is 5 to 1

(1 to 4 wrong answers do not result in a penalty; 5 to 9 wrong answers cancel one correct answer; 10 to 14 wrong answers cancel two correct answers; and so on)

- Mark your last name on the computer card with a pencil
- Mark your ID number on the computer card with a pencil
- When using an eraser, make sure you erased well
- Make sure to write your name and ID number on the question sheet and the scratch booklet
- You are required to return the computer card and the question sheet within the scratch booklet


*** OP-AMPS ARE IDEAL AND OPERATING IN THEIR LINEAR REGION.**

*** NOTATION:**

V_{TH} : THEVENIN VOLTAGE
 I_N : NORTON CURRENT
 R_{TH} : THEVENIN RESISTANCE

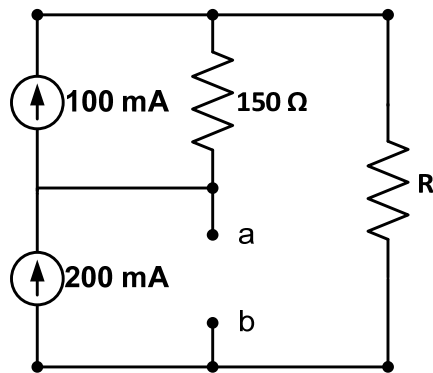*** NOTE THAT QUESTIONS ARE ARRANGED BY TOPIC AND FOR EACH TOPIC THE DEGREE OF DIFFICULTY VARIES**


In the circuit shown below, $R = 100 \Omega$. Refer to this circuit for questions 1 and 2.



1. Determine V_{Th} (in V) with respect to the terminals a-b.
 a) 115 b) 35 c) 75 d) 55 e) 95

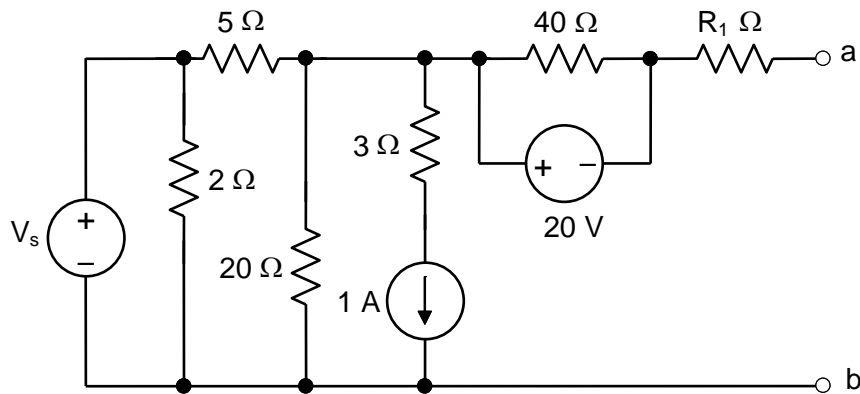2. Determine the Norton current I_N (in mA) with respect to the terminals a-b.
 a) 172.7 b) 166.7 c) 140.0 d) 176.9 e) 157.1


Refer to the circuit shown below for questions 3 and 4.



3. Find V_{Th} (in V) with respect to the terminals a-b when $R_1 = 1 \Omega$ and $V_s = 5 \text{ V}$.
 a) -16 b) -8 c) -4 d) -12 e) -20

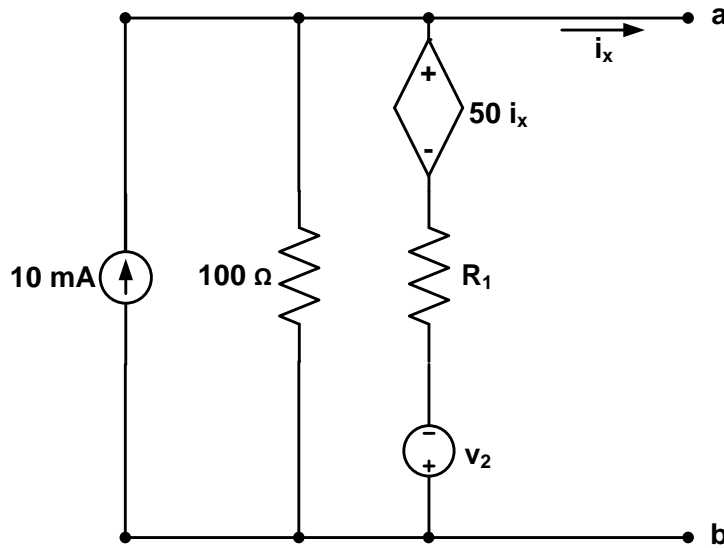4. Find R_{Th} (in Ω) with respect to the terminals a-b when $R_1 = 2 \Omega$ and $V_s = 30 \text{ V}$.
 a) 6 b) 10 c) 9 d) 7 e) 8

In the circuit shown below, $R_1 = 100 \Omega$. Refer to this circuit for questions 5, 6, and 7.



5. To find V_{Th} with respect to the terminals a-b we apply superposition. What is the contribution of just the current source to V_{Th} (in V)?

- a) 0.60 b) 0.71 c) 0.50 d) 0.75 e) 0.67

6. Now we consider the contribution of both sources. For what value of v_2 (in V) do we obtain $V_{Th} = 0$ V?


- a) 2.0 b) 2.5 c) 3.0 d) 1.0 e) 1.5

7. What is the value of R_{Th} (in Ω) with respect to the terminals a-b?


- a) 25.0 b) 57.1 c) 40.0 d) 62.5 e) 50.0

8. In the circuit shown below, $R_1 = 5 \text{ k}\Omega$, $R_2 = R_3 = 10 \text{ k}\Omega$, and $v_o = 1 \text{ V}$. Determine the value of i_s (in mA).

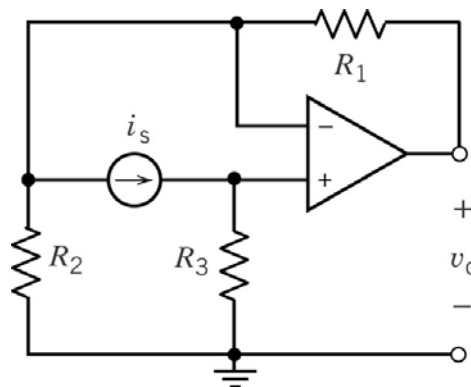
- a) 0.10 b) 0.25 c) 0.15 d) 0.05 e) 0.20



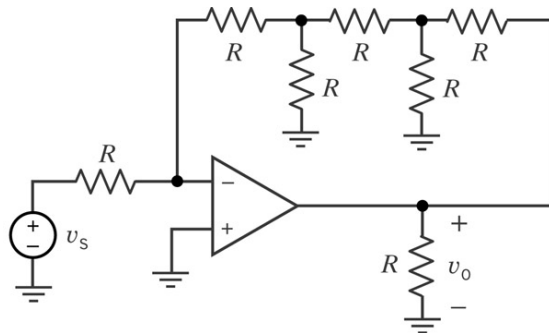
9. In the circuit shown below, $R = 0.5 \text{ k}\Omega$ and the output voltage $v_o = -8 \text{ V}$. Determine the power (in mw) supplied by the input voltage source v_s .
 a) 0.125 b) 2 c) 0.5 d) 1 e) 0.25



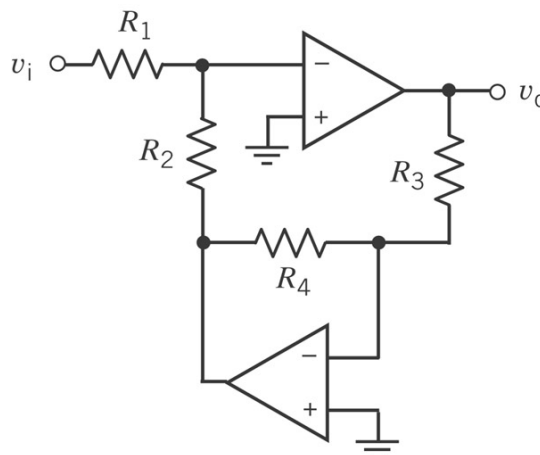
10. In the circuit shown below, $R_1 = R_4 = 10 \text{ k}\Omega$, $R_2 = 40 \text{ k}\Omega$, $R_3 = 50 \text{ k}\Omega$, and $v_i = 0.1 \text{ V}$. Determine the value of v_o (in V).
 a) 8 b) 10 c) 4 d) 6 e) 2



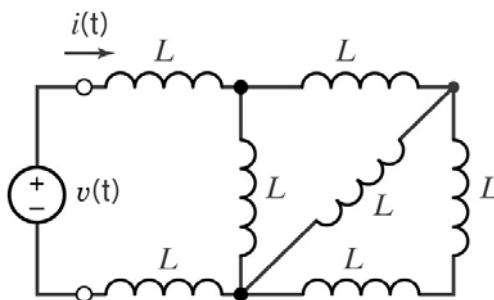
11. The circuit shown below has seven inductors, each having inductance $L = 1 \text{ H}$. The source voltage is given by $v(t) = 4 \cos(3t) \text{ V}$ for $t \geq 0$. Find the current $i(t)$ for $t \geq 0$ (in mA) given that $i(0) = 0$.
 a) $254.0 \sin(3t)$ b) $101.6 \sin(3t)$ c) $169.3 \sin(3t)$ d) $127.0 \sin(3t)$ e) $507.9 \sin(3t)$



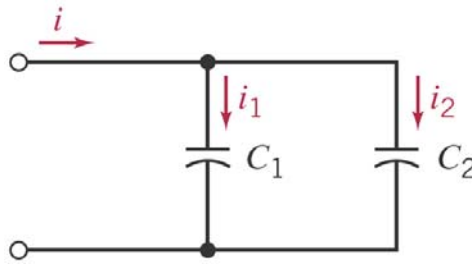
12. In the circuit shown below, $C_1 = 1 \text{ pF}$, $C_2 = 3 \text{ pF}$, and $i(t) = 4te^{-t} \text{ mA}$ for $t > 0$. Find $i_1(t)$ for $t > 0$ (in mA).
- a) $0.5te^{-t}$ b) te^{-t} c) $0.4te^{-t}$ d) $0.25te^{-t}$ e) $0.8te^{-t}$



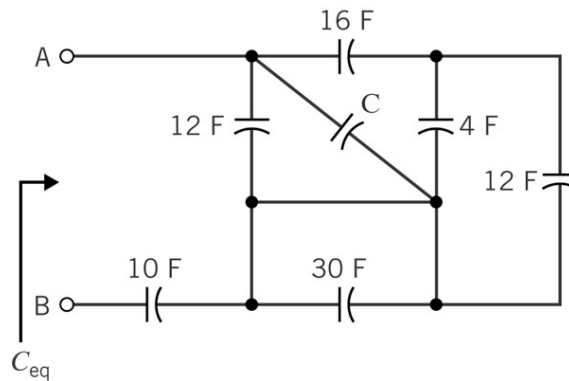
13. Determine the value of the capacitance C (in F) in the circuit shown below, given that $C_{eq} = 7.5 \text{ F}$.
- a) 10 b) 70 c) 95 d) 20 e) 170



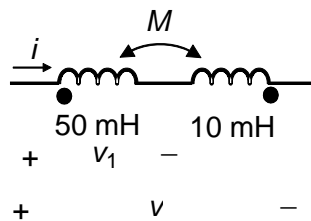14. In the circuit shown below, determine the ratio v_1/v if $M = 5 \text{ mH}$.
- a) 1.75 b) 1.125 c) 0.9 d) 1 e) 1.5



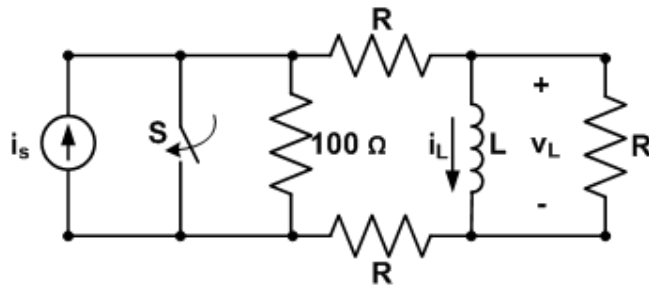In the circuit shown below, the switch S has been open for a long time before it closes at $t=0$. $i_s = 1.5$ A, $R = 50 \Omega$, $L = 200$ mH. Refer to this circuit for questions 15 and 16.



15. Find the value of the time constant τ , that governs the behavior of the circuit for $t > 0$, in ms.


- a) 2.4 b) 6.0 c) 2.0 d) 3.0 e) 4.0

16. Find the value of $v_L(0^+)$ in V.


- a) -37.5 b) -30.0 c) -25.0 d) -35.7 e) -33.3

17. The circuit shown below is at steady state before the switch closes at time $t = 0$. Determine the energy stored in the capacitor (in J) at time $t = 0.5$ s. The following values are given: $R_1 = R_2 = 4 \Omega$, and $C = 1$ F.

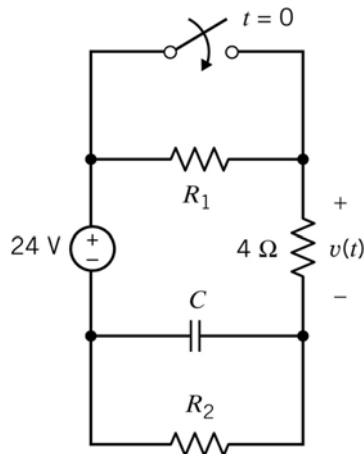- a) 51.11 b) 69.63 c) 45.83 d) 61.69 e) 39.47



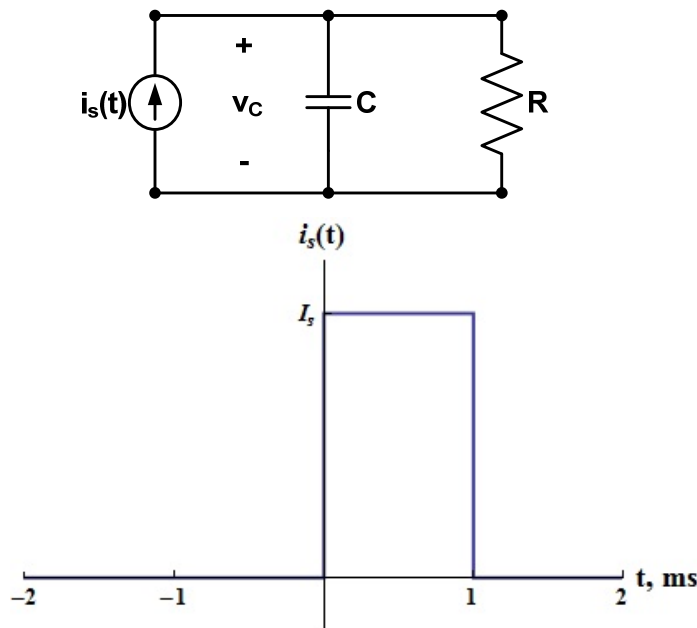In the circuit shown below, the maximum value of the pulse is $I_s = 1 \text{ mA}$, $C = 1 \text{ }\mu\text{F}$, $R = 2 \text{ k}\Omega$. The energy stored in the capacitor is zero for $t < 0$. Refer to this circuit for questions 18 and 19.



18. Determine the maximum value of $v_C(t)$ in V that will occur over time as a response to the current pulse $i_s(t)$, which as a function of time is indicated in the graph shown above.

- a) 3.93 b) 1.57 c) 0.79 d) 3.15 e) 2.36

19. What is the total energy delivered by the current source in μJ ?

- a) 1.70 b) 0.43 c) 10.65 d) 3.83 e) 6.82

20. The circuit shown below is at steady state before the switch closes at time $t = 0$. Determine the inductor current $i(t)$ in A at time $t = 0.2 \text{ s}$.

- a) -1.549 b) 0.596 c) -0.774 d) 1.016 e) -1.834

