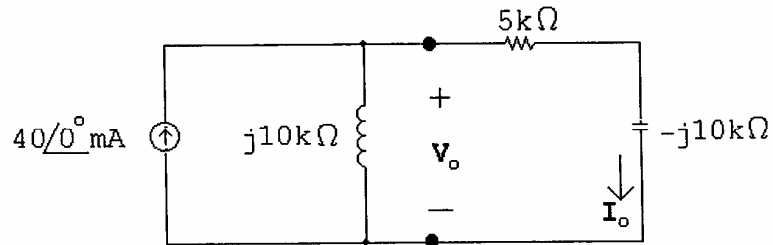


Homework 10

P 10.9 $\mathbf{I}_g = 40\angle 0^\circ \text{ mA}$

$$j\omega L = j10,000 \Omega; \quad \frac{1}{j\omega C} = -j10,000 \Omega$$



$$\mathbf{I}_o = \frac{j10,000}{5000} (40\angle 0^\circ) = 80\angle 90^\circ \text{ mA}$$

$$P = \frac{1}{2} |\mathbf{I}_o|^2 (5000) = \frac{1}{2} (0.08)^2 (5000) = 16 \text{ W}$$

$$Q = \frac{1}{2} |\mathbf{I}_o|^2 (-10,000) = -32 \text{ VAR}$$

$$S = P + jQ = 16 - j32 \text{ VA}$$

$$|S| = 35.78 \text{ VA}$$

P 10.13 $Z_f = -j10,000 \parallel 20,000 = 4000 - j8000 \Omega$

$$Z_i = 2000 - j2000 \Omega$$


$$\therefore \frac{Z_f}{Z_i} = \frac{4000 - j8000}{2000 - j2000} = 3 - j1$$

$$\mathbf{V}_o = -\frac{Z_f}{Z_i} \mathbf{V}_g; \quad \mathbf{V}_g = 1\angle 0^\circ \text{ V}$$

$$\mathbf{V}_o = (3 - j1)(1) = 3 - j1 = 3.16\angle -18.43^\circ \text{ V}$$

$$P = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} \frac{(10)}{1000} = 5 \times 10^{-3} = 5 \text{ mW}$$

P 10.21

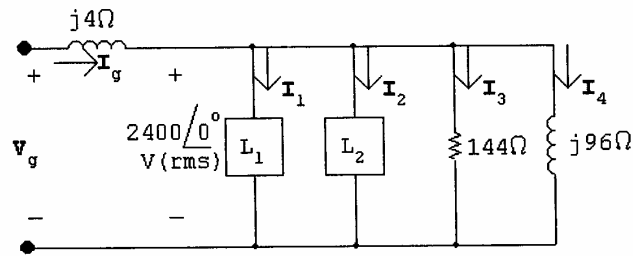

$$2400\mathbf{I}_1^* = 60,000 + j40,000$$

$$\mathbf{I}_1^* = 25 + j16.67; \quad \therefore \mathbf{I}_1 = 25 - j16.67 \text{ A(rms)}$$

$$2400\mathbf{I}_2^* = 20,000 - j10,000$$

$$\mathbf{I}_2^* = 8.33 - j4.167; \quad \therefore \mathbf{I}_2 = 8.33 + j4.167 \text{ A(rms)}$$

$$\mathbf{I}_3 = \frac{2400\angle 0^\circ}{144} = 16.67 + j0 \text{ A}; \quad \mathbf{I}_4 = \frac{2400\angle 0^\circ}{j96} = 0 - j25 \text{ A}$$

$$\mathbf{I}_g = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 + \mathbf{I}_4 = 50 - j37.5 \text{ A}$$

$$\mathbf{V}_g = 2400 + (j4)(50 - j37.5) = 2550 + j200 = 2557.83\angle 4.48^\circ \text{ V(rms)}$$

P 10.25 [a] $\mathbf{I} = \frac{465\angle 0^\circ}{124 + j93} = 2.4 - j1.8 = 3\angle -36.87^\circ \text{ A(rms)}$

$$P = (3)^2(4) = 36 \text{ W}$$

[b] $Y_L = \frac{1}{120 + j90} = 5.33 - j4 \text{ mS}$

$$\therefore X_C = \frac{1}{-4 \times 10^{-3}} = -250 \Omega$$

[c] $Z_L = \frac{1}{5.33 \times 10^{-3}} = 187.5 \Omega$

[d] $\mathbf{I} = \frac{465\angle 0^\circ}{191.5 + j3} = 2.43\angle -0.9^\circ \text{ A}$

$$P = (2.43)^2(4) = 23.58 \text{ W}$$

[e] $\% = \frac{23.58}{36}(100) = 65.5\%$

Thus the power loss after the capacitor is added is 65.6% of the power loss before the capacitor is added.


P 10.38 [a] First find the Thévenin equivalent:

$$j\omega L = j3000 \Omega$$

$$Z_{Th} = 6000 \parallel 12,000 + j3000 = 4000 + j3000 \Omega$$

$$\mathbf{V}_{Th} = \frac{12,000}{6000 + 12,000}(180) = 120 \angle 0^\circ \text{ V}$$

$$\frac{-j}{\omega C} = -j1000 \Omega$$

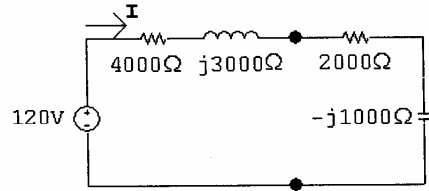

$$\mathbf{I} = \frac{120}{6000 + j2000} = 18 - j6 \text{ mA}$$

$$P = \frac{1}{2} |\mathbf{I}|^2 (2000) = 360 \text{ mW}$$

[b] Set $C_o = 0.1 \mu\text{F}$ so $-j/\omega C = -j2000 \Omega$ $j3000 - j2000 = j1000 \Omega$
Set R_o as close as possible to

$$R_o = \sqrt{4000^2 + 1000^2} = 4123.1 \Omega$$

$$\therefore R_o = 4000 \Omega$$

$$\text{[c] } \mathbf{I} = \frac{120}{8000 + j1000} = 14.77 - j1.85 \text{ mA}$$

$$P = \frac{1}{2} |\mathbf{I}|^2 (4000) = 443.1 \text{ mW}$$

Yes; $443.1 \text{ mW} > 360 \text{ mW}$

$$\text{[d] } \mathbf{I} = \frac{120}{8000} = 15 \text{ mA}$$

$$P = \frac{1}{2} (0.015)^2 (4000) = 450 \text{ mW}$$

[e] $R_o = 4000 \Omega$; $C_o = 66.67 \text{ nF}$

[f] Yes; $450 \text{ mW} > 443.1 \text{ mW}$