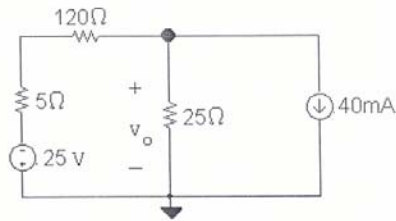


Homework 3 Solution

P 4.6




Note that we have chosen the lower node as the reference node, and that the voltage at the upper node with respect to the reference node is v_o . Write a KCL equation (node voltage equation) by summing the currents leaving the upper node:

$$\frac{v_o + 25}{120 + 5} + \frac{v_o}{25} + 0.04 = 0$$

Solve by multiplying both sides of the KCL equation by 125 and collecting the terms involving v_o on one side of the equation and the constants on the other side of the equation:

$$v_o + 25 + 5v_o + 5 = 0 \quad \therefore \quad 6v_o = -30 \quad \text{so} \quad v_o = -30/6 = -5 \text{ V}$$

P 4.11 [a]

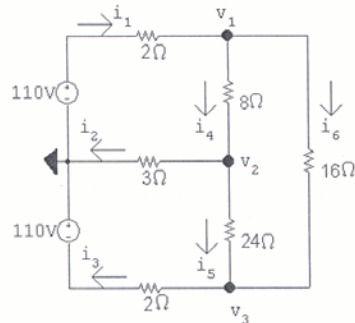

$$\frac{v_1 - 110}{2} + \frac{v_1 - v_2}{8} + \frac{v_1 - v_3}{16} = 0 \quad \text{so} \quad 11v_1 - 2v_2 - v_3 = 880$$

$$\frac{v_2 - v_1}{8} + \frac{v_2}{3} + \frac{v_2 - v_3}{24} = 0 \quad \text{so} \quad -3v_1 + 12v_2 - v_3 = 0$$

$$\frac{v_3 + 110}{2} + \frac{v_3 - v_2}{24} + \frac{v_3 - v_1}{16} = 0 \quad \text{so} \quad -3v_1 - 2v_2 + 29v_3 = -2640$$

Solving, $v_1 = 74.64 \text{ V}$; $v_2 = 11.79 \text{ V}$; $v_3 = -82.5 \text{ V}$

$$\text{Thus, } i_1 = \frac{110 - v_1}{2} = 17.68 \text{ A} \quad i_4 = \frac{v_1 - v_2}{8} = 7.86 \text{ A}$$

$$i_2 = \frac{v_2}{3} = 3.93 \text{ A} \quad i_5 = \frac{v_2 - v_3}{24} = 3.93 \text{ A}$$


$$i_3 = \frac{v_3 + 110}{2} = 13.75 \text{ A} \quad i_6 = \frac{v_1 - v_3}{16} = 9.82 \text{ A}$$

[b] $\sum P_{\text{dev}} = 110i_1 + 110i_3 = 3457.14 \text{ W}$

$$\sum P_{\text{dis}} = i_1^2(2) + i_2^2(3) + i_3^2(2) + i_4^2(8) + i_5^2(24) + i_6^2(16) = 3457.14 \text{ W}$$

P 4.12

P 4.14

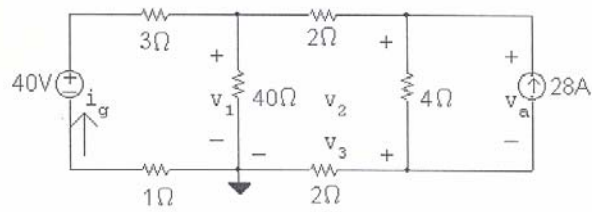

The three node voltage equations are:

$$\frac{v_1 - 40}{4} + \frac{v_1}{40} + \frac{v_1 - v_2}{2} = 0$$

$$\frac{v_2 - v_1}{2} + \frac{v_2 - v_3}{4} - 28 = 0$$

$$\frac{v_3}{2} + \frac{v_3 - v_2}{4} + 28 = 0$$


Place these equations in standard form:

$$v_1 \left(\frac{1}{4} + \frac{1}{40} + \frac{1}{2} \right) + v_2 \left(-\frac{1}{2} \right) + v_3(0) = \frac{40}{4}$$

$$v_1 \left(-\frac{1}{2} \right) + v_2 \left(\frac{1}{2} + \frac{1}{4} \right) + v_3 \left(-\frac{1}{4} \right) = 28$$

$$v_1(0) + v_2 \left(-\frac{1}{4} \right) + v_3 \left(\frac{1}{2} + \frac{1}{4} \right) = -28$$

P 4.33

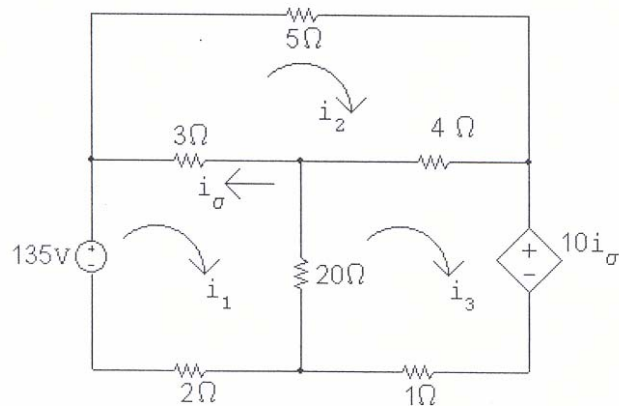

$$-135 + 3(i_1 - i_2) + 20(i_1 - i_3) + 2i_1 = 0$$

$$5i_2 + 4(i_2 - i_3) + 3(i_2 - i_1) = 0$$

$$10i_\sigma + 1i_3 + 20(i_3 - i_1) + 4(i_3 - i_2) = 0$$

The dependent source constraint equation is:

$$i_\sigma = i_2 - i_1$$

Place these equations in standard form:

$$i_1(3 + 20 + 2) + i_2(-3) + i_3(-20) + i_\sigma(0) = 135$$

$$i_1(-3) + i_2(5 + 4 + 3) + i_3(-4) + i_\sigma(0) = 0$$

$$i_1(-20) + i_2(-4) + i_3(1 + 20 + 4) + i_\sigma(10) = 0$$

$$i_1(1) + i_2(-1) + i_3(0) + i_\sigma(1) = 0$$


Solving, $i_1 = 64.8 \text{ A}$, $i_2 = 39 \text{ A}$; $i_3 = 68.4 \text{ A}$; $i_\sigma = -25.8 \text{ A}$

Calculate the power:

$$p_{20\Omega} = 20(68.4 - 64.8)^2 = 259.2 \text{ W}$$

Thus the 20Ω resistor dissipates 259.2 W.

P 4.34

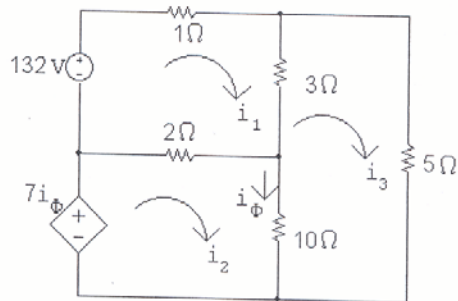

The mesh current equations:

$$-132 + 1i_1 + 3(i_1 - i_3) + 2(i_1 - i_2) = 0$$

$$-7i_\phi + 2(i_2 - i_1) + 10(i_2 - i_3) = 0$$

$$5i_3 + 10(i_3 - i_2) + 3(i_3 - i_1) = 0$$

The dependent source constraint equation:

$$i_\phi = i_2 - i_3$$

Place these equations in standard form:

$$i_1(1 + 3 + 2) + i_2(-2) + i_3(-3) + i_\phi(0) = 132$$

$$i_1(-2) + i_2(10 + 2) + i_3(-10) + i_\phi(-7) = 0$$

$$i_1(-3) + i_2(-10) + i_3(5 + 10 + 3) + i_\phi(0) = 0$$

$$i_1(0) + i_2(-1) + i_3(1) + i_\phi(1) = 0$$

Solving, $i_1 = 48 \text{ A}$; $i_2 = 36 \text{ A}$; $i_3 = 28 \text{ A}$; $i_\phi = 8 \text{ A}$

Solve for the power:

$$p_{\text{dep source}} = -7(i_\phi)i_2 = -7(8)(36) = -2016 \text{ W}$$

Thus, the dependent source is developing 2016 W.