

## Homework 4

### Solution

P 5.5 [a]  $i_a = \frac{25 \times 10^{-3}}{5000} = 5 \mu\text{A}$

$$v_a = -50 \times 10^3 i_a = -250 \text{ mV}$$

[b]  $\frac{v_a}{50,000} + \frac{v_a}{10,000} + \frac{v_a - v_o}{40,000} = 0$

$$\therefore 4v_a + 20v_a + 5v_a - 5v_o = 0$$

$$\therefore v_o = 29v_a/5 = -1.45 \text{ V}$$

[c]  $i_a = 5 \mu\text{A}$

[d]  $i_o = \frac{-v_o}{30,000} + \frac{v_a - v_o}{40,000} = 78.33 \mu\text{A}$

P 5.16 [a] This circuit is an example of an inverting summing amplifier.

[b]  $v_o = -\frac{220}{33}v_a - \frac{220}{22}v_b - \frac{220}{80}v_c = -8 + 15 - 11 = -4 \text{ V}$

[c]  $v_o = -19 - 10v_b = \pm 6$

$$\therefore v_b = -1.3 \text{ V} \quad \text{when } v_o = -6 \text{ V};$$

$$v_b = -2.5 \text{ V} \quad \text{when } v_o = 6 \text{ V}$$

$$\therefore -2.5 \text{ V} \leq v_b \leq -1.3 \text{ V}$$

P 5.25 [a] The circuit is a non-inverting summing amplifier.

$$\text{[b]} \frac{v_p - v_a}{3.3 \times 10^3} + \frac{v_p - v_b}{4.7 \times 10^3} = 0$$

$$\therefore v_p = 0.5875v_a + 0.4125v_b$$

$$\frac{v_n}{10,000} + \frac{v_n - v_o}{100,000} = 0$$

$$\therefore v_o = 11v_n = 11v_p = 6.4625v_a + 4.5375v_b = 8.03 \text{ V}$$

$$\text{[c]} v_p = v_n = \frac{v_o}{11} = 730 \text{ mV}$$

$$i_a = \frac{v_a - v_p}{3.3 \times 10^3} = -100 \mu\text{A}$$

$$i_b = \frac{v_b - v_p}{4.7 \times 10^3} = 100 \mu\text{A}$$

[d] 6.4625 for  $v_a$

4.5375 for  $v_b$

$$\text{P 5.31 [a]} v_o = \frac{R_d(R_a + R_b)}{R_a(R_c + R_d)}v_b - \frac{R_b}{R_a}v_a = \frac{47(110)}{10(80)}(0.80) - 10(0.67)$$

$$v_o = 5.17 - 6.70 = -1.53 \text{ V}$$

$$\text{[b]} v_n = v_p = \frac{(800)(47)}{80} = 470 \text{ mV}$$

$$i_a = \frac{(670 - 470)10^{-3}}{10 \times 10^3} = 20 \mu\text{A}$$

$$R_a = \frac{v_a}{i_a} = \frac{670 \times 10^{-3}}{20 \times 10^{-6}} = 33.5 \text{ k}\Omega$$

$$\text{[c]} R_{\text{in}b} = R_c + R_d = 80 \text{ k}\Omega$$

$$\text{P 5.32} \quad v_p = \frac{v_b R_b}{R_a + R_b} = v_n$$

$$\frac{v_n - v_a}{4700} + \frac{v_n - v_o}{R_f} = 0$$

$$v_n \left( \frac{R_f}{4700} + 1 \right) - \frac{v_a R_f}{4700} = v_o$$

$$\therefore \left( \frac{R_f}{4700} + 1 \right) \frac{R_b}{R_a + R_b} v_b - \frac{R_f}{4700} v_a = v_o$$

$$\therefore \frac{R_f}{4700} = 10; \quad R_f = 47 \text{ k}\Omega$$

$$\therefore \frac{R_f}{4700} + 1 = 11$$

$$\therefore 11 \left( \frac{R_b}{R_a + R_b} \right) = 10$$

$$11R_b = 10R_b + 10R_a \quad R_b = 10R_a$$

$$R_a + R_b = 220 \text{ k}\Omega$$

$$11R_a = 220 \text{ k}\Omega$$

$$R_a = 20 \text{ k}\Omega$$

$$R_b = 220 - 20 = 200 \text{ k}\Omega$$