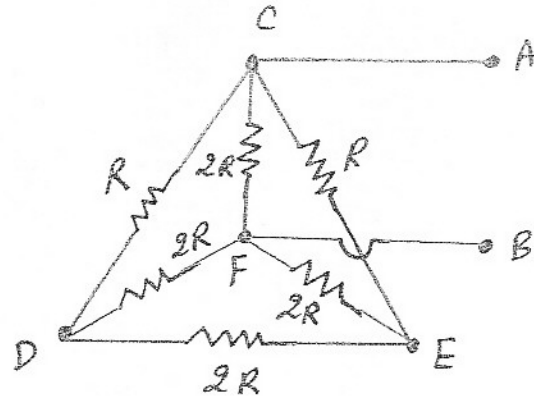



1. Determine the resistance between terminals A and B in the circuit below.

- a. $6R/7$
- b. $3R/7$
- c. $4R/7$
- d. $5R/7$
- e. none of the above




2. Determine the values of resistances R_1 and R_2 in the network below such that I_1 and I_2 are equal to 4A and 6A respectively.

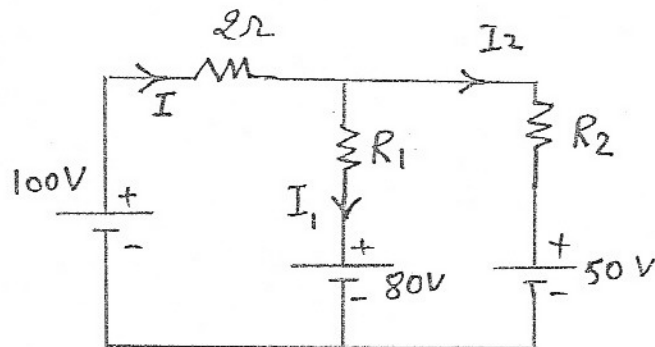- a. $R_1 = 0\Omega, R_2 = 11.6\Omega$
- b. $R_1 = 10\Omega, R_2 = 5\Omega$
- c. $R_1 = 0\Omega, R_2 = 5\Omega$
- d. $R_1 = 10\Omega, R_2 = 11.6\Omega$
- e. none of the above




3. The op amp in the circuit below is ideal. Calculate V_o .

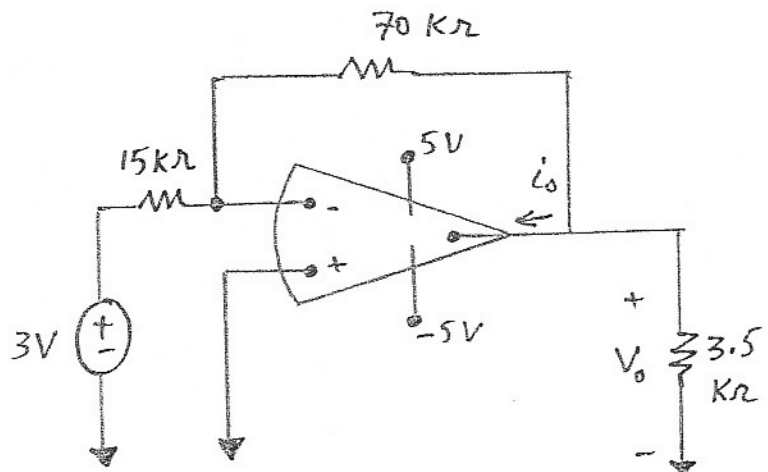- a. 10V
- b. -18V
- c. -14V
- d. -12V
- e. none of the above



4. Find V_o in the circuit shown if $V_a = 0.1V$ and $V_b = 0.25V$.

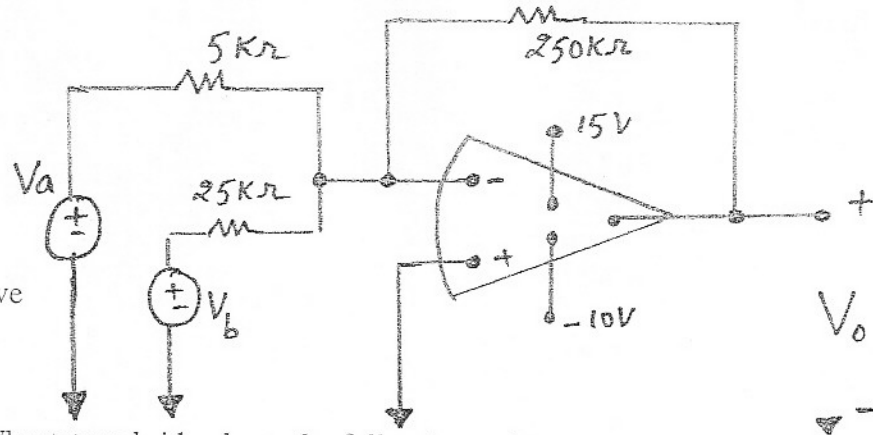- a. 0.15V
- b. -7.5V
- c. -2.5V
- d. 0.25V
- e. none of the above




5. The four arms of a Wheatstone bridge have the following resistances:

$AB = 100\ \Omega$, $BC = 10\ \Omega$, $CD = 4\ \Omega$, $DA = 50\ \Omega$.

A $20\ \Omega$ resistance is connected across BD. Compute the Thevenin voltage between terminals B-D when a potential difference of 10V is maintained across AC.

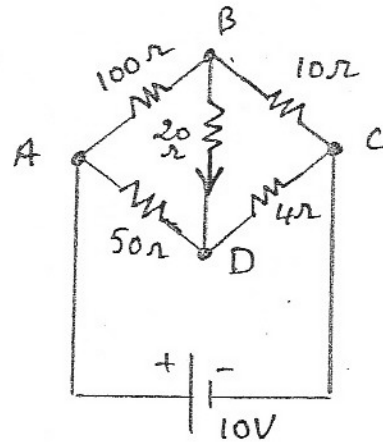- a. $\sim 0.168\ V$
- b. $\sim 0.741\ V$
- c. $\sim 0.554\ V$
- d. $\sim 0.909\ V$
- e. none of the above




6. In problem 5, find the current flowing through the $20\ \Omega$ resistance between terminals B-D

- a. $\sim 6\ mA$
- b. $\sim 4\ mA$
- c. $\sim 3\ mA$
- d. $\sim 5\ mA$
- e. none of the above

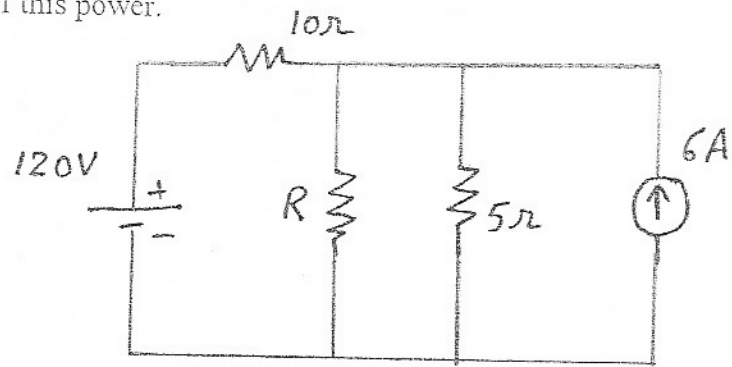
7. Calculate the value of R which will absorb maximum power from the circuit shown below. Also compute the value of this power.

- $5\ \Omega$, 720W
- $10/3\ \Omega$, 270W
- $10\ \Omega$, 1800W
- $10/3\ \Omega$, 1080W
- none of the above




8. Find the Thevenin voltage V_{TH} shown in the circuit below

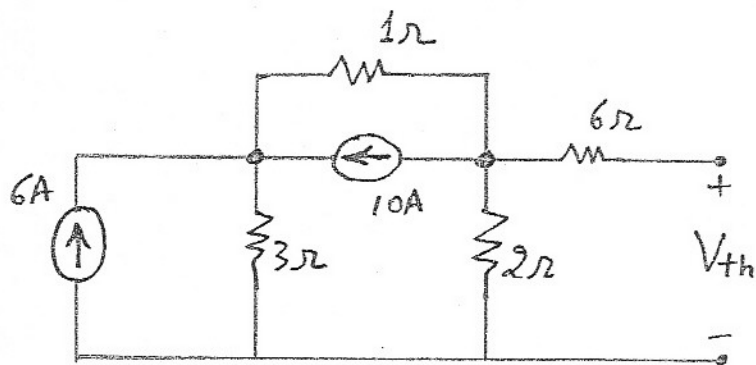- 3.87V
- 2.67V
- 1.45V
- 5.62V
- none of the above



9. A network excited only by current sources is shown below. Determine the voltage at Node 1.

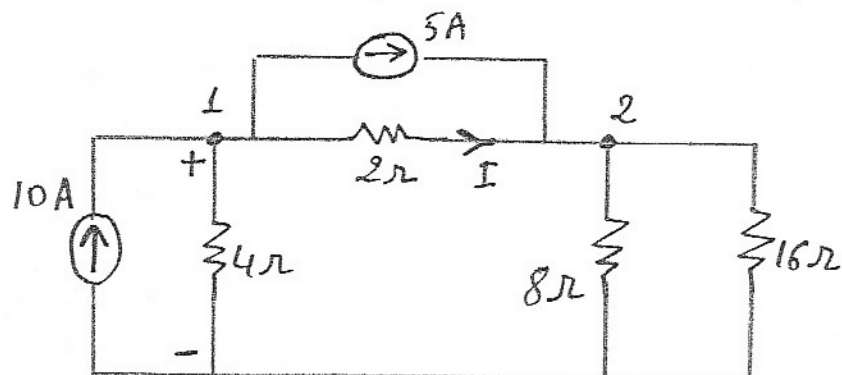- 18.65V
- 26.43V
- 31.33V
- 22.35V
- none of the above




10. In problem 9, find the current through the $2\ \Omega$ resistance.

- -0.856A
- -5A
- -1.350A
- -0.588A
- none of the above

11. For the circuit below, find the voltage V .

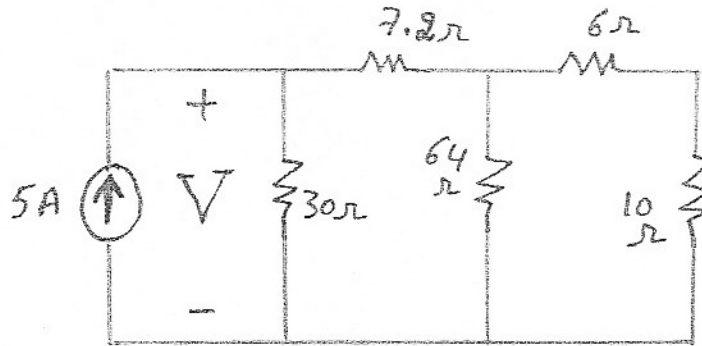- a. 40V
- b. 60V
- c. 50V
- d. 70V
- e. none of the above




12. In problem 11, find the power delivered to the circuit by the current source.

- a. 400W
- b. 300W
- c. 200W
- d. 500W
- e. none of the above

American University of Beirut
Department of Electrical and Computer Engineering
EECE 210 – Electric Circuits – Spring 2004

Q1 - solution

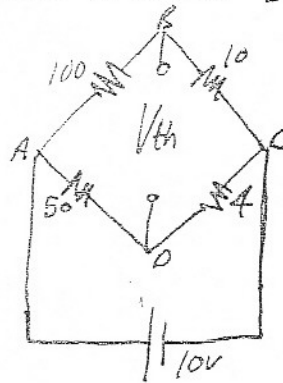1. WHEN THE GALVANOMETER IS REMOVED, WE GET THE CIRCUIT BELOW:




* LET US NOW FIND THE OPEN-CIRCUIT VOLTAGE (V_{th}). REMEMBERING THAT ABC (AS WELL AS ADC) IS A POTENTIAL DIVIDER ON WHICH A 10V DROP TAKES PLACE, WE GET:

$$\text{Potential of B w.r.t C} = 10 \times 10 / 110 = 0.909V.$$

$$\text{Potential of D w.r.t C} = 10 \times 4 / 54 = 0.741V.$$

$$\Rightarrow \text{Potential between B \& D} = V_{th} = 0.909 - 0.741 = 0.168V.$$

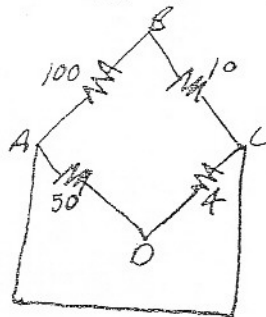* NOW REMOVE THE 10V BATTERY BY SHORTING PTS. A & C.







* NEXT FIND THE EQUIVALENT RESISTANCE OF THE CIRCUIT AS SEEN BY TERMINALS B & D. NOTE THE POTENTIALS A & C ARE NOW THE SAME, $BA \parallel BC$ & $AD \parallel CD$.
 $\Rightarrow R_{BD} = 12.79 \Omega$.

* NOW, SO FAR AS POINTS B & D ARE CONCERNED, THE NETWORK HAS A VOLTAGE OF 0.168V AND RESISTANCE 12.79 Ω .

* CONNECTING BACK THE GALVANOMETER TO THE THEVENIN SOURCE, WE CAN CALCULATE THE CURRENT I FLOWING THROUGH IT:


$$I = 0.168 / (12.79 + 20) = 0.005 = 5mA.$$

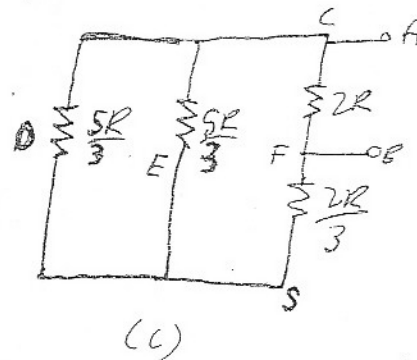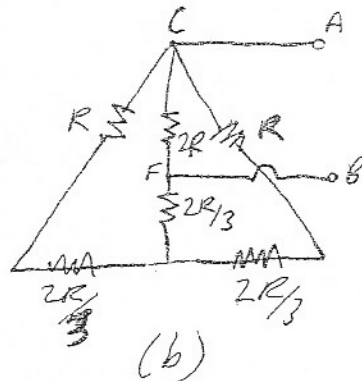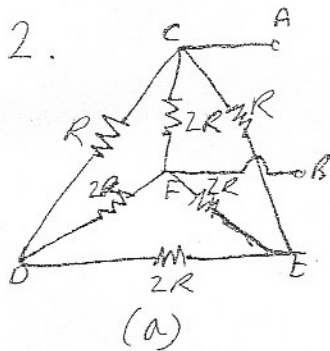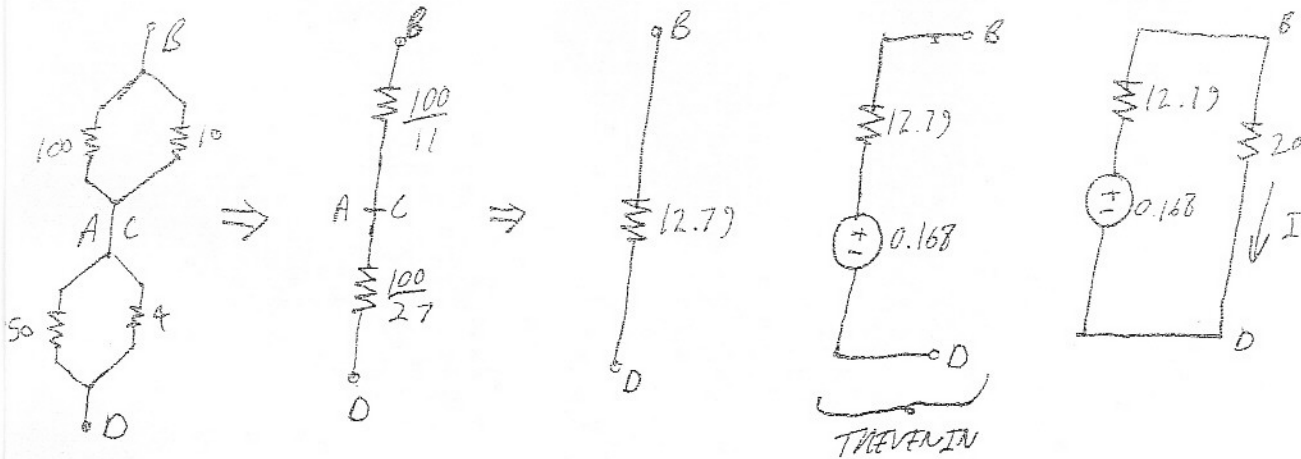THE FOLLOWING CIRCUITS SHOULD SIMPLIFY MATTERS:



THE Δ FDE MAY BE REPLACED BY ITS EQUIVALENT Y , AS SHOWN IN (b). IN (c) TWO SERIES RESISTANCES ALONG CES & COS HAVE BEEN REPLACED BY SINGLE RESISTANCE.

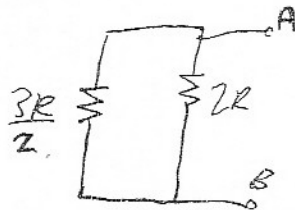FURTHER SIMPLIFICATION GIVES THE CIRCUIT BELOW:




$$\Rightarrow R_{AB} = \frac{3R}{2} \parallel 2R = \frac{6R}{7}$$

3. FOR FINDING POWER, AN EQUATION RELATING I TO R MUST BE FOUND.

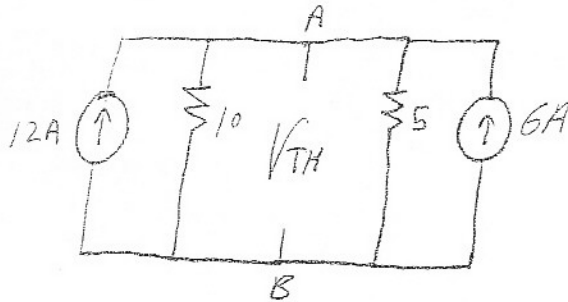(2)

* REMOVE R AND FIND V_{TH} ACROSS AB . IT IS HELPFUL TO CONVERT THE $120V$, 10Ω TO A CURRENT SOURCE IN $\parallel$ TO A RESISTOR, AS SHOWN BELOW:




A KCL YIELDS:

$$\frac{V_{th}}{10} + \frac{V_{th}}{5} = 12 + 6 \Rightarrow V_{th} = 60V.$$

* TO FIND R_{TH} , THE SOURCES ARE REMOVED.

$$\Rightarrow R_{TH} = 10 \parallel 5 = 10/3 \Omega.$$

* THE EQUIVALENT CIRCUIT:

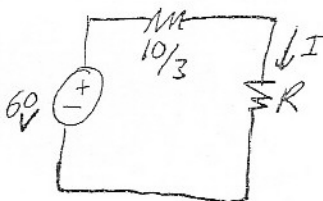


2022-2023 Academic Year

* R WILL ABSORB MAXIMUM POWER WHEN IT EQUALS $10/3 \Omega$.

$$\Rightarrow I = 60 / 20/3 = 9A.$$

$$P_{max} = I^2 R = 9^2 \times 10/3 = 270W.$$

4. $I = I_1 + I_2 = 4 + 6 = 10A$.

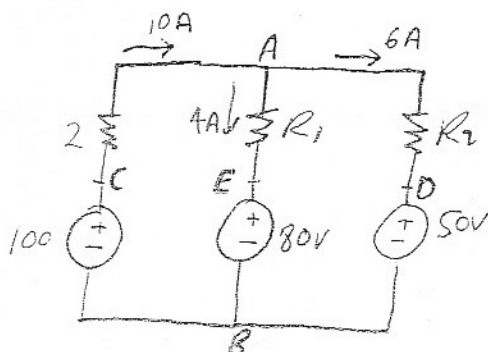

THE THREE PATHS ARE $\parallel$ ACROSS AB .

$$V_{AB} \text{ VIA PATH } BCA = 100 - (2 \times 10) = 80V.$$

SINCE $80V$ ALREADY EXISTS IN PATH AEB , THERE IS NO V DROP ACROSS R_1 . $\Rightarrow R_1 = 0\Omega$.

IN BRANCH ADB , V DROP ACROSS R_2 IS $80 - 50 = 30V$.

$$\Rightarrow 6R_2 = 30 \Rightarrow R_2 = 5\Omega.$$

5. AT NODE ①; (NOTE THAT $V_2 = V_{TH}$)

$$6 + 10 = \frac{V_1}{3} + \frac{V_1 - V_{TH}}{1} \Rightarrow 48 = 4V_1 - 3V_{TH}$$

AT NODE ②;

$$10 + \frac{V_{TH}}{2} = \frac{V_1 - V_{TH}}{1} \Rightarrow 20 = 2V_1 - 3V_{TH}$$

Solving, $V_{TH} = 2.67V$.

6. AT NODE ①;

$$10 = \frac{V_1}{4} + 5 + \frac{V_1 - V_2}{2} \Rightarrow \boxed{3V_1 - 2V_2 = 20} \quad (1)$$

AT NODE ②;

$$5 + \frac{V_1 - V_2}{2} = \frac{V_2}{8} + \frac{V_2}{16} \Rightarrow \boxed{-8V_1 + 11V_2 = 80} \quad (2)$$

Solving Eq. (1) & (2)

$$V_1 = 22.353V$$

$$V_2 = 23.529V$$

$$I_{2\Omega} = I = \frac{V_1 - V_2}{2} = \frac{22.353 - 23.529}{2} = -0.588A$$

7). (a). $V = 60V$

(b). $P = 300W$,

(c). $P_{10\Omega} = 57.6W$.

9). (a) $-7.5V$, (b) $0.15V$, (c) $0.5V$, (d) $-2.5, 0.25 \& 2V$.