

Prof. R. Chedid

FACULTY OF ENGINEERING
& ARCHITECTURE

SPRING TERM 2004-05

Name:.....

March 22, 2005

ID:.....

V.1

(EECE 210) ELECTRIC CIRCUITS & ELECTRONICS


CLOSED BOOK (1 ½ HRS)

Programmable Calculators are not allowed
Provide your answers on the computer's card only
Return the computer's card attached to the question sheet
Mark with a pencil your name and your ID-No
Use pencil for marking your answers
When using eraser, be sure that you have erased well

!!! PENALTY IS 6 TO 1 !!!


1. For the circuit shown find R_{eq} seen from terminals a-b

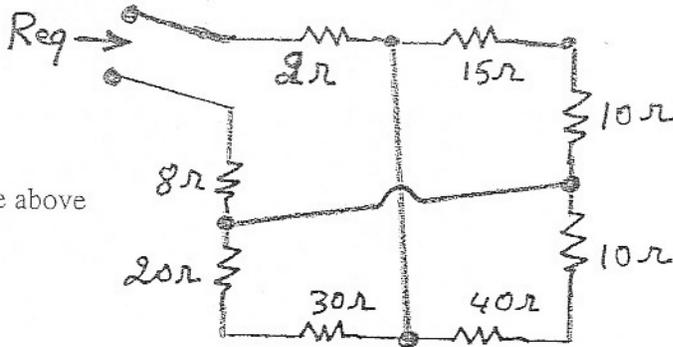- a. 25Ω
- b. 14.5Ω
- c. 22.5Ω
- d. 20.5Ω
- e. None of the above



2. Find the Thevenin equivalent voltage V_{th} seen from terminals a-b in the circuit shown:

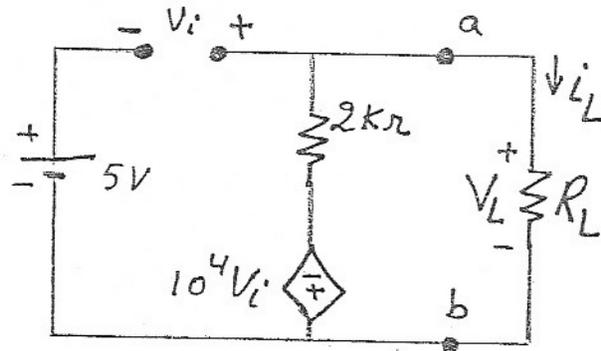- a. 5V
- b. 10V
- c. $5 \times 10^4 V$
- d. 2.5V
- e. None of the above




3. Find the equivalent Thevenin resistance seen from terminals a-b in the circuit shown in problem 2.

- a. 0.5Ω
- b. 1Ω
- c. 5Ω
- d. 0.2Ω
- e. None of the above

4. Find the Thevenin equivalent voltage V_{th} as seen from terminals a-b in the circuit shown

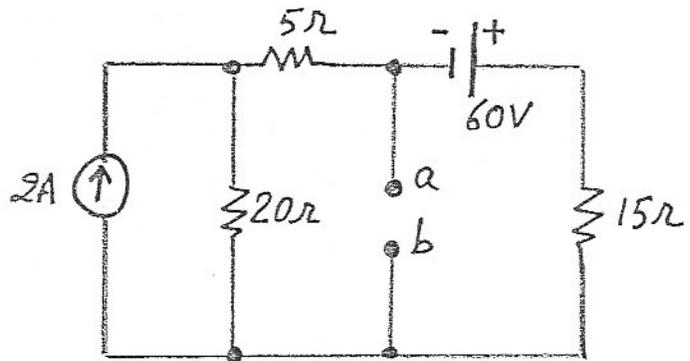- a. $V_{th}=97.5V$
- b. $V_{th}=22.5V$
- c. $V_{th}=-22.5V$
- d. $V_{th}=-37.5V$
- e. None of the above



$$+V_i + 10^4 V_i - 5V = 0$$

$$V_i \left(\frac{2+10^4}{10^4} \right) = 5$$

$$V_i = 5 \times 10^{-4}$$

$$V_{ab} = -10^4 V_i$$


$$= \frac{1}{10^4} \times 5 \times 10^{-4}$$

5. Find the equivalent Thevenin resistance seen from terminals a-b in the circuit shown in Problem 4.

- a. 6.74Ω
- b. 9.37Ω
- c. 12.6Ω
- d. 16.32Ω
- e. None of the above


6. Find the absolute value of the power delivered by the circuit

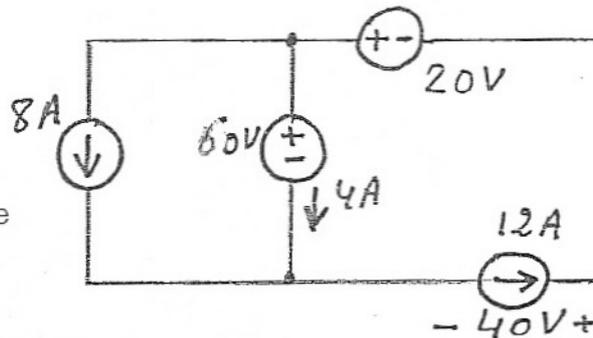- a. 480W
- b. 240W
- c. 720W
- d. 450W
- e. None of the above




7. Find the absolute value of the power delivered by the dependent voltage source.

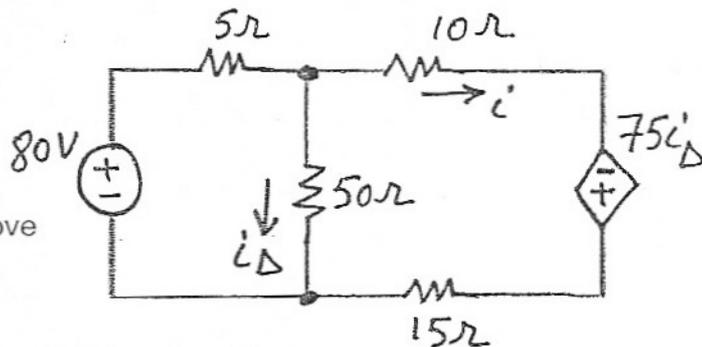- a. 150W
- b. 75W
- c. 375W
- d. 500W
- e. None of the above




8. For the circuit shown, find the current i .

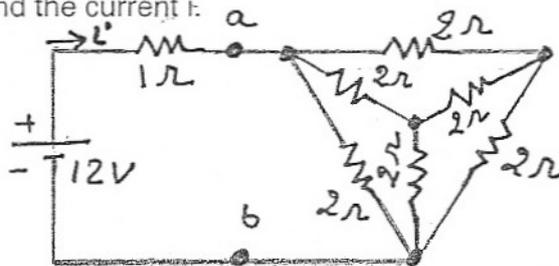- a. 2A
- b. 4A
- c. 8A
- d. 6A
- e. None of the above




9. Solve for the current i in the 10Ω resistor in the circuit shown

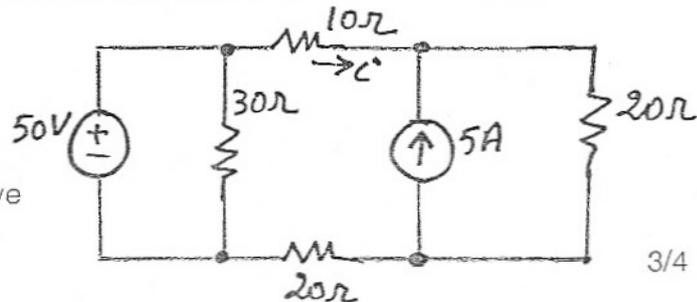- a. -1.5A
- b. -1A
- c. 0.6A
- d. 1.6A
- e. None of the above




10. Find the current I in the circuit shown.

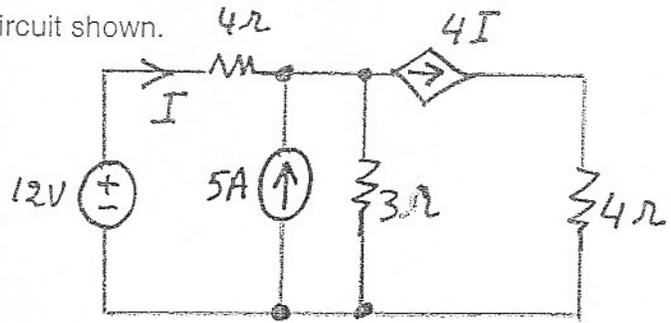- a. 6A
- b. 1A
- c. 3.2A
- d. 0.6A
- e. None of the above




11. Find the voltage V in the circuit shown.

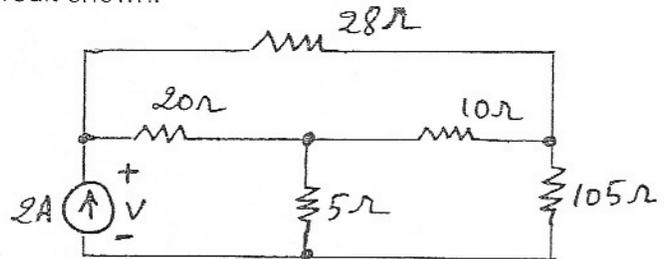- a. 43.2V
- b. 22.6V
- c. 35V
- d. 39V
- e. None of the above




12. Find the equivalent inductance seen from terminals a-b in the circuit shown.

- a. ~2.8H
- b. ~21.8H
- c. ~18.5H
- d. ~3.3H
- e. None of the above



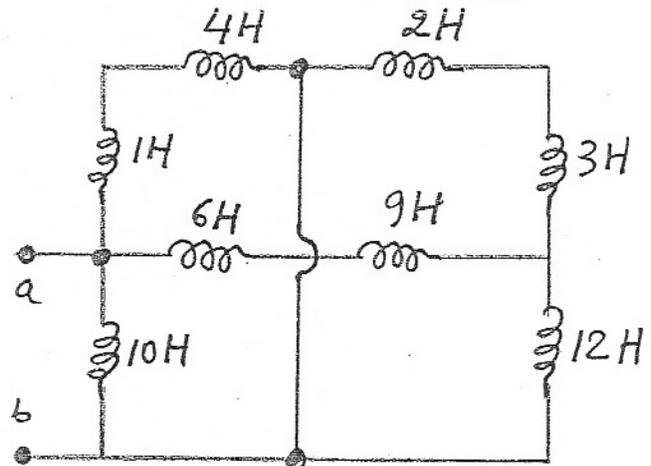


Problem 1: www.amal-aub.org

Find R_{eq} for the resistive network.

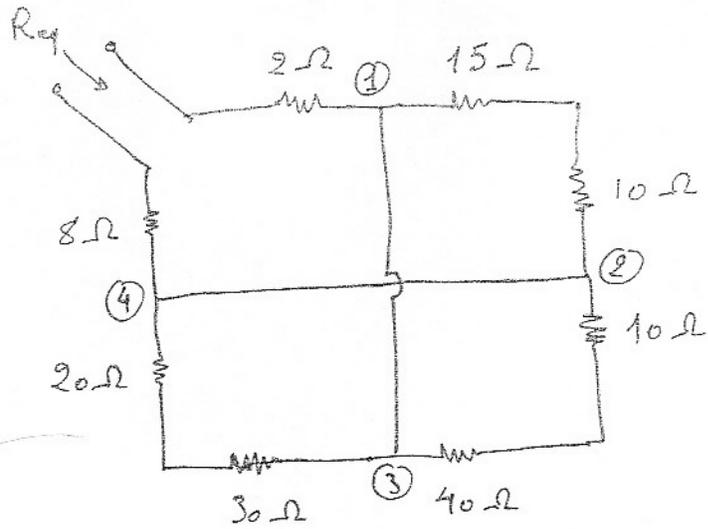

Solution:

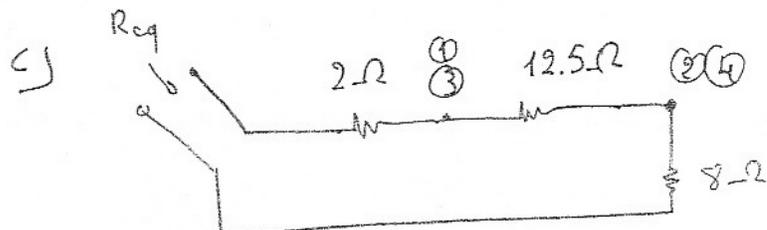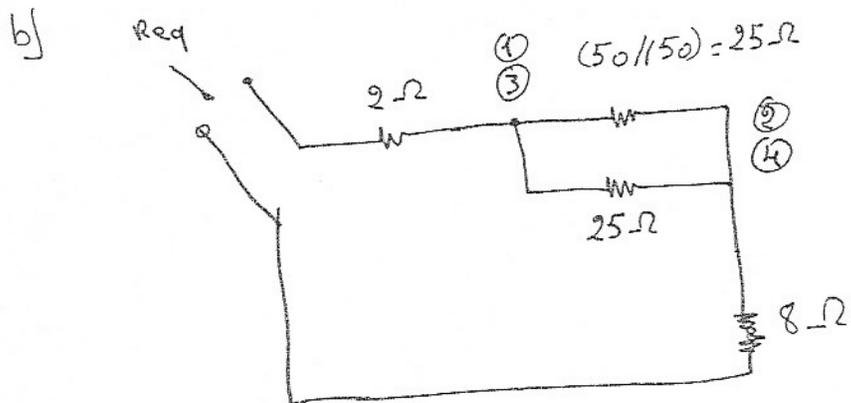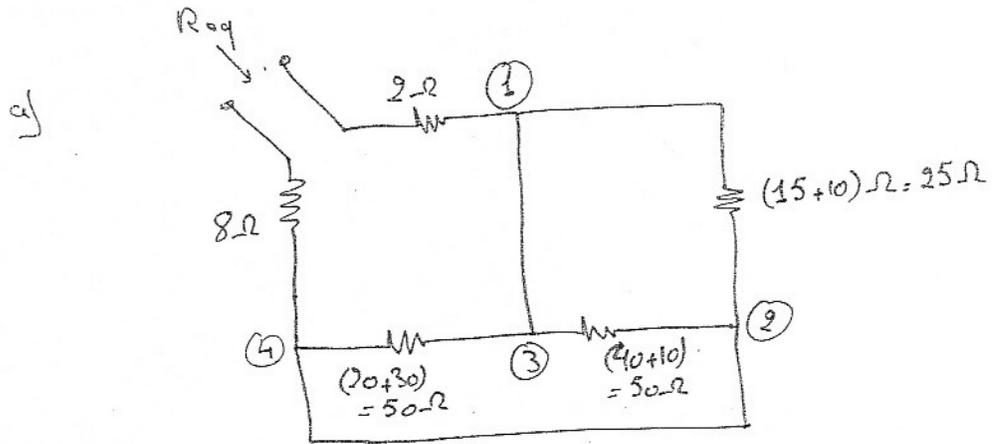


d) $R_{eq} = 22.5 \Omega$

Problem 2:

www.amal-aub.org

$v_{th} = ??$

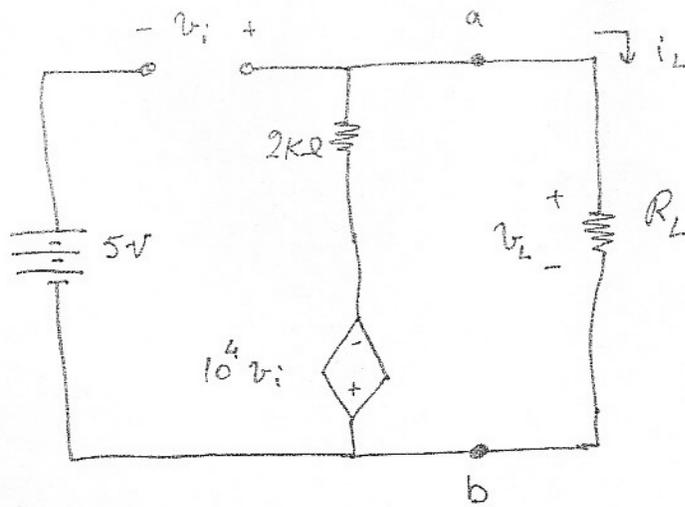

with $v_s = 5V$, $R_i = \infty$, $A = 10^4$ and $R_o = 2K\Omega$, To find $v_{L_{oc}}$ we set $R_L = \infty$, or we simply consider it to be removed from the circuit. There now can be no current through the resistor, and therefore

$$v_{L_{oc}} = -10^4 v_i$$

where

$$v_i = v_{L_{oc}} - 5$$

Therefore

$$v_{L_{oc}} = \frac{10^4 (5)}{10001} = 5.00V$$

Next we need a value for i_{sc} ; we replace R_L by a short circuit. Around the right mesh, KVL gives

$$10^4 v_i + 2000 i_{L_{sc}} = 0$$

with the application of KVL around the perimeter of the circuit gives:

$$-5 - v_i = 0$$

$$\text{Therefore: } 10^4 (-5) + 2000 i_{L_{sc}} = 0$$

$$\text{and } i_{L_{sc}} = 25.0A$$

Problem 3:

www.amal-aub.org





R_{th} for problem 2 = ??

$$R_{th} = \frac{V_{loc}}{i_{lsc}} = \frac{5.00}{25.0} = 0.2 \Omega$$

Thus, the Thevenin equivalent presented to R_L at @-@ by the voltage follower is 5.00V in series with a very low value of resistance 0.2Ω.

Problem 4:

find $V_{th} = ??$

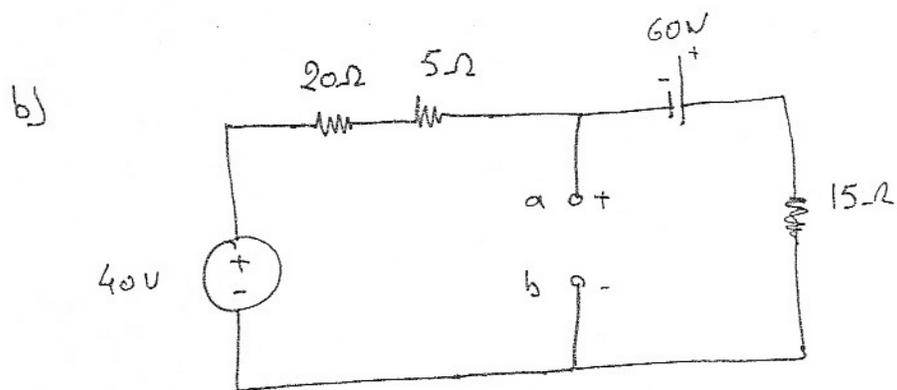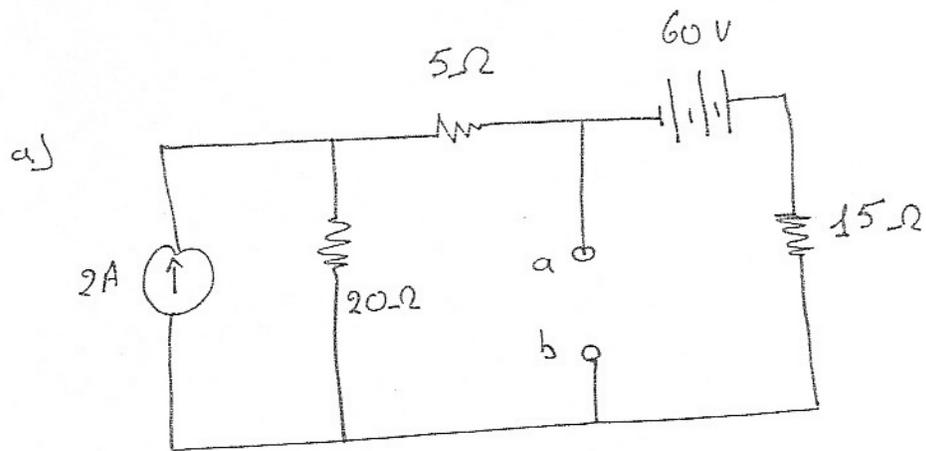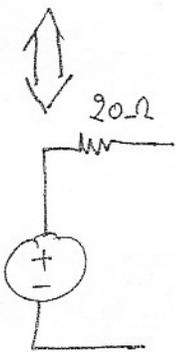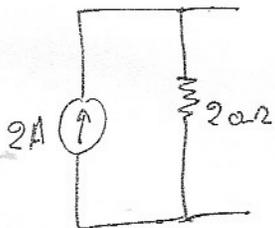

$$\Rightarrow -40 + 25i - 60 + 15i = 0$$

$$\Rightarrow 40i = 100 \Rightarrow i = \frac{10}{4}$$

$$\& -V_{ab} - 60 + 15 \times \frac{10}{4} = 0$$

$$\Rightarrow V_{ab} = \frac{150}{4} - 60 = -22.5 \text{ V}$$

Problem 5:

www.amal-aub.org

Find R_{th} for problem (4)

$i_{sc} = ??$


$$i = i_1 + i_2$$

$$= \frac{40}{25} - \frac{60}{15} = \frac{40}{25} - 4 = 1.6 - 4 = -2.4$$

$$\Rightarrow R_{th} = \frac{2 \cdot 2.5}{2.4} = 9.37 \Omega.$$

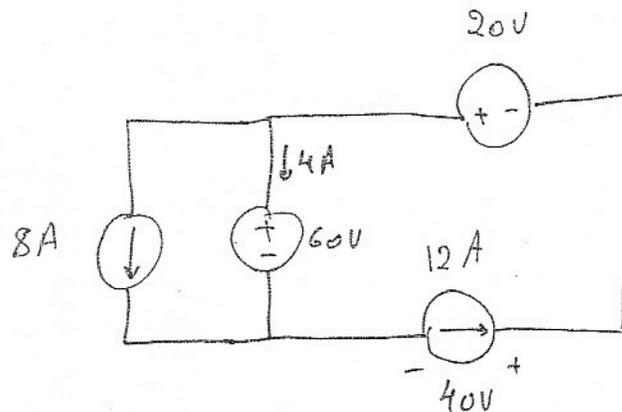Problem 6:

Find the absolute value of the power delivered by the circuit.




$$(KVL) : -60 + 20 + 40 = 0$$

$$(KCL) : 10 + 4 + 12 = 0$$

$$\Sigma P_{dev} = 4(60) + 8(60) = 720 \text{ W}$$

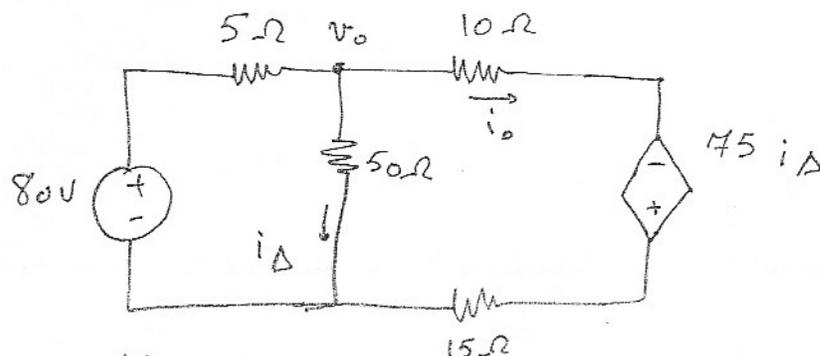Problem 7:

Find the absolute value of the power delivered by the dependent voltage source.



$$\frac{v_o - 80}{5} + \frac{v_o}{50} + \frac{v_o + 75 i_\Delta}{25} = 0 \dots (1)$$

$$i_\Delta = \frac{v_o}{50} \dots (2)$$

Solving eq (1) & (2), $v_o = 50 \text{ V}$ & $i_D = 1 \text{ A}$.
www.amal-aub.org






$$i_o = \frac{50 - (-175)(1)}{25} = 5 \text{ A}$$

$$P_{75i_D} = 75 i_D \cdot i_o = -375 \text{ W}$$

\Rightarrow The dependent voltage source delivers 375 W to the circuit

Problem 8:


Find the current i

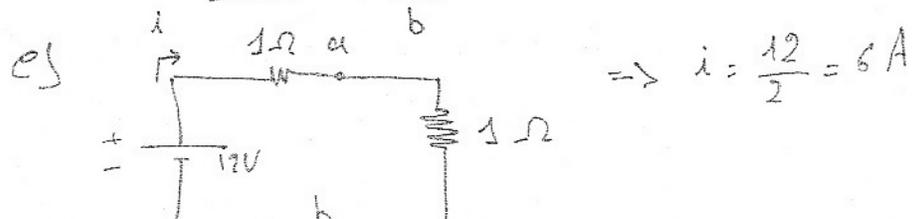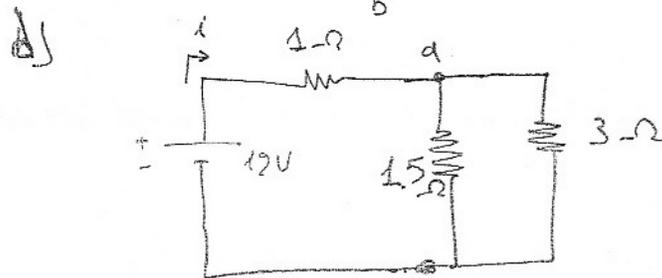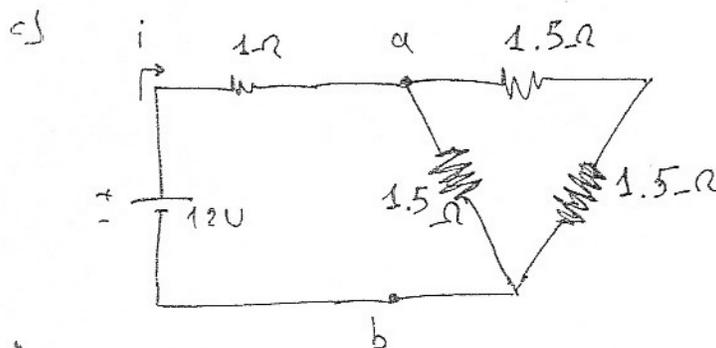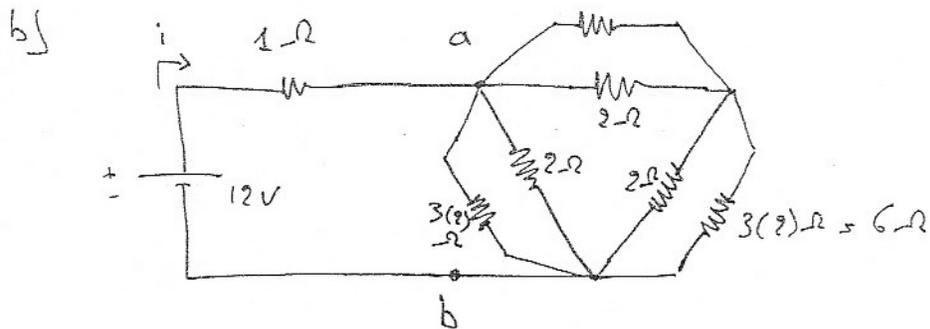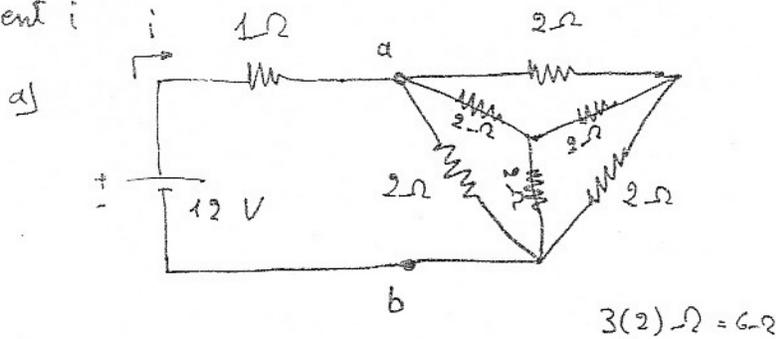

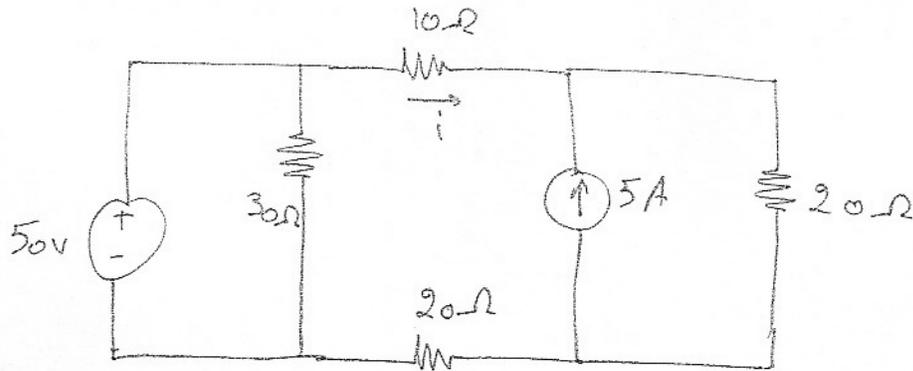
Problem 9:

www.amal-aub.org

Solve for the current i in the 10Ω resistor in the circuit shown



by source transformation we obtain:

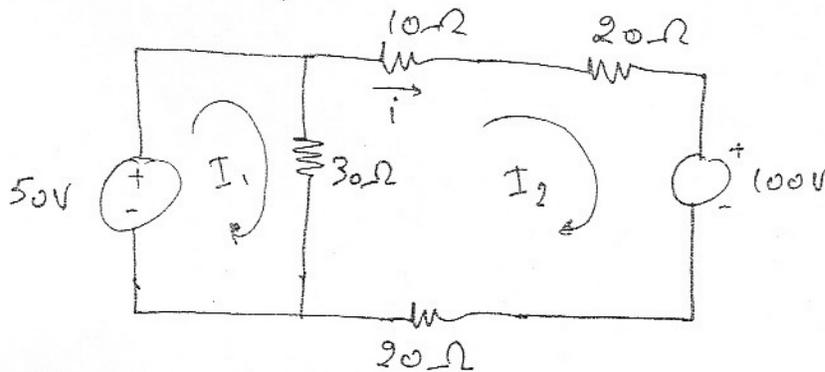

Thus,

$$50 = 30I_1 - 30I_2 \quad \& \quad -100 = -30I_1 + 80I_2$$

Solving


these eqs:

$$\Rightarrow -50 = 50I_2$$

$$\Rightarrow I_2 = I_{10\Omega} = -1 \text{ A}$$

Problem 10:

Find the current I

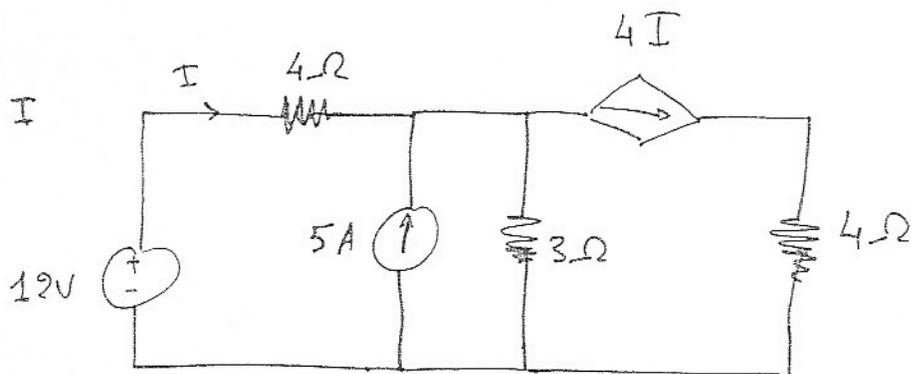

Writing the nodal equations \Rightarrow

$$\frac{12 - V}{4} + 5 = \frac{V}{3} + 4I \quad \& \quad I = \frac{12 - V}{4}$$

Solving these equations \Rightarrow


$$I = 0.6 \text{ A}$$

Problem 11:


www.amal-aub.org

Find the voltage V


a)

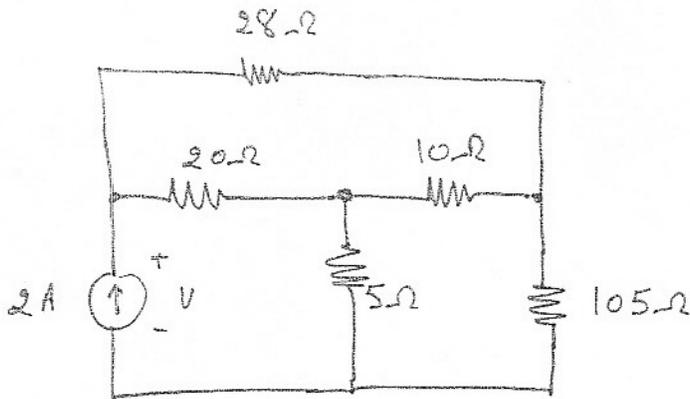


b)

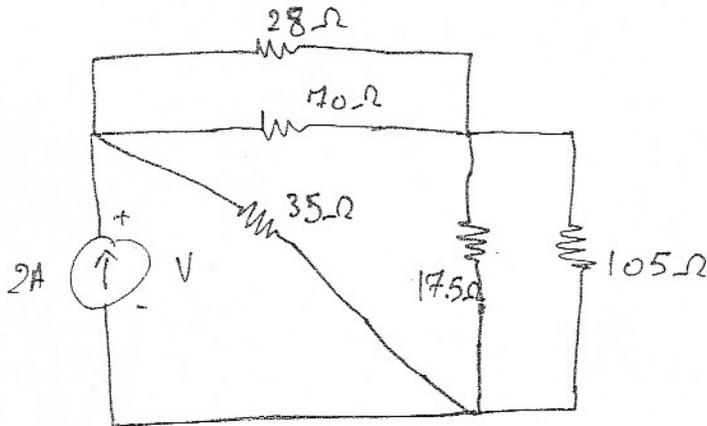

c)



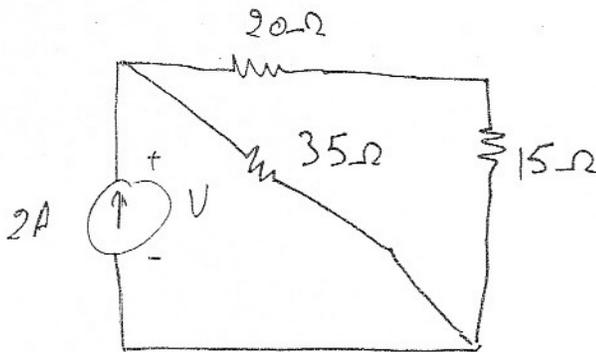


d)

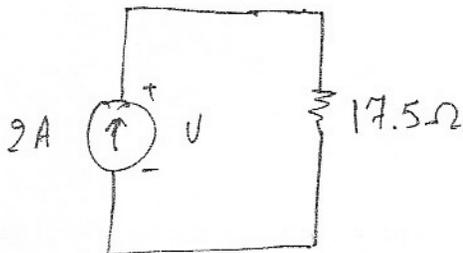

$$\Rightarrow V = RI = 17.5 \times 2 = 35 \text{ V}$$

Problem 12:
www.amal-aub.org

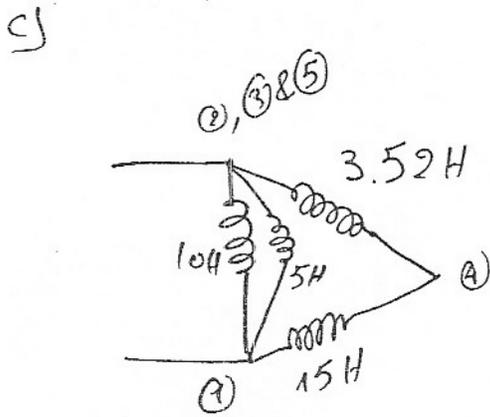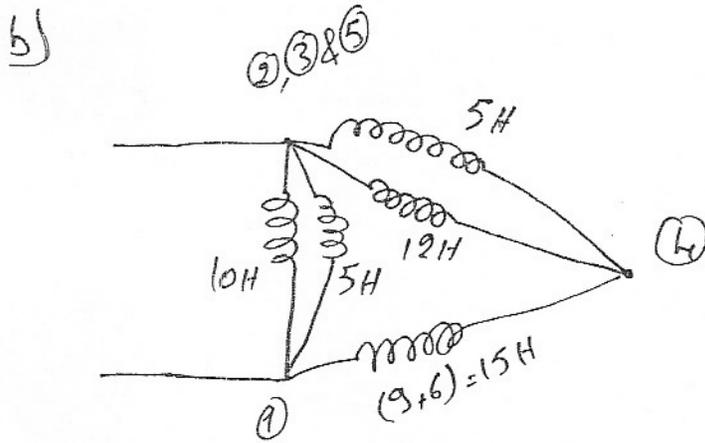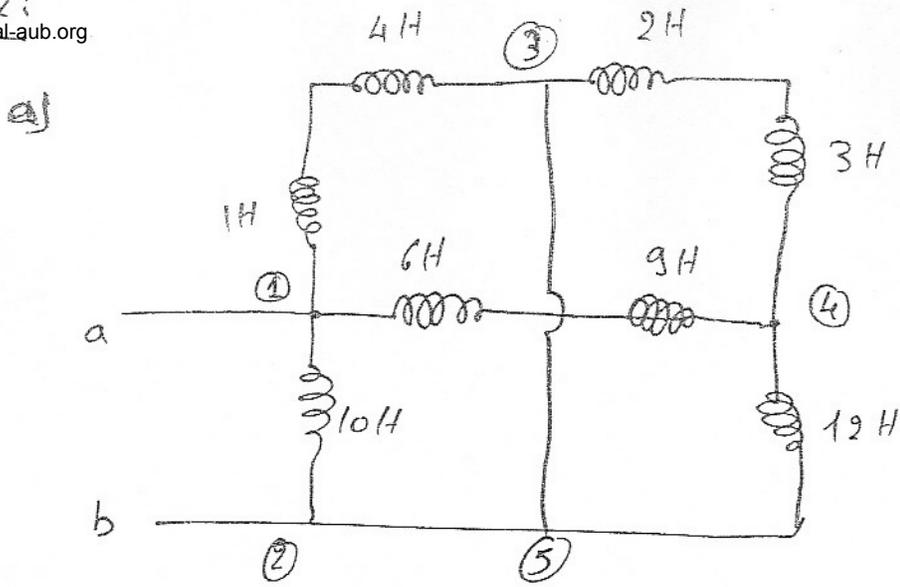

d)

$$\frac{1}{L_{eq}} = \frac{1}{10} + \frac{1}{5} + \frac{1}{18.52}$$

$$\Rightarrow L_{eq} = 2.82 \text{ H}$$