

Prof. N. Sabah
R. Chedid
L. Chaar
I. Mougharbel

FACULTY OF ENGINEERING
& ARCHITECTURE

FALL TERM 20

Name:.....
Major:.....
Instructor.....

NOV , 20

TEST ID 2000

(ELEG 310) ELECTRIC CIRCUITS

CLOSED BOOK (1 ½ HRS)

Programmable Calculators are not allowed
Provide your answers on the computer's card only
Return the computer's card attached to the question sheet
Mark with a pencil your name and your ID-No
Use pencil for marking your answers
When using eraser, be sure that you have erased well

!!! PENALTY IS 6 TO 1 !!!

Profs. N. Sabah
R. Chedid
L. Chaar
I. Mougharbel

FACULTY OF ENGINEERING
& ARCHITECTURE

FALL TERM 20

Name:.....
Major:.....
Instructor.....

NOV , 20

TEST ID 2000

(ELEG 310) ELECTRIC CIRCUITS

CLOSED BOOK (1 ½ HRS)


Programmable Calculators are not allowed
Provide your answers on the computer's card only
Return the computer's card attached to the question sheet
Mark with a pencil your name and your ID-No
Use pencil for marking your answers
When using eraser, be sure that you have erased well

!!! PENALTY IS 6 TO 1 !!!

1. An impedance $Z_1 = (4+j4) \Omega$ is connected in parallel with an impedance $Z_2 = (12+j6) \Omega$. If the input reactive power is 1000 VAR (lagging), what is the total active (average) power ?

- A. 1210 W
- B. 3025 W
- C. 826.39 W
- D. 1150 W
- E. None of the above

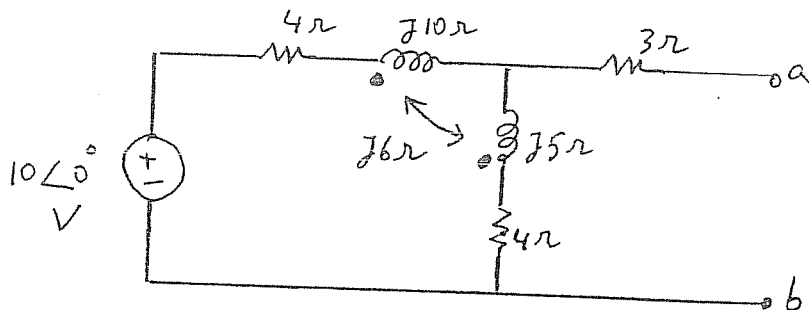2. In the circuit shown below, find the Thevenin equivalent circuit as seen from terminals a-b.



- A. $V_{Thev} = 4.82 \angle -34.60^\circ$ V, $Z_{Thev} = 8.62 \angle -40.38^\circ \Omega$
- B. $V_{Thev} = 48.2 \angle -34.60^\circ$ V, $Z_{Thev} = 86.2 \angle -48.79^\circ \Omega$
- C. $V_{Thev} = 5 \angle -34.60^\circ$ V, $Z_{Thev} = 8.1 \angle -48.79^\circ \Omega$
- D. $V_{Thev} = 4.82 \angle -34.60^\circ$ V, $Z_{Thev} = 8.62 \angle -48.79^\circ \Omega$
- E. None of the above


3. The conjugate of the complex power delivered by a current source is $200 - j200$ VA. If the source current is $\frac{10}{\sqrt{2}} \angle 45^\circ$ A peak, determine the rms voltage across the source.

- A. 40 V rms
- B. $j40$ V rms
- C. 80 V rms
- D. $-j40$ V rms
- E. None of the above

4. In the figure shown, $v_S = 10\cos 100\pi t$ V rms, $L_1 = 120$ mH, $L_2 = 30$ mH, $R = 100$ ohms, $N_1 = 500$ turns, and $N_2 = 1500$ turns. Determine the coupling coefficient so that no current flows in the 100 ohm resistor.


- A. 0.4
 B. 0.5
 C. 0.6
 D. 0.8
 E. None of the above

ignore

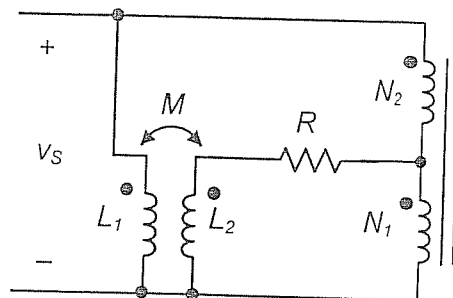


5. Given a balanced three-phase system in which the load consumes 50 kW at 0.8 p.f. lagging. The line impedance $Z_l = 0.5 + j 0.5 \Omega$. Capacitors are connected at the load terminals so that the p.f. at the supply terminals abc is unity. If the line current I is 100 A rms, determine the rms line voltage at the load terminals. (Answers are rounded to three significant figures.)

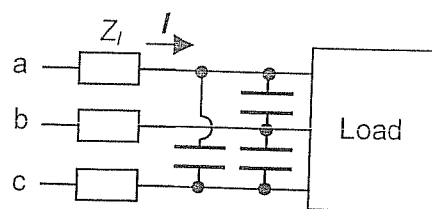- A. 579 V rms
 B. 367 V rms
 C. 301 V rms
 D. 262 V rms
 E. None of the above



6. Find the maximum average power given that R_L is adjusted for maximum power transfer.

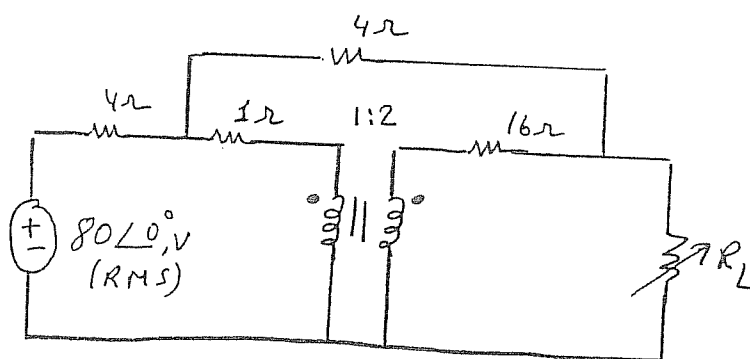- A. 300 W
 B. 800 W
 C. 200 W
 D. 25 W
 E. None of the above



7. A three-phase line has an impedance of $(0.1 + j 0.8) \Omega/\phi$, the line feeds two-balance three-phase load connected in parallel. The first load absorbs a total of 540 kW and 720 kVAR. The second load is Y connected and has an impedance of $20 - j 6.67 \Omega/\phi$, the line-to-neutral voltage at the load is $4 \text{ kV}_{\text{rms}}$. Find the line voltage at the source.

- A. 6990.63 V
- B. 6973.6 V
- C. 6987.47 V
- D. 6951.82 V
- E. None of the above

8. Consider a source V_s supplying the primary of a transformer. The secondary is connected to a purely capacitive load Z_c . The primary impedance is Z_1 , the secondary impedance is Z_2 , and the mutual impedance between primary and secondary is Z_m . Calculate the currents I_1 at primary and I_2 at secondary.

Given: $V_s = 300 \angle 0^\circ \text{ V}$, $Z_1 = j3600 \Omega$, $Z_2 = j2500 \Omega$, $Z_m = j1200 \Omega$, $Z_c = -j1800$

- A. $I_1 = 132 \angle +90^\circ \text{ mA}$, $I_2 = 333 \angle -90^\circ \text{ mA}$
- B. $I_1 = 132 \angle 0^\circ \text{ mA}$, $I_2 = 333 \angle +180^\circ \text{ mA}$
- C. $I_1 = 280 \angle -90^\circ \text{ mA}$, $I_2 = 560 \angle +90^\circ \text{ mA}$
- D. $I_1 = 280 \angle 0^\circ \text{ mA}$, $I_2 = 560 \angle +180^\circ \text{ mA}$
- E. None of the above


9. A 3 phase source of voltage is supplying simultaneously two kinds of load. The first one is a 3 phase Y connected inductive load with a power factor of 0.8, and the second one is a 3 phase Δ connected purely capacitive load. The system is perfectly balanced and the voltage between phase A and neutral is considered as reference. The rms phase current in the inductive load is I_L , and the rms phase current in the capacitive load is I_C .

If $I_L = 10\text{A}$, $I_C = 8\text{A}$, calculate the power factor of the total load and say if it is leading or lagging.

- A. 0.97 lagging
- B. 0.89 lagging
- C. 0.97 leading
- D. 0.89 leading
- E. None of the above

10. Find the input impedance Z_{AB} in the circuit shown below.

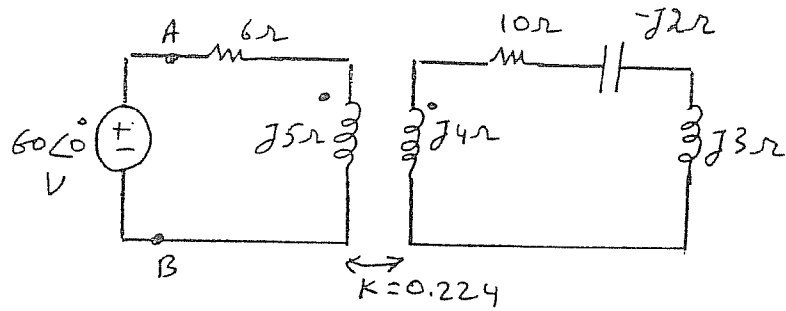- A. $6.1 + j5 \Omega$
- B. $3.8 + j9.2 \Omega$
- C. $6 + j5.896 \Omega$
- D. $8.3 + j4.7 \Omega$
- E. None of the above



11. Determine the value of C in the circuit shown if C takes 5 VAR. The operating frequency is 50 Hz.

- A. $12.63 \mu\text{F}$
- B. $14.74 \mu\text{F}$
- C. $17.68 \mu\text{F}$
- D. $3 \mu\text{F}$
- E. None of the above

