


Solution - Quiz 1

Problem 1:

$$I_2 = \frac{V - 2V_\Delta}{1} = -2V$$


$$I_3 = \frac{V + 2V_\Delta}{1} \Rightarrow V_\Delta = 1I_3$$
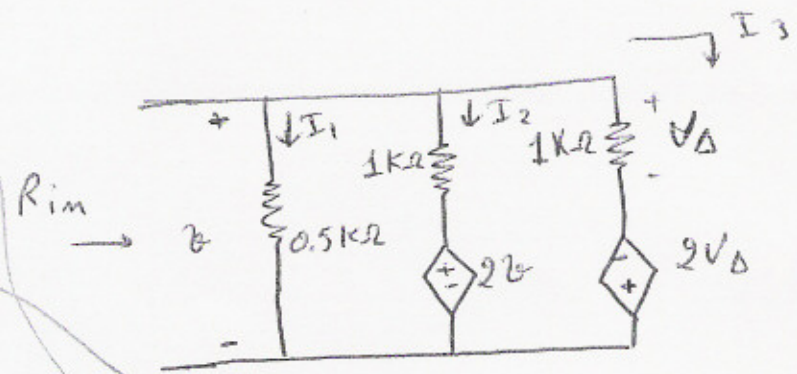
$$\Rightarrow I_3 = V + 2I_3 \Rightarrow I_3 = \frac{V}{-1}$$



$$I = I_1 + I_2 + I_3 = \frac{V}{1} \left[2 + (1-2) \left(-\frac{1}{1} \right) \right]$$

$$\Rightarrow \frac{V}{I} = \frac{1}{0} \Rightarrow R_{in} \rightarrow \text{inf. } (\infty)$$

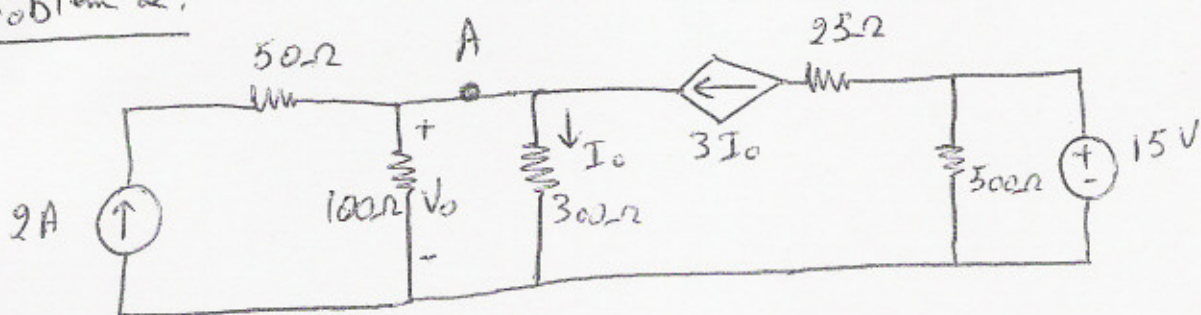
Problem 2:On node A:

$$2 + 3I_0 = I_0 + \frac{V_0}{100} \quad \& \quad V_0 = 300 I_0$$


$$\Rightarrow 2 + 3I_0 = I_0 + 3I_0 \Rightarrow I_0 = 2A$$

Problem 5:


$R = 100\ \Omega$

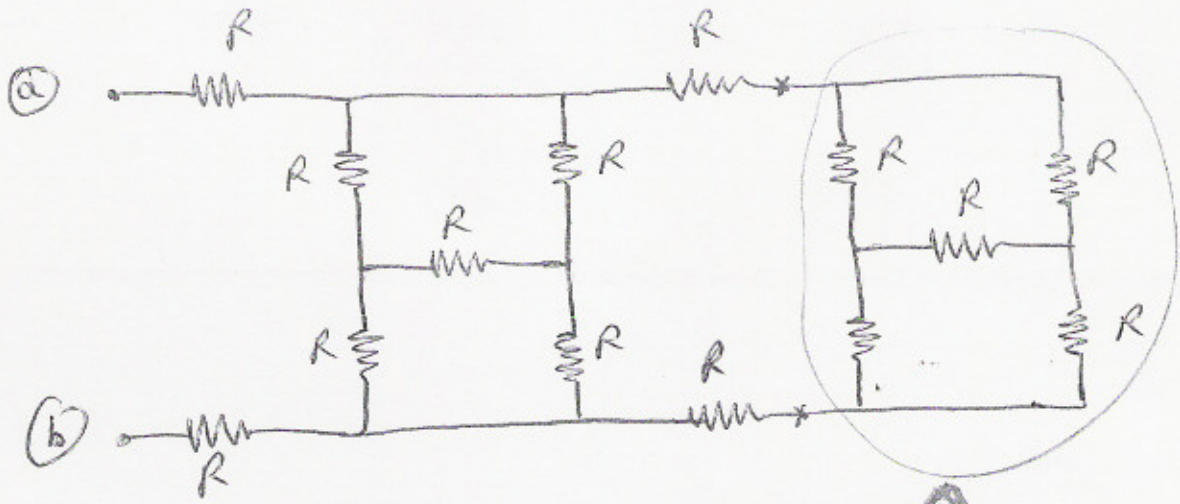


using Δ -Y

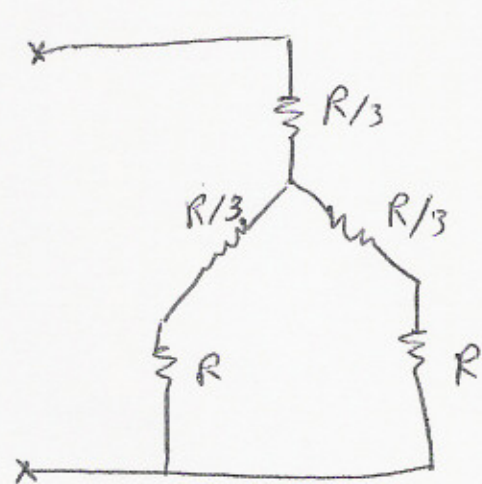

(i)

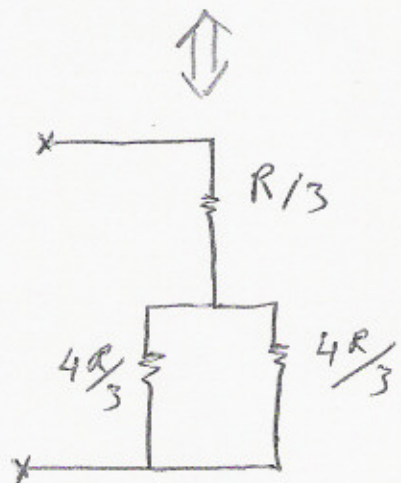


(ii)

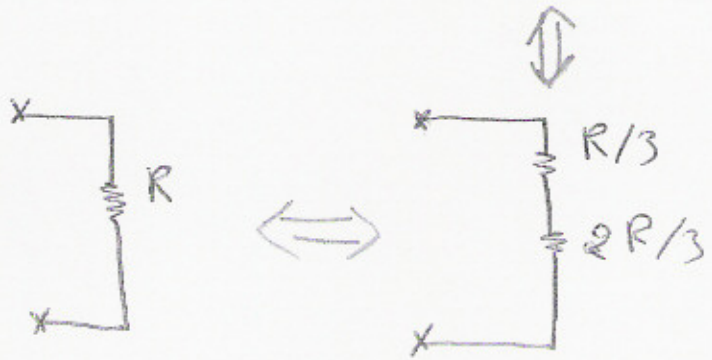


(iv)

(iii)

The circuit will be:

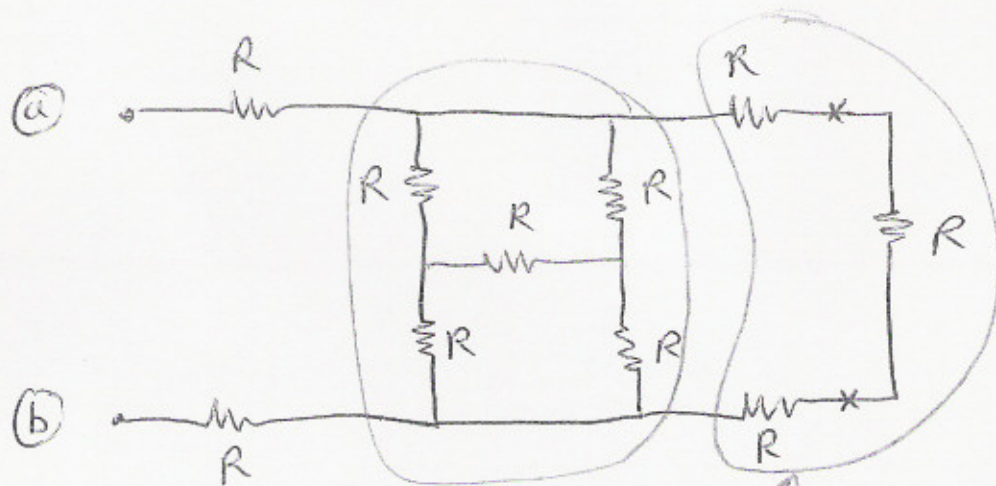

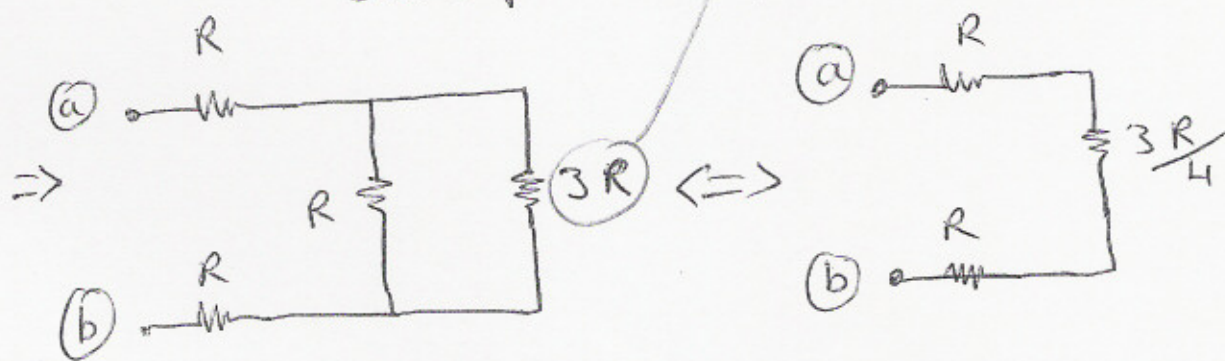Same procedure from i - ii - iii \rightarrow iv



if $R = 100\Omega \Rightarrow R_{ab} = 275\Omega$.


Problem 4:

$V_o = V_p = V_m$


$I = \frac{5V}{5K\Omega} = 1mA$

$V_o - I(2) = 10$

$\Rightarrow V_o = 10 + 2 = 12V$

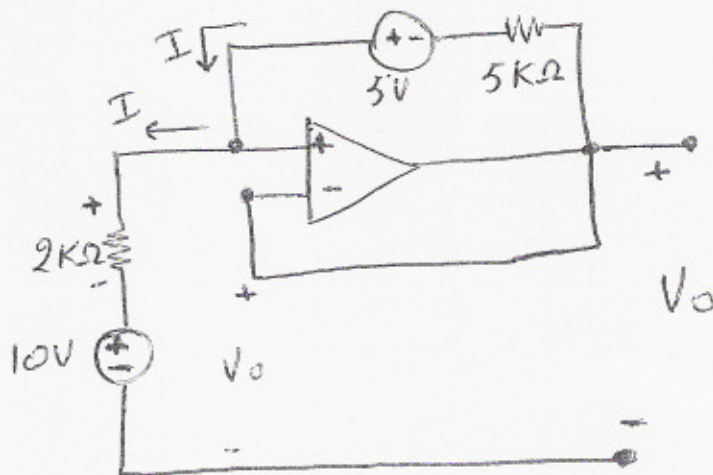


Problem 5:

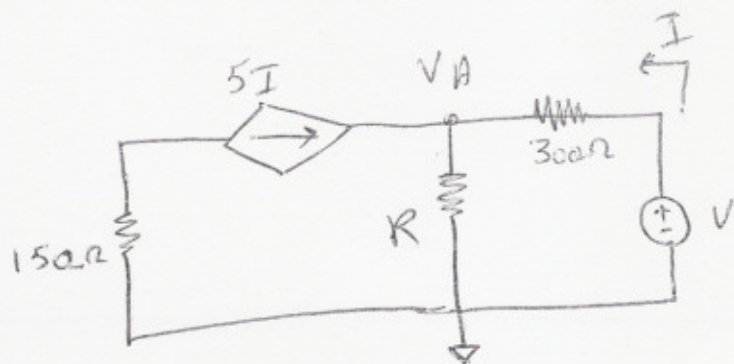

V_{Th} is obtained by removing R

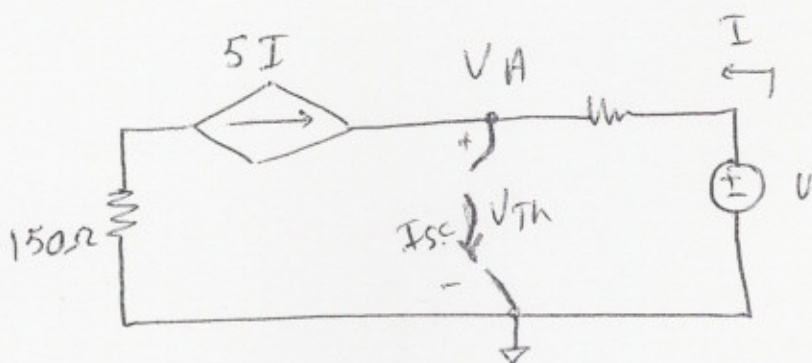On node A $5I = I \Rightarrow I = 0$
 $\Rightarrow V_{Th} = V$




Producing a short circuit between A & the ground,


$I_{sc} = I + 5I = 6I$ & $I = \frac{V}{300}$

$\Rightarrow I_{sc} = \frac{6V}{300} \Rightarrow R_{Th} = \frac{300}{6} = 50\Omega$

Problem 6:

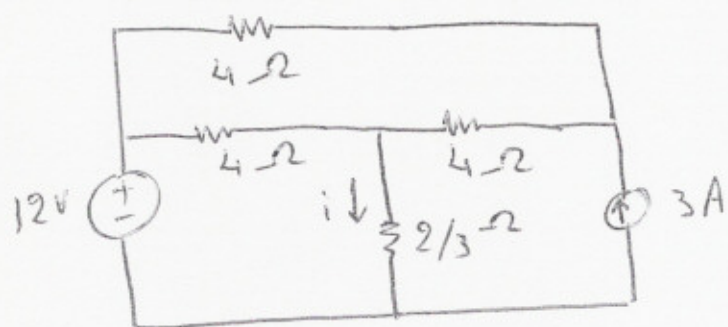

\Leftrightarrow

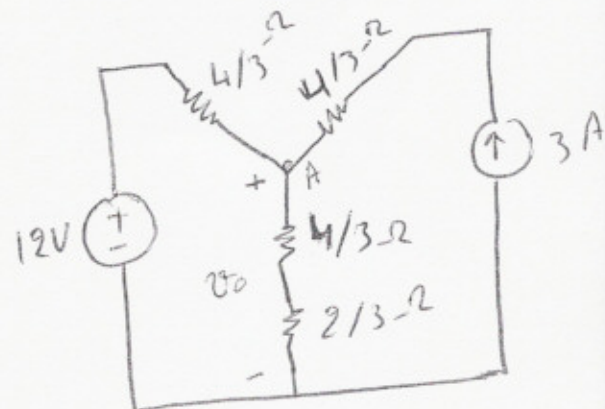


On node A:


$$\frac{v_o - 12}{4/3} + \frac{v_o}{2} - 3 = 0 \Rightarrow v_o = 9.6$$

$$\Rightarrow i = \frac{9.6}{2} = 4.8 \text{ A.}$$

Problem 7:

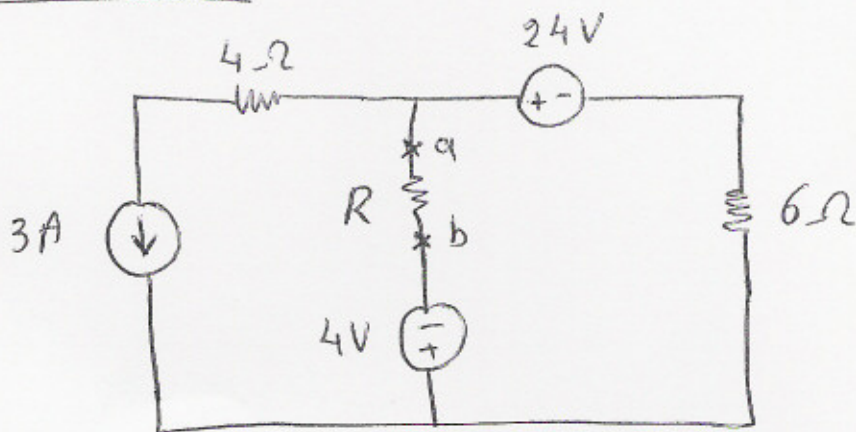

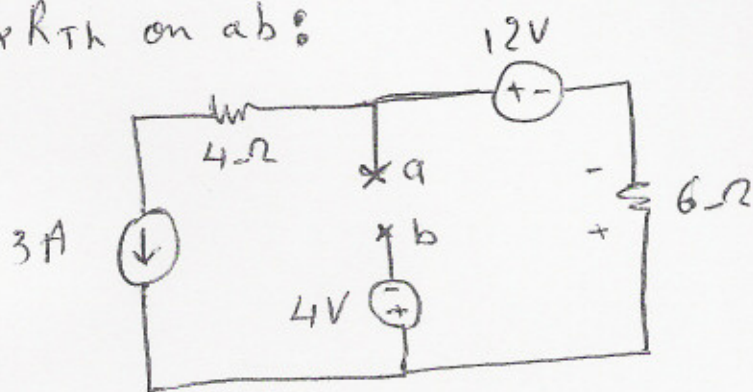To find max. Power delivered to R , we should find v_{oc} & R_{Th} on ab :



$$v_{6\Omega} = 18V = 3 \times 6 = 18V$$

by KVL:


$$v_{ab} - 4 + v_o - 24 = 0$$

$$\Rightarrow v_{ab} = 10V$$

$$\text{or } R_{Th} = 6\Omega.$$


For max Power transfer, $R_{Th} = R$

$$\Rightarrow P_R = I^2 R$$

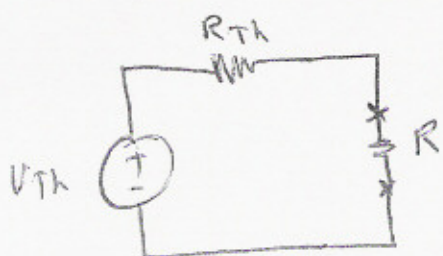


$$\Rightarrow P_R = \left(\frac{V}{2R}\right)^2 R = \left(\frac{10}{12}\right)^2 \times 6 = 4.166 \text{ W.}$$

Problem 8:

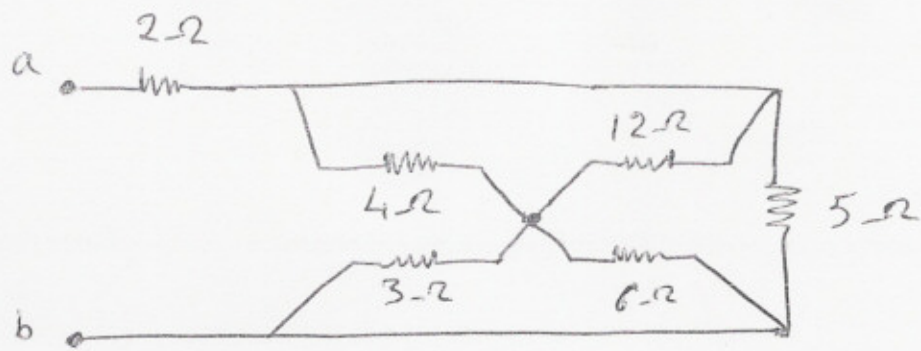

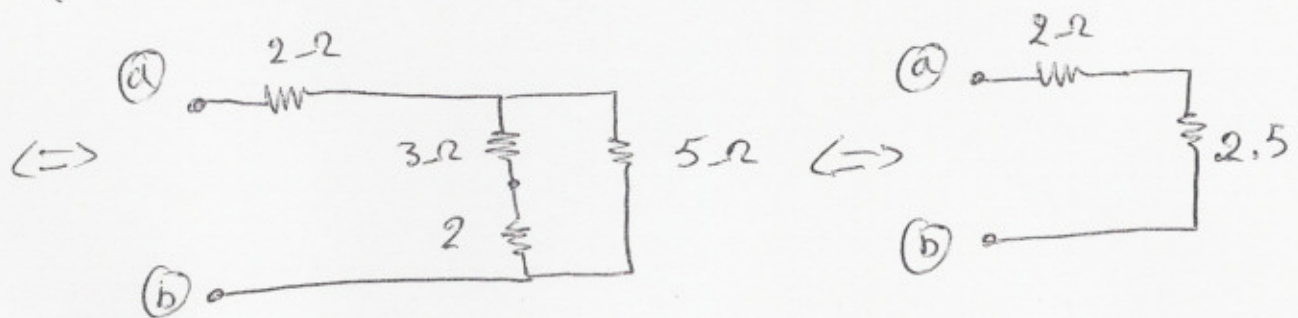
(4Ω) & (12Ω) are in parallel
 (3Ω) & (6Ω) are in parallel



$$\Rightarrow R_{ab} = 4.5\Omega$$

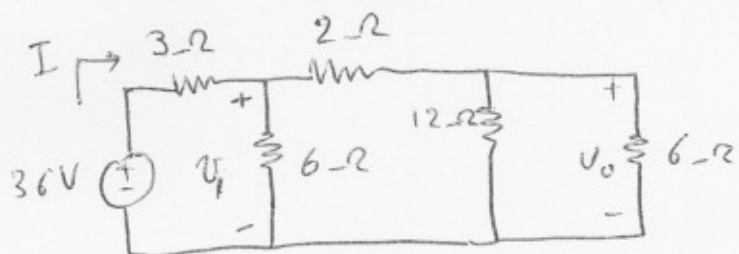Problem 9:

due to 36V only, the circuit will reduce to:



$$(12 \parallel 6) = \frac{6 \times 12}{18} = 4\Omega$$


$$4 \text{ \& } 2 \text{ are in series} = 4 + 2 = 6\Omega$$

$$(6 \text{ \& } 6 \text{ are } \parallel) = 3$$

$$3 \text{ \& } 3 \text{ are in series} \Rightarrow V_1 = \frac{3 \times 36}{6} = 18V$$

$$\Rightarrow V_0 = \frac{4}{6} \times 18 = 12V$$

Problem 10:

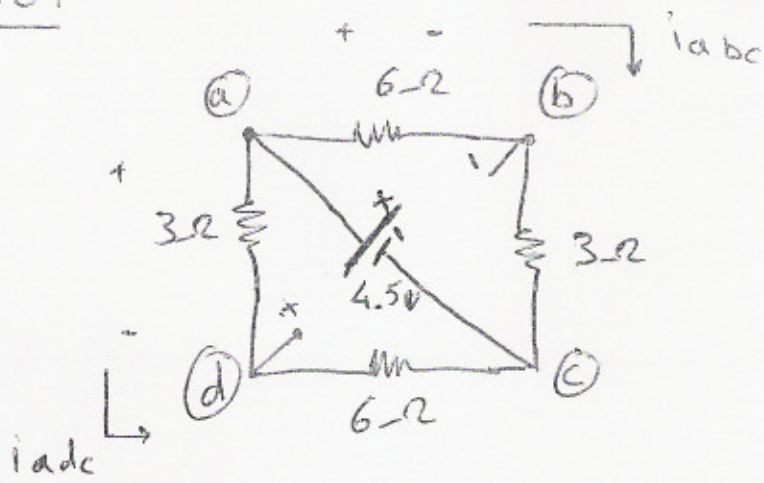

$$i_{abc} = \frac{4.5}{9} = 0.5$$

$$i_{adc} = \frac{4.5}{9} = 0.5$$


$$V_{ad} = 3 \times 0.5 = 1.5 \text{ V}$$

$$V_{ab} = 6 \times 0.5 = 3 \text{ V}$$


KVL on (a b d): $V_{ab} - V_{Th} - V_{ad} = 0$
 $\Rightarrow V_{Th} = 1.5 \text{ V}$

Problem 11:

$$R_{Th} = 2 \left(\frac{18}{9} \right) = 4 \Omega$$

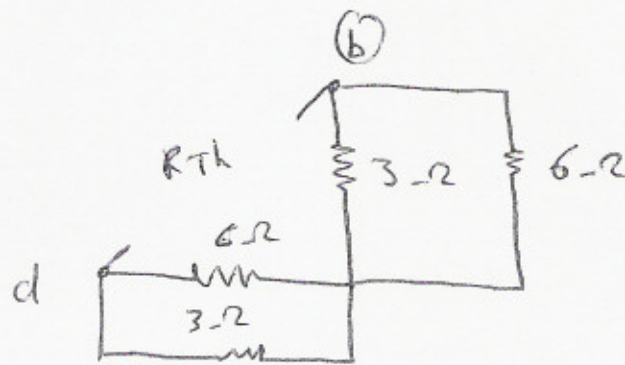

Problem 12:

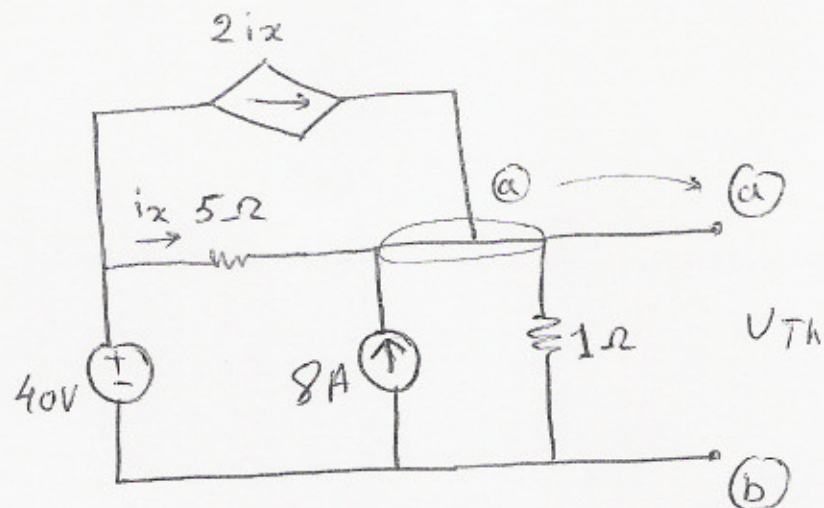


Node voltage method on (a):

$$\frac{V_{TH}}{1} - 8 + \frac{V_{TH} - 40}{5} - 2i_x = 0$$

$$\text{or } i_x = \frac{40 - V_{TH}}{5}$$

$$\Rightarrow V_{TH} = 20 \text{ V.}$$

Problem 13:

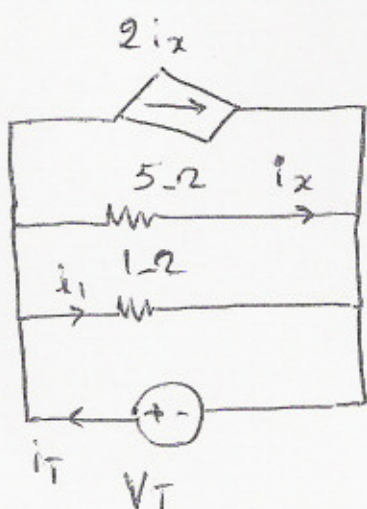

We must inject current into this circuit to find R_{TH}

$$R_{TH} = \frac{V_T}{i_T}$$

$$i_T = i_1 + i_x + 2i_x$$

$$= \frac{V_T}{1} + \frac{V_T}{5} + \frac{2V_T}{5} = \frac{8V_T}{5}$$

$$\Rightarrow R_{TH} = \frac{V_T}{i_T} = \frac{5}{8} = 0.625 \Omega$$