

Prof. R. Chedid  
K. Kabalan  
F. Karameh  
L. El-Haj

FACULTY OF ENGINEERING  
& ARCHITECTURE  
DEPARTMENT OF ELECTRICAL  
& COMPUTER ENGINEERING

FALL TERM 2007-08

QUIZ #1

Name:.....  
ID:.....  
Professor:.....

Nov. 15, 2007

V.L


(EECE 210) ELECTRIC CIRCUITS

CLOSED BOOK (1 ½ HRS)

1. Programmable Calculators are not allowed
2. Provide your answers on the computer's card only
3. Return the computer's card attached to the question sheet
4. Mark with a pencil your last name.
5. Mark your AUB ID NO.
6. The test ID No. is your exam version. Mark it in the box titled ' Test ID'.
7. Use pencil for marking your answers
8. When using eraser, be sure that you have erased well

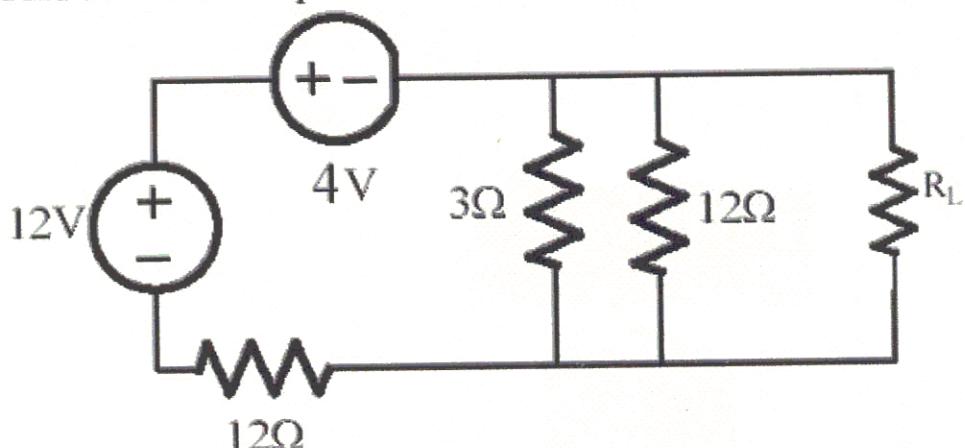**Problem 1**


Find the maximum power that can be transferred to  $R_L$ .



- a. 0.6666 W
- b. 0.2222 W
- c. 0.6530 W
- d. 0.8888 W
- e. None of the above

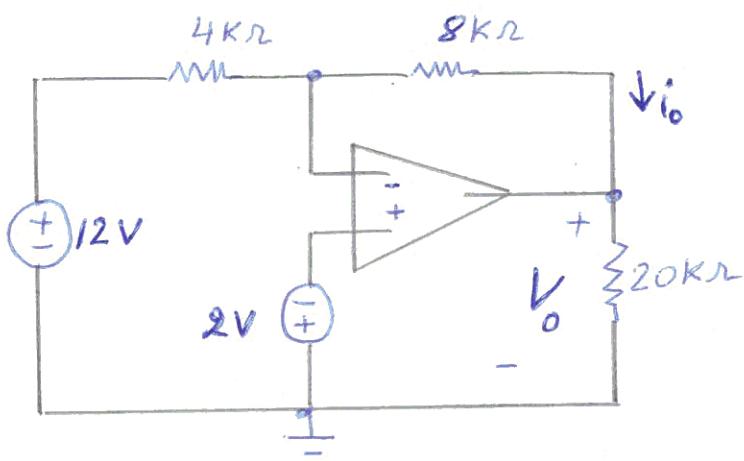**Problem 2**


Find  $i_0$  and  $v_o$  in the circuit shown below



- a. + 7.5 V, + 3/8 mA
- b. -26 V, -3.5 mA
- c. + 30 V, + 3.5 mA
- d. -30 V, +3.5 mA
- e. None of the above
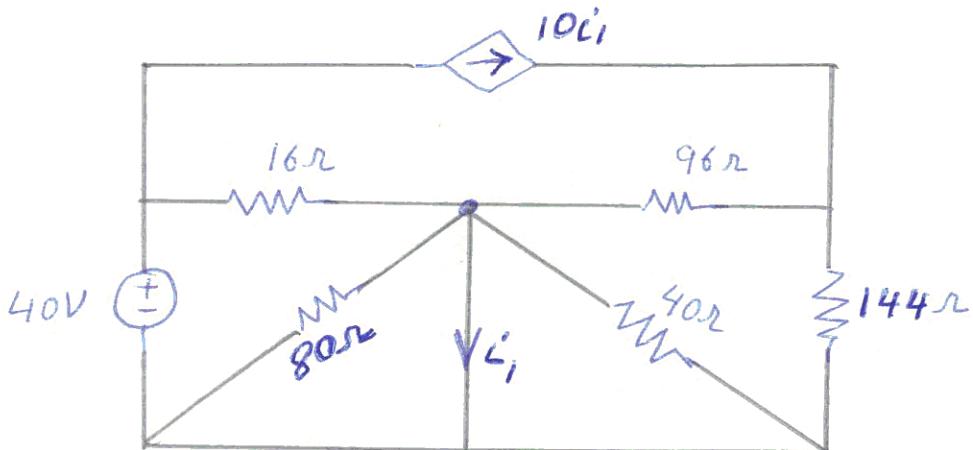
### Problem 3


Find the current  $i_1$  in the circuit shown below



- a. -7.5 A
- b. -0.5 A
- c. 2.5 A
- d. 3 A
- e. None of the above

### Problem 4


Solve for  $I_x$

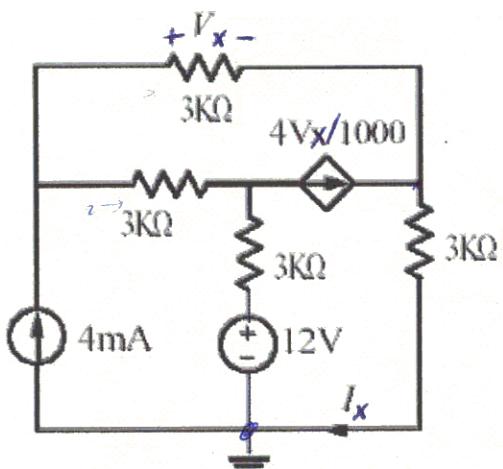

- a. 5.57 mA
- b. 1.857 mA
- c. -1.857 mA
- d. -5.57 mA
- e. None of the above

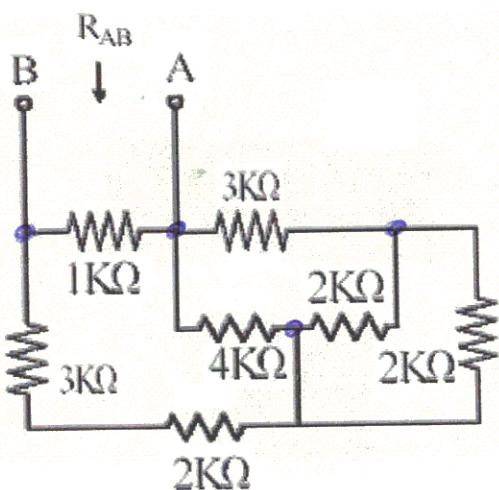**Problem 5**


Find  $R_{AB}$  the equivalent resistance between terminals A and B.



- a. 0.875 KΩ
- b. 0.588 KΩ
- c. 0.982 KΩ
- d. 8 KΩ
- e. None of the above

**Problem 6**


Find  $i_x$  in the circuit shown below

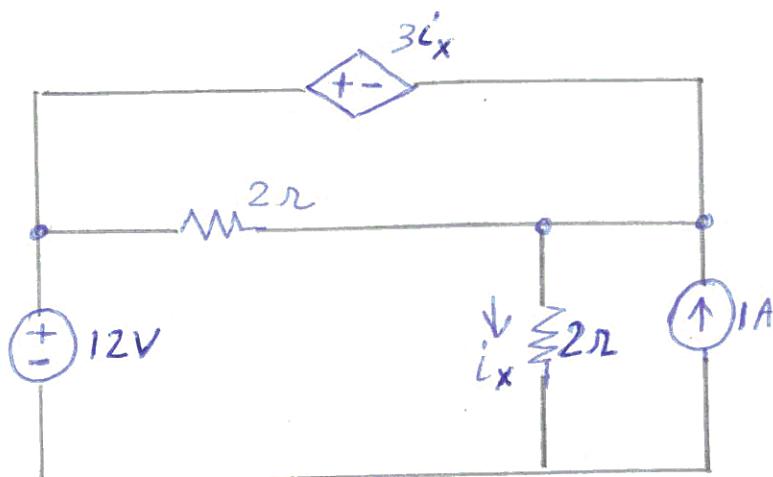

- a. 1.2 A
- b. 2.4 A
- c. -2.4 A
- d. -12 A
- e. None of the above

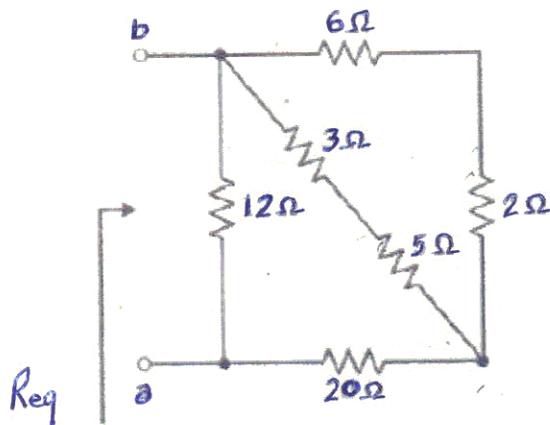**Problem 7**


For the circuit shown below, find  $R_{eq}$  if the voltage  $V_{ab}=40$  Volts



- a.  $24 \Omega$
- b.  $30 \Omega$
- c.  $8 \Omega$
- d.  $12 \Omega$
- e. None of the above

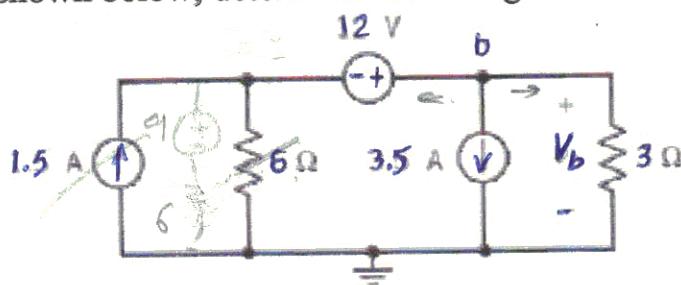**Problem 8**


For the circuit shown below, determine the voltage at node b.



- a. -12 Volts
- b. 0 Volts
- c. 4 Volts
- d. 6 Volts
- e. None of the above

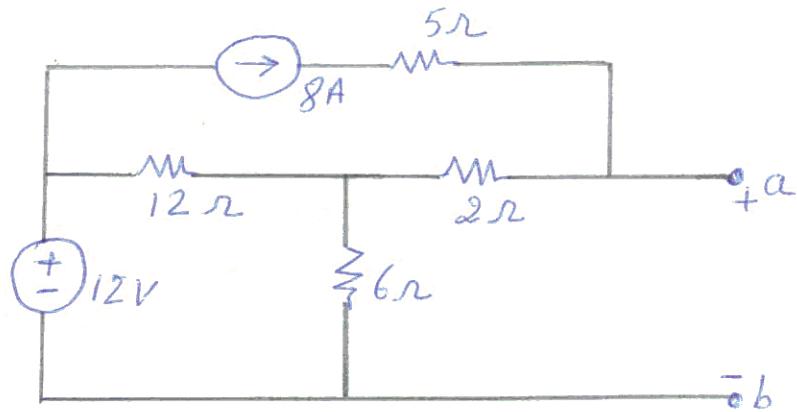**Problem 9**


Find  $V_{ab}$  in the circuit shown below



- a. 52 Volts
- b. 16 Volts
- c. 28 Volts
- d. 36 Volts
- e. None of the above

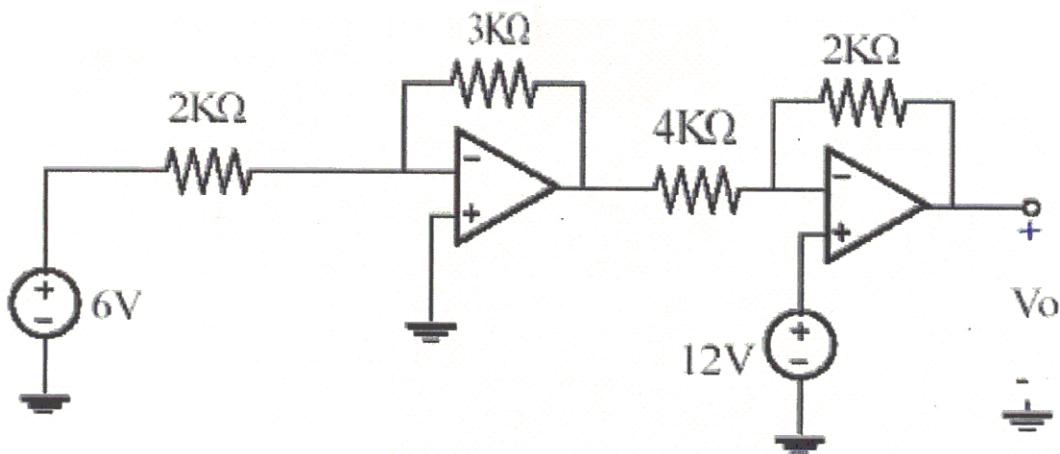**Problem 10**


In the circuit shown below, solve for  $V_0$



- a. 12 V
- b. 22.5 V
- c. 13.5 V
- d. 1.5 V
- e. None of the above
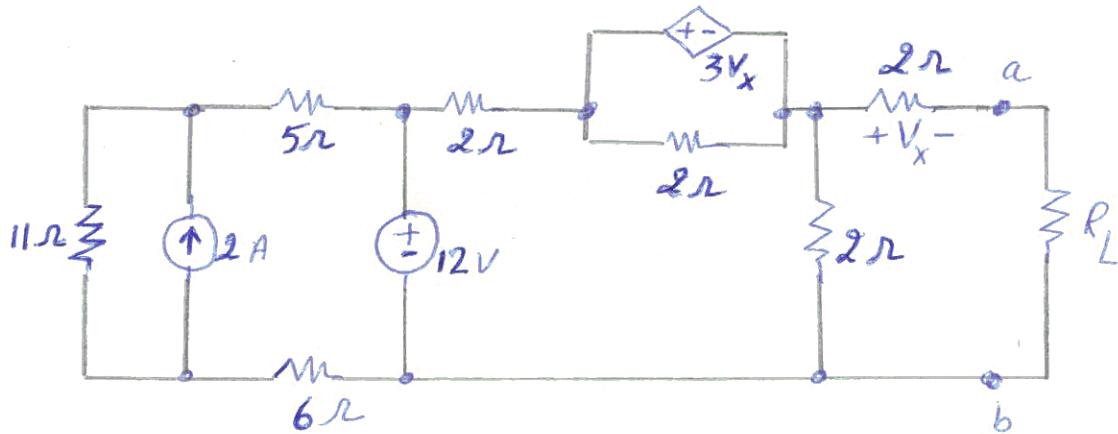
### Problem 11

Find Thevenin Equivalent across the terminals a and b on the figure shown below




- a.  $V_{th} = 3 \text{ V}$
- b.  $V_{th} = 6 \text{ V}$
- c.  $V_{th} = 4 \text{ V}$
- d.  $V_{th} = 4 \text{ V}$
- e. None of the above

### Problem 12

Given the circuit of an ideal operation amplifier.

Determine  $V_o$  assuming  $V_s = 10 \text{ V}$ .

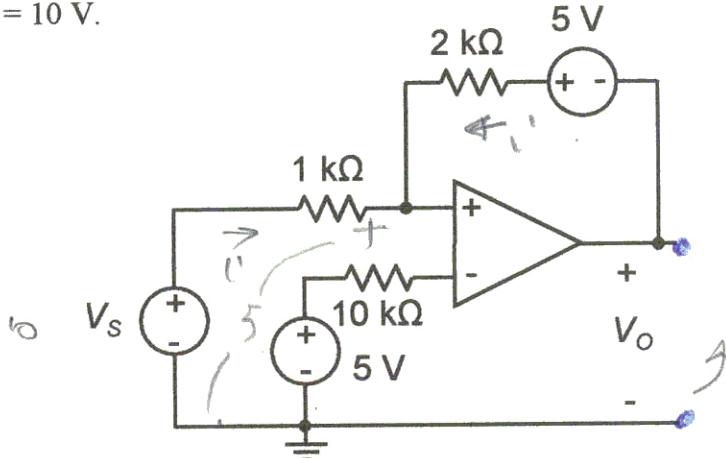- A. +5 V
- B. -5 V
- C. +10 V
- D. -10 V**
- E. None of the above



$$V_o = 5 \text{ mV}$$

~~$$-V_o - 5 + 2000(1) + 5 = 0 \quad ?$$~~

$$V_o = 2000 \times 5 \text{ mV} = 10$$