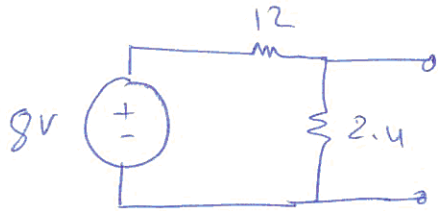


Solution

1)



R_{th} - seen from a-b:



$$R_{th} = \frac{12 \times 2.4}{14.4} = 2$$

$$V_{th} = \frac{8 \times 2.4}{14.4} = 1.33$$
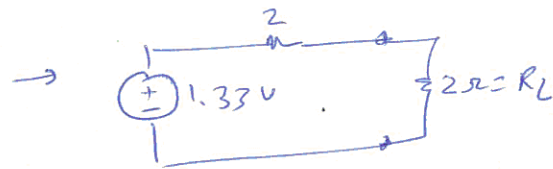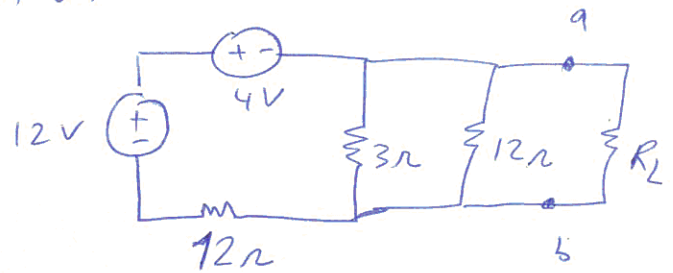
$$I = \frac{1.33}{4} \quad \& \quad P_{max} = \left(\frac{1.33}{4}\right)^2 \cdot 2 = 0.222 \text{ W}$$




2)

$$V_+ = V_- \rightarrow V_- = -2 \text{ V}$$

$$i_i = \frac{12 - (-2)}{4 \text{ k}\Omega} = \frac{14}{4 \text{ k}\Omega}$$
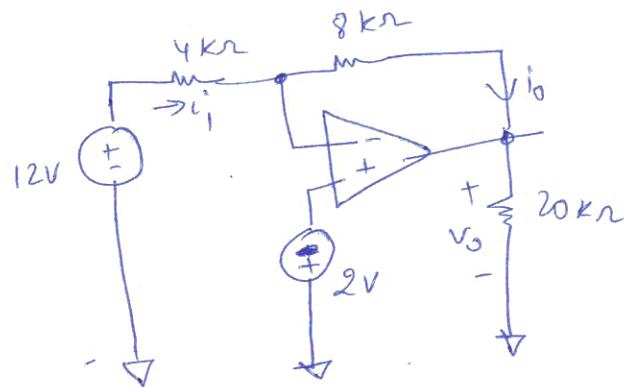
$$i_o = i_i = \frac{14}{4 \text{ k}\Omega} = 3.5 \text{ mA}$$





by KVL: $-V_- + 8 \text{ k}\Omega i_o + V_o = 0$

$$V_o = V_- - 8 \text{ k}\Omega i_o = -2 - 8000 \times 3.5 \times 10^{-3} = -30 \text{ V}$$

3/ $i_x = ?$

the circuit can be redrawn as

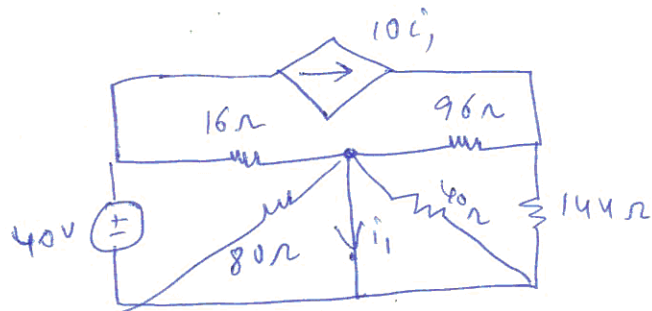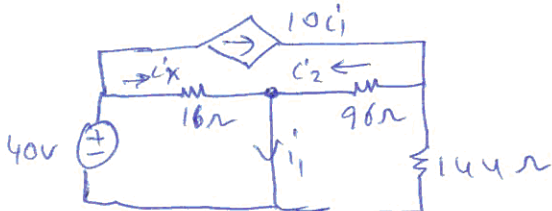

$$i_x = \frac{40}{16} = 2.5 \quad \& \quad i_2 = \frac{10 i_1 \times 144}{96 + 144} = 6 i_1$$

Hence $C_1 = C_1' + C_2' = 2.5 + 6 \mu F$


or $5C_1' = -2.5$ & $C_1' = -0.5 \mu F$.

4)

$I_1 = 4 \text{ mA}$

Super mesh:

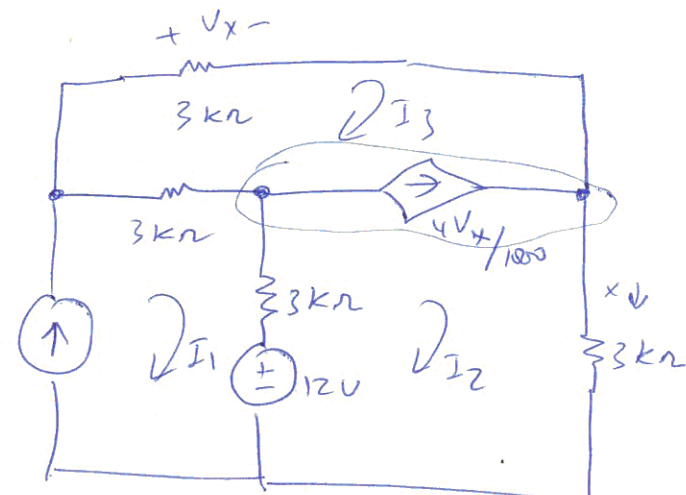$3000 I_2 - 12 + 3000(I_2 - I_1) + 3000(I_3 - I_1) + 3000 I_3 = 0$



or $3000 I_2 - 12 + 3000 I_2 - 3000 \times 4 \times 10^{-3} + 3000 I_3 - 3000 \times 4 \times 10^{-3} + 3000 I_3 = 0$

also $I_2 - I_3 = 4 \frac{V_x}{1000} = \frac{4 \times 3000 \times I_3}{1000}$

or $I_2 - I_3 = 12 I_3 \rightarrow 13 I_3 = I_2$

or $2 \times 3000 \times 13 I_3 - 12 + 12 + 2 \times 3000 I_3 - 12 = 0$





$\rightarrow 14 \times 2 \times 3000 I_3 = 36$

$I_3 = \frac{36}{14 \times 2 \times 3000} = 0.428$

& $I_2 = 13 I_3 = 13 \times 0.428 = 5.57 \text{ mA}$

& $I_x = I_2 = 5.57 \text{ mA}$

5)

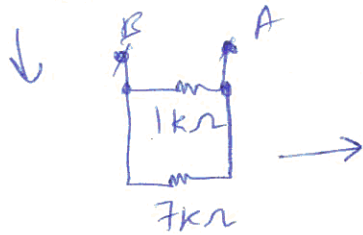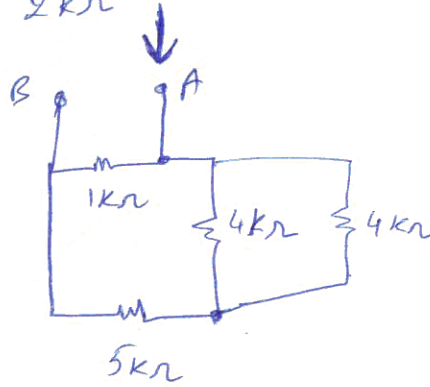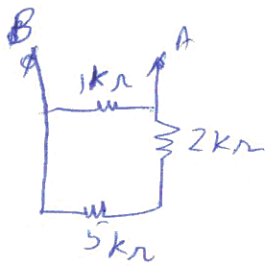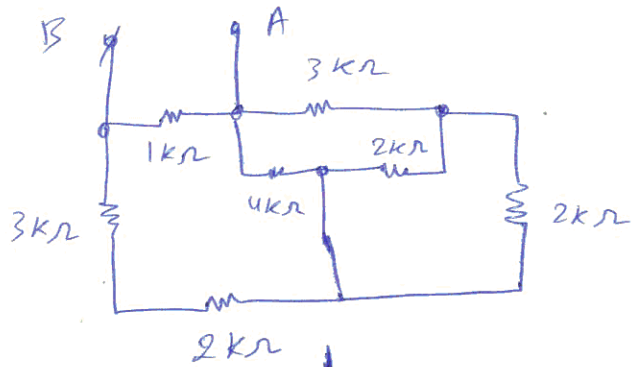

$$\frac{7k\Omega \times 1k\Omega}{8k\Omega} = 0.875k\Omega$$


6/

by KVL:



$$-12 + 2 \times \frac{3i_x}{2} + 2i_x = 0$$

$$12 = 5i_x$$

$$i_x = \frac{12}{5} = 2.4A$$

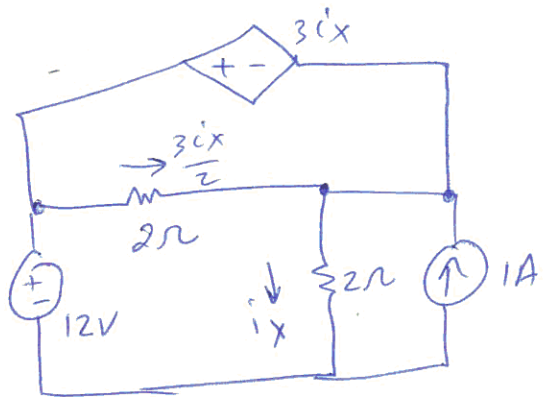

7/

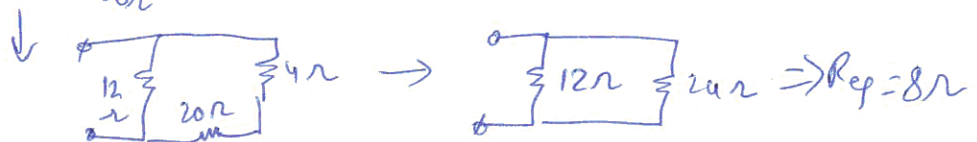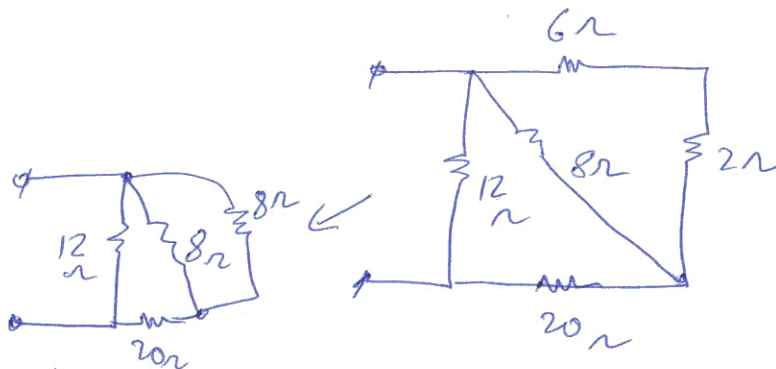


8/

By N.V.M:

$$\frac{V_b}{3} + 3.5 + \frac{V_b - 21}{6} = 0$$

$$V_b \left(\frac{1}{3} + \frac{1}{6} \right) = \frac{21}{6} - 3.5 = 0$$

$$\Rightarrow V_b = 0$$

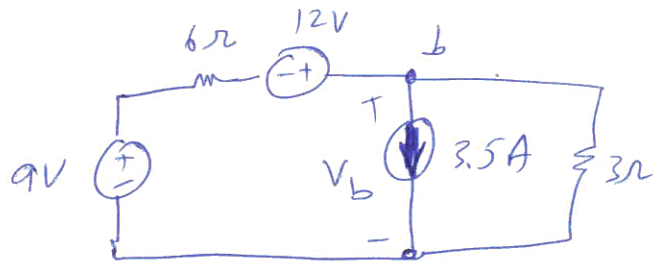

9) $V_{ab} = ?$

$$-V_{ab} + 8 \times 2 + V = 0$$


$$V_{ab} = V + 16$$

by N.V.M:


$$\frac{V}{6} - 8 + \frac{V - 12}{12} = 0 \rightarrow V \left(\frac{1}{6} + \frac{1}{12} \right) = 9$$

$$V = 36$$

$$\therefore V_{ab} = 36 + 16 = 52V$$

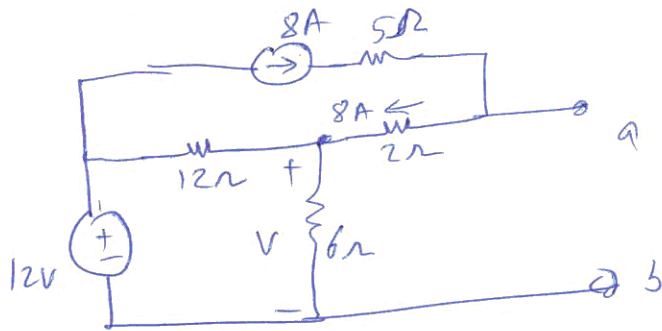

10) $V_o = ?$

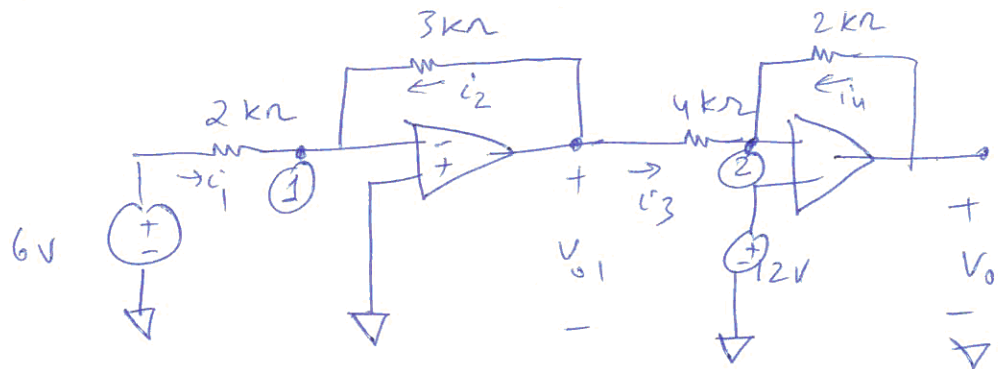

$$V_1 = 0 \Rightarrow i_1 = \frac{6}{2k\Omega} = 3mA$$

$$i_2 = -i_1 = -3mA \text{ \& kVL: } -V_{o1} + 3k\Omega \times (-3mA) + 0 = 0$$


$$\Rightarrow V_{o1} = -9V$$

$$V_2 = 12V \text{ \& } i_3 = \frac{V_{o1} - 12}{4k\Omega} = \frac{-9 - 12}{4k\Omega} = -\frac{21}{4}mA$$

$$i_u = -i_3 = +\frac{21}{4}mA \text{ \& kVL: } -V_o + 2k\Omega \times \frac{21}{4}mA + 12 = 0$$

Hence: $V_o = \frac{21}{2} + 12 = 22.5V$


11/

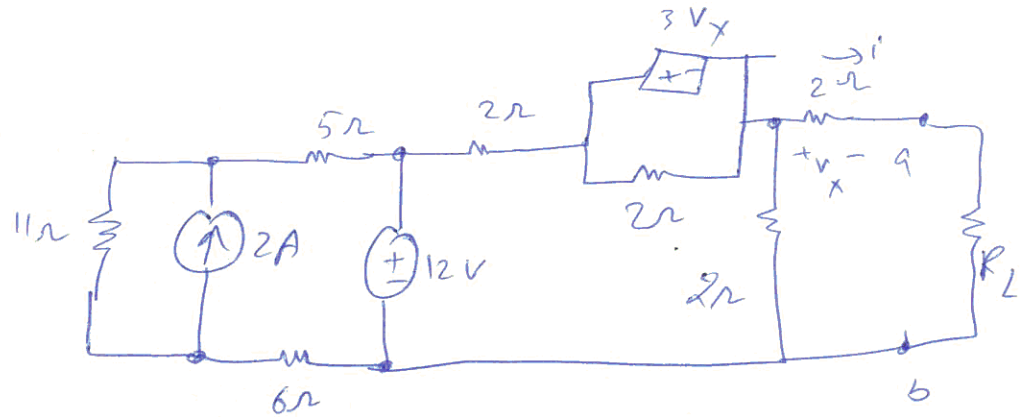

$V_{th} = ?$ assume open circuit at a-b $\rightarrow i = 0 \rightarrow V_x = 0$

if $V_x = 0 \rightarrow$

$$i_1 = \frac{12}{4} = 3$$

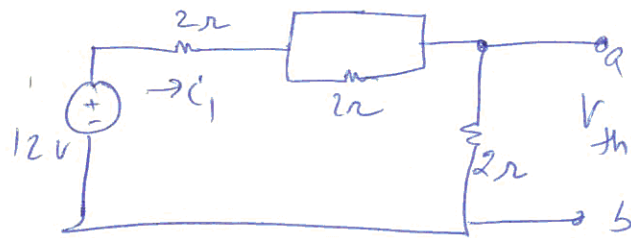

$\& V_{th} = 2 \times 3 = 6V$

12/ $V_o = ?$

$V_+ = V_- \rightarrow V_1 = 5V.$

$$i_1 = \frac{10 - 5}{1k\Omega} = 5mA$$

$i_2 = -i_1 = -5mA$

by kvl: $-V_o - 5V + 2k\Omega \times (-5mA) + 5V = 0$

$V_o = 2 \times -5 = -10V.$

