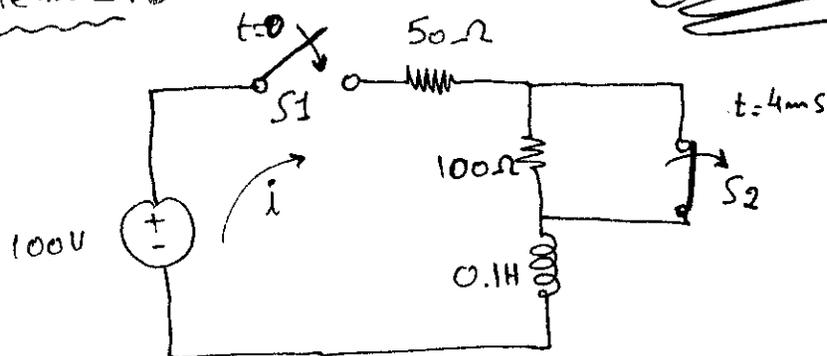


Solution:

Problem 1:

ECE 210
Ch 1, 2



Eng. & Arch. Library

As there is always inductance in the circuit, the current is a continuous function at all times. In the interval $0 \leq t \leq 4\text{ms}$, with the 100Ω shorted out and a time constant $\tau = (0.1\text{H})/50\Omega = 2\text{ms}$, i starts at zero and builds toward $100\text{V}/50\Omega = 2\text{A}$, even though it never gets close to that value. Hence,

$$i = 2(1 - e^{-t/2})\text{A} \quad (0 \leq t \leq 4)$$

where t is measured in ms. In particular,


$$i(4) = 2(1 - e^{-2}) = 1.729\text{A}$$

In the interval $t \geq 4\text{ms}$, i starts at 1.729A and decays toward $100/150 = 0.667\text{A}$, with a time constant $0.1/150 = \frac{2}{3}\text{ms}$. Therefore, with t again in ms

$$i = (1.729 - 0.667)e^{-(t-4)/(2/3)} + 0.667$$
$$= 428.4 e^{-3t/2} + 0.667\text{A} \quad t \geq 4$$

Steps 2 & 3 ✓


✓

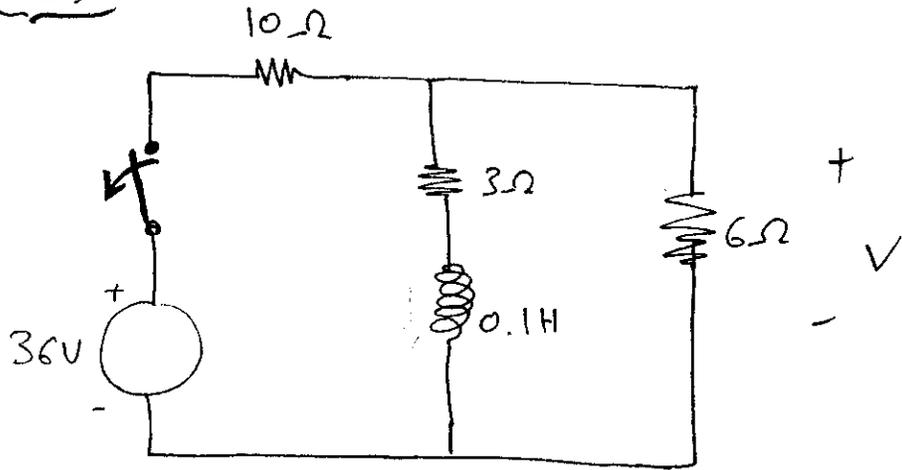

Eng. & Arch. Library

$$i_2(0^-) = \frac{36 (6/9)}{10 + (3)(6)/(3+6)} = 2 \text{ A}$$

Then we will obtain

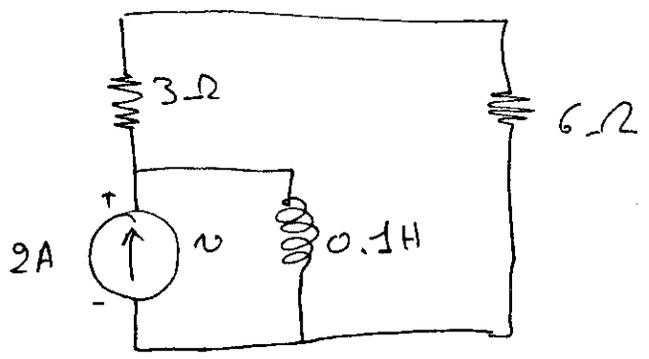


for which;

$$2 = \frac{v}{9} + \frac{1}{0.1} \int_0^t v dt \quad (1)$$

The solution to Eq. (1) is $v = 18e^{-90t}$ V. Hence the voltage across the resistance becomes $v_{6\Omega} = \frac{6}{9} (18e^{-90t}) = 12e^{-90t}$ V.

stem 4 ✓

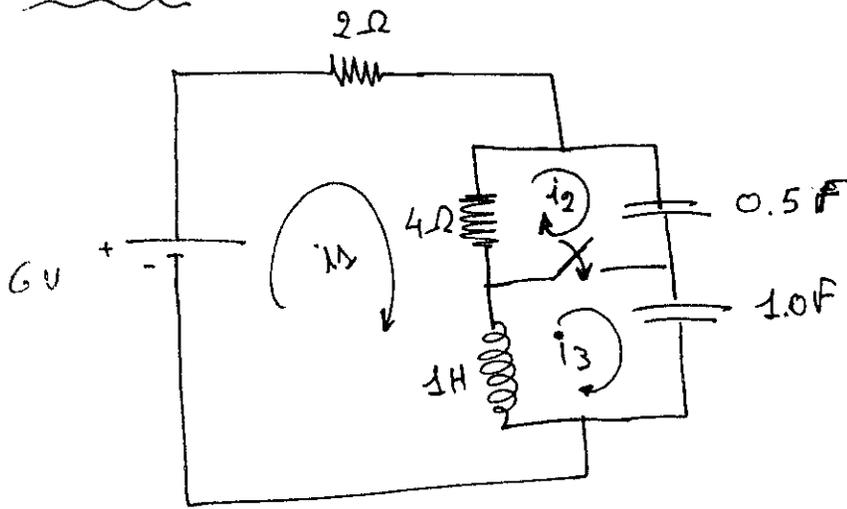

Before the switch is closed, $t < 0$

$$i_{4\Omega}(0_-) = i_{1H}(0_-) = \frac{6}{2+4} = 1 \text{ A}$$

$$v_{0.5F} + v_{1.0F} = \frac{(4)(6)}{4+2} = 4 \text{ V.} \dots\dots(1)$$

Eng. & Arch. Library

When the switch is closed, $t > 0$

$$2i_1 = 6 - (v_{0.5F} + v_{1.0F}) = 6 - 4 = 2 \quad \text{or } i_1(0_+) = 1 \text{ A}$$

$$i_1(0_+) - i_3(0_+) = i_{1H}(0_+) = i_{1H}(0_-) = 1 \text{ A}$$

$$i_3(0_+) = i_1(0_+) - 1 = 1 - 1 = 0 \text{ A}$$

Since $v_{0.5F}(0_-) = v_{0.5F}(0_+)$ and $v_{1.0F}(0_-) = v_{1.0F}(0_+)$

$$i_1(0_+) - i_2(0_+) = \frac{v_{0.5F}(0_+)}{4} \dots\dots(2)$$


Because the capacitors are connected in series

$$\frac{v_{0.5F}}{v_{1.0F}} = \frac{1}{0.5} = 2 \quad \text{or } v_{0.5F} = 2v_{1.0F} \dots\dots(3)$$

From (1) & (3) we finally obtain:

$$i_2(0_+) = \frac{1}{3} = 0.33 \text{ A}$$

stem 5: ✓

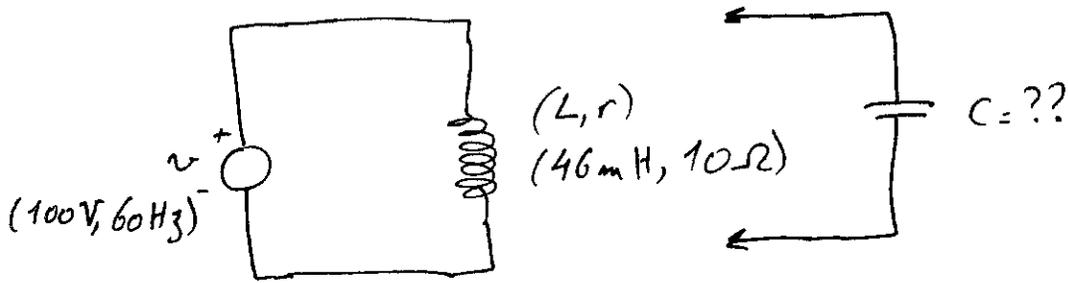


The admittance of the parallel combination will be

$$1/Z_L + j\omega C = 1/(10 + j17.34) + j377C =$$

$$= \frac{1}{40} + j(377C - 0.0434)$$

For unity power factor, the imaginary part must vanish, yielding $C = 0.0434/377 = 115 \mu\text{F}$.

Problem 6: ✓

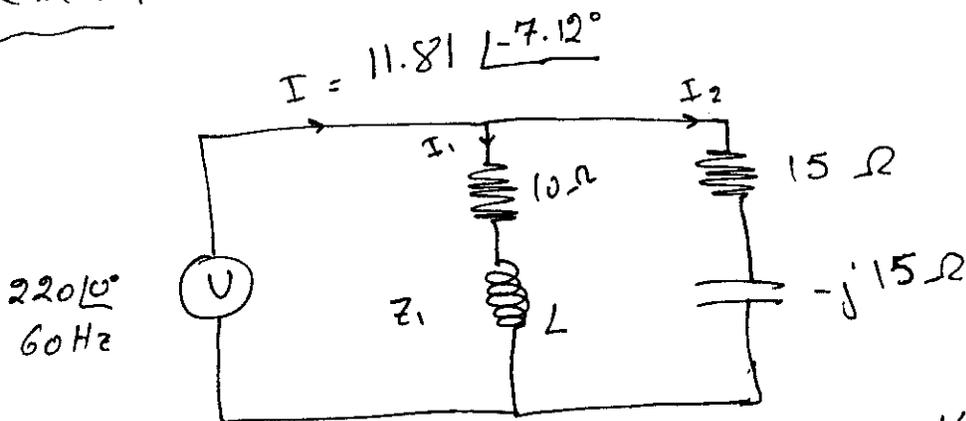

$$I_2 = \frac{V}{Z_2} = \frac{220 \angle 0^\circ}{15 - j15} = \frac{220 \angle 0^\circ}{21.2 \angle -45^\circ} = 10.35 \angle 45^\circ = 7.34 + j7.34$$


$$I_1 = I - I_2 = 11.81 \angle -7.12^\circ - (7.34 + j7.34) = 4.38 - j8.8 = 9.83 \angle -63.6^\circ \text{ A} = \frac{V}{Z_1} = \frac{220 \angle 0^\circ}{10 + jX_L}$$

from which

$$X_L = 20 \Omega = \omega L = 377L \quad \text{or} \quad L = 53.05 \text{ mH}$$

Eng. & Arch. Library

Problem 7:

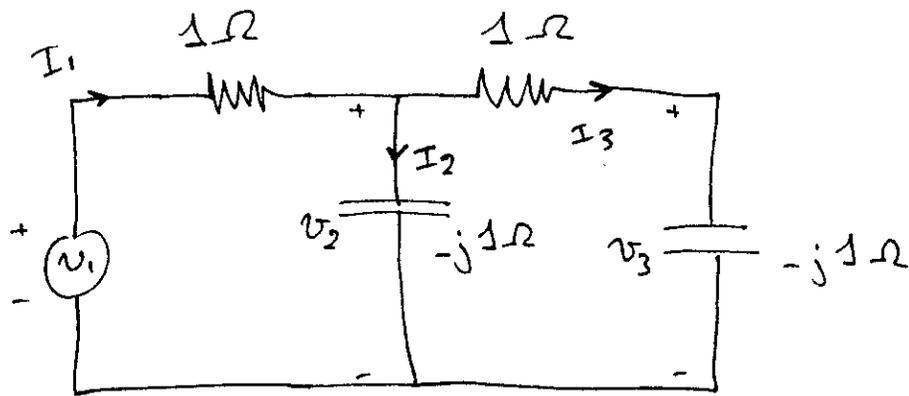

In term of maximum values,

$$v_2 = 2 \angle 0^\circ \quad v_3 = \frac{v_2}{1-j1} (-j1) = \frac{-j2}{1-j1} = 1.414 \angle -45^\circ \text{ V}$$

$$\text{or } v_3(t) = 1.414 \cos(2t - 45^\circ) \text{ V}$$

$$I_1 = I_2 + I_3 = \frac{v_2}{-j1} + \frac{v_2}{1-j1} = \frac{2 \angle 0^\circ}{-j} + \frac{2 \angle 0^\circ}{1-j1} = j2 + 1 + j1 = 1 + j3 \text{ A}$$

$$v_1 = 1(1 + j3) + v_2 = 1 + j3 + 2 = 3 + 3j = 4.24 \angle 45^\circ \text{ V}$$

$$\text{or } v_1(t) = 4.24 \cos(2t + 45^\circ) \text{ V}$$

Problem 8:


In this case, we have

$$4 \angle 25^\circ = \frac{60 \angle 0^\circ + I_2 (j48)}{3.9 + j65} = \frac{60 \angle 0^\circ + I_2 (j48)}{65.11 \angle 86.6^\circ}$$

$$\text{or } 260.46 \angle 111.6^\circ - 60 \angle 0^\circ = I_2 (48 \angle 90^\circ)$$


$$\text{Hence, } I_2 = 6 \angle 32.7^\circ$$

Eng. & Arch. Library

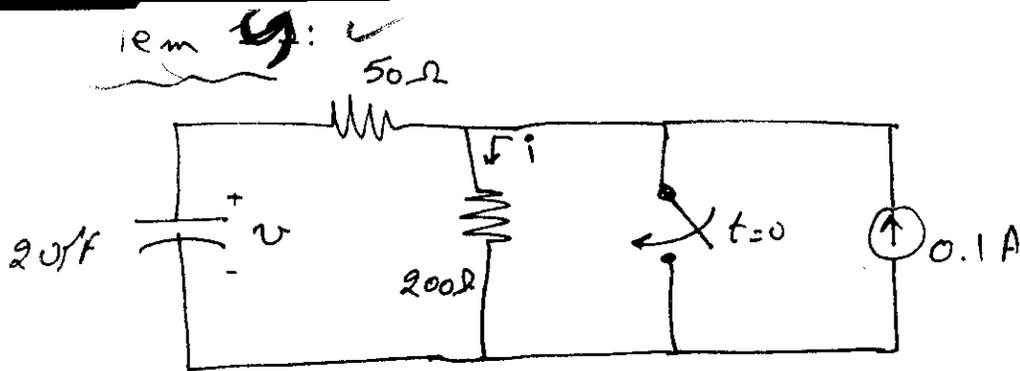

$(10^{-4}) \times 0$
 $V(200) = 2.71V$

Prob. 10 :

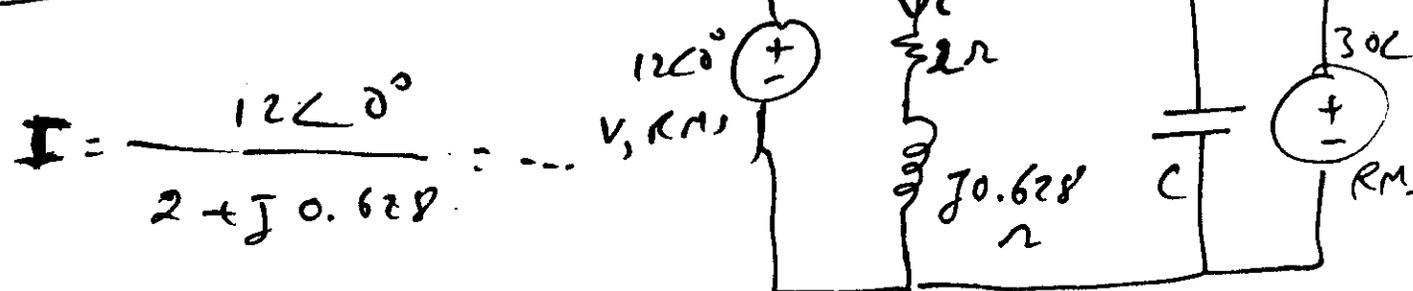

$I = \frac{12\angle 0^\circ}{2 + j0.628}$

Q, in the inductor


$= |I|^2 X_L = \dots = 20.59 \text{ VAR}$

Prob 11.

$Q = \frac{V^2}{X_C} = \frac{30^2}{X_C} = 5 \text{ V}$

$\Rightarrow X_C = \dots \rightarrow X_C = \frac{1}{\omega C} \Rightarrow C = 14.$

problem 12: c

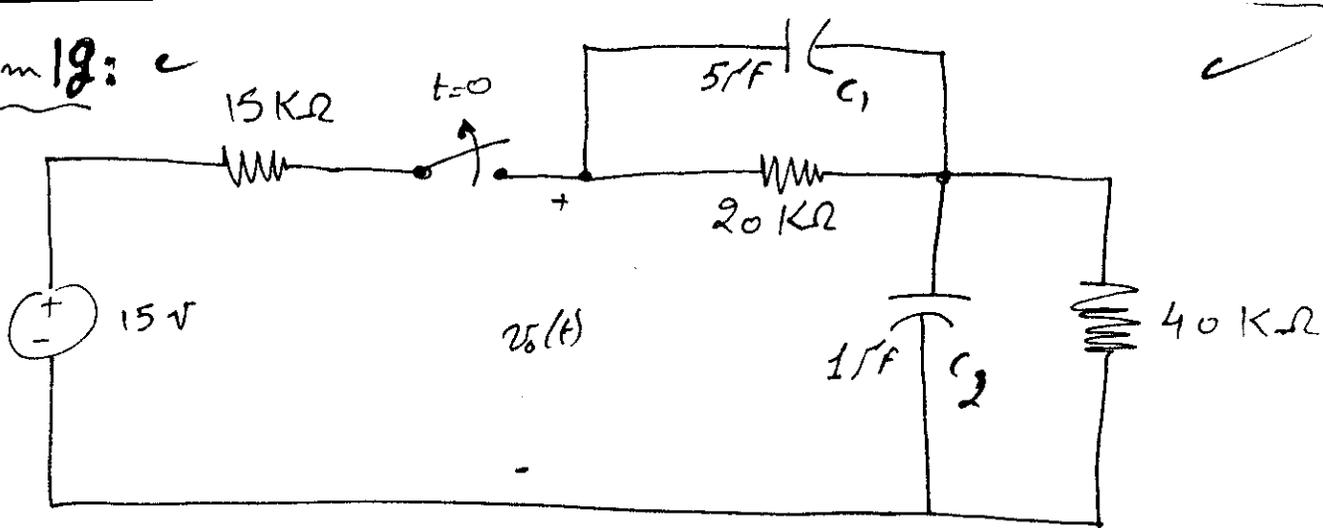

$$v_o(t) = 8e^{-\frac{t}{\tau_1}} + 4e^{-\frac{t}{\tau_2}}$$

$$i(0^-) = \frac{15}{(15+60) \times 10^3} = \frac{15}{75 \times 10^3} = 0.2 \times 10^{-3}$$

$$V(C_2 \text{ at } 0^-) = 0.2 \times 40 \times 10^3 = 8 \text{ V} = V_{C_1}(0^+)$$

$$V(C_1 \text{ at } 0^-) = 0.2 \times 20 \times 10^3 = 4 \text{ V} = V_{C_2}(0^+)$$

for $t \geq 0$; $v_o(t) = v_{o1}(t) + v_{o2}(t)$
 $= 8e^{-\frac{t}{\tau_1}} + 4e^{-\frac{t}{\tau_2}}$

$$\tau_2 = 20 \times 10^3 \times 5 \times 10^{-6} = 0.1$$

$$\tau_1 = 40 \times 10^3 \times 1 \times 10^{-6} = 0.04$$

so $v_o(t) = 8e^{-25t} + 4e^{-10t}$, V
 $= 8e^{-25t} + 4e^{-10t}$, V.