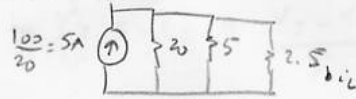


AMERICAN UNIVERSITY OF BEIRUT
FACULTY OF ENGINEERING AND ARCHITECTURE
EECE210 – FALL 2004
QUIZ 2 SOLUTIONS

PROBLEM 1


1) for $t < 0$
 L is a short

source transformation




$$R_1 = 20 \parallel 5 = \frac{20 \times 5}{25} = 4 \Omega$$
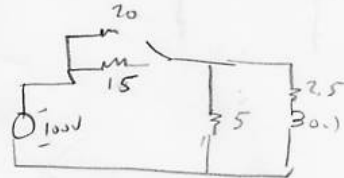
$$\Rightarrow i_L = \frac{4 \times 5}{4 + 2.5} = \frac{20}{6.5} = \frac{200}{65} \text{ A}$$



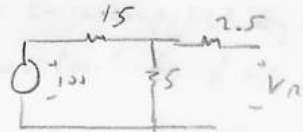2) for $t \geq 0$ - let's find Thevenin equivalent:

$$V_R = \frac{5 \times 100}{20} = 25 \text{ V}$$




$$R_R = 5 \parallel 15 + 2.5 = \frac{75}{20} + 2.5 = 3.75 + 2.5 = 6.25 \Omega$$

$$i_L(t) = [i_L(0) - i_L(\infty)] e^{-\frac{t}{\tau}} + i_L(\infty)$$

$$i_L(0) = i_L(0^+) = \frac{200}{65} \quad ; \quad i_L(\infty) = \frac{25}{6.25}$$

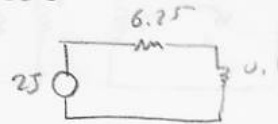
$$\tau = \frac{L}{R_R} = \frac{0.1}{6.25} \text{ sec}$$



$$\Rightarrow i_L(t) = \frac{200}{65} e^{-62.5t} + 4(1 - e^{-62.5t}) \text{ Ams} \quad t \geq 0$$

$$W_{\max} \text{ occurs for } i_{L\max} = 0.4 \text{ A} \Rightarrow W_{\max} = \frac{1}{2} L I_{\max}^2 = \frac{1}{2} \times 0.1 \times (4)^2 = 0.8 \text{ J}$$

PROBLEM 2

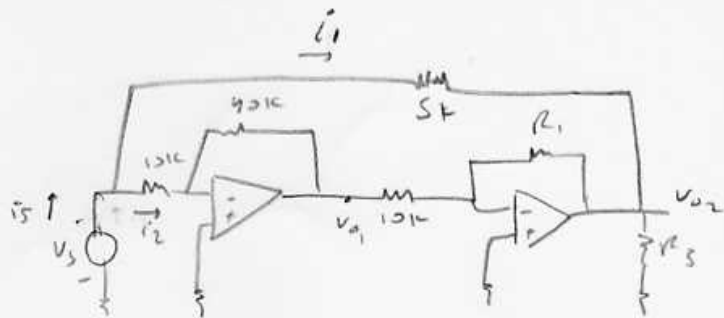

$$V_{o1} = -\frac{40}{10} \cdot V_s = -4V_s$$

$$V_{o2} = -\frac{R_1}{10} \cdot V_{o1} = +0.4 R_1 V_s \quad \dots (1)$$

$$\text{for } i_s = 0 \Rightarrow i_1 = -i_2 \Rightarrow \frac{V_s - V_{o2}}{5} = -\frac{V_s}{10} \Rightarrow V_{o2} = V_s + \frac{5}{10} V_s$$

$$\boxed{V_{o2} = 1.5 V_s} \quad \dots (2)$$


$$(1) \text{ \& } (2) \Rightarrow 0.4 R_1 V_s = 1.5 V_s$$

$$\Rightarrow R_1 = \frac{1.5}{0.4} = \frac{15}{4} = \underline{\underline{3.75 \text{ k}\Omega}}$$

R_3 does not affect the current supplied by source
hence only constrained by power limitations of op-amp.

PROBLEM 3

(a)

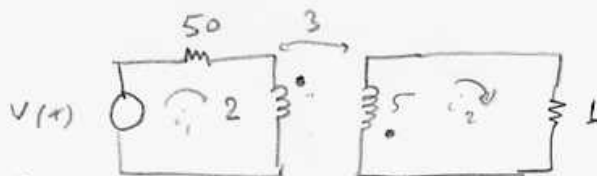

$$-V(t) + 50 i_1 + 2 \frac{di_1}{dt} + 3 \frac{di_2}{dt} = 0$$

and

$$i_2 + 5 \frac{di_2}{dt} + 3 \frac{di_1}{dt} = 0$$

(b) substitute currents into equations:

$$\boxed{i_1(t) = 0.24 - 4e^{-t} ; i_2(t) = 3e^{-t}} \quad V(t) = 12 - 20e^{-t}$$


$$\begin{aligned} \Rightarrow -12 + 20e^{-t} + 50(0.24 - 4e^{-t}) + 2(4)e^{-t} + 3(-3e^{-t}) \\ = -12 + 12 + (20 - 200 + 8 - 9)e^{-t} = 0 \end{aligned}$$

$$i(s): 3e^{-t} + 5(-3e^{-t}) + 3(4e^{-t}) = (3 + 12 - 15)e^{-t} = 0$$

2

PROBLEM 3 - (b)

Phasor circuit shown:

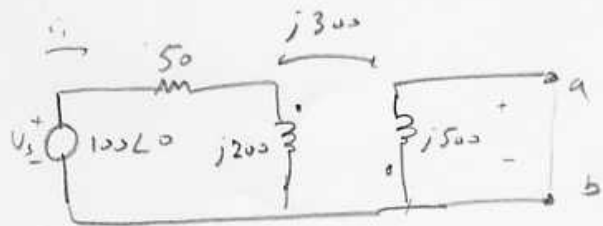

$$V_{oc} = V_R = -j300 \cdot I_1$$

$$I_1 = \frac{V_s}{50 + j200} = \frac{100 \angle 0^\circ}{50 + j200}$$


$$\Rightarrow V_{oc} = \frac{-j3 \times 10^4}{50 + j200} = \frac{3 \times 10^4 \angle -90^\circ}{206.15 \angle 1.32} = \underline{\underline{145.52 \angle -165.96^\circ \text{ Volts}}}$$

$$Z_{Th} = \frac{V_{oc}}{I_{sc}} \Rightarrow \text{find } I_{sc}$$

$$I_{sc} = I_2$$

$$j500 I_2 + j300 I_1 = 0$$
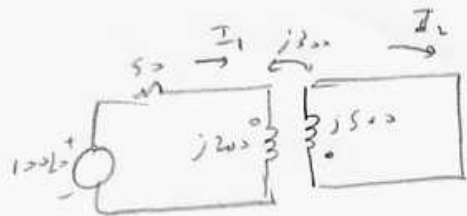
$$\Rightarrow \left[I_1 = -\frac{5}{3} I_2 \right]$$



$$-100 \angle 0^\circ + 50 I_1 + j200 I_1 + j300 I_2 = 0$$

$$\Rightarrow \left[(50 + j200) \left(-\frac{5}{3}\right) + j300 \right] I_2 = 100 \angle 0^\circ$$

$$(-250 + j1000 + j900) I_2 = 300 \angle 0^\circ$$

$$\Rightarrow I_2 = \frac{300 \angle 0^\circ}{-250 - j100} = I_{sc}$$

$$Z_{Th} = \frac{V_{oc}}{I_{sc}} = 145.52 \angle -165.96^\circ \times \left(\frac{-250 - j100}{300} \right)$$

$$= 130.608 \angle -324.15^\circ$$

$$= 130.608 \angle +35.84^\circ \Omega$$

$$\boxed{Z_{Th} = 105.9 + j76.5 \Omega}$$

PROBLEM 4

$$i_4 = \frac{12-8}{4k} = 1 \text{ mA}$$

$$i_5 = \frac{8}{2} = 4 \text{ mA}$$

$$i_6 = \frac{8}{2} = 4 \text{ mA}$$

$$i_5 + i_6 = i_4 + i_3$$


$$\Rightarrow i_3 = 7 \text{ mA} \Rightarrow V_{o2} = 0.2 \times 7 + 8$$

$$\boxed{V_{o2} = 9.4 \text{ V}}$$

$$i_2 = \frac{12-9.4}{2k} = \frac{2.6}{2} = 1.3 \text{ mA}$$

$$i_1 = i_2 + i_4 = 1.3 + 1 = 2.3 \text{ mA} \Rightarrow V_{o1} = (2.3)(1) + 12$$

$$\boxed{V_{o1} = 14.3 \text{ V}}$$

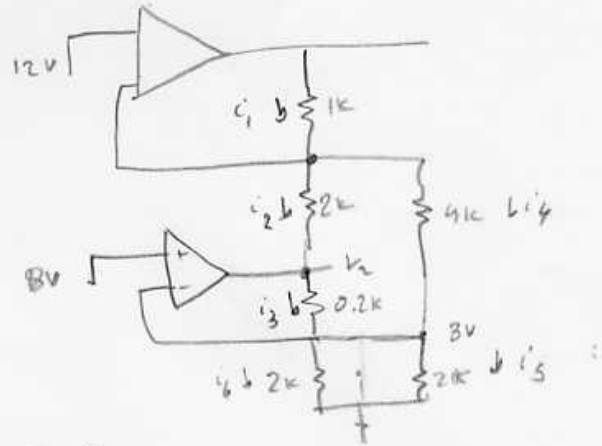

PROBLEM 5

Solve by superposition:

for DC source: $\left. \begin{array}{l} L \text{ short} \\ C \text{ open} \end{array} \right\} \Rightarrow$


Note

$$\frac{V_1}{1} = 1 + \frac{V_1 - 0.67I_1}{1} = 0$$

$$I_1 = -\frac{V_1}{1} = -V_1 \Rightarrow V_1 - 1 + V_1 + 0.67V_1 = 0$$


$$\Rightarrow V_1 = \frac{1}{2.67} \text{ Volts}$$
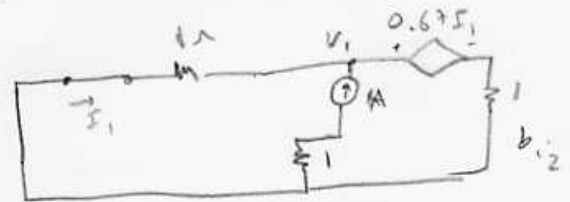
$$\Rightarrow i_{2(1A)} = \frac{V_1 - 0.67I_1}{1} = 1.67V_1 = \frac{1.67}{2.67} \text{ A} \downarrow$$



FOR AC SOURCE:

phasor ckt:

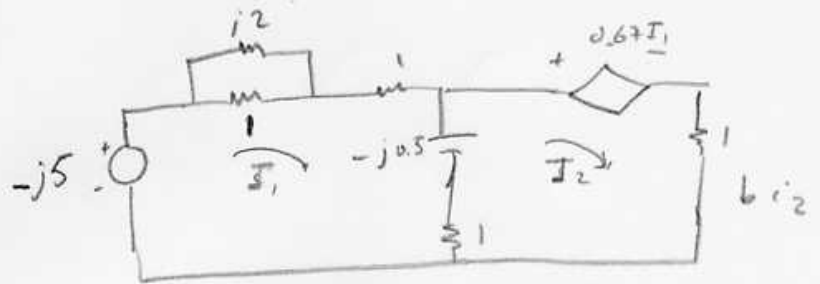

mesh analysis

$$+j5 + \left(\frac{j2}{1+j2}\right) I_1 + I_1 + (1-j0.5j)(I_1 - I_2) = 0 \quad \dots \textcircled{1}$$

$$(1-j0.5j)(I_2 - I_1) + 0.67I_1 + I_2 = 0 \quad \dots \textcircled{2}$$

$$\textcircled{1} \Rightarrow \left(\frac{j2}{1+j2} + 2 - j0.5j\right) I_1 + (0.5j - 1) I_2 = -j5$$

$$\textcircled{2} \Rightarrow (-0.33 + 0.5j) I_1 + (2 - 0.5j) I_2 = 0$$

$$\textcircled{2} \Rightarrow I_1 = \left[\frac{0.5j - 2}{0.5j - 0.33} \right] I_2$$

$$\text{Substitute in } \textcircled{1} \Rightarrow \left[\frac{(j2 + 2 + j4 - 0.5j + 1)}{1+j2} \left(\frac{0.5j - 2}{0.5j - 0.33} \right) + (0.5j - 1) \right] I_2 = -j5$$

$$\left[\frac{(3 + j3.5)(0.5j - 2)}{(1+j2)(0.5j - 0.33)} + (0.5j - 1) \right] I_2 = -j5$$

$$\Rightarrow I_2 = -0.394 + j0.369$$


$$= 0.5393 \angle -2.38^\circ \text{ A}$$

$$I_2 = 0.539 \angle -136.89^\circ \text{ A}$$

$$\therefore \left[\begin{aligned} i_2(t) &= 0.539 \cos(2t - 136.89^\circ) + \frac{1.67}{2.67} \text{ A} \\ i_2(t) &= 0.6255 + 0.539 \cos(2t - 2.38^\circ) \text{ A} \end{aligned} \right]$$

5

PROBLEM 6

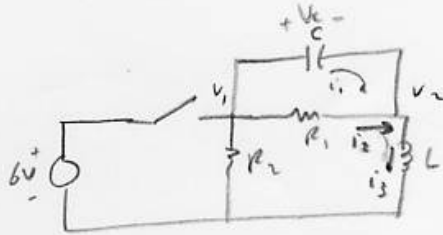

for $t < 0$ $i_L(t) = v_C(t) = 0$

for $t > 0$

$$i_3 = i_2 + i_1$$

$$i_1 = C \frac{dv_C}{dt} = C \frac{d(v_1 - v_2)}{dt}$$

$$i_2 = \frac{v_1 - v_2}{R_1}$$

$$i_3 = \frac{1}{L} \int v_2(t) dt$$

$$\Rightarrow \frac{di_3}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt}$$

$$\Rightarrow \frac{1}{L} v_2 = C \frac{d^2(v_1 - v_2)}{dt^2} + \frac{1}{R_1} \frac{d(v_1 - v_2)}{dt}$$

$$v_1 = 6V = \text{constant}$$

$$\Rightarrow -C \frac{d^2 v_2}{dt^2} - \frac{1}{R_1} \frac{dv_2}{dt} = \frac{1}{L} v_2$$

OR $\left[\frac{d^2 v_2}{dt^2} + \frac{1}{R_1 C} \frac{dv_2}{dt} + \frac{1}{LC} v_2 = 0 \right]$ O.D.E. (similar to what we know)

characteristic poly: $s^2 + \frac{1}{R_1 C} s + \frac{1}{LC} = 0 \Rightarrow s = \frac{-1}{2R_1 C} \pm \sqrt{\left(\frac{1}{2R_1 C}\right)^2 - \frac{1}{LC}}$

a) for $R_1 = 3$, $L = 5$, $C = 4$, $R_2 = 2\Omega$

$$s = \frac{-1}{2+3 \cdot 4} \pm \sqrt{\left(\frac{1}{2 \cdot 4}\right)^2 - \frac{1}{20}} = \frac{-1}{24} \pm \sqrt{\left(\frac{1}{24}\right)^2 - \frac{1}{20}}$$

$$s_{1,2} = -0.0417 \pm j0.2197$$

$$v_C(t) = v_{CN}(t) + v_{CF}(t)$$

$$v_C(0) = K$$

Note Now that $V_c = V_1 - V_2 \Rightarrow V_2 = V_1 - V_c$

$$\Rightarrow \frac{d^2}{dt^2} (V_1 - V_c) + \frac{1}{R_1 C} \frac{d(V_1 - V_c)}{dt} + \frac{1}{LC} (V_1 - V_c) = 0$$

$$V_1 = 6V \Rightarrow \boxed{\frac{d^2 V_c}{dt^2} + \frac{1}{R_1 C} \frac{dV_c}{dt} + \frac{1}{LC} V_c = \frac{1}{LC} V_1}$$

$$V_{CF}(t) = K_0 \Rightarrow \frac{K_0}{LC} = \frac{1}{LC} V_1 \Rightarrow K_0 = V_1$$

$$V_{CN}(t) = \text{Natural response where } s_{1,2} = -0.0417 \pm j0.2197$$

$$V_{CN}(t) = A e^{-0.0417t} \cos(0.2197t) + B e^{-0.0417t} \sin(0.2197t)$$

so

$$V_c(t) = 6 + e^{-0.0417t} (A \cos(0.2197t) + B \sin(0.2197t))$$

Apply initial conditions:

$$V_c(0) = 0 \Rightarrow 6 + A = 0 \Rightarrow \boxed{A = -6}$$

$$i_L(0) = 0 \text{ but } i_L = i_C + i_{R_1} = C \frac{dV_c}{dt} + \frac{V_c}{R_1}$$

$$i_L(0) = C \frac{dV_c}{dt} + \frac{V_c}{R_1}$$

$$\Rightarrow \frac{dV_c}{dt}(0) = i_L(0) - \frac{V_c(0)}{R_1} = 0$$

$$\Rightarrow \frac{dV_c}{dt}(0) = 0$$

$$\left. \frac{dV_c}{dt} \right|_{t=0} = -0.0417A + 0.2197B = 0$$

$$\Rightarrow B = \frac{0.0417A}{0.2197} = \frac{0.0417 \times 6}{0.2197} = 1.14$$

$$\text{so } V_c(t) = 6 + e^{-0.0417t} (-6 \cos 0.2197t + 1.14 \sin 0.2197t)$$

$t \geq 0$

Volts

(b) since $s_{1,2}$ are complex, response is oscillatory
 \Rightarrow it is underdamped.

(c) for $L=5$; $C=4$

$$\text{need } \left(\frac{1}{2R_1C}\right)^2 = \frac{1}{LC} \Rightarrow \frac{1}{2R_1C} = \frac{1}{\sqrt{LC}} \Rightarrow \frac{1}{R_1} = 2\sqrt{\frac{C}{L}}$$

$$\text{or } \boxed{R_1 = \frac{1}{2}\sqrt{\frac{L}{C}}}$$

$$* R_1 = \frac{1}{2}\sqrt{\frac{5}{4}} = \frac{\sqrt{5}}{2} = \underline{\underline{0.559 \Omega}}$$

* R_2 has no effect on the response.

